

# Computer-Aided Engineering

Adapted from


C.N.Nightingale and J.K.Fidler ., Computer-Aided  
Circuit and System Design.,U.K +IEEE papers

Lecture 5

**Prof .Dr.Eng.ARN**
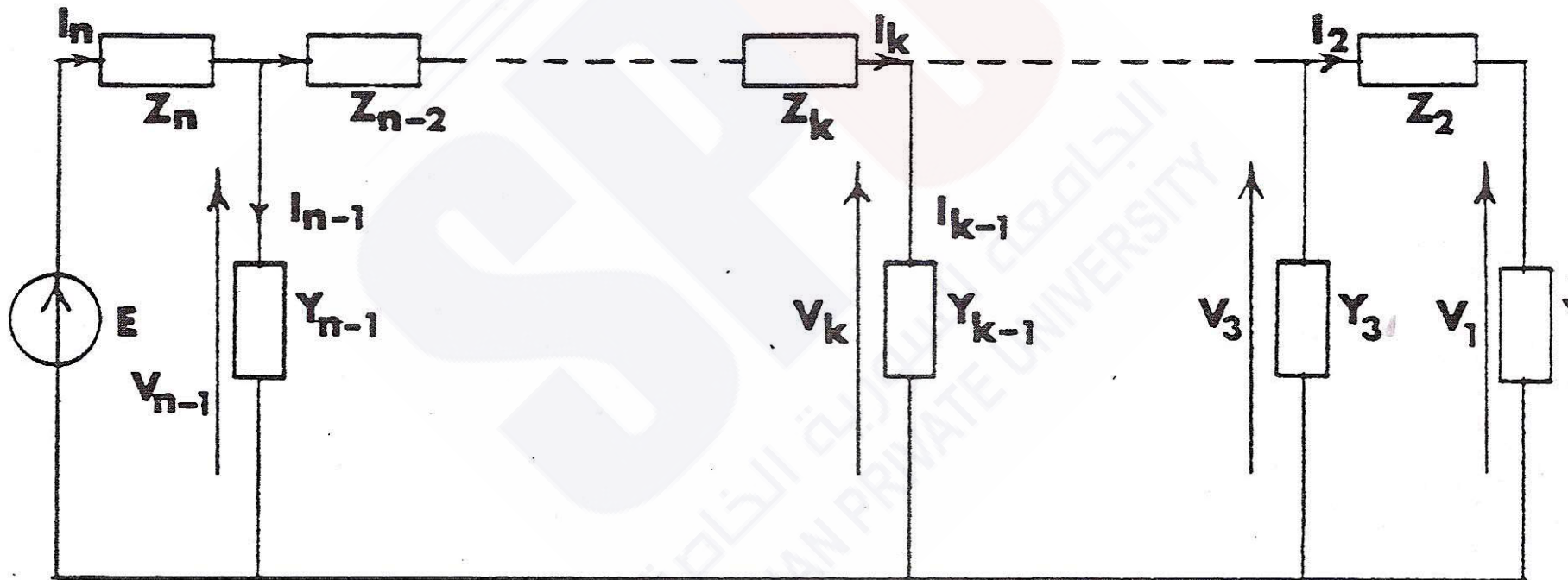
# Bashkow's Analysis Method for Ladder Networks

Consider a ladder network consisting of  $n$  branches and excited by a voltage source  $E$  as shown in Figure



General  $n$ -branch doubly terminated ladder network

# Bashkow's Analysis Method for Ladder Networks

Applying Kirchhoff's voltage and current laws alternately leads to the following equations:-

$$E = I_n Z_n + V_{n-1}$$

$$0 = -I_n + V_{n-1} Y_{n-1} + I_{n-2}$$

$$0 =$$

.

.

.

.

$$0 = -V_3 + Z_2 I_2 + V_1$$

$$0 = -I_2 + V_1 Y_1$$

(2.1)

# Bashkow's Analysis Method for Ladder Networks

these equations may be rewritten in matrix notations form as:-

$$\begin{array}{c}
 \left| \begin{array}{c} E \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{array} \right| = \left| \begin{array}{ccccccc}
 Z_n & 1 & 0 & \dots & \dots & \dots & \dots \\
 -1 & Y_{n-1} & 1 & \dots & \dots & \dots & \dots \\
 0 & -1 & Z_{n-2} & \dots & \dots & \dots & \dots \\
 & & & Y_k & & & \\
 & & & & & & \\
 & & & & -1 & Y_3 & 1 & 0 \\
 & & & & 0 & -1 & Z_2 & 1 \\
 & & & & & 0 & -1 & Y_1
 \end{array} \right| \left| \begin{array}{c} I_n \\ V_{n-1} \\ I_{n-2} \\ V_k \\ V_3 \\ I_2 \\ V_1 \end{array} \right| \quad (2.2)
 \end{array}$$

## Bashkow's Analysis Method for Ladder Networks

or simply as:—  $b = A \cdot x$  (2.3)

It can be shown that the determinant of matrix A can be written as a sequence of the following determinant equations:—

$$\begin{aligned}d_1 &= Y_1 \\d_2 &= Z_2 Y_1 + 1 \\d_3 &= Y_3 (Z_2 Y_1 + 1) + Y_1 = Y_3 d_2 + d_1 \\&\vdots \\d_n &= (Z_n \text{ or } Y_n) d_{n-1} + d_{n-2}\end{aligned} \quad (2.4)$$

## Bashkow's Analysis Method for Ladder Networks

assuming that  $d_0 = 1$ , and  $d_{-1} = 0$ .  $d_n$  is the value of the determinant of A. Now assuming Cramer's rule to solve equation (2.3) for the  $x_i$ , i.e.  $I_i$  or  $V_i$ , where  $i = 1, 2, 3, \dots, n$ , gives:-

$$x_i = \frac{\Delta_i}{\Delta} \quad (2.5)$$

where  $\Delta = d_n$ , and  $\Delta_i$  is the matrix in which the  $i$ 'th column of matrix A is replaced by vector b.

From Figure 2.1, the voltage transfer function of the ladder is:-

$$F(s) = \frac{V_1}{E} \quad (2.6)$$

Using Cramer's rule to find the voltage transfer function leads to

the following;-

1. Replace the b-matrix in column n of A as:-

$$\Delta_n = \begin{vmatrix} Z_n & 1 & 0 & 0 & \dots & 0 & E \\ -1 & Y_{n-1} & 1 & & & & 0 \\ 0 & -1 & Z_{n-2} & 1 & & & 0 \\ & & & & & & \\ & & & & & & \\ & & & & & & \\ & & & & -1 & Y_3 & 1 & 0 \\ & & & & -1 & Z_2 & & 0 \\ 0 & 0 & & & 0 & -1 & & 0 \end{vmatrix} \quad (2.7)$$





## Bashkow's Analysis Method for Ladder Networks

or

$$\Delta_n = -E \cdot M \quad (2.9)$$

The determinant of matrix  $M$  is equal to  $-1$  as the product of the principle diagonal elements, i.e.

$$\Delta_n = E \quad (2.10)$$

therefore

$$F(s) = \frac{V_1}{E} = \frac{\Delta_n}{\Delta} \cdot \frac{1}{E} = \frac{1}{\Delta} \cdot \text{Or in general}$$

$$(V_k \text{ or } I_k)/E = d_{k-1}/\Delta = \frac{d_{k-1}}{d_n} \quad (2.11)$$

## Bashkow's Analysis Method for Ladder Networks

Each branch ( $Z_k$  or  $Y_k$ )  $IM_k$  will be considered as a ratio of

two polynomials in the complex frequency variable, i.e.

$$IM_k = \frac{N_k(s)}{D_k(s)} \quad (2.12)$$

Substituting (2.12) into individual sequence of the determinants  $d_i$

of (2.4) gives:-

# Bashkow's Analysis Method for Ladder Networks

$$\begin{aligned}d_1 &= \frac{N_1(s)}{D_1(s)} \\d_2 &= \frac{N_2(s)}{D_2(s)} \cdot \frac{N_1(s)}{D_1(s)} + 1 \\&= \frac{N_2(s)N_1(s) + D_1(s)D_2(s)}{D_1(s)D_2(s)}\end{aligned}$$

or in general

$$d_k = \frac{A_k(s)}{B_k(s)} = \frac{N_k(s)}{D_k(s)} \cdot \frac{A_{k-1}(s)}{B_{k-1}(s)} + \frac{A_{k-2}(s)}{B_{k-2}(s)} \quad (2.13)$$

where  $A_k(s) = D_k(s)D_{k-1}(s) \dots D_1(s)$

hence  $A_{k-1}(s) = N_{k-1}(s) A_{k-2}(s)$  (2.14)

and  $B_{k-1}(s) = D_{k-1}(s) B_{k-2}(s)$

Taking into consideration equations (2.14) and substituting them into equation (2.13), it follows that an expression is obtained without common factor as:-

$$d_k = \frac{N_k(s) A_{k-1}(s) + D_k(s) D_{k-1}(s) A_{k-2}(s)}{D_k(s) D_{k-1}(s)} \quad (2.15)$$

where  $A_0 = B_0 = D_0 = 1$  and  $A_{-1} = 0$ ,  $k = 1, 2, \dots, n$ .

Thus:-

$$F(s) = \frac{V_1}{E} = \frac{1}{d_n} = \frac{B_n(s)}{A_n(s)}$$

$$= \frac{D_n(s) D_{n-1}(s) \dots D_1(s)}{A_n(s)} \quad (2.16)$$

The formulation of (2.15) provides a simply programmed method of evaluation  $d_k = \frac{A_k(s)}{B_k(s)}$ , therefore the required voltage transfer function is found as:-

$$F(s) = \frac{B_k(s)}{A_k(s)} \quad (2.17)$$

Equation (2.11) can be used to evaluate the other network functions:  
in the present application, only the voltage transfer function is required.

Input data corresponding LCR-prototype topology

\*\*\*\*\*

No. branches?4

Analyses required till termination ?1E12

No. coeffs in num & den (Max:14,14) ?3,4

Num coeffs(specification):(Lowest degree 1st):

1,0.112525,0.123951

Den coeffs(specification):(lowest degree 1st)=1:

1,1.463014,1.091287,0.574221

Req'd den const(DCFL):?4

Lossy(0) or Lossless(1) realization req'd:?0

Topology 1,2,3,4,5 OR 6

Branch 1?1

Value :R(Even)/G(Odd)?1

Branch 2?3

Value :L?1

Branch 3?4

Values:L,1/Q1,R1,C,1/Qc,Gc,G1?1,0,1,1,0,0,0

Branch 4?5

Values:L,Rs?1,1

Optimization strategy required

\*\*\*\*\*

Least square method:1 Fletcher-Powell method:2?

1


Read i/p data for E04GAF 1-s optm.method

Method 1,2,3=?1

Iter-print 0,1=?0

Maxcal=?1E12

Ifail=? 0

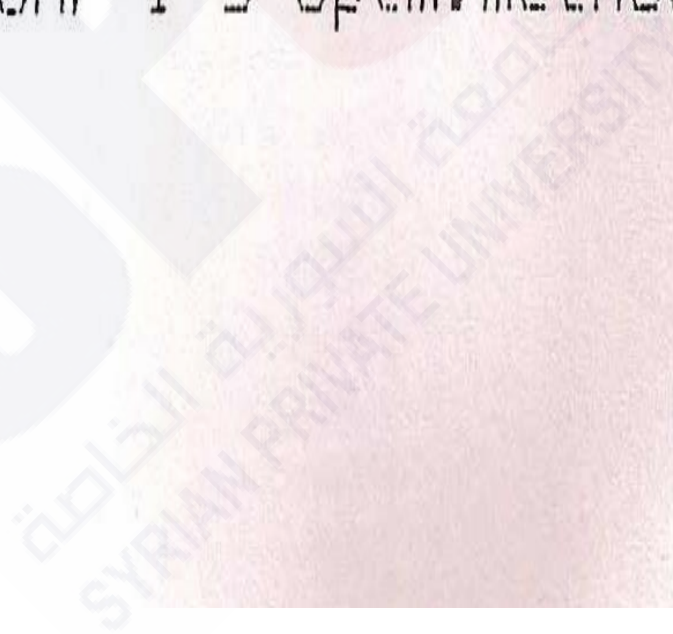

Final sum of squares is .8150598E-14

At the prototype element values

3.000000

0.694954

0.101510

1.221068

0.092153

0.698675

Residuals are

0.000000

0.000000

0.000000

0.000000



This has error number 0

End of E046AF optimization process

No. of VTF analyses were :

132

Num coeffs (Lowest degree 1st) :

1.000000E+00s<sup>0</sup>

1.125250E-01s<sup>1</sup>

1.239510E-01s<sup>2</sup>

Den coeffs (Lowest degree 1st) :

4.000000E+00s<sup>0</sup>

5.852056E+00s<sup>1</sup>

4.365148E+00s<sup>2</sup>

2.296884E+00s<sup>3</sup>

# Coefficient sensitivity analysis:

Elem:	1:	Num:	.000000E+00	.000000E+00	.000000E+00		
		Den:	.750000E+00	.772115E+00	.776163E+00	.100000E+01	
Elem:	2:	Num:	.000000E+00	.000000E+00	.000000E+00		
		Den:	.000000E+00	.356262E+00	.636945E+00	.886888E+00	
Elem:	3:	Num:	.000000E+00	.000000E+00	.100000E+01		
		Den:	.000000E+00	.000000E+00	.113582E+00	.225621E+00	
Elem:	4:	Num:	.000000E+00	.100000E+01	.100000E+01		
		Den:	.000000E+00	.285569E+00	.100000E+01	.100000E+01	
Elem:	5:	Num:	.000000E+00	.100000E+01	.000000E+00		
		Den:	.000000E+00	.769131E-01	.107775E+00	.000000E+00	
Elem:	6:	Num:	.000000E+00	.000000E+00	.000000E+00		
		Den:	.000000E+00	.358169E+00	.249473E+00	.887491E+00	
Elem:	7:	Num:	.000000E+00	.000000E+00	.000000E+00		
		Den:	.750000E+00	.266341E+00	.668388E+00	.000000E+00	

Transfer function sensitivities analyses:

No. of frequency ranges? 1

Start, stop freqs. (Rad/sec)? 0, 5

No. points do you want: (Max=500)? 500

Ampl T.F sens: maximum (Range 0.0 to 5.0 Rad/sec)			AT W=1
Elem. 1:	-0.9904	at 5.0000 Rad/s	-0.6295
Elem. 2:	-1.0321	at 1.8100 Rad/s	-0.0928
Elem. 3:	1.6232	at 3.4500 Rad/s	-0.0091
Elem. 4:	-2.2316	at 2.2900 Rad/s	-0.0736
Elem. 5:	0.9681	at 2.8400 Rad/s	-0.1225
Elem. 6:	-0.8494	at 5.0000 Rad/s	-0.0472
Elem. 7:	-0.7500	at 0.0000 Rad/s	-0.4315

Max. Ampl.T.F. sensitivity: -2.2316 at 2.2900 Rad/sec? - Elem. 4

Max. Ampl.sens. at W=1 Rad/sec: -0.6295 - Elem 1

# FDNR sensitivity required ?1

Branch 1:

Elmt. 1:C:.3000000E+01

Branch 2:

Elmt. 2:R:.6949541E+00

Branch 3:

Elmt. 3:R:.1015103E+00

FDNR ellipt, 4, 5 and 6 : C1(&C3) and R2:.2170306E+02.2592376E-02

Branch 4:

Elmt. 7:R:.6986751E+00

Elmt. 8:C:.1000000E+01

Rmax is :	6.986751E-01	Rmin is :	2.592376E-03
Cmax is :	2.170306E+01	Cmin is :	1.000000E+00
R-spread is :	2.695115E+02	C-spread is :	2.170306E+01