

# **EE2003**

# **Circuit Theory**

## **Chapter 1**

## **Basic Concepts**

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



# Basic Concepts - Chapter 1

1.1 Systems of Units.

1.2 Electric Charge.

1.3 Current.

1.4 Voltage.

1.5 Power and Energy.

1.6 Circuit Elements.

# 1.1 System of Units (1)

## Six basic units

Quantity	Basic unit	Symbol
Length	meter	m
Mass	kilogram	Kg
Time	second	s
Electric current	ampere	A
Thermodynamic temperature	kelvin	K
Luminous intensity	candela	cd

# 1.1 System of Units (2)

The derived units commonly used in electric circuit theory

Quantity	Unit	Symbol
electric charge	coulomb	C
electric potential	volt	V
resistance	ohm	$\Omega$
conductance	siemens	S
inductance	henry	H
capacitance	farad	F
frequency	hertz	Hz
force	newton	N
energy, work	joule	J
power	watt	W
magnetic flux	weber	Wb
magnetic flux density	tesla	T

Factor	Prefix	Symbol
$10^9$	giga	G
$10^6$	mega	M
$10^3$	kilo	k
$10^{-2}$	centi	c
$10^{-3}$	milli	m
$10^{-6}$	micro	$\mu$
$10^{-9}$	nano	n
$10^{-12}$	pico	p

Decimal multiples and submultiples of SI units



# 1.2 Electric Charges

- **Charge** is an electrical property of the atomic particles of which matter consists, measured in **coulombs (C)**.
- The charge **e** on one electron is negative and equal in magnitude to  **$1.602 \times 10^{-19}$  C** which is called as electronic charge. The charges that occur in nature are **integral multiples** of the electronic charge.




# 1.3 Current (1)

- Electric current  $i = dq/dt$ . The unit of ampere can be derived as  $1 \text{ A} = 1\text{C/s}$ .
- A **direct current (dc)** is a current that remains constant with time.
- An **alternating current (ac)** is a current that varies sinusoidally with time.  
(reverse direction)


# 1.3 Current (2)

- The direction of current flow

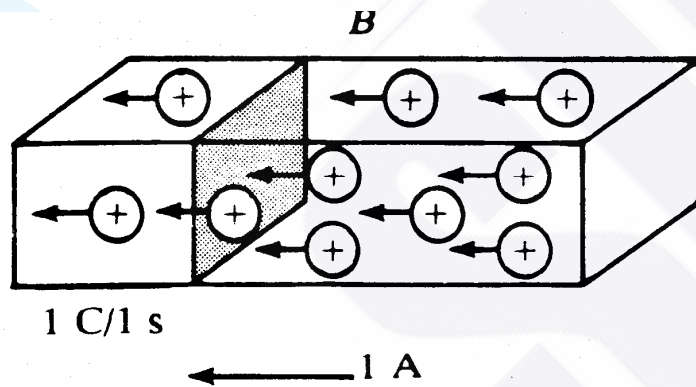

(a)

Positive ions

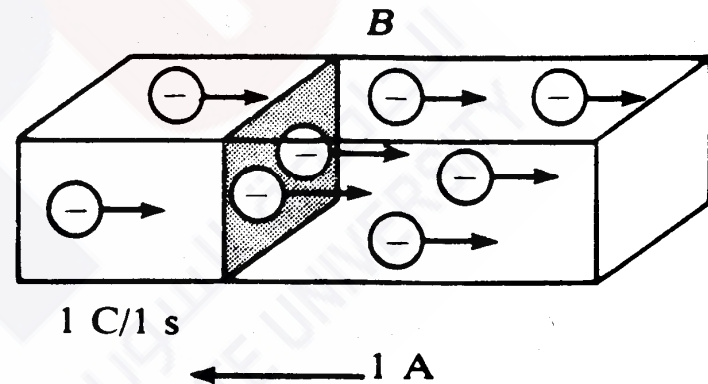

(b)

Negative ions

# 1.3 Current (3)

## Example 1

A conductor has a constant current of 5 A.

How many electrons pass a fixed point on the conductor in one minute?



## 1.3 Current (4)

### Solution

Total no. of charges pass in 1 min is given by  
 $5 \text{ A} = (5 \text{ C/s})(60 \text{ s/min}) = 300 \text{ C/min}$

Total no. of electronics pass in 1 min is given

$$\frac{300 \text{ C/min}}{1.602 \times 10^{-19} \text{ C/electron}} = 1.87 \times 10^{21} \text{ electrons/min}$$


# 1.4 Voltage (1)

- Voltage (or potential difference) is the **energy** required to move a **unit charge** through an element, measured in volts (V).
- Mathematically,  $v_{ab} = dw / dq$  (volt)
  - $w$  is energy in joules (J) and  $q$  is charge in coulomb (C).
- Electric voltage,  $v_{ab}$ , is always **across the circuit element** or **between two points in a circuit**.
  - $v_{ab} > 0$  means the potential of **a** is higher than potential of **b**.
  - $v_{ab} < 0$  means the potential of **a** is lower than potential of **b**.
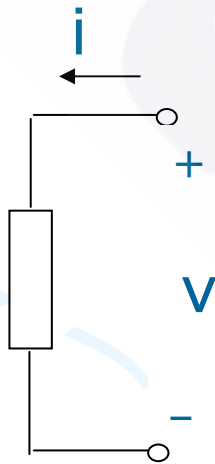
# 1.5 Power and Energy (1)


- Power is the time rate of expending or absorbing energy, measured in watts (W).

- Mathematical expression: 
$$p = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = vi$$



**$P = +vi$**   
**absorbing power**

**Passive sign convention**

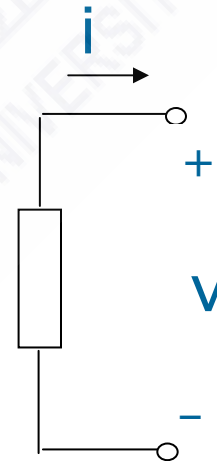

**$p = -vi$**   
**supplying power**

# 1.5 Power and Energy (2)

- The law of conservation of energy

$$\sum p = 0$$


- Energy is the capacity to do work, measured in joules (J).

- Mathematical expression  $w = \int_{t_0}^t p dt = \int_{t_0}^t v i dt$

# 1.6 Circuit Elements (1)

## Active Elements

## Passive Elements

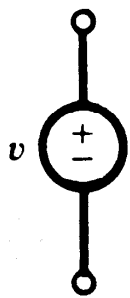

(a)



(b)



(c)



(d)



(e)



(f)



(g)

Independent sources      Dependant sources

- A dependent source is an active element in which the source quantity is controlled by another voltage or current.
- They have four different types: VCVS, CCVS, VCCS, CCCS. Keep in mind the signs of dependent sources.

# 1.6 Circuit Elements (2)

## Example 2

Obtain the voltage  $v$  in the branch shown in Figure 2.1.1P for  $i_2 = 1\text{A}$ .

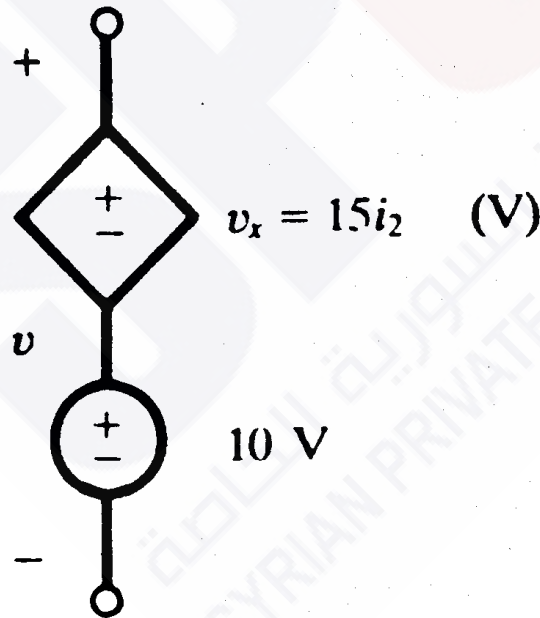


Figure 2.1.1P

## 1.6 Circuit Elements (3)

### Solution

Voltage  $v$  is the sum of the current-independent 10-V source and the current-dependent voltage source  $v_x$ .

Note that the factor 15 multiplying the control current carries the units  $\Omega$ .

$$\text{Therefore, } v = 10 + v_x = 10 + 15(1) = 25 \text{ V}$$