

The background features several large, colorful, abstract swirls in shades of purple, green, and blue. Interspersed among these are numerous small, yellow, triangular shapes that resemble rays of light or sparks. The overall aesthetic is bright and dynamic.

EE2003

Circuit Theory

Chapter 2

Basic Laws

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Basic Laws - Chapter 2

2.1 Ohm's Law.

2.2 Nodes, Branches, and Loops.

2.3 Kirchhoff's Laws.

2.4 Series Resistors and Voltage Division.

2.5 Parallel Resistors and Current Division.


2.6 Wye-Delta Transformations.

2.1 Ohms Law (1)

- Ohm's law states that the voltage across a resistor is directly proportional to the current I flowing through the resistor.
- Mathematical expression for Ohm's Law is as follows:

$$v = iR$$

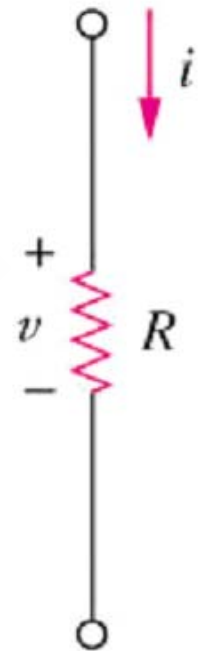- Two extreme possible values of R : **0 (zero)** and ∞ (**infinite**) are related with two basic circuit concepts: **short circuit** and **open circuit**.



2.1 Ohms Law (2)

- Conductance is the ability of an element to conduct electric current; it is the reciprocal of resistance R and is measured in mhos or siemens.

$$G = \frac{1}{R} = \frac{i}{v}$$

- The power dissipated by a resistor:

$$p = vi = i^2 R = \frac{v^2}{R}$$


2.2 Nodes, Branches and Loops (1)

- A **branch** represents a single element such as a voltage source or a resistor.
- A **node** is the point of connection between two or more branches.
- A **loop** is any closed path in a circuit.
- A network with b branches, n nodes, and l independent loops will satisfy the fundamental theorem of network topology:


$$b = l + n - 1$$

2.2 Nodes, Branches and Loops (2)

Example 1

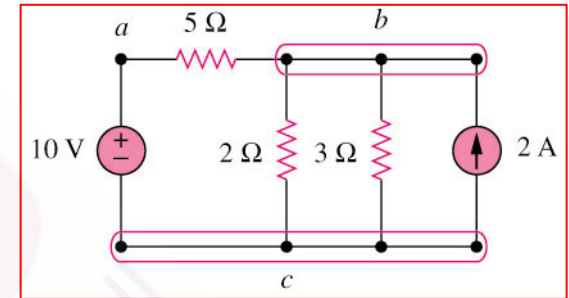

Original circuit

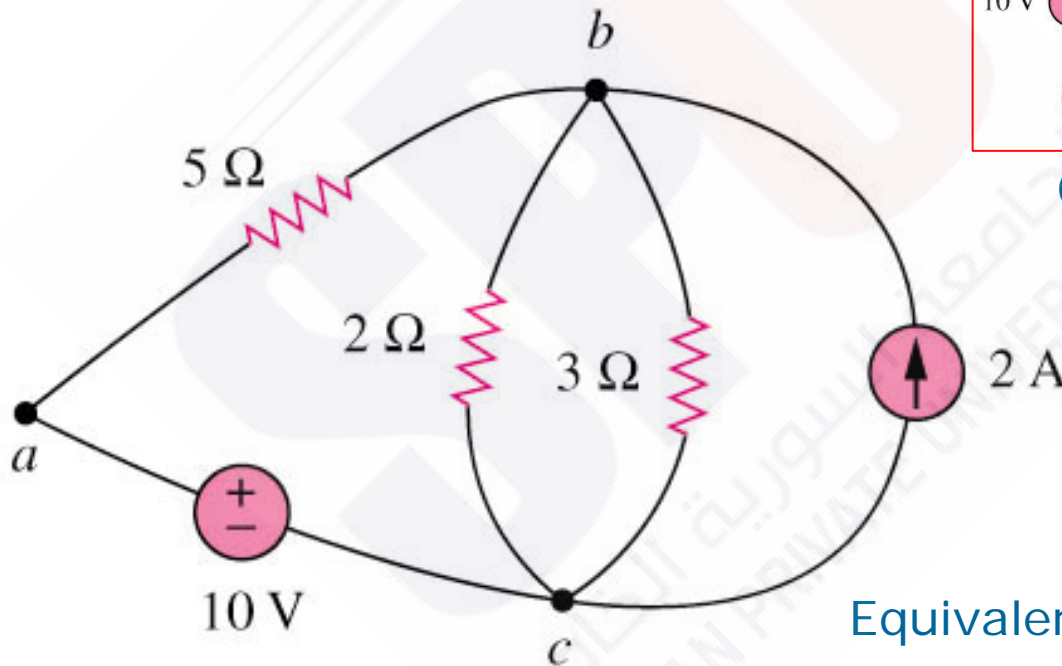


Equivalent circuit

How many branches, nodes and loops are there?

2.2 Nodes, Branches and Loops (3)

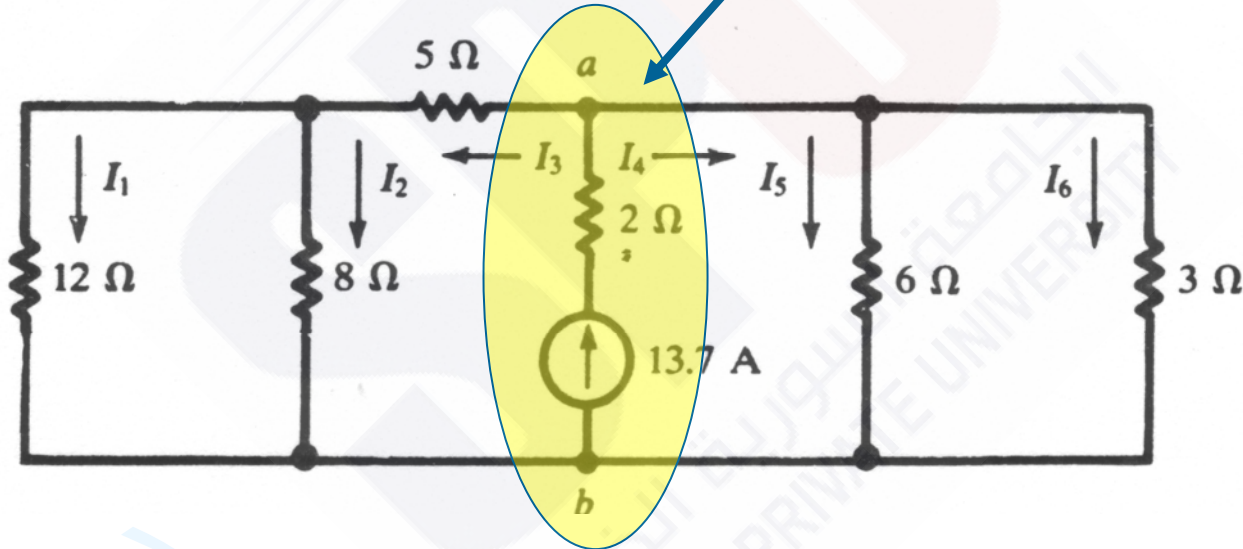Example 2


Should we consider it as one branch or two branches?



How many branches, nodes and loops are there?

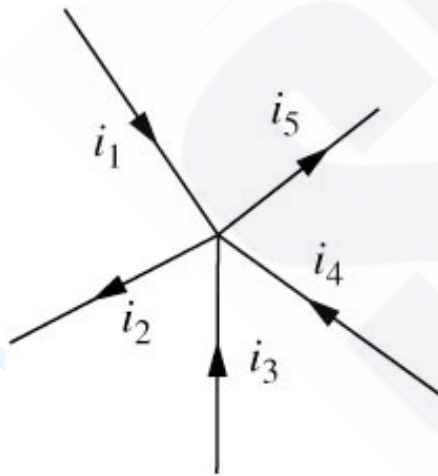
2.3 Kirchhoff's Laws (1)

- Kirchhoff's current law (KCL) states that the algebraic sum of currents entering a node (or a closed boundary) is zero.



Mathematically,


$$\sum_{n=1}^N i_n = 0$$

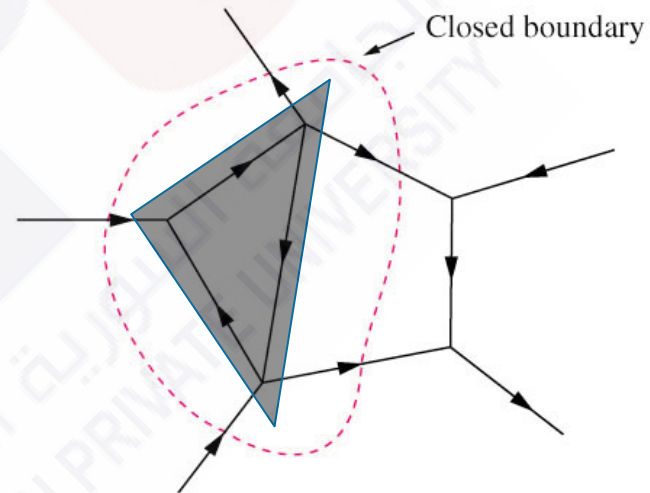

2.3 Kirchhoff's Laws (2)

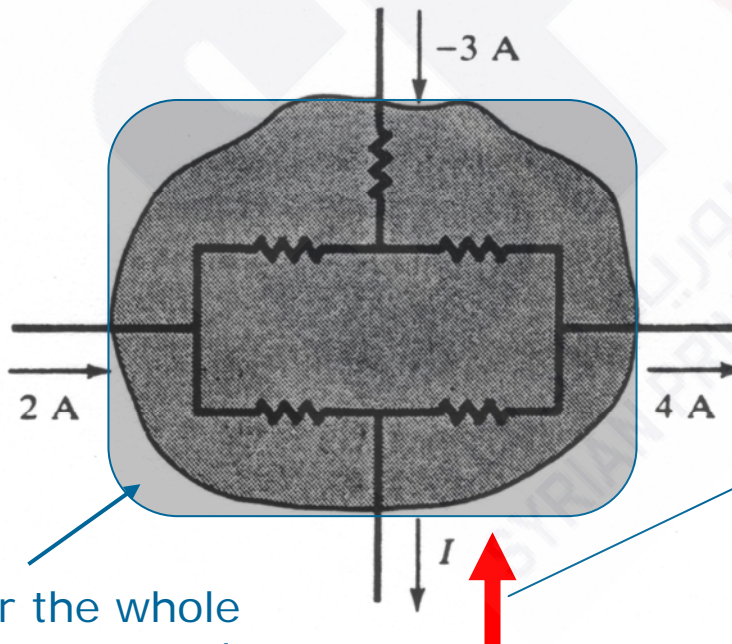Example 4

- Determine the current I for the circuit shown in the figure below.




$$I + 4 - (-3) - 2 = 0$$
$$\Rightarrow I = -5\text{A}$$

This indicates that the actual current for I is flowing in the opposite direction.

We can consider the whole enclosed area as one "node".

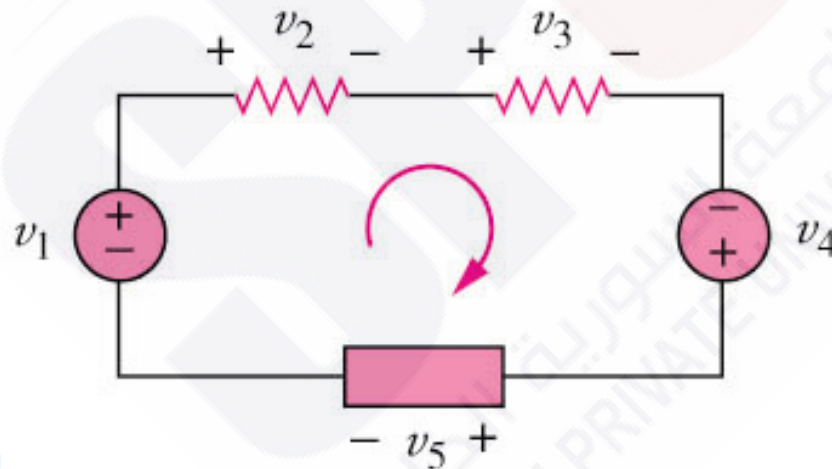2.3 Kirchhoff's Laws (3)

- Kirchhoff's voltage law (KVL) states that the algebraic sum of all voltages around a closed path (or loop) is zero.




Mathematically,

$$\sum_{m=1}^M v_n = 0$$

2.3 Kirchhoff's Laws (4)

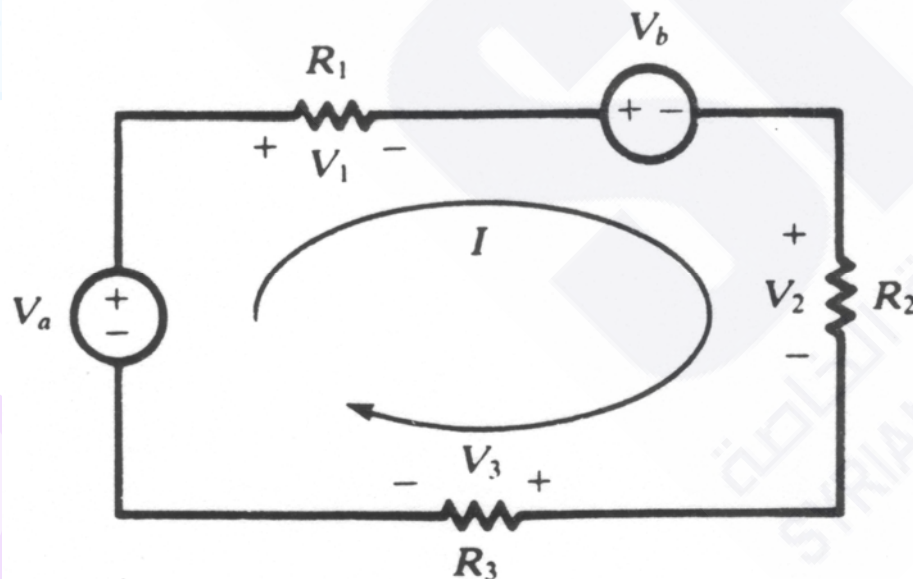Example 5

- Applying the KVL equation for the circuit of the figure below.



$$V_a - V_1 - V_b - V_2 - V_3 = 0$$

$$V_1 = IR_1 \quad V_2 = IR_2 \quad V_3 = IR_3$$

$$\Rightarrow V_a - V_b = I(R_1 + R_2 + R_3)$$

$$I = \frac{V_a - V_b}{R_1 + R_2 + R_3}$$

2.4 Series Resistors and Voltage Division (1)

- Series: Two or more elements are in series if they are cascaded or connected sequentially and consequently carry the same current.
- The equivalent resistance of any number of resistors connected in a series is the sum of the individual resistances.


$$R_{eq} = R_1 + R_2 + \dots + R_N = \sum_{n=1}^N R_n$$

- The voltage divider can be expressed as

$$v_n = \frac{R_n}{R_1 + R_2 + \dots + R_N} v$$

2.4 Series Resistors and Voltage Division (1)

Example 3

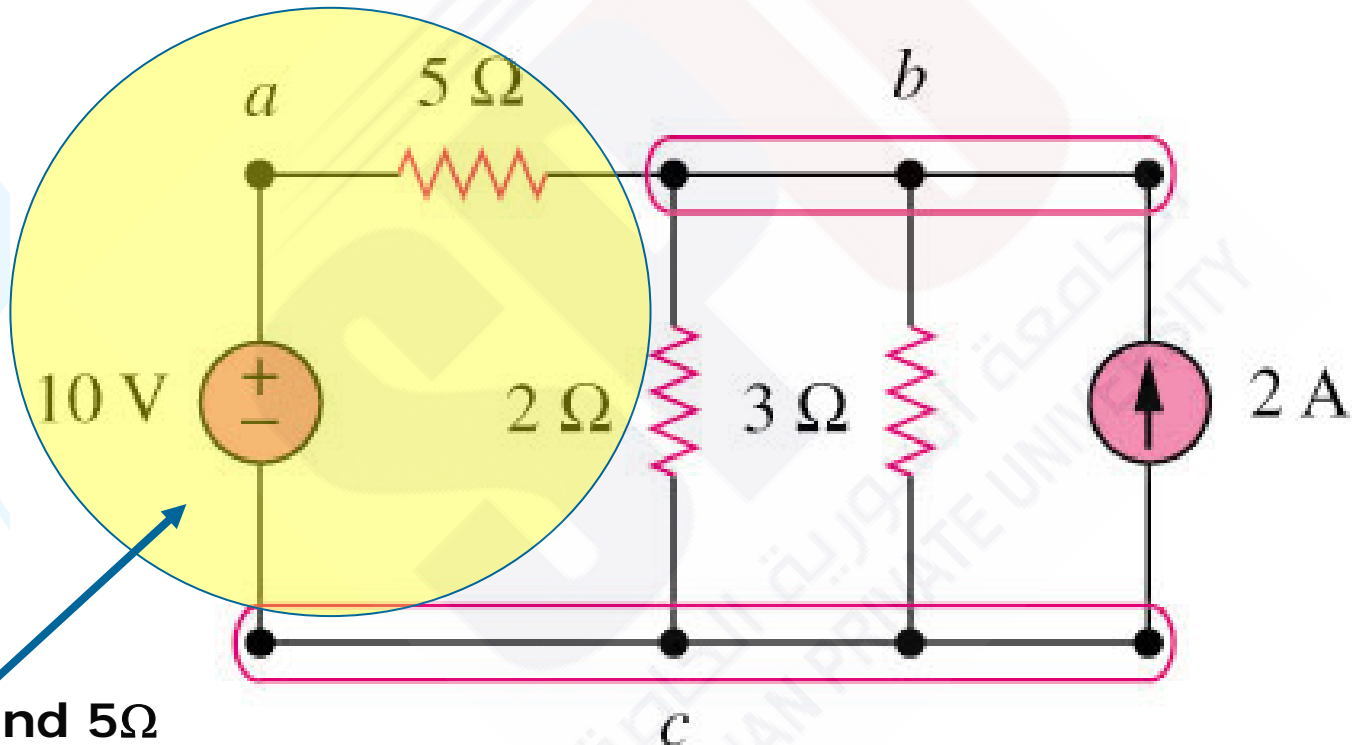

10V and 5Ω
are in series

2.5 Parallel Resistors and Current Division (1)

- Parallel: Two or more elements are in parallel if they are connected to the same two nodes and consequently have the same voltage across them.
- The equivalent resistance of a circuit with N resistors in parallel is:


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

- The total current i is shared by the resistors in inverse proportion to their resistances. The current divider can be expressed as:

$$i_n = \frac{v}{R_n} = \frac{iR_{eq}}{R_n}$$

2.5 Parallel Resistors and Current Division (1)

Example 4

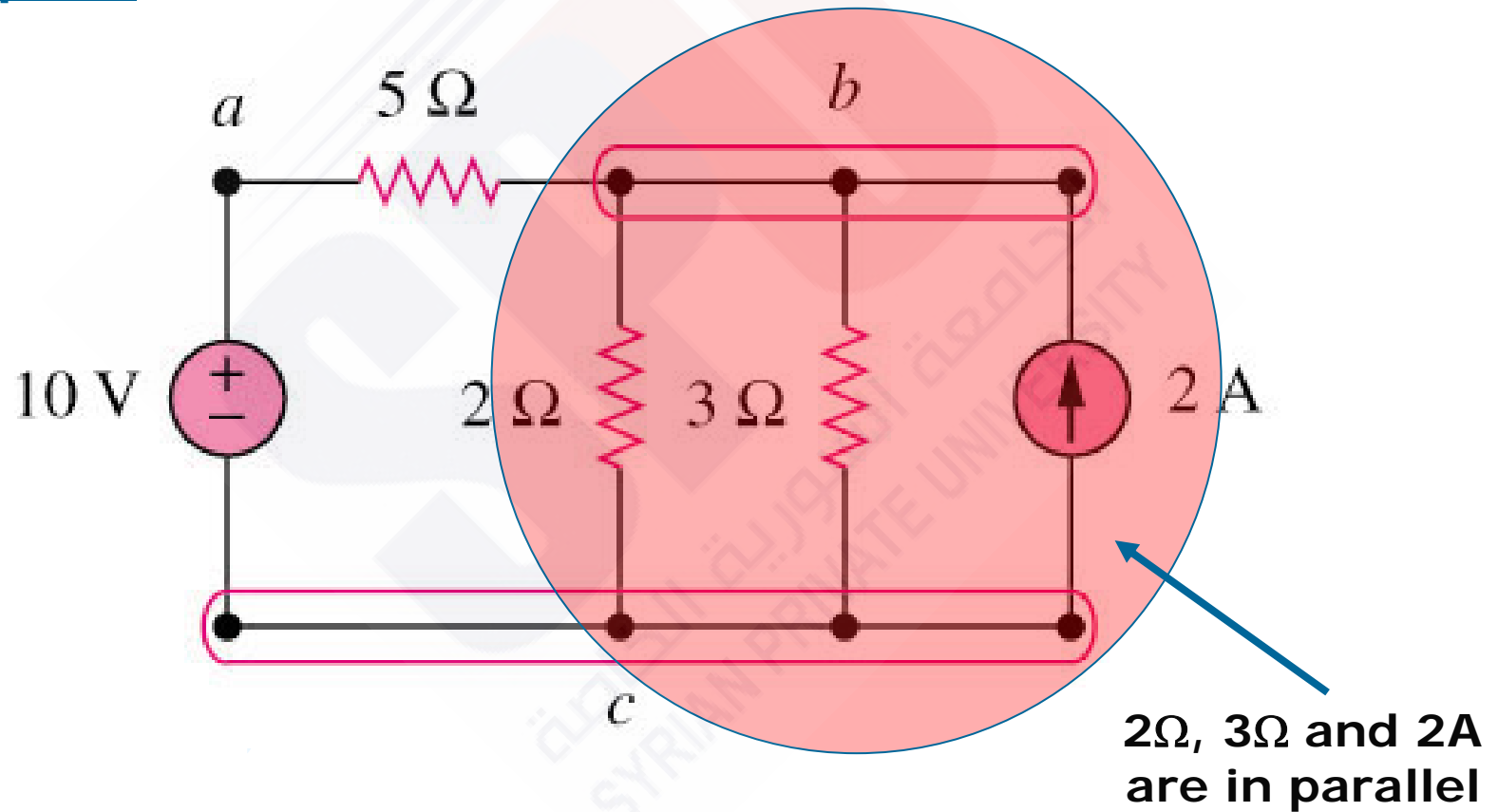


2.6 Wye-Delta Transformations

Delta -> Star

$$R_1 = \frac{R_b R_c}{(R_a + R_b + R_c)}$$

$$R_2 = \frac{R_c R_a}{(R_a + R_b + R_c)}$$
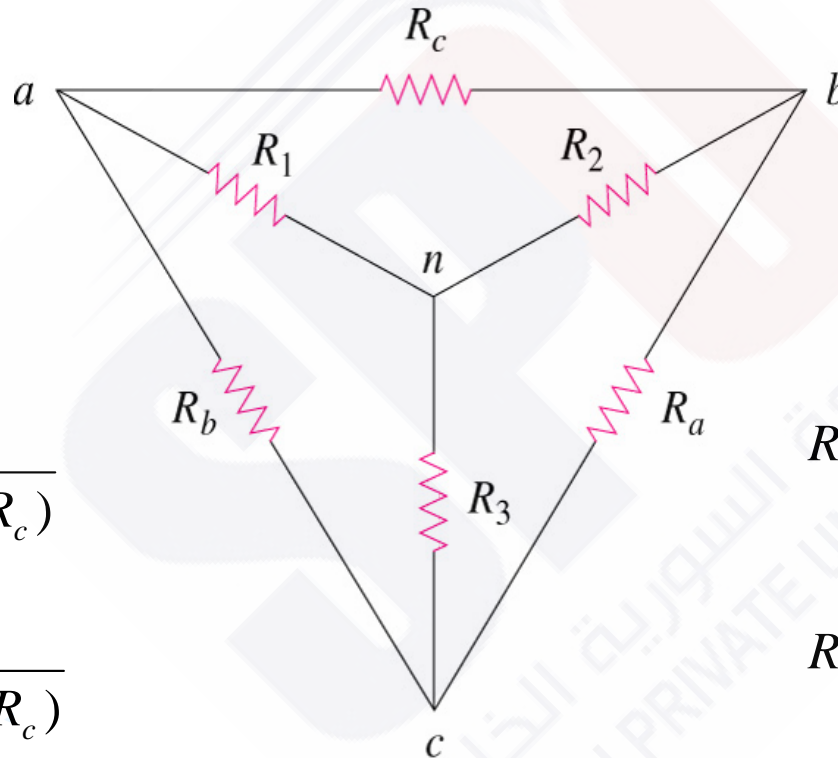
$$R_3 = \frac{R_a R_b}{(R_a + R_b + R_c)}$$



Star -> Delta

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$