

# EE2003 Circuit Theory

## Chapter 7 First-Order Circuits

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




# First-Order Circuits

## Chapter 7

- 7.1 The Source-Free RC Circuit
- 7.2 The Source-Free RL Circuit
- 7.3 Unit-step Function
- 7.4 Step Response of an RC Circuit
- 7.5 Step Response of an RL Circuit
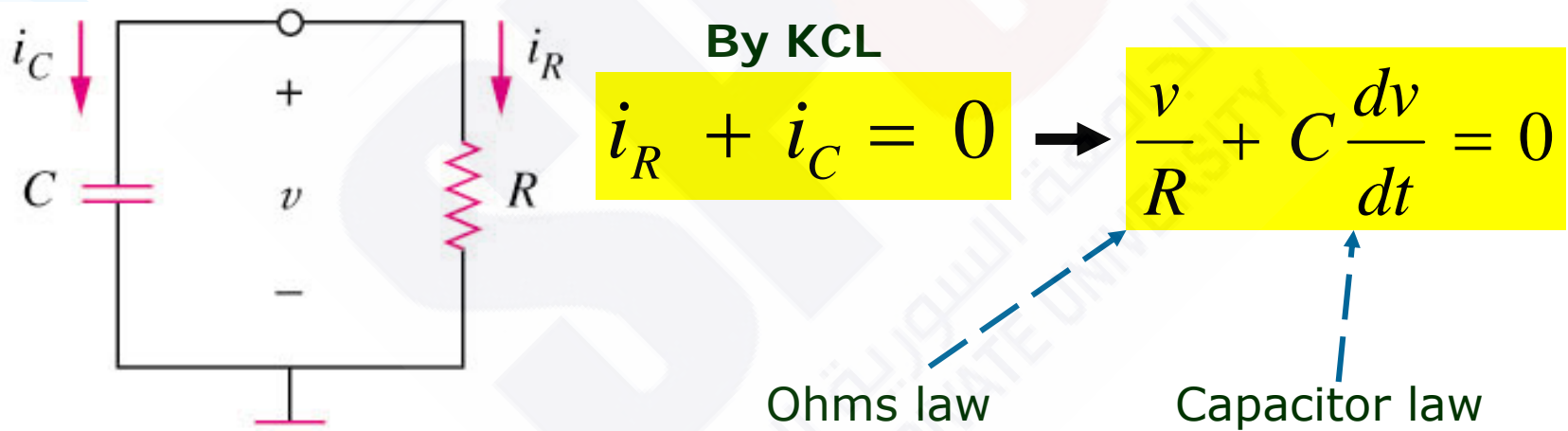
# 7.1 The Source-Free RC Circuit (1)


- A **first-order circuit** is characterized by a first-order differential equation.



- Apply Kirchhoff's laws to purely resistive circuit results in algebraic equations.
- Apply the laws to RC and RL circuits produces differential equations.
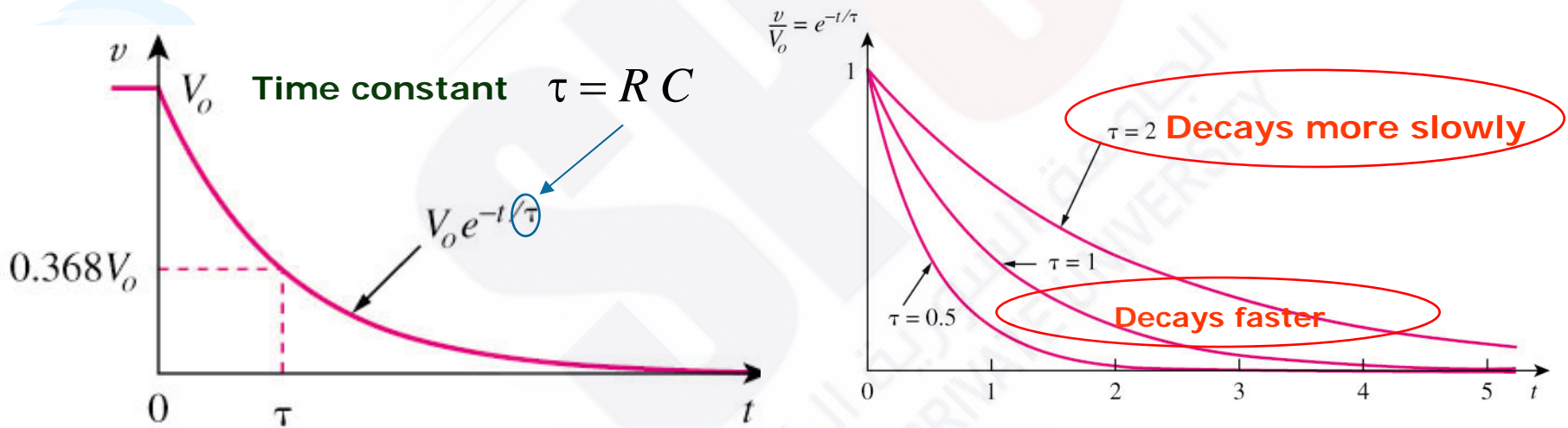
# 7.1 The Source-Free RC Circuit (2)

- The **natural response** of a circuit refers to the behavior (in terms of voltages and currents) of the circuit itself, with no external sources of excitation.




- The **time constant**  $\tau$  of a circuit is the time required for the response to decay by a factor of  $1/e$  or 36.8% of its initial value.
- $v$  decays **faster** for small  $\tau$  and **slower** for large  $\tau$ .
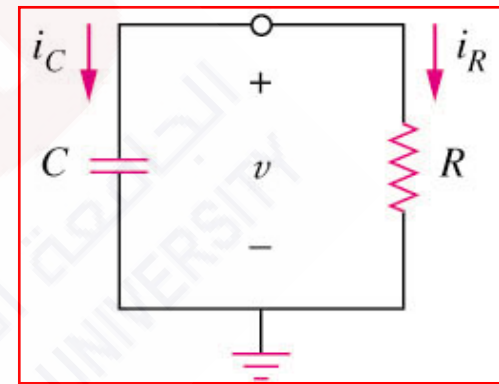
# 7.1 The Source-Free RC Circuit (3)

The key to working with a source-free RC circuit is finding:

$$v(t) = V_0 e^{-t/\tau} \quad \text{where} \quad \tau = RC$$




1. The initial voltage  $v(0) = V_0$  across the capacitor.
2. The time constant  $\tau = RC$ .

# 7.1 The Source-Free RC Circuit (4)

## Example 1

Refer to the circuit below, determine  $v_C$ ,  $v_x$ , and  $i_o$  for  $t \geq 0$ .

Assume that  $v_C(0) = 30$  V.

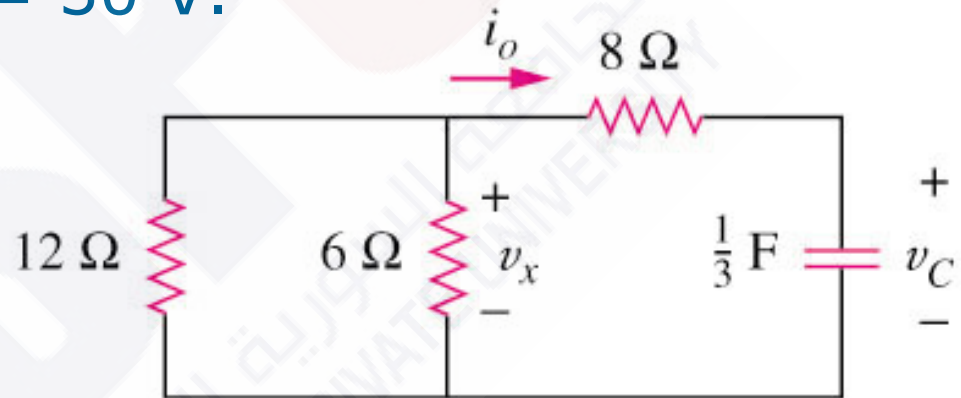


- Please refer to lecture or textbook for more detail elaboration.

Answer:  $v_C = 30e^{-0.25t}$  V ;  $v_x = 10e^{-0.25t}$  ;  $i_o = -2.5e^{-0.25t}$  A

# 7.1 The Source-Free RC Circuit (5)
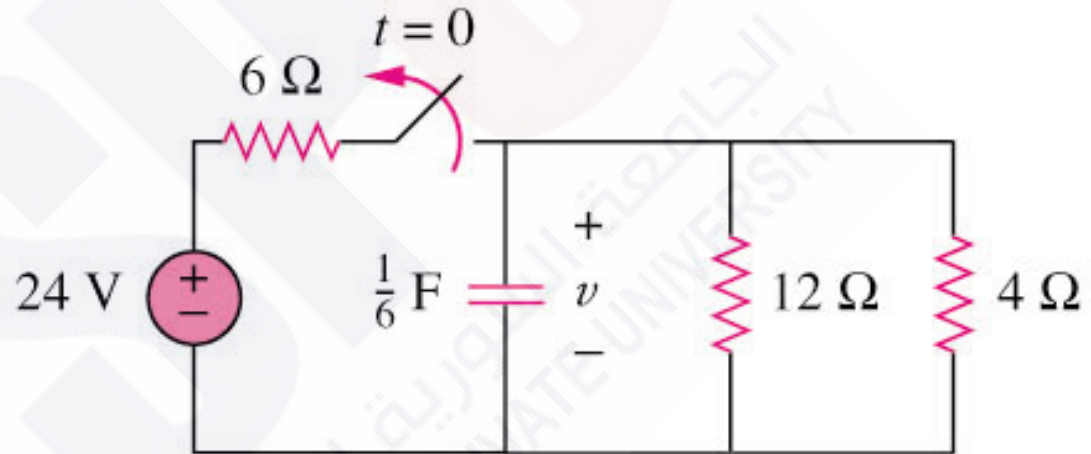
## Example 2

The switch in circuit below is opened at  $t = 0$ , find  $v(t)$  for  $t \geq 0$ .




- Please refer to lecture or textbook for more detail elaboration.

Answer:  $V(t) = 8e^{-2t} \text{ V}$
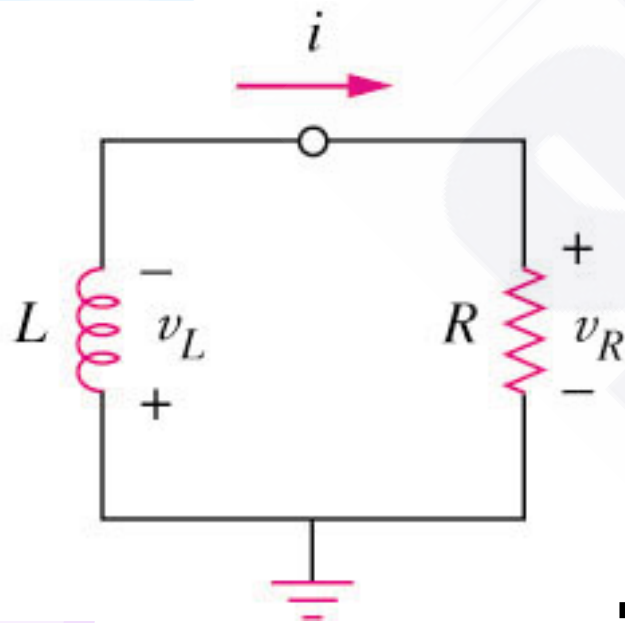
# 7.2 The Source-Free RL Circuit (1)

- A **first-order RL circuit** consists of a inductor  $L$  (or its equivalent) and a resistor (or its equivalent)



By KVL

$$v_L + v_R = 0$$

$$L \frac{di}{dt} + iR = 0$$

Inductors law


Ohms law

$$\frac{di}{i} = -\frac{R}{L} dt$$

$$i(t) = I_0 e^{-Rt/L}$$



## 7.2 The Source-Free RL Circuit (2)

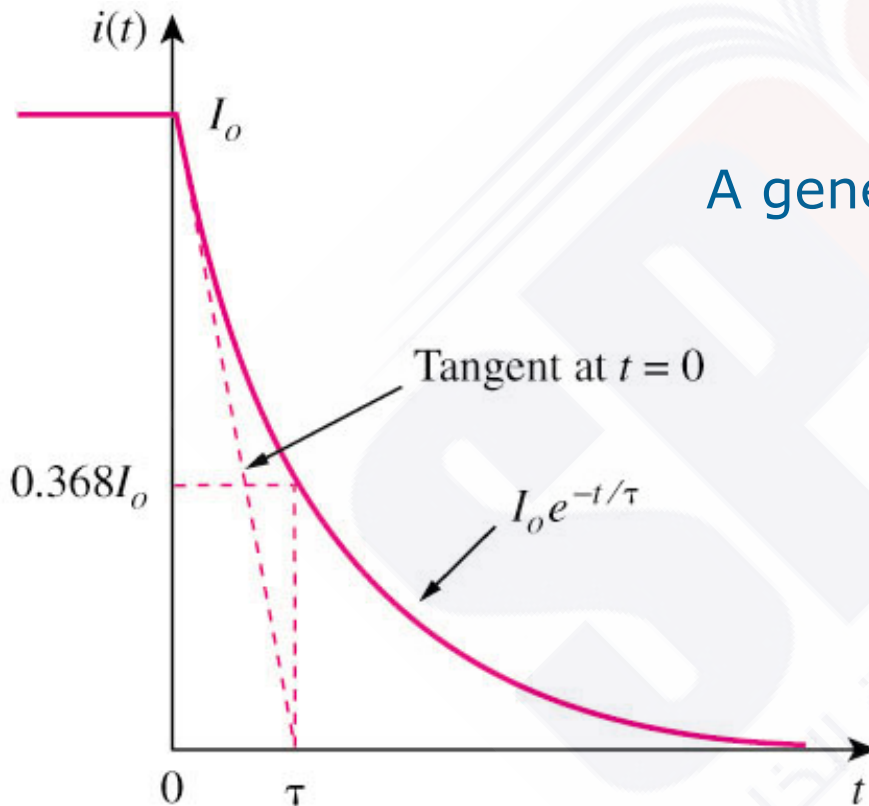

A general form representing a RL

$$i(t) = I_0 e^{-t/\tau}$$

where  $\tau = \frac{L}{R}$


- The **time constant**  $\tau$  of a circuit is the time required for the response to decay by a factor of  $1/e$  or 36.8% of its initial value.
- $i(t)$  decays **faster for small  $\tau$**  and **slower for large  $\tau$** .
- The general form is **very similar** to a RC source-free circuit.

# 7.2 The Source-Free RL Circuit (3)
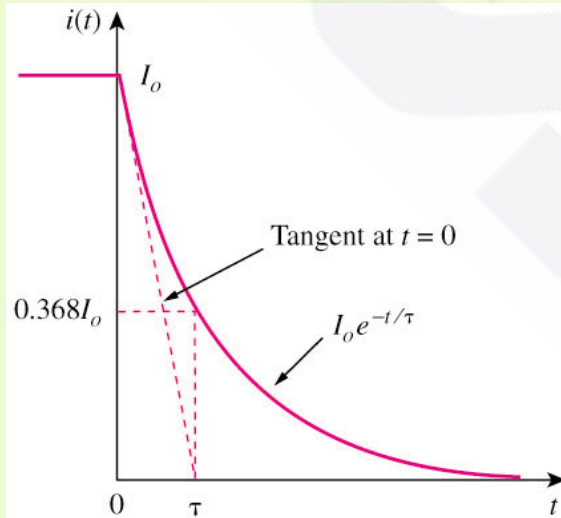
## Comparison between a RL and RC circuit


A RL source-free circuit

$$i(t) = I_0 e^{-t/\tau} \quad \text{where} \quad \tau = \frac{L}{R}$$



A RC source-free circuit

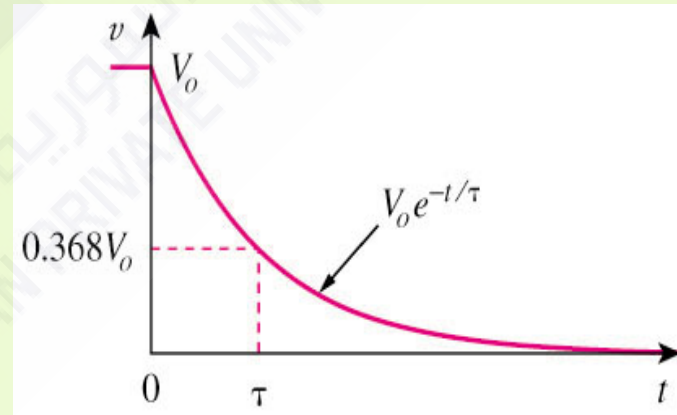
$$v(t) = V_0 e^{-t/\tau} \quad \text{where} \quad \tau = RC$$


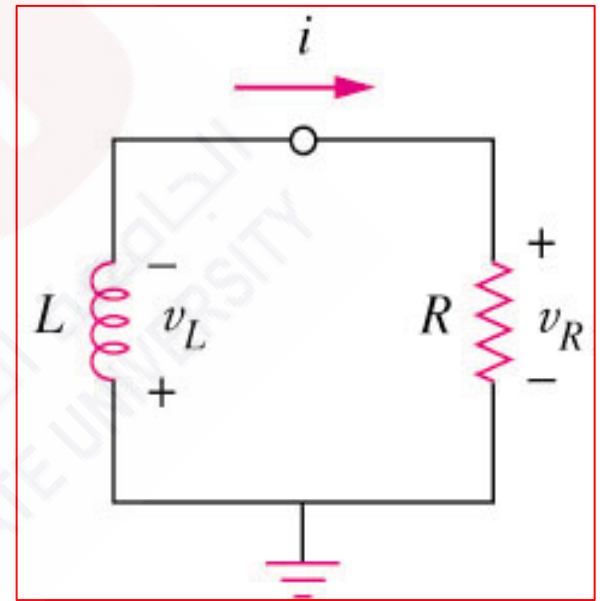
## 7.2 The Source-Free RL Circuit (4)

The key to working with a source-free RL circuit is finding:

$$i(t) = I_0 e^{-t/\tau} \quad \text{where} \quad \tau = \frac{L}{R}$$




1. The initial voltage  $i(0) = I_0$  through the inductor.
2. The time constant  $\tau = L/R$ .

## 7.2 The Source-Free RL Circuit (5)

### Example 3

Find  $i$  and  $v_x$  in the circuit.

Assume that  $i(0) = 5$  A.

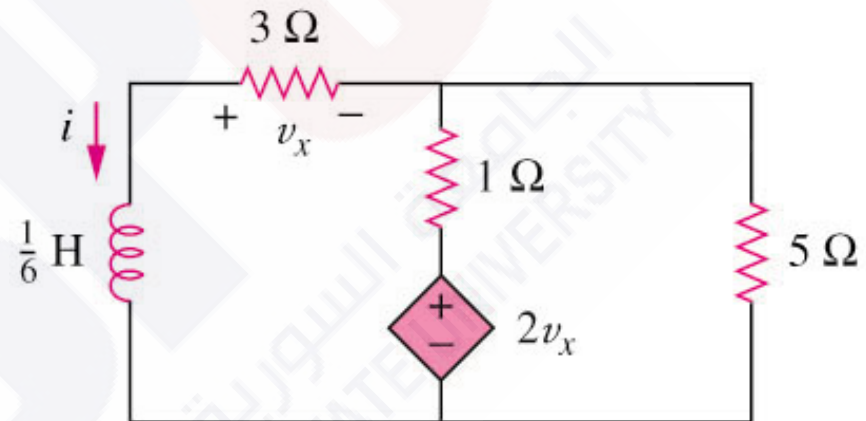


- Please refer to lecture or textbook for more detail elaboration.

Answer:  $i(t) = 5e^{-53t}$  A

## 7.2 The Source-Free RL Circuit (6)
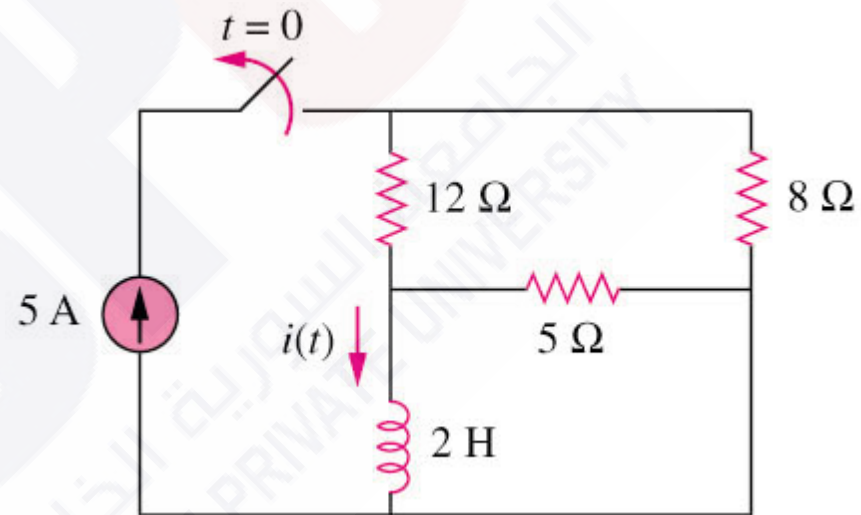
### Example 4

For the circuit, find  $i(t)$  for  $t > 0$ .




- Please refer to lecture or textbook for more detail elaboration.

Answer:  $i(t) = 2e^{-2t} \text{ A}$

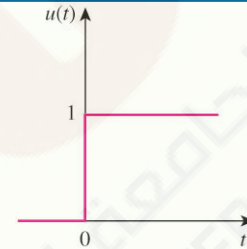
# 7.3 Unit-Step Function (1)

- The **unit step function**  $u(t)$  is 0 for negative values of  $t$  and 1 for positive values of  $t$ .


$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$


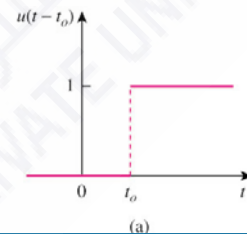
$$u(t - t_o) = \begin{cases} 0, & t < t_o \\ 1, & t > t_o \end{cases}$$



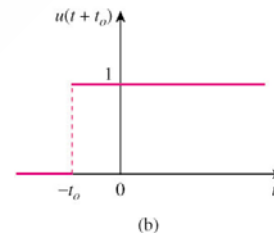
$$u(t + t_o) = \begin{cases} 0, & t < -t_o \\ 1, & t > -t_o \end{cases}$$




# 7.3 Unit-Step Function (2)

Represent an abrupt change for:

1. voltage source.

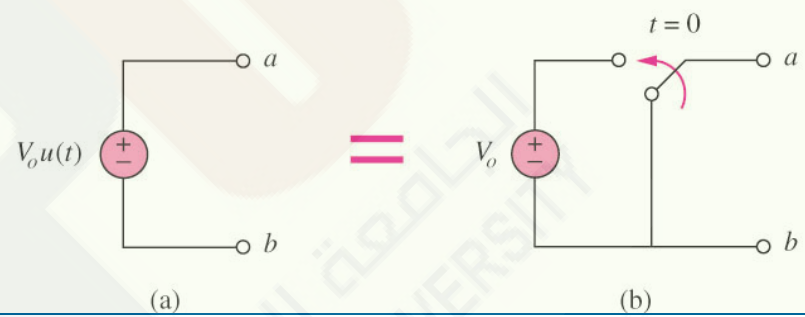


2. for current source:

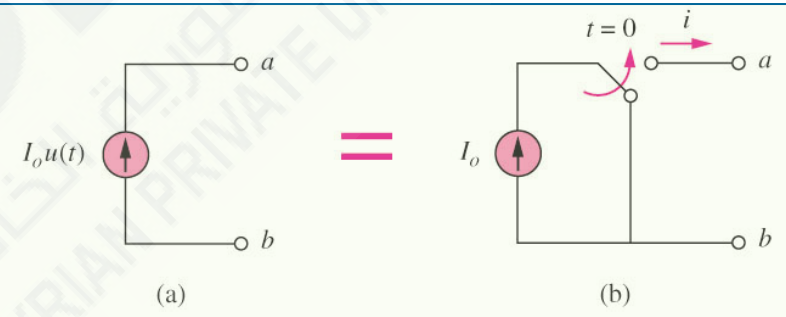
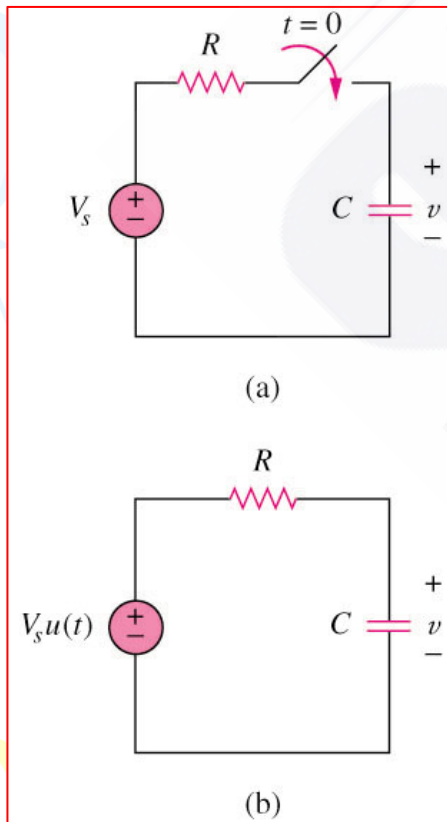
# 7.4 The Step-Response of a RC Circuit (1)

- The **step response** of a circuit is its behavior when the excitation is the step function, which may be a voltage or a current source.



- Initial condition:**

$$v(0^-) = v(0^+) = V_0$$

- Applying KCL,

$$C \frac{dv}{dt} + \frac{v - V_s u(t)}{R} = 0$$

or


$$\frac{dv}{dt} = -\frac{v - V_s}{RC} u(t)$$

- Where  $u(t)$  is the unit-step function


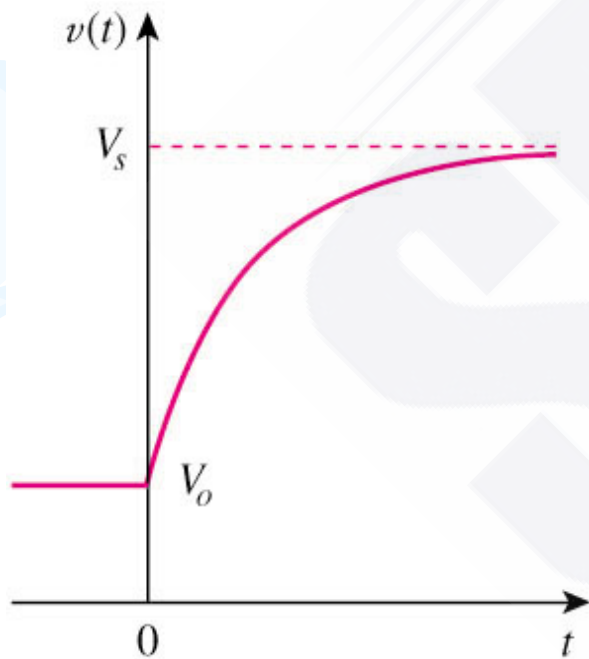
# 7.4 The Step-Response of a RC Circuit (2)

- Integrating both sides and considering the initial conditions, the solution of the equation is:



$$v(t) = \begin{cases} V_0 & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$

Final value  
at  $t \rightarrow \infty$

Initial value  
at  $t = 0$

Source-free  
Response

$$\begin{aligned} \text{Complete Response} &= \text{Natural response (stored energy)} + \text{Forced Response (independent source)} \\ &= V_0 e^{-t/\tau} + V_s (1 - e^{-t/\tau}) \end{aligned}$$

## 7.4 The Step-Response of a RC Circuit (3)

Three steps to find out the step response of an RC circuit:

1. The initial capacitor voltage  $v(0)$ .
2. The final capacitor voltage  $v(\infty)$  — DC voltage across C.
3. The time constant  $\tau$ .


$$v(t) = v(\infty) + [v(0+) - v(\infty)]e^{-t/\tau}$$

Note: The above method is a short-cut method. You may also determine the solution by setting up the circuit formula directly using KCL, KVL, ohms law, capacitor and inductor VI laws.

# 7.4 The Step-Response of a RC Circuit (4)
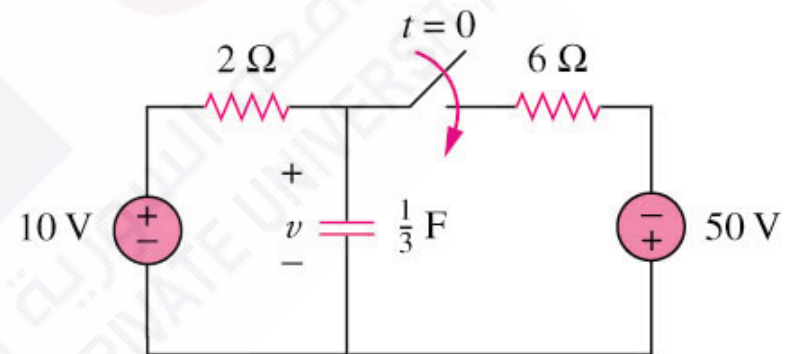
## Example 5

Find  $v(t)$  for  $t > 0$  in the circuit in below. Assume the switch has been open for a long time and is closed at  $t = 0$ . Calculate  $v(t)$  at  $t = 0.5$ .




- Please refer to lecture or textbook for more detail elaboration.

Answer:  $v(t) = 15e^{-2t} - 5$  and  $v(0.5) = 0.5182V$
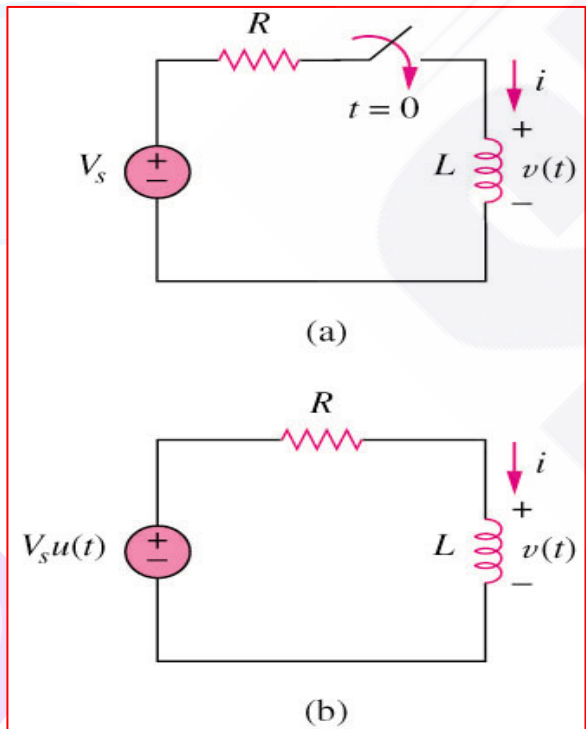
# 7.5 The Step-response of a RL Circuit (1)

- The **step response** of a circuit is its behavior when the excitation is the step function, which may be a voltage or a current source.



- Initial current**  
 $i(0^-) = i(0^+) = I_o$
- Final inductor current**  
 $i(\infty) = V_s/R$
- Time constant  $\tau = L/R$

$$i(t) = \frac{V_s}{R} + \left( I_o - \frac{V_s}{R} \right) e^{-\frac{t}{\tau}} u(t)$$

## 7.5 The Step-Response of a RL Circuit (2)

Three steps to find out the step response of an RL circuit:

1. The initial inductor current  $i(0)$  at  $t = 0+$ .
2. The final inductor current  $i(\infty)$ .
3. The time constant  $\tau$ .

$$i(t) = i(\infty) + [i(0+) - i(\infty)] e^{-t/\tau}$$


Note: The above method is a short-cut method. You may also determine the solution by setting up the circuit formula directly using KCL, KVL, ohms law, capacitor and inductor VI laws.

# 7.5 The Step-Response of a RL Circuit (4)

## Example 6

The switch in the circuit shown below has been closed for a long time. It opens at  $t = 0$ .

Find  $i(t)$  for  $t > 0$ .

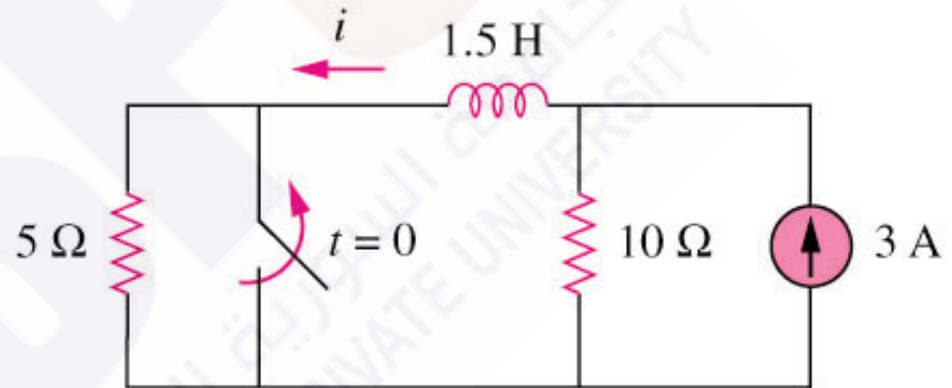

- Please refer to lecture or textbook for more detail elaboration.

Answer:  $i(t) = 2 + e^{-10t}$