

Electronic Circuits-1

Prof.Dr.Eng.Ahmad Rateb Al-Najjar

CONTENT

1. BJT Amplifier
2. FET Amplifier
3. Frequency Response of Amplifier
4. Operational Amplifier
- 5. Audio Power Amplifier**
6. Linear-Digital ICs
7. Power Supplies
8. IC Technology (optional)

Chapter 6: Audio Power Amplifier

6.1 Introduction

6.2 Series-Fed Class-A Amplifier

6.3 Transformer-Coupled Class-A amplifier

6.4 Class-B Amplifier Operation

6.5 Class-B Amplifier Circuits

6.6 Amplifier Distortion

6.7 Power Transistor Heat Sinking

6.8 Class-C and Class-D Amplifiers

6.1 Introduction

Voltage Amplifier:


Small swing, Power efficiency & Power handling are of little concern

Power Amplifier: Large swing, Power efficiency, Power handling and Impedance matching are the main Concern.


Characterizing Power Amp By classes: A, AB, B, C, D.

Amp Classes represent the amount of O/P signal varies over one cycle of operation for a full cycle of I/P signal.

6.1 Introduction

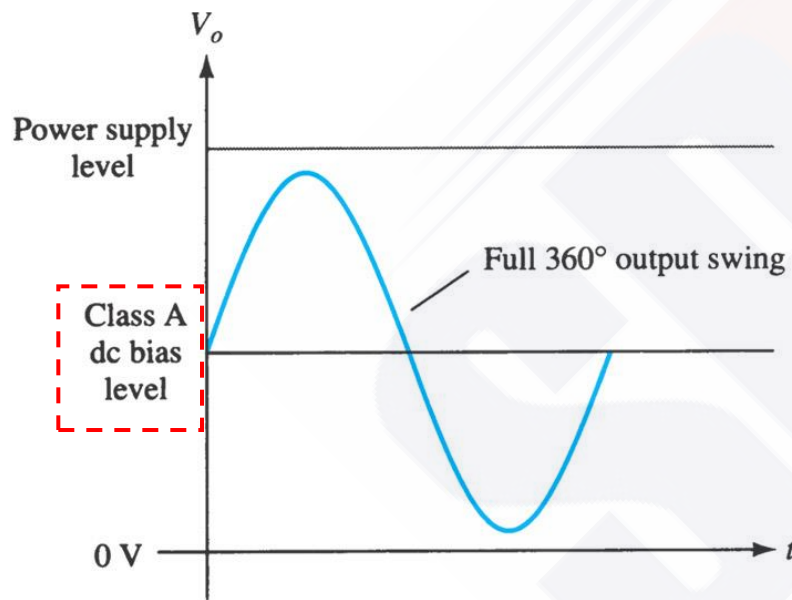

(a)

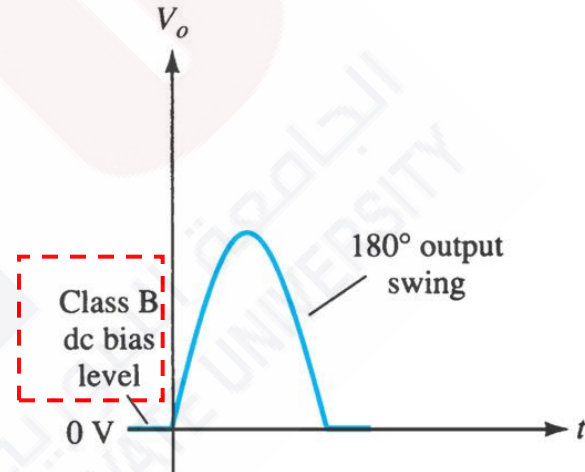

(b)

Amplifier operating classes

Comparison of Amplifier Classes

Amplifier Class	A	AB	B	C	D
Power Cycle	360°	180° to 360°	180°	Less than 180°	Pulse Operation
Power Efficiency	25% to 50%	Between 25% (50%) and 78.5%	78.5%	Better than 78.5%	Over 90%

The input power from the voltage supply is

$$P_i(\text{dc}) = V_{CC}I_{CQ}$$

The power developed across the load

(R_C) by the ac signal can be expressed in a number of ways.

$$\begin{aligned} P_o(\text{ac}) &= I_C^2(\text{rms})R_C = \frac{V_{CE}^2(\text{rms})}{R_C} \\ &= \left(\frac{I_C(\text{peak})}{\sqrt{2}}\right)^2 R_C = \frac{V_{CE}^2(\text{peak})}{2R_C} \\ &= \frac{I_C^2(\text{p-p})R_C}{8} = \frac{V_{CE}^2(\text{p-p})}{8R_C} \end{aligned}$$

$$\text{maximum } V_{CE}(\text{p-p}) = V_{CC}$$

$$\text{maximum } I_C(\text{p-p}) = \frac{V_{CC}}{R_C}$$

$$\text{maximum } P_o(\text{ac}) = \frac{I_C(\text{p-p})V_{CE}(\text{p-p})}{8} = \frac{(V_{CC}/R_C)V_{CC}}{8} = \frac{V_{CC}^2}{8R_C}$$

For the quiescent point of

$$I_C = \frac{V_{CC}/R_C}{2}$$

the dc power from the supply voltage is

$$\text{maximum } P_i(\text{dc}) = V_{cc} I_C = V_{cc} \left(\frac{V_{cc}}{2R_C} \right) = \frac{V_{cc}^2}{2R_C}$$

The efficiency of an amplifier given by Eq. (12.7) can be calculated for the maximum conditions as

$$\begin{aligned} \text{maximum } \% \eta &= \frac{\text{max } P_o(\text{ac})}{\text{max } P_i(\text{dc})} \times 100\% \\ &= \frac{V_{cc}^2/8R_C}{V_{cc}^2/2R_C} \times 100\% = 25\% \end{aligned}$$

$$\begin{aligned}
 P_o(\text{ac}) &= I_C(\text{rms})V_{CE}(\text{rms}) \\
 &= \frac{I_C(\text{peak})}{\sqrt{2}} \frac{V_{CE}(\text{peak})}{\sqrt{2}} \\
 &= \frac{I_C(\text{peak})V_{CE}(\text{peak})}{2} \\
 &= \frac{I_C(\text{p-p})}{2\sqrt{2}} \frac{V_{CE}(\text{p-p})}{2\sqrt{2}}
 \end{aligned}$$

$$P_o(\text{ac}) = \frac{I_C(\text{p-p})V_{CE}(\text{p-p})}{8}$$

Assuming that all the power not delivered to the load must be dissipated by the transistor,

$$P_{\text{transistor}} = P_Q = P_i(\text{dc}) - P_o(\text{ac})$$

(12.8)

Using RMS signals. The ac power delivered to the load (R_C) may be expressed using

$$P_o(\text{ac}) = V_{CE(\text{rms})}I_C(\text{rms}) \quad (12.5\text{a})$$

$$P_o(\text{ac}) = I_C^2(\text{rms})R_C \quad (12.5\text{b})$$

$$P_o(\text{ac}) = \frac{V_C^2(\text{rms})}{R_C} \quad (12.5\text{c})$$

Using peak signals. The ac power delivered to the load may be expressed using

$$P_o(\text{ac}) = \frac{V_{CE(\text{p})}I_C(\text{p})}{2} \quad (12.6\text{a})$$

$$P_o(\text{ac}) = \frac{I_C^2(\text{p})}{2} R_C \quad (12.6\text{b})$$

$$P_o(\text{ac}) = \frac{V_{CE(\text{p})}^2}{2R_C} \quad (12.6\text{c})$$


Using peak-to-peak signals. The ac power delivered to the load may be expressed using

$$P_o(\text{ac}) = \frac{V_{CE(\text{p-p})}I_C(\text{p-p})}{8} \quad (12.7\text{a})$$

$$P_o(\text{ac}) = \frac{I_C^2(\text{p-p})}{8} R_C \quad (12.7\text{b})$$

$$P_o(\text{ac}) = \frac{V_{CE(\text{p-p})}^2}{8R_C} \quad (12.7\text{c})$$

6.2 Series-Fed Class-A Amplifier

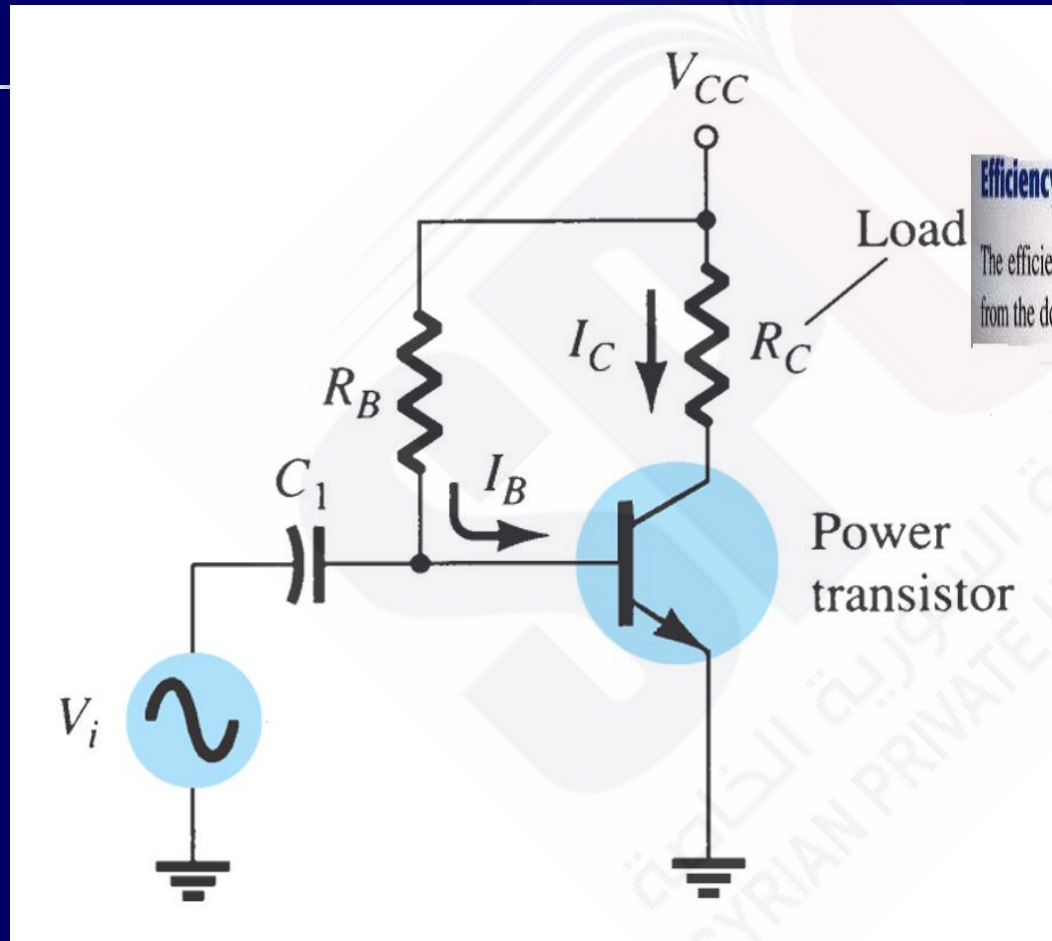


Efficiency

The efficiency of an amplifier represents the amount of ac power delivered (transferred) from the dc source. The efficiency of the amplifier is calculated using

$$\% \eta = \frac{P_o(ac)}{P_i(dc)} \times 100\%$$

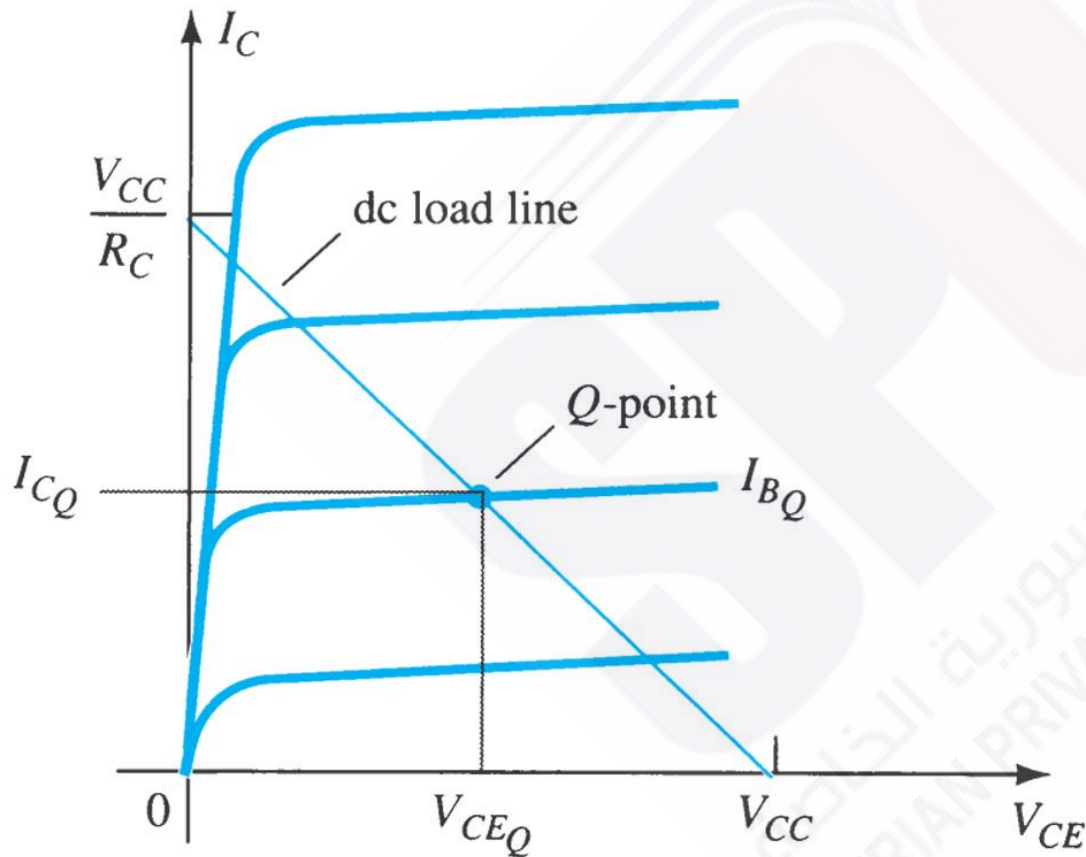(12.8)

Transistor characteristic showing load line and Q-point



$$\eta = \frac{P_o(ac)}{P_i(dc)} \times 100\%$$

$$P_o(ac) = \frac{V_{CE}(p)I_C(p)}{2}$$

$$P_o(ac)_{\max} = \frac{V_{CC}(V_{CC}/R_C)}{8}$$


$$P_i(dc) = V_{CC}I_{CQ}, \quad P_i(dc)_{\max} = V_{CC}I_{C\max}$$

$$\eta_{\max} = \frac{V_{CC}^2/8R_C}{V_{CC}^2/2R_C} = 25\%$$

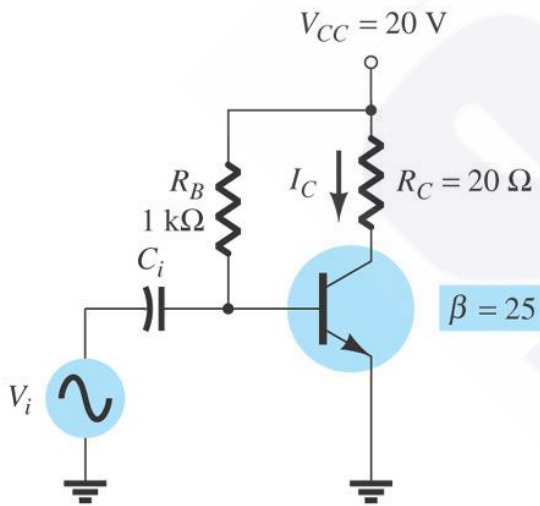
Example

$I_{b\max} = 10 \text{ mA}$
 $I_{BQ} = 19.3 \text{ mA}$
 $I_{CQ} = 482 \text{ mA}$
 $V_{CEQ} = 10.4 \text{ V}$
 $I_c(p) = \beta I_b = 250 \text{ mA peak}$
 $P_o(ac) = I_c I_c R_c / 2 = 625 \text{ mW}$
 $P_i(dc) = V_{cc} I_{CQ} = 9.6 \text{ W}$
 $\eta = P_o / P_i = 6.5\%$

$$I_C = \frac{V_{CC}}{R_C} = \frac{20 \text{ V}}{20 \Omega} = 1000$$




(a)

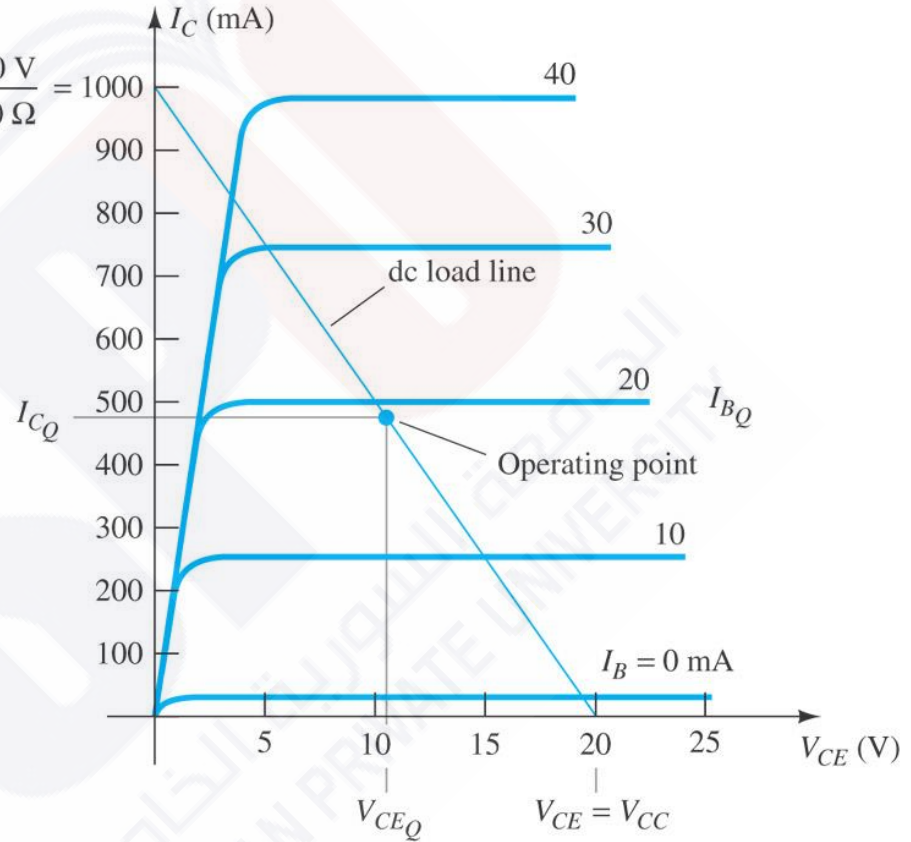

(b)

6.3 Transformer-Coupled Class-A amplifier

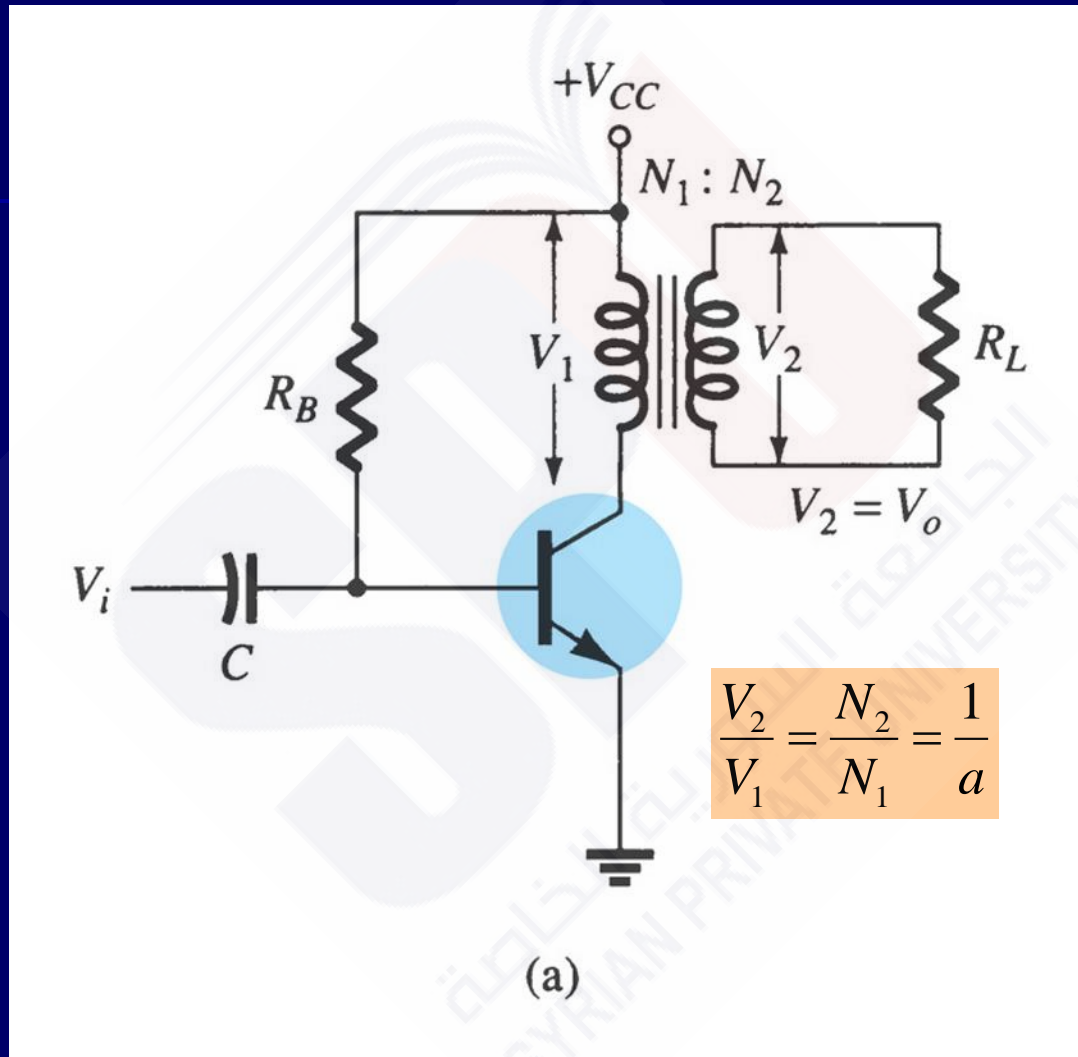

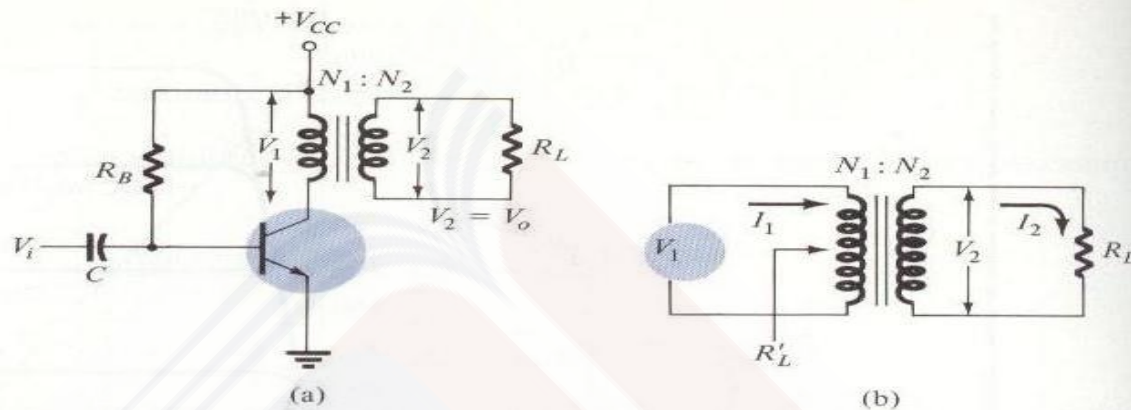


Figure 12.5 Transformer-coupled audio power amplifier.

primary resistance may be expressed as follows:

$$\frac{R_L'}{R_L} = \frac{V_1/I_1}{V_2/I_2} = \frac{V_1}{I_1} \frac{I_2}{V_2} = \frac{V_1}{V_2} \frac{I_2}{I_1} = \frac{N_1}{N_2} \frac{N_1}{N_2} = \left(\frac{N_1}{N_2}\right)^2$$

where $V_1/V_2 = N_1/N_2$ and $I_2/I_1 = N_1/N_2$. Hence the ratio of the transformer input and output resistance varies directly as the *square* of the transformer turns ratio:

$$\boxed{\frac{R_L'}{R_L} = \left(\frac{N_1}{N_2}\right)^2 = a^2} \quad (12.9)$$

and


$$\boxed{R_L' = a^2 R_L = \left(\frac{N_1}{N_2}\right)^2 R_L} \quad (12.10)$$

where R_L = resistance of load connected across the transformer secondary

R_L' = effective resistance seen looking into primary of transformer

$a = N_1/N_2$ is the step-down turns ratio needed to make the load resistance appear as a larger effective resistance seen from the transformer primary

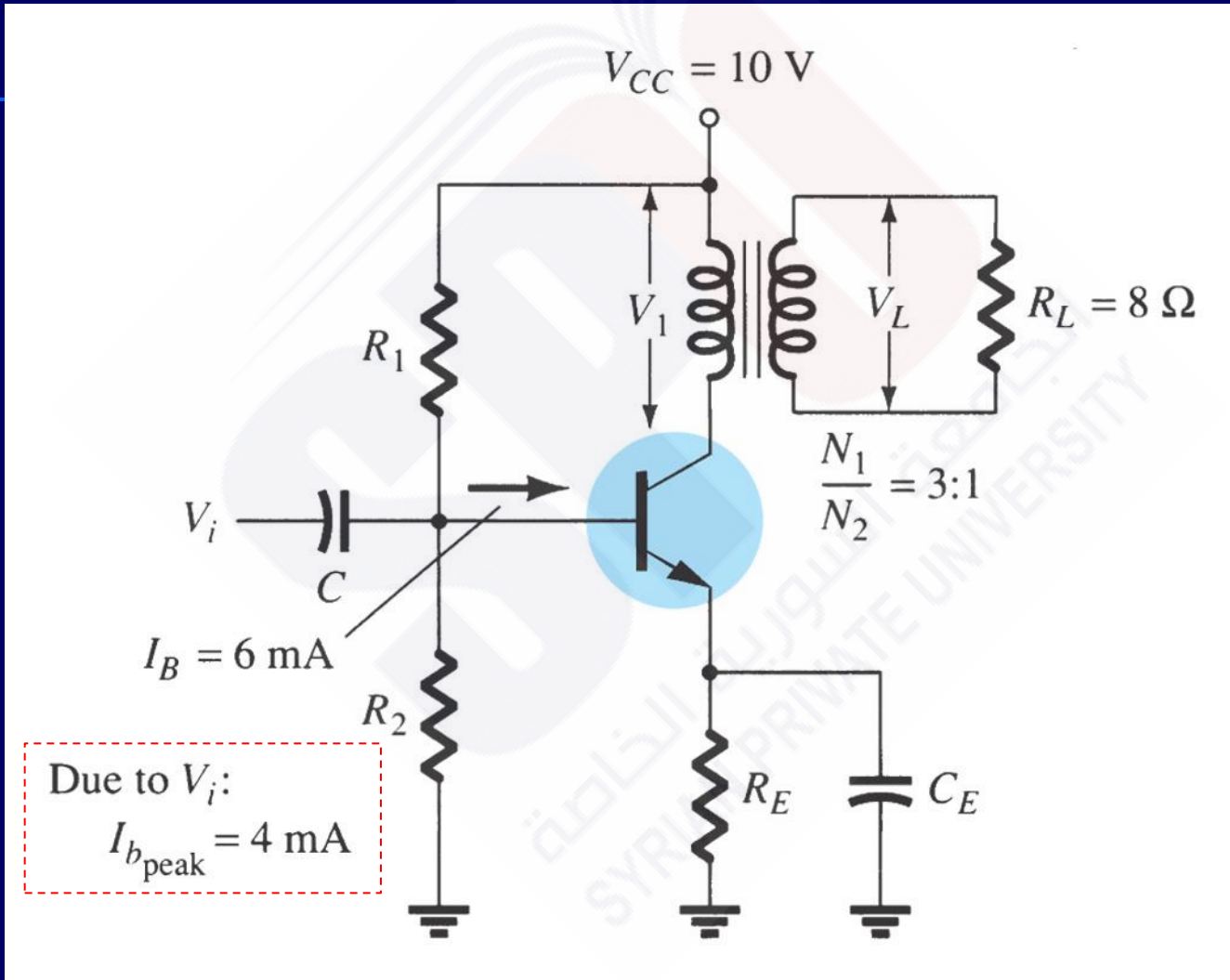Transformer-coupled class A amplifier: Example



$$V_{CEQ} = V_{CC} = 10 \text{ V}$$

For $I_B = 6 \text{ mA}$, the operating point on Fig. 12.11 is

$$V_{CEQ} = 10 \text{ V} \quad \text{and} \quad I_{CQ} = 140 \text{ mA}$$

The effective ac resistance seen at the primary is

$$R'_L = \left(\frac{N_1}{N_2} \right)^2 R_L = (3)^2(8) = 72 \Omega$$

The ac load line can then be drawn of slope $-1/72$ going through the indicated operating point. To help draw the load line, consider the following procedure. For a current swing of

$$I_C = \frac{V_{CE}}{R'_L} = \frac{10 \text{ V}}{72 \Omega} = 139 \text{ mA}$$

mark a point A:


$$I_{CEQ} + I_C = 140 \text{ mA} + 139 \text{ mA} = 279 \text{ mA} \text{ along the y-axis}$$

Connect point A through the Q -point to obtain the ac load line. For the given base current swing of 4 mA peak, the maximum and minimum collector current and collector-emitter voltage obtained from Fig. 12.11 are, respectively,

$$\begin{aligned} V_{CE_{\min}} &= 1.7 \text{ V} & I_{C_{\min}} &= 25 \text{ mA} \\ V_{CE_{\max}} &= 18.3 \text{ V} & I_{C_{\max}} &= 255 \text{ mA} \end{aligned}$$



The ac power delivered to the load can then be calculated using Eq. (12.13):
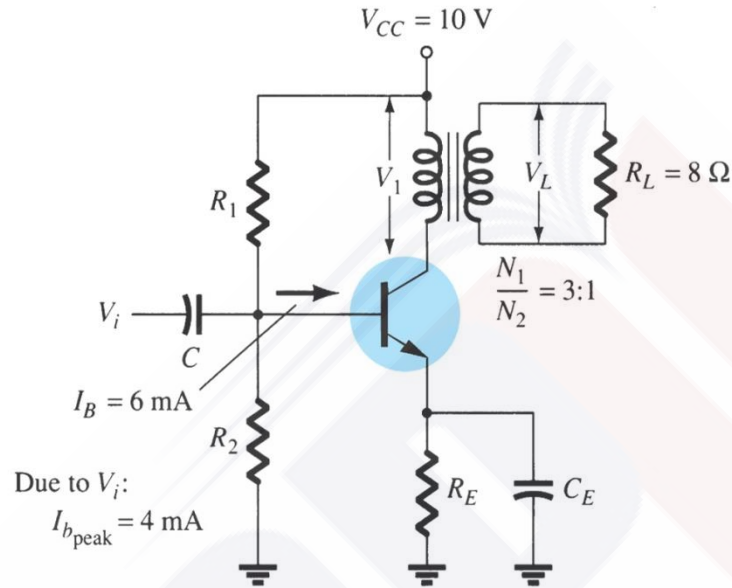
$$\begin{aligned} P_o(\text{ac}) &= \frac{(V_{CE_{\max}} - V_{CE_{\min}})(I_{C_{\max}} - I_{C_{\min}})}{8} \\ &= \frac{(18.3 \text{ V} - 1.7 \text{ V})(255 \text{ mA} - 25 \text{ mA})}{8} = \mathbf{0.477 \text{ W}} \end{aligned}$$




$$I_L(\text{rms}) = \frac{N_1}{N_2} I_C(\text{rms})$$

$$P_L = I_L^2(\text{rms}) R_L$$

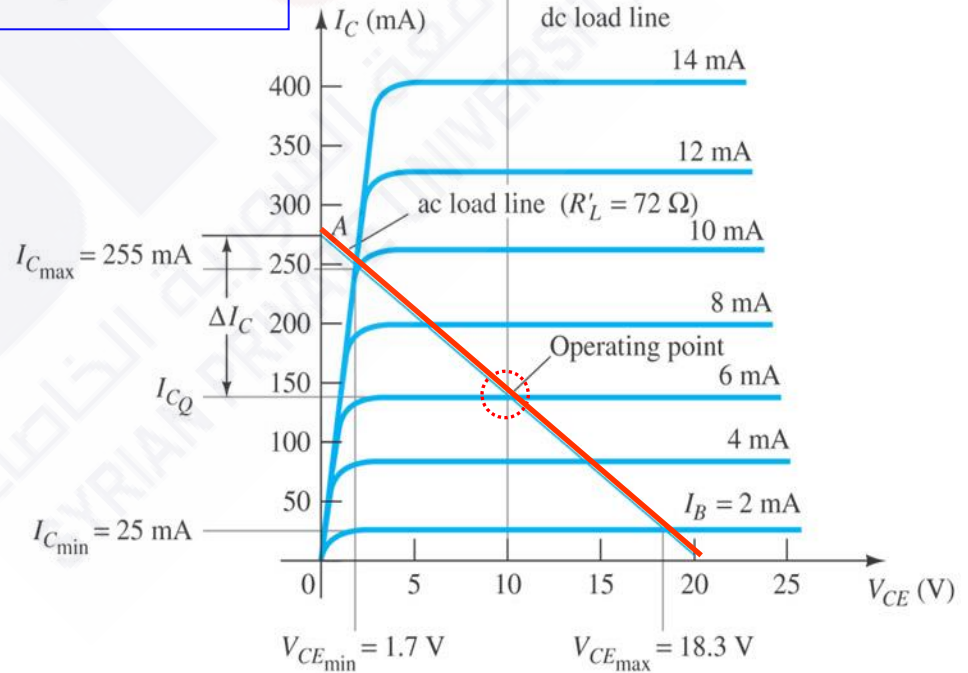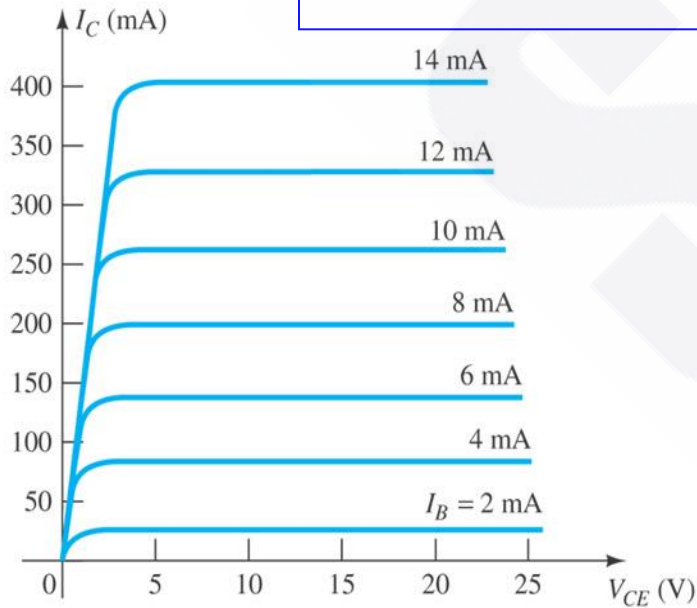


Load lines for class A transformer-coupled amplifier

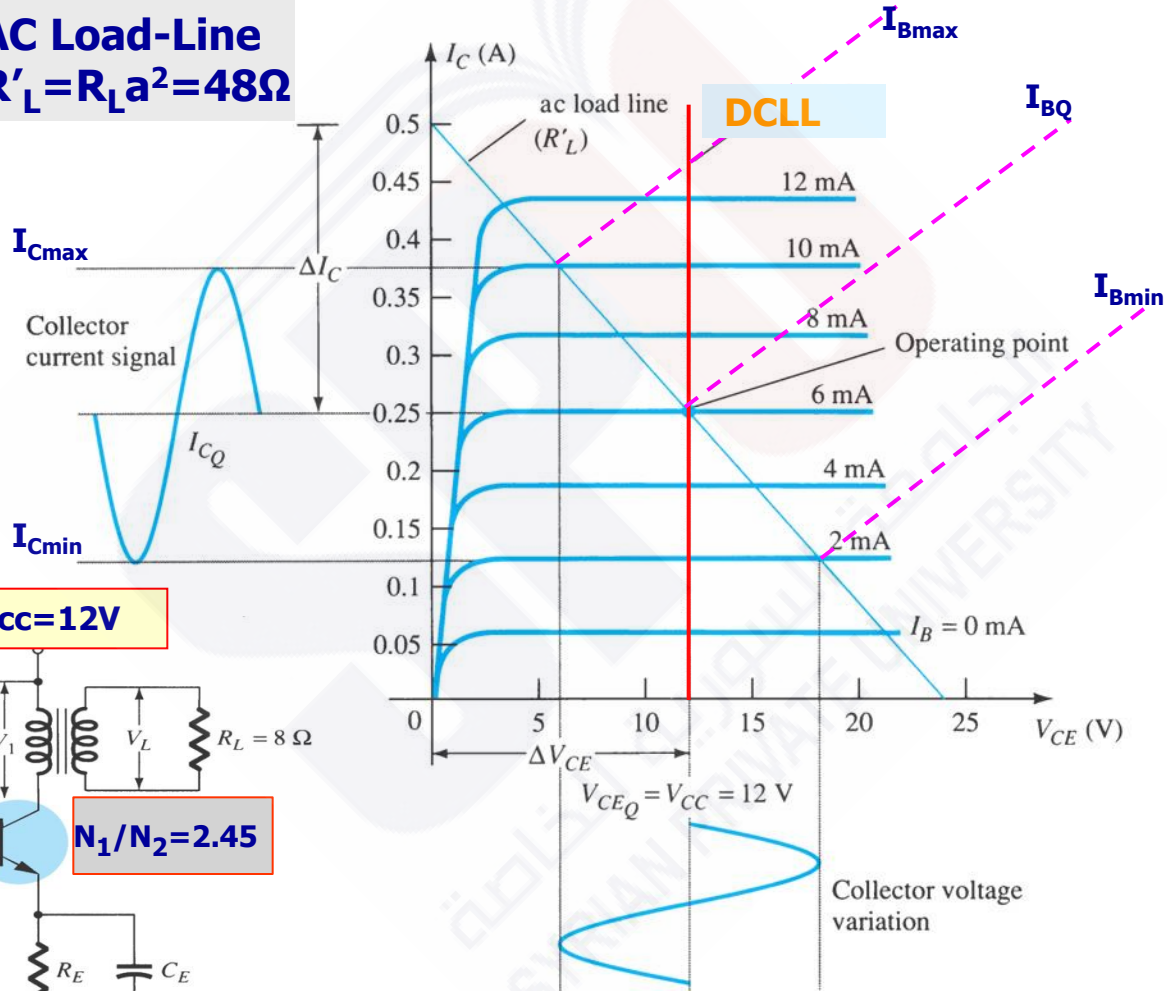AC Load-Line
 $R'_L = R_L a^2 = 48\Omega$




V_{CC} = 12V

N₁/N₂ = 2.45

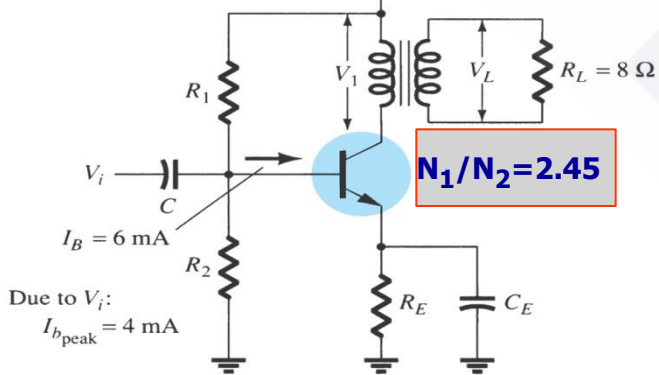

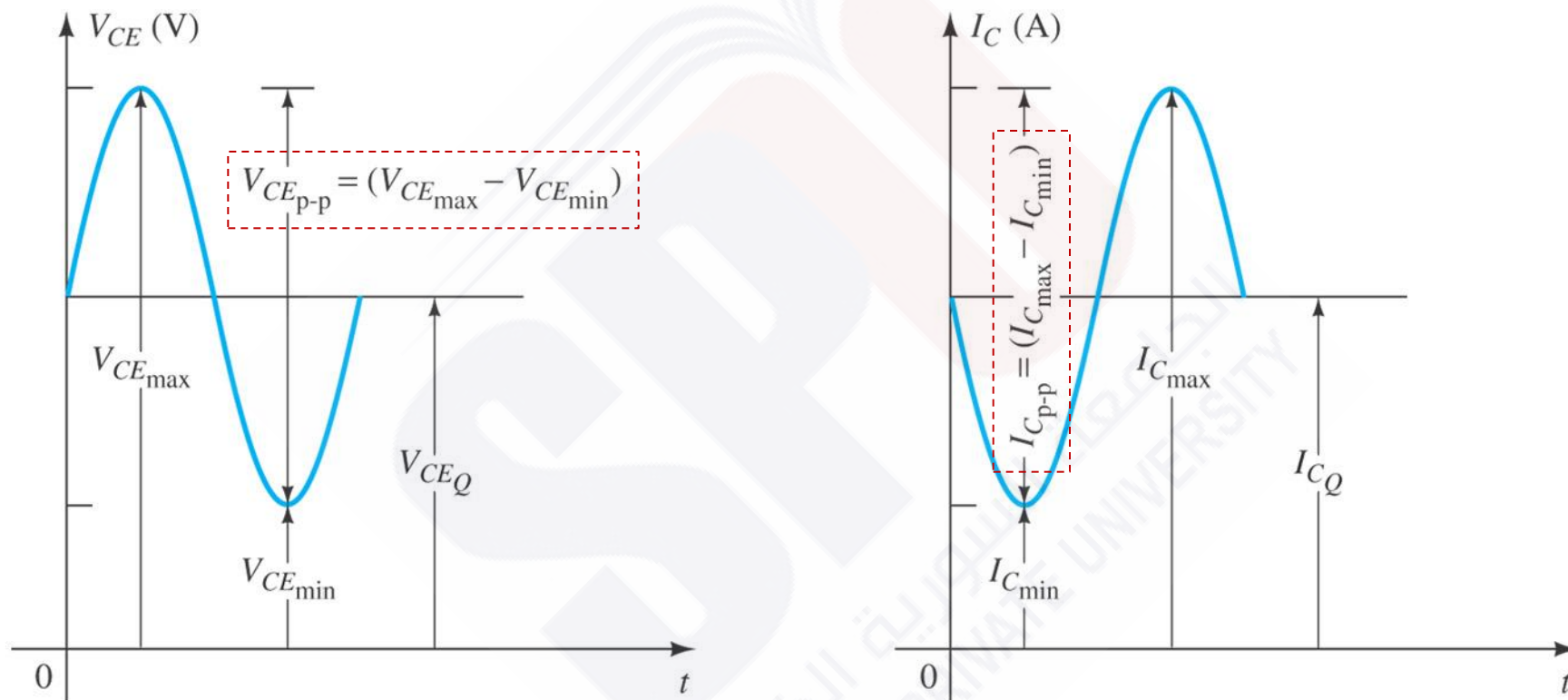Graphical operation of transformer-coupled class A amplifier



$$P_o(ac) = \frac{(V_{CE_{max}} - V_{CE_{min}})(I_{C_{max}} - I_{C_{min}})}{8}$$

$P_Q = P_i(dc) - P_o(ac)$: Dissipated Power by Transistor

Signal Swing and Output AC Power

From the signal variations shown in Figs. 12.6b and 12.6c the values of the peak-to-peak signal swings are

$$V_{\text{swing}} = V_{CE}(\text{p-p}) = (V_{CE_{\text{max}}} - V_{CE_{\text{min}}}) \quad (12.12)$$

$$I_{\text{swing}} = I_C(\text{p-p}) = (I_{C_{\text{max}}} - I_{C_{\text{min}}}) \quad (12.13)$$

The ac power developed across the transformer primary can be calculated to be

$$\begin{aligned} P_o(\text{ac}) &= V_{CE}(\text{rms}) I_C(\text{rms}) \\ &= \frac{V_{CE}(\text{peak})}{\sqrt{2}} \frac{I_C(\text{peak})}{\sqrt{2}} \\ &= \frac{V_{CE}(\text{p-p})/2}{\sqrt{2}} \times \frac{I_C(\text{p-p})/2}{\sqrt{2}} \end{aligned}$$

$$P_o(\text{ac}) = \frac{(V_{CE_{\text{max}}} - V_{CE_{\text{min}}})(I_{C_{\text{max}}} - I_{C_{\text{min}}})}{8} \quad (12.14)$$

Maximum Theoretical Efficiency

(Transformer-Coupled)

$$\eta_{\max th} = \frac{P_{Oth}}{P_i} = \frac{(V_{CE_{\max}} - V_{CE_{\min}})(I_{C_{\max}} - I_{C_{\min}})}{8V_{CC}I_{CQ}} = \frac{(V_{CE_{\max}} - V_{CE_{\min}})^2}{(R_C)8V_{CC}I_{CQ}}$$

$$V_{CC}I_{CQ} = \frac{(V_{CE_{\max}} + V_{CE_{\min}})}{2} I_{CQ} = \frac{(V_{CE_{\max}} + V_{CE_{\min}}) V_{CC}}{2 R_C} = \frac{(V_{CE_{\max}} + V_{CE_{\min}})^2}{4R_C}$$

$$\eta_{\max th} = 50\% \frac{(V_{CE_{\max}} - V_{CE_{\min}})^2}{(V_{CE_{\max}} + V_{CE_{\min}})^2} = 50\% \text{ at } V_{peak} = 12V$$

$$\eta_{\max th} = 50\% \frac{(V_{CE_{\max}} - V_{CE_{\min}})^2}{(V_{CE_{\max}} + V_{CE_{\min}})^2} = 12.5\% \text{ at } V_{peak} = 6V$$

$$= 50\% \frac{(V_{CE_{\max}} - V_{CE_{\min}})^2}{(V_{CE_{\max}} + V_{CE_{\min}})^2} = 1.39\% \text{ at } V_{peak} = 2V$$

Find η for
o/p:

$V(\text{peak})=12V$

$V(\text{peak})=6V$

$V(\text{peak})=2V$

If $V_{CEQ}=V_{CC}$

a. Since $V_{CEQ} = V_{CC} = 12 \text{ V}$, the maximum and minimum of the voltage swing are, respectively,

$$V_{CE_{\max}} = V_{CEQ} + V(p) = 12 \text{ V} + 12 \text{ V} = 24 \text{ V}$$

$$V_{CE_{\min}} = V_{CEQ} - V(p) = 12 \text{ V} - 12 \text{ V} = 0 \text{ V}$$

resulting in

$$\% \eta = 50 \left(\frac{24 \text{ V} - 0 \text{ V}}{24 \text{ V} + 0 \text{ V}} \right)^2 \% = \mathbf{50\%}$$

b.

$$V_{CE_{\max}} = V_{CEQ} + V(p) = 12 \text{ V} + 6 \text{ V} = 18 \text{ V}$$

$$V_{CE_{\min}} = V_{CEQ} - V(p) = 12 \text{ V} - 6 \text{ V} = 6 \text{ V}$$


resulting in

$$\% \eta = 50 \left(\frac{18 \text{ V} - 6 \text{ V}}{18 \text{ V} + 6 \text{ V}} \right)^2 \% = \mathbf{12.5\%}$$

$$V_{CE_{\max}} = V_{CEQ} + V(p) = 12 \text{ V} + 2 \text{ V} = 14 \text{ V}$$


$$V_{CE_{\min}} = V_{CEQ} - V(p) = 12 \text{ V} - 2 \text{ V} = 10 \text{ V}$$

6.4 Class-B Amplifier Operation

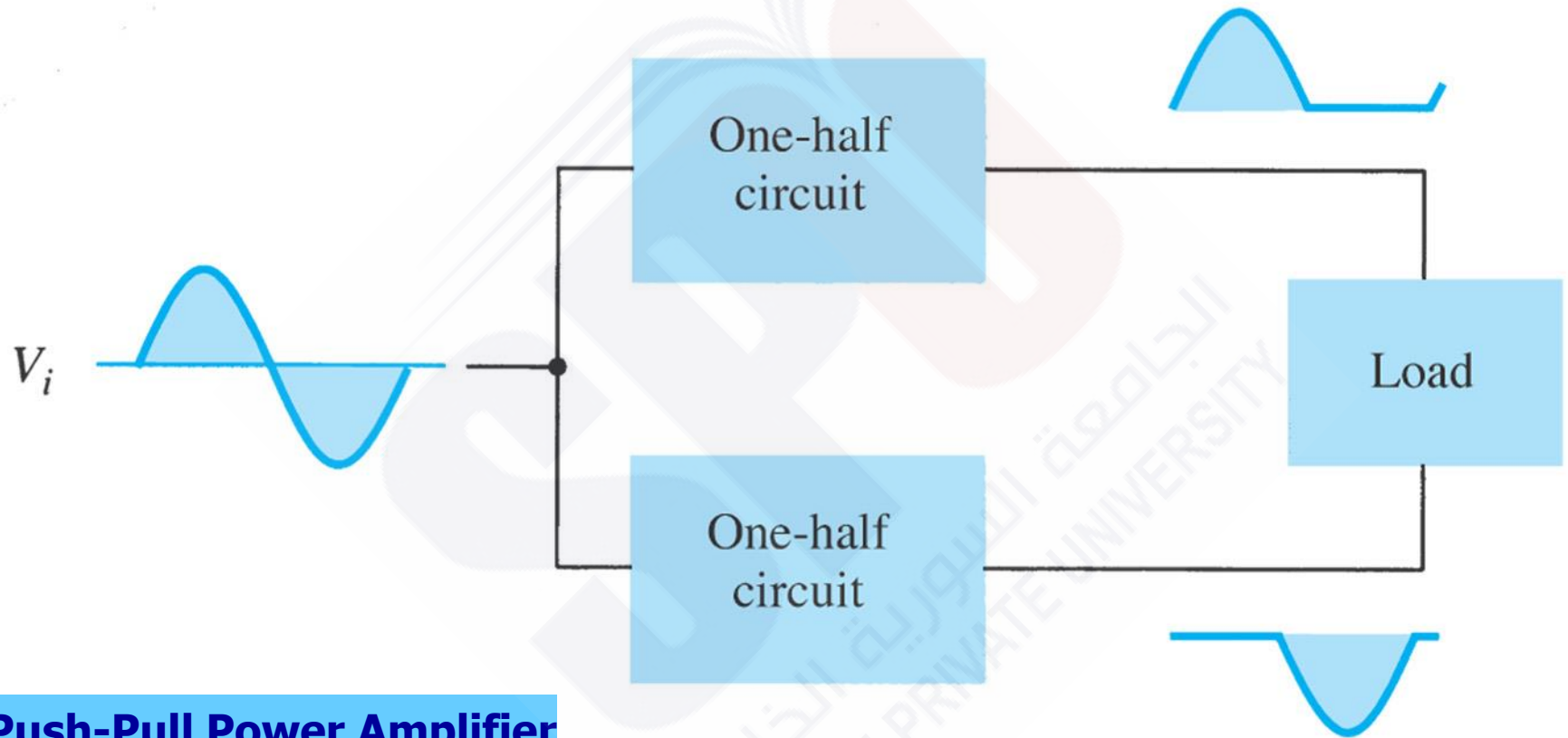

Push-Pull Power Amplifier

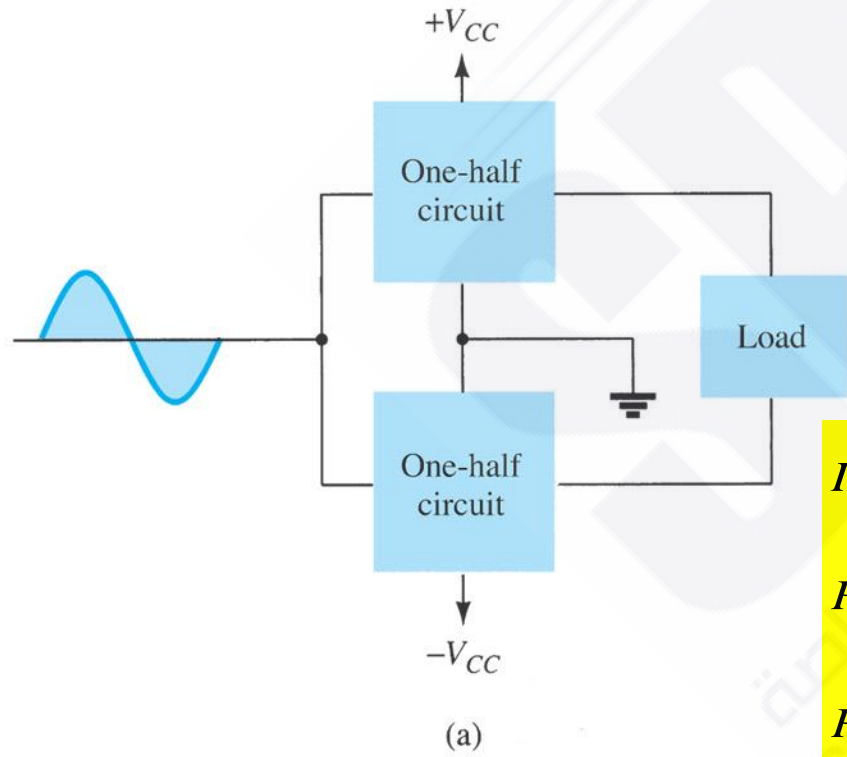
Connection of push–pull amplifier to load: (a) using two voltage supplies; (b) using one voltage supply



$$I_{dc} = \frac{2}{\pi} I(p)$$

$$P_i(dc) = V_{CC} \left(\frac{2}{\pi} I(p) \right)$$

$$P_o(ac) = \frac{V_L^2(rms)}{R_L}$$

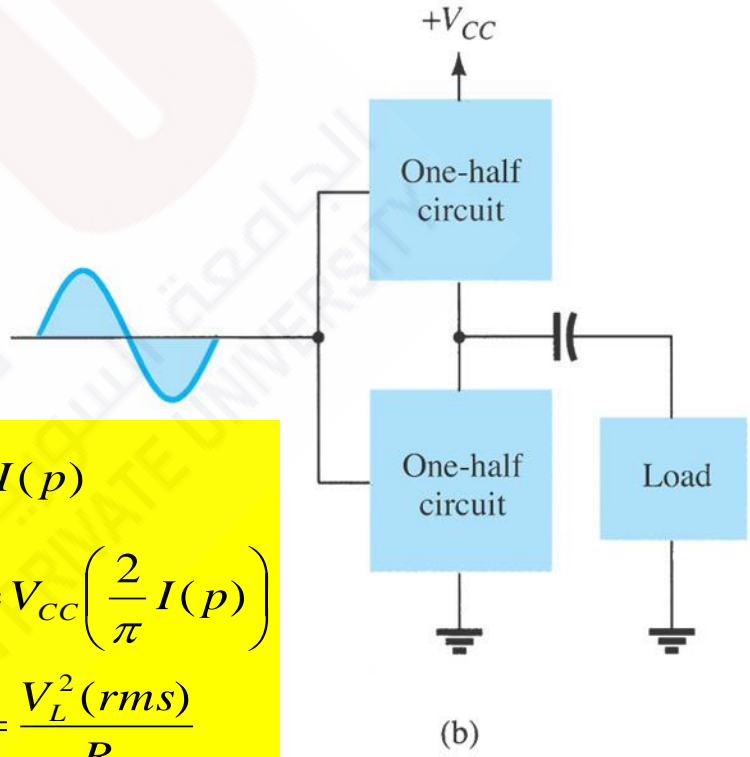

Efficiency of Class-B Amplifier

$$\eta = \frac{P_o(ac)}{P_i(dc)} \times 100\%$$

$$\eta = \frac{V_L^2(p) / 2R_L}{V_{CC} [(2/\pi)I(p)]} \times 100\% = \frac{\pi}{4} \frac{V_L(p)}{V_{CC}} \times 100\%$$
$$\eta_{\max} = \frac{\pi}{4} \times 100\% = 78.5$$

$$P_{2Q} = P_i(dc) - P_o(ac)$$

P_{2Q} : The Power Dissipated by O/P Transistors

When the input signal results in less than the maximum output signal swing, the circuit efficiency is less than 78.5%.

For class B operation, the maximum power dissipated by the output transistors does not occur at the maximum power input or output condition. The maximum power dissipated by the two output transistors occurs when the output voltage across the load is

$$V_L(p) = 0.636V_{CC} \quad \left(= \frac{2}{\pi}V_{CC} \right)$$

for a maximum transistor power dissipation of

$$\text{maximum } P_{2Q} = \frac{2V_{CC}^2}{\pi^2 R_L}$$

The maximum efficiency of a class B amplifier can also be expressed as follows:

$$P_o(\text{ac}) = \frac{V_L^2(p)}{2R_L}$$

$$P_i(\text{dc}) = V_{CC}I_{dc} = V_{CC} \left[\frac{2V_L(p)}{\pi R_L} \right]$$

so that

$$\% \eta = \frac{P_o(\text{ac})}{P_i(\text{dc})} \times 100\% = \frac{V_L^2(p)/2R_L}{V_{CC}[(2/\pi)(V_L(p)/R_L)]} \times 100\%$$

$$\% \eta = 78.54 \frac{V_L(p)}{V_{CC}} \%$$

(12.)

Example

1. For Class-B amp determine: $P_{i\max}$, $P_{o\max}$, P_Q and η if $V_{CC}=30V$ and $R_L=16\Omega$

2. Find η for $V_o(\text{peak})=22V$ and $6V$ if $V_{CC}=24V$

$$P_o = V_{CC}^2 / 2R_L = 28.125 \text{ W}$$

$$P_i = 2V_{CC}^2 / \pi R_L = 35.81 \text{ W}$$

$$\text{Max } \eta = 28.125 / 35.81 = 78.54\%$$


$$P_Q = P_{2Q} / 2 = 0.5(2V_{CC}^2 / \pi^2 R_L) = 5.7 \text{ W}$$

$$\text{When } V_o = 22V : \eta = \eta_{\max} V_o / V_{CC} = 78.54 \times 22 / 24 = 72\%$$


$$\text{When } V_o = 6V : \eta = \eta_{\max} V_o / V_{CC} = 78.54 \times 6 / 24 = 19.6\%$$

6.5 Class-B Amplifier Circuits


Phase-splitter circuits

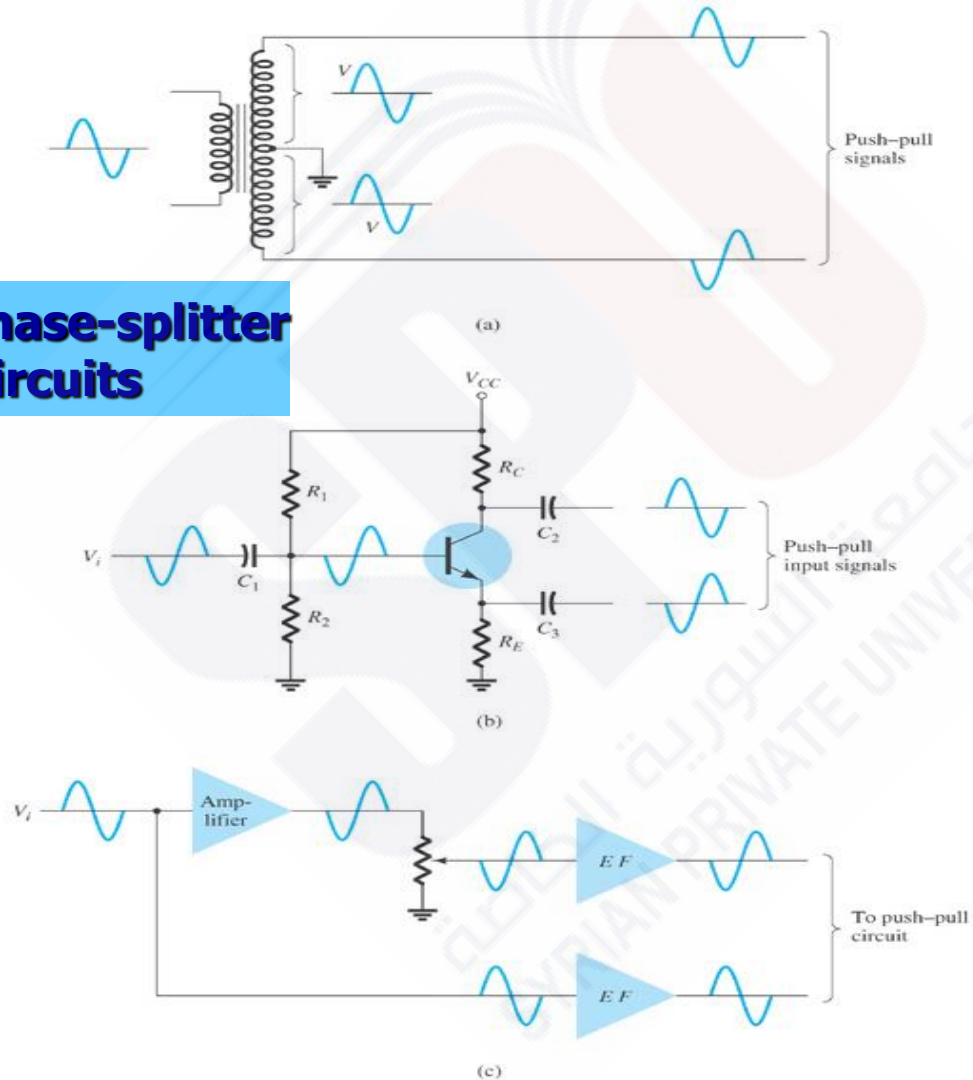


Transformer-Coupled Push-Pull Amp

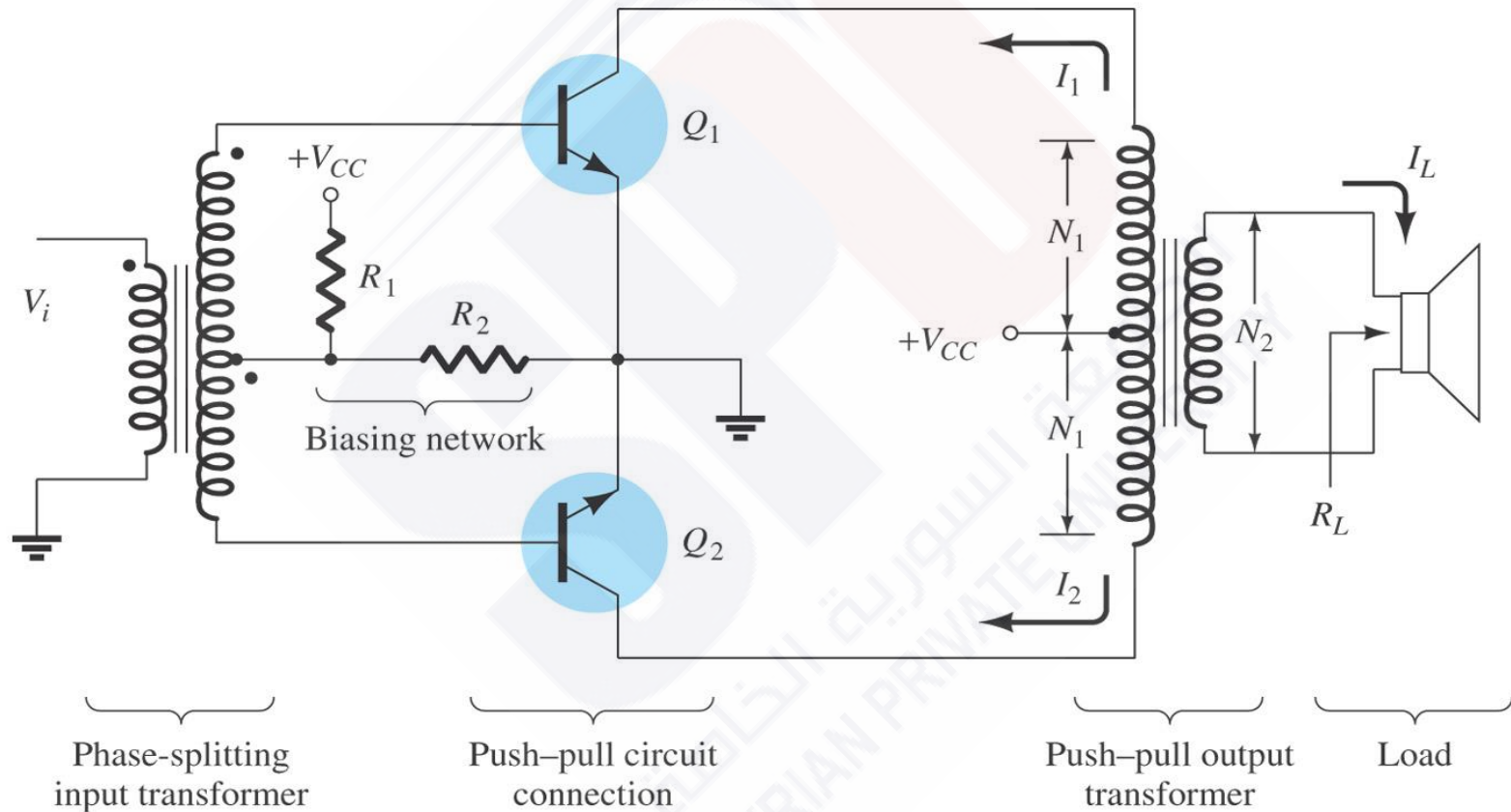

Complementary-symmetry push-pull circuit

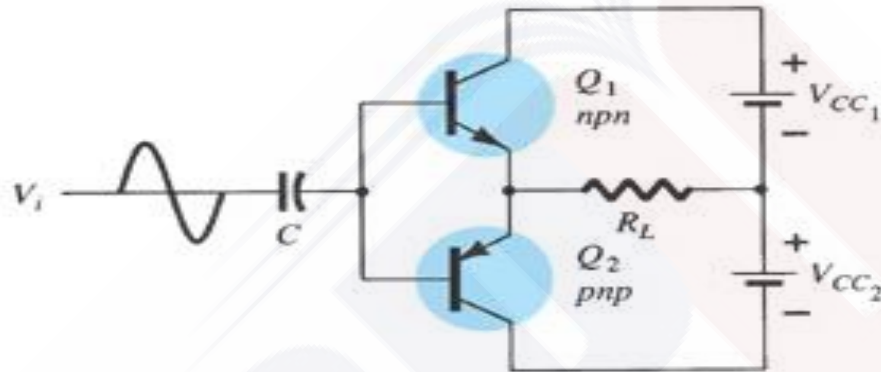


(a)

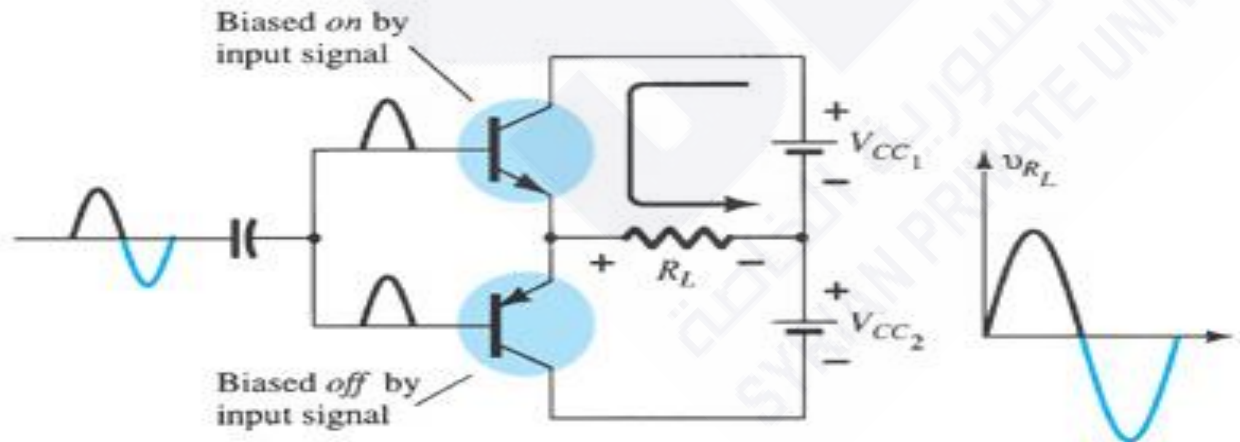


Complementary-symmetry push-pull circuit

Complementary needs 2 Power Supply

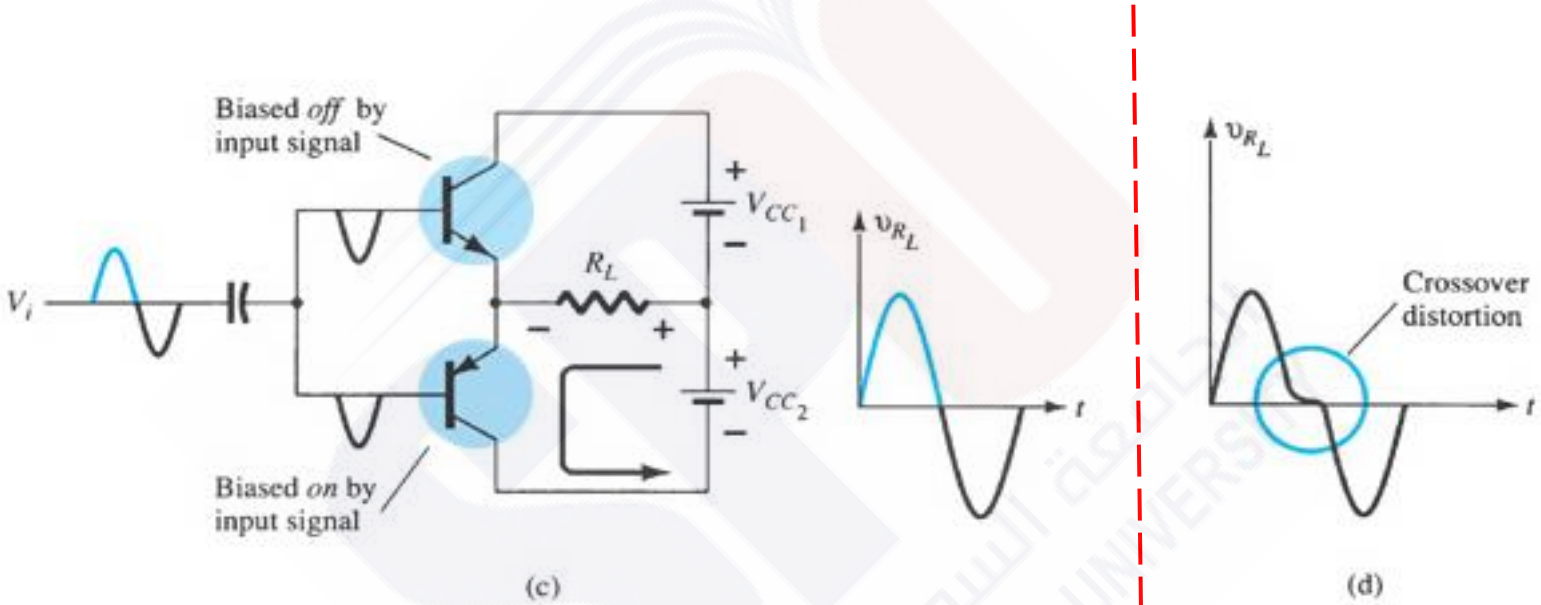


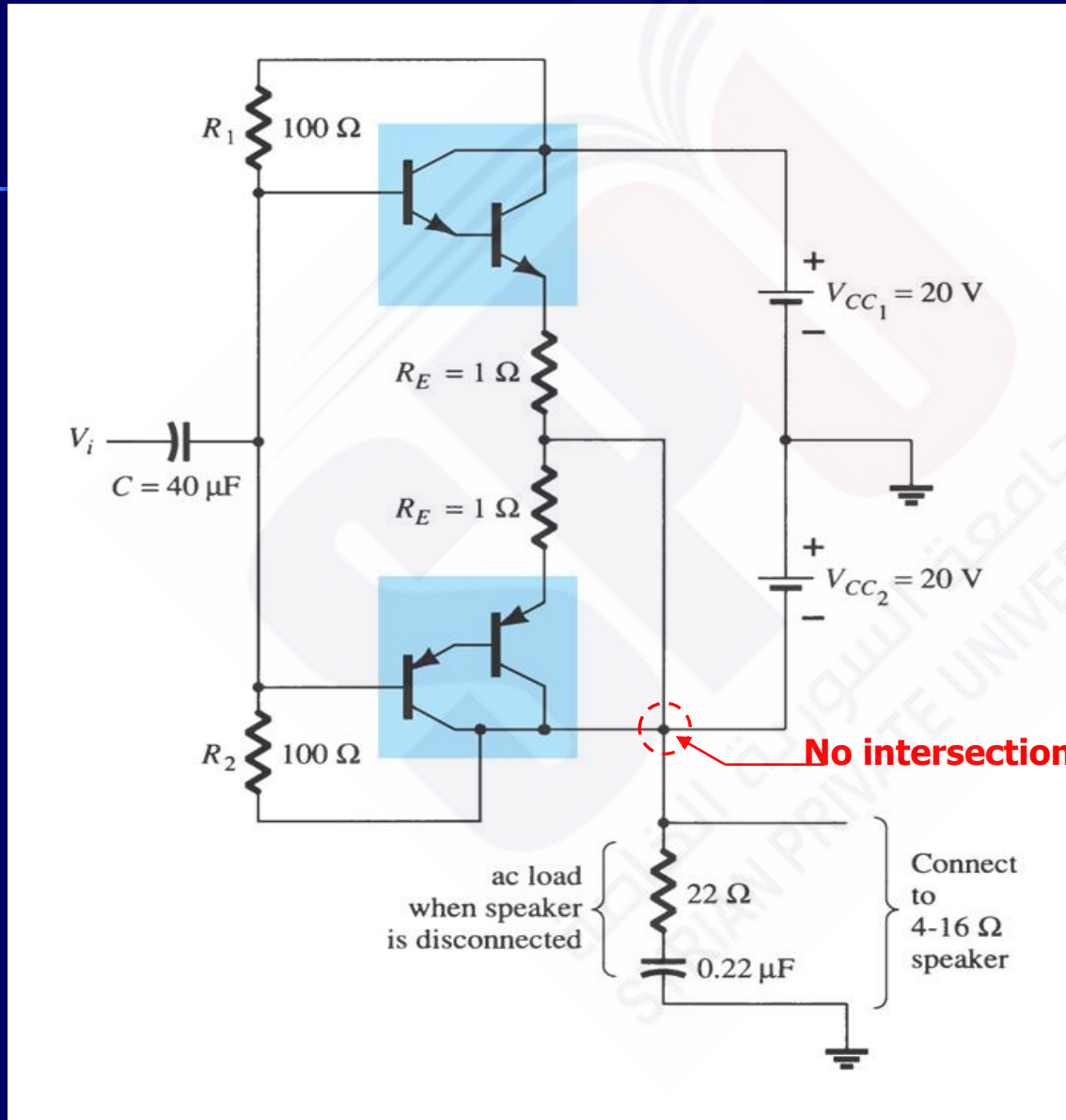Complementary-symmetry push-pull circuit using Darlington transistors



Quasi-complementary push-pull transformer-less power amplifier

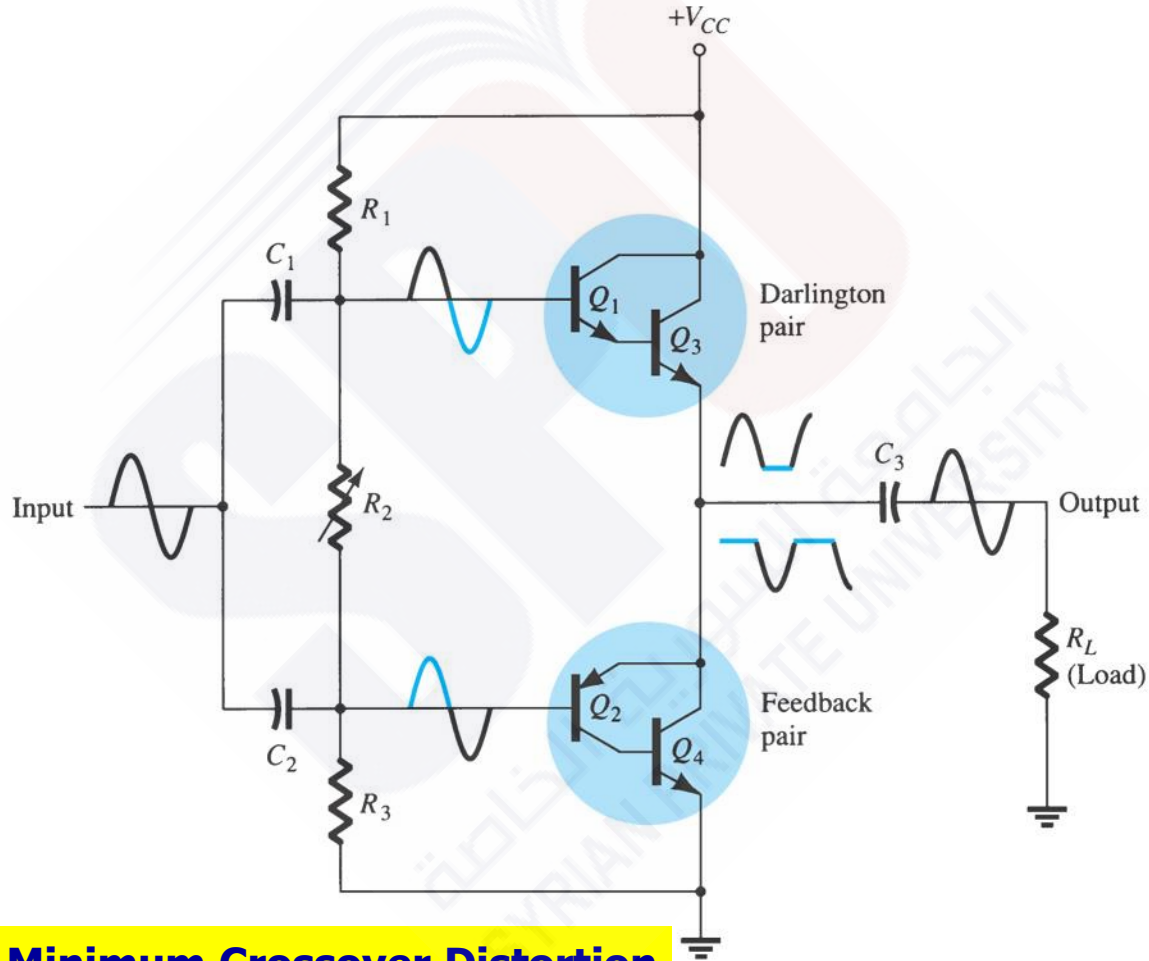
The Most Popular Form of Power Amps: Single Supply



R2: Adjust for Minimum Crossover Distortion

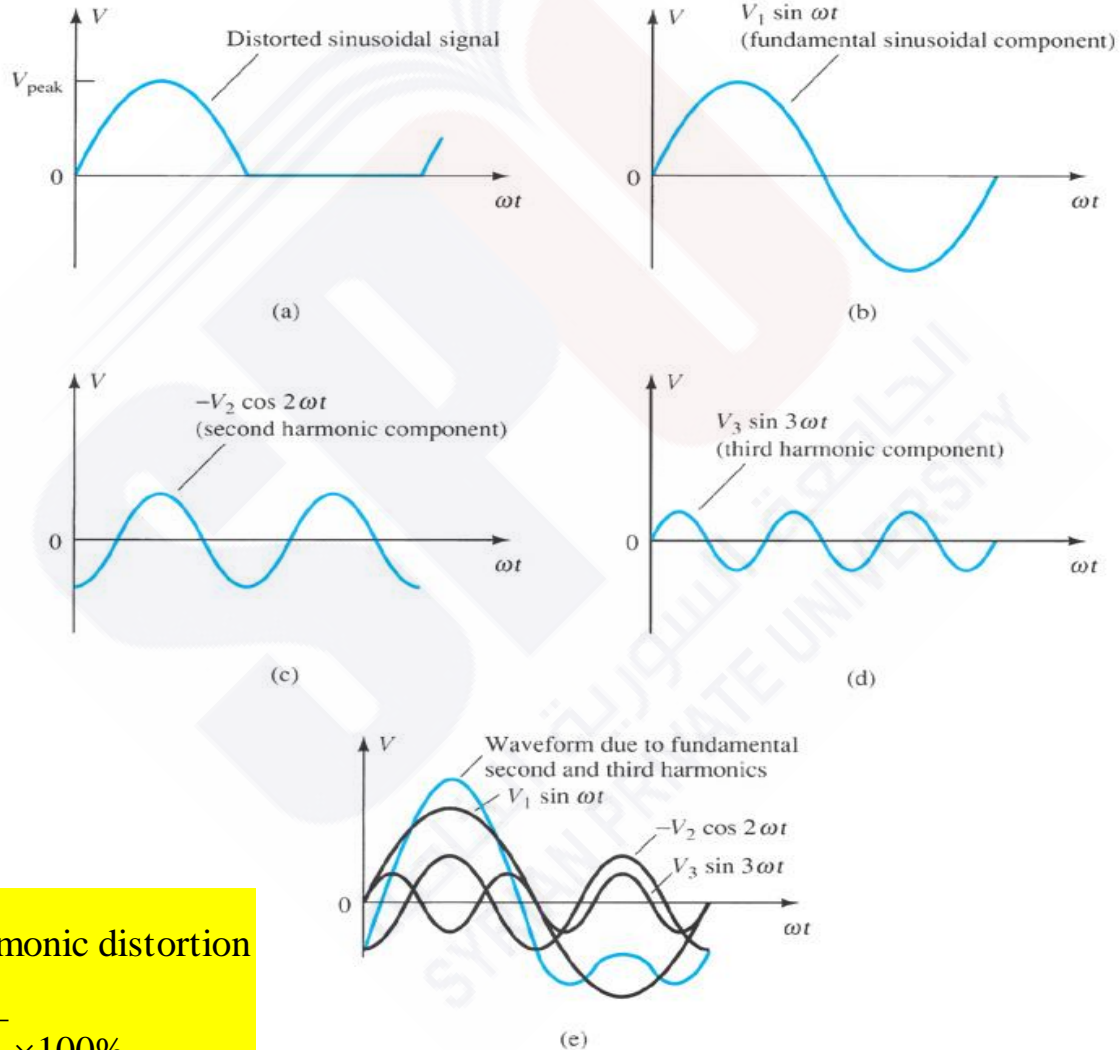6.6 Amplifier Distortion


Graphical representation of a distorted signal through the use of harmonic components



$$\% D_n = \frac{|A_n|}{|A_1|} \times 100\% : \% \text{ nth harmonic distortion}$$


$$THD = \sqrt{D_2^2 + D_3^2 + D_4^2 + \dots} \times 100\%$$

6.7 Power Transistor Heat Sinking

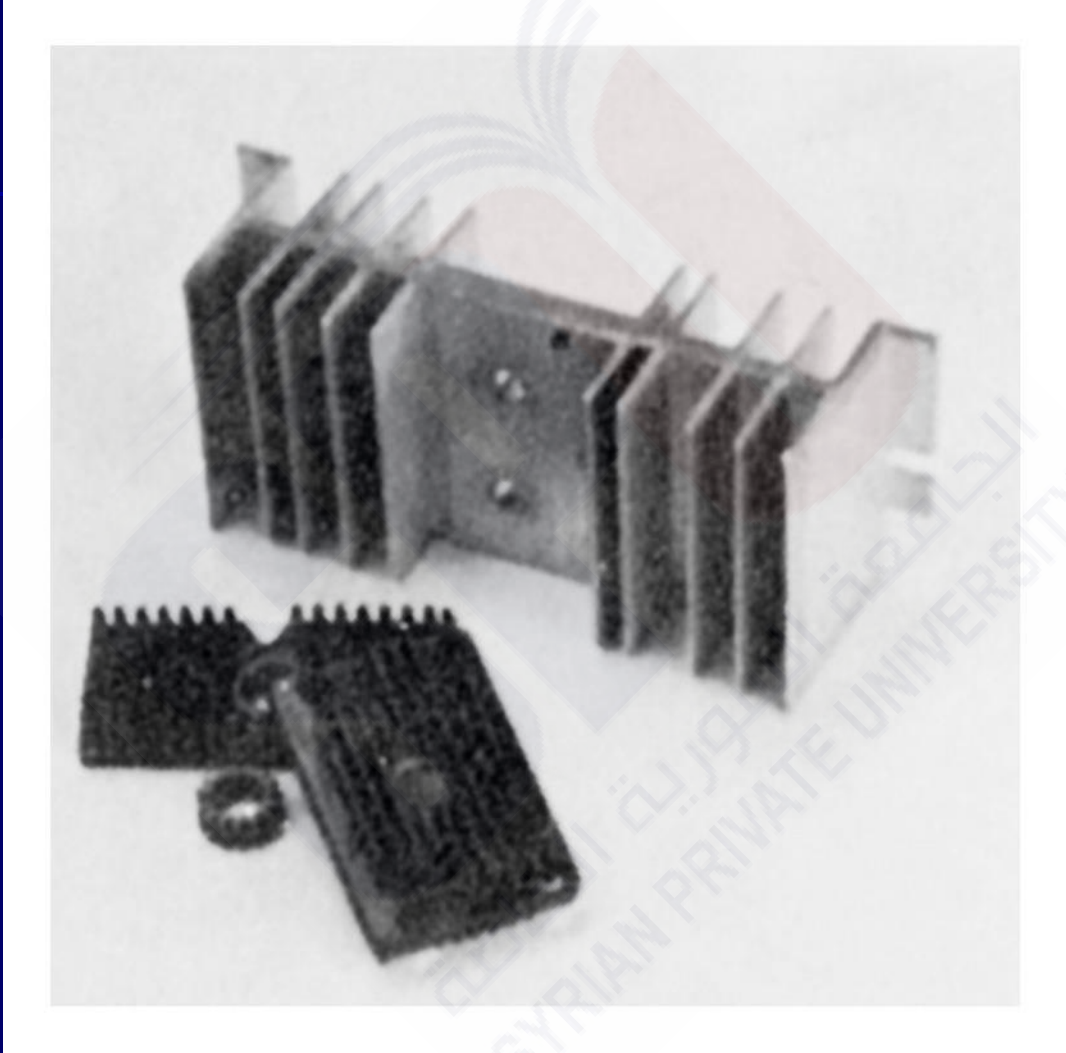


Typical power heat sinks

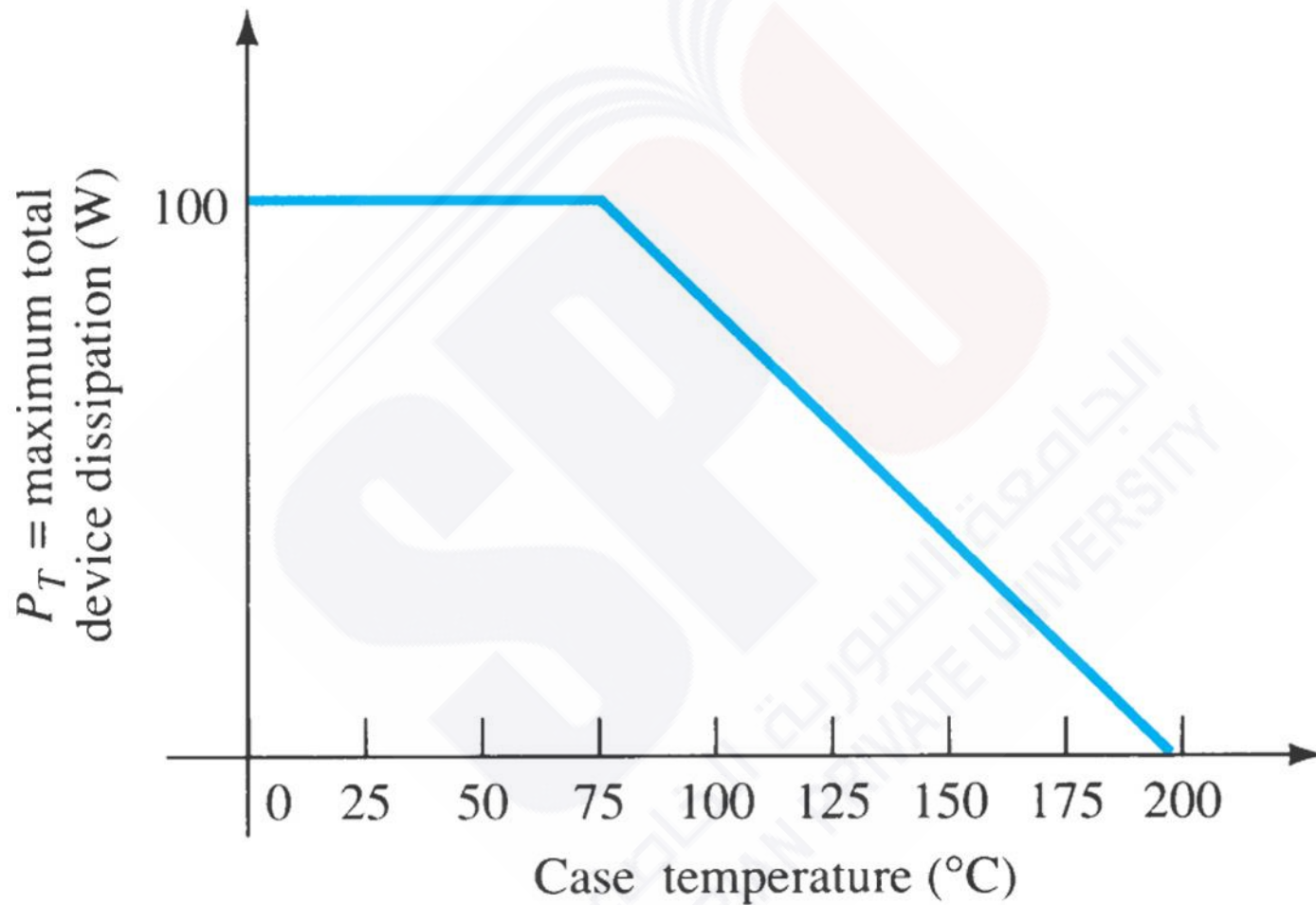Typical power derating curve for silicon transistors




Thermal-to-electrical analogy

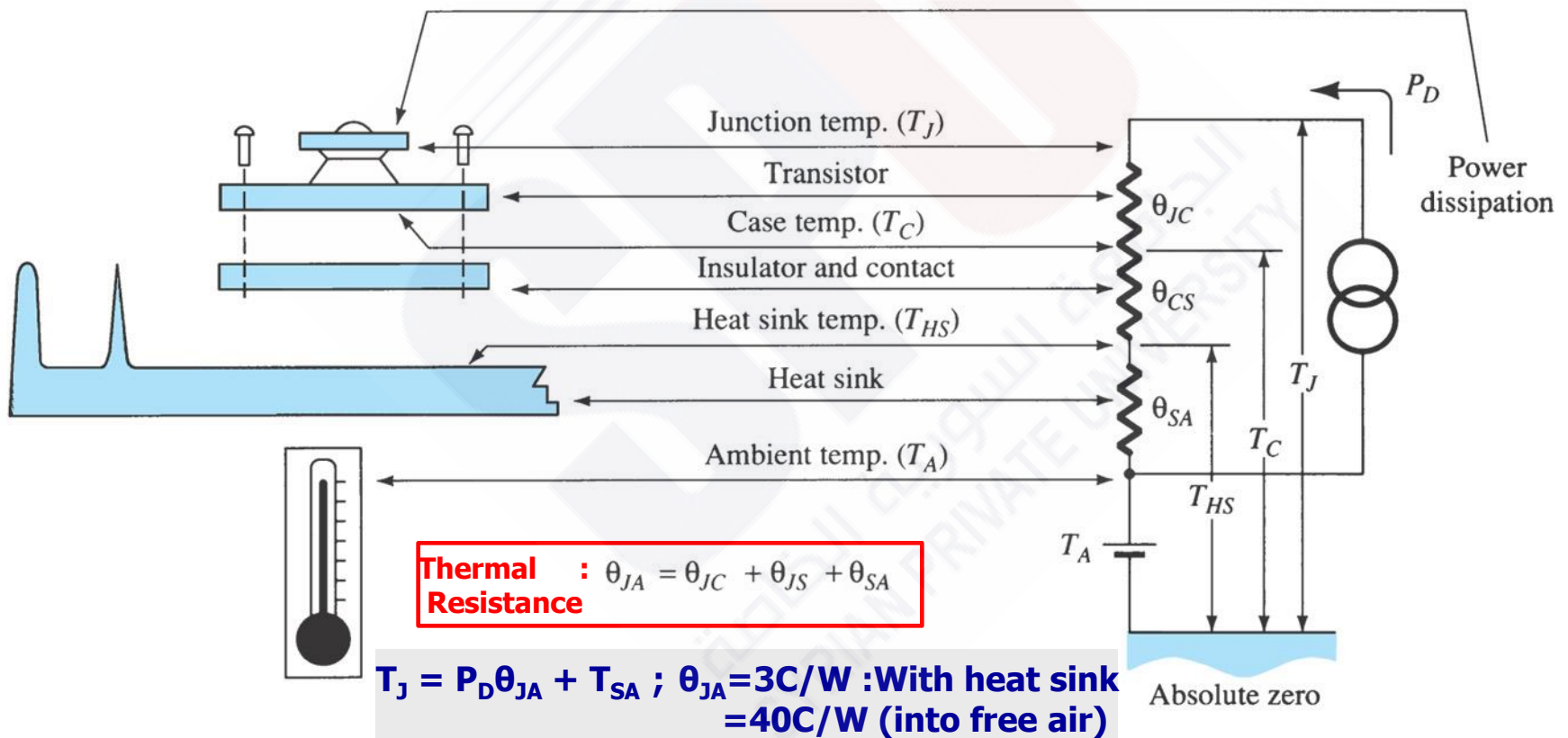


6.8 Class-C and Class-D Amplifiers


**Class C
amplifier
circuit**

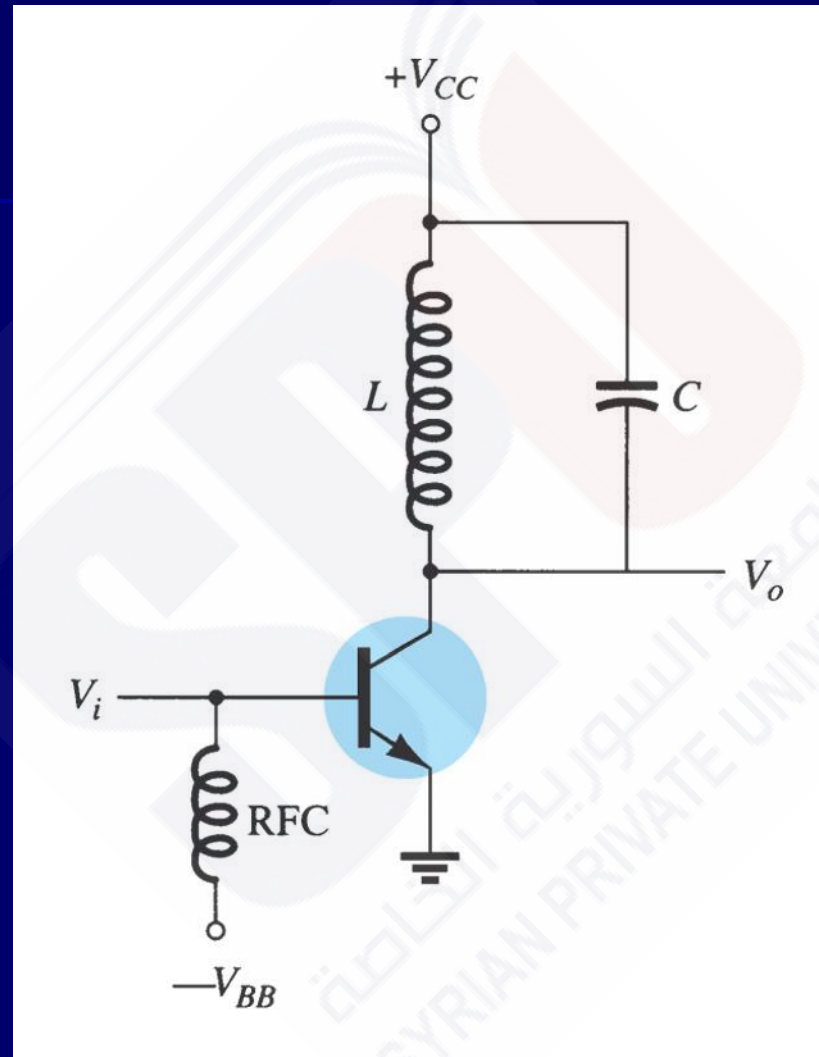

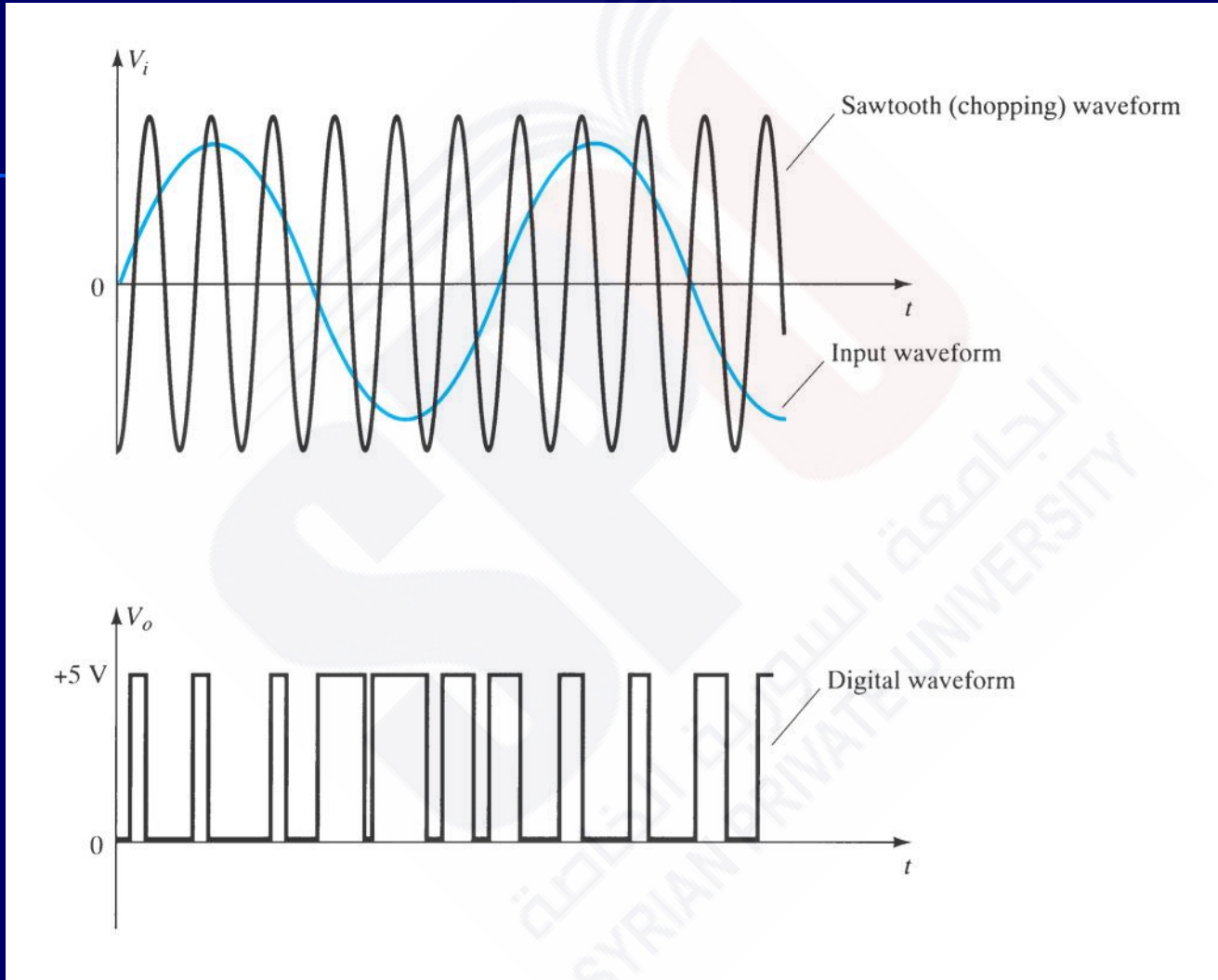Chopping of a sinusoidal waveform to produce a digital Waveform




Block diagram of class D amplifier

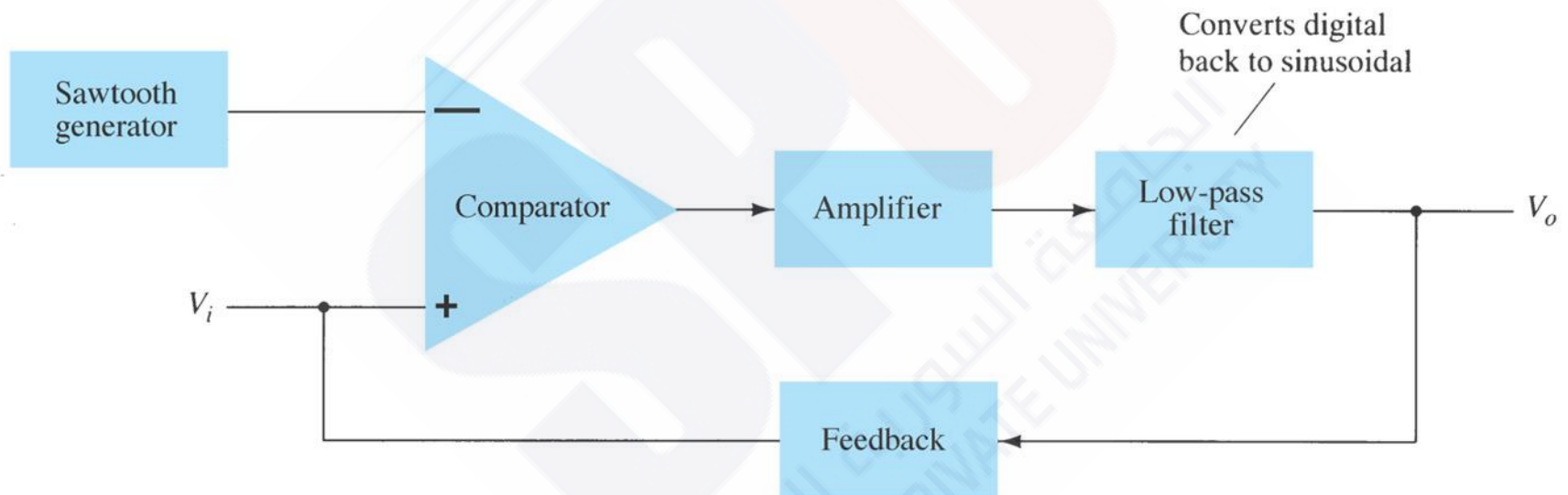

Po: Transistor I only for very short time → very high eff.

Examples

Series-Fed Class A amplifier

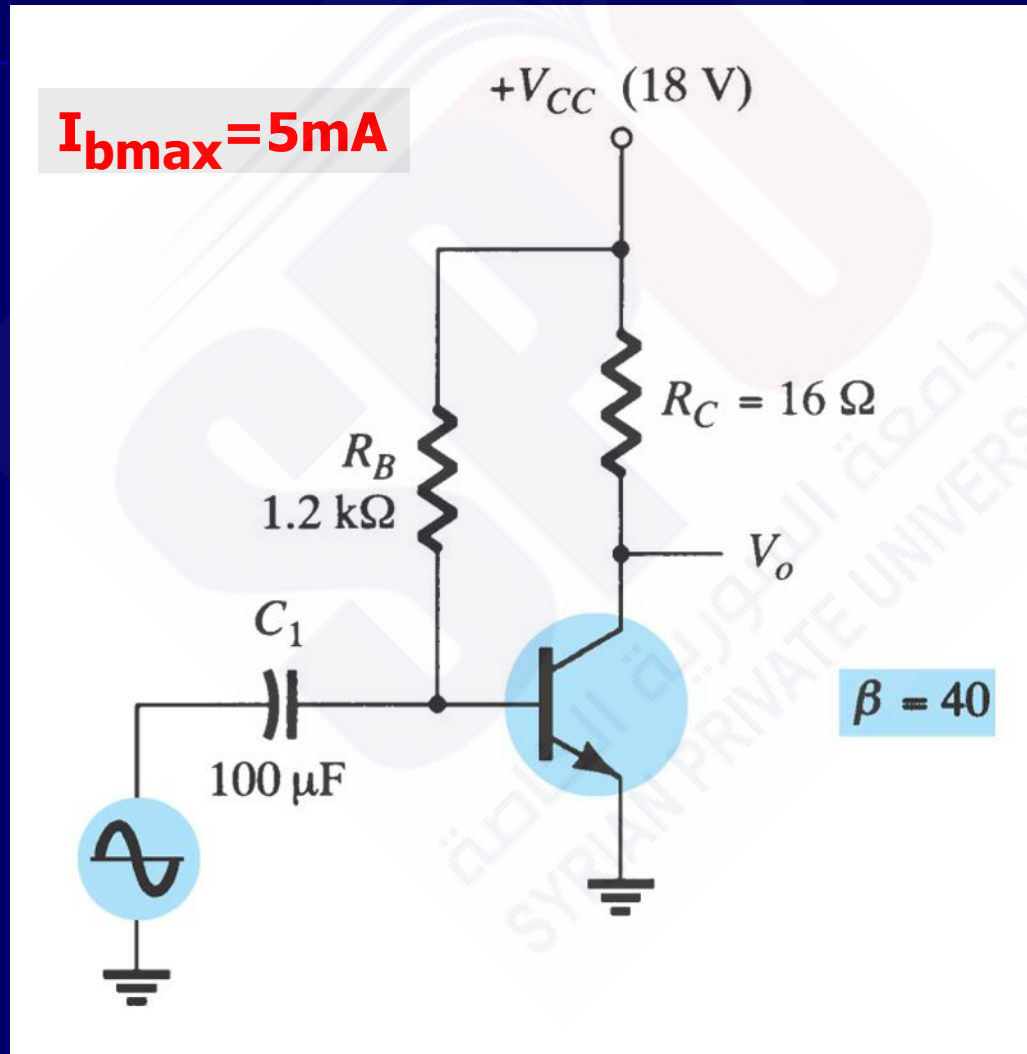

Example:

Class B amplifier Circuit > Refer to p.682 to solve this example

