

Electronic Circuits-1

Prof.Dr.Eng.Ahmad Rateb Al- Najjar
Head of Communication & Networkong Department-SPU

CONTENT

1. BJT Amplifier
2. FET Amplifier
3. Frequency Response of Amplifier
4. Operational Amplifier
5. Audio Power Amplifier
6. Linear-Digital ICs
- 7. Power Supplies**
8. IC Technology (optional)

Chapter 8- Power Supplies

8.1 Introduction

8.2 General Filter Considerations

8.3 Capacitor Filter


8.4 RC Filter

8.5 Discrete Transistor Voltage Regulation

8.6 IC Voltage Regulators


8.7 Applications

8.1 Introduction

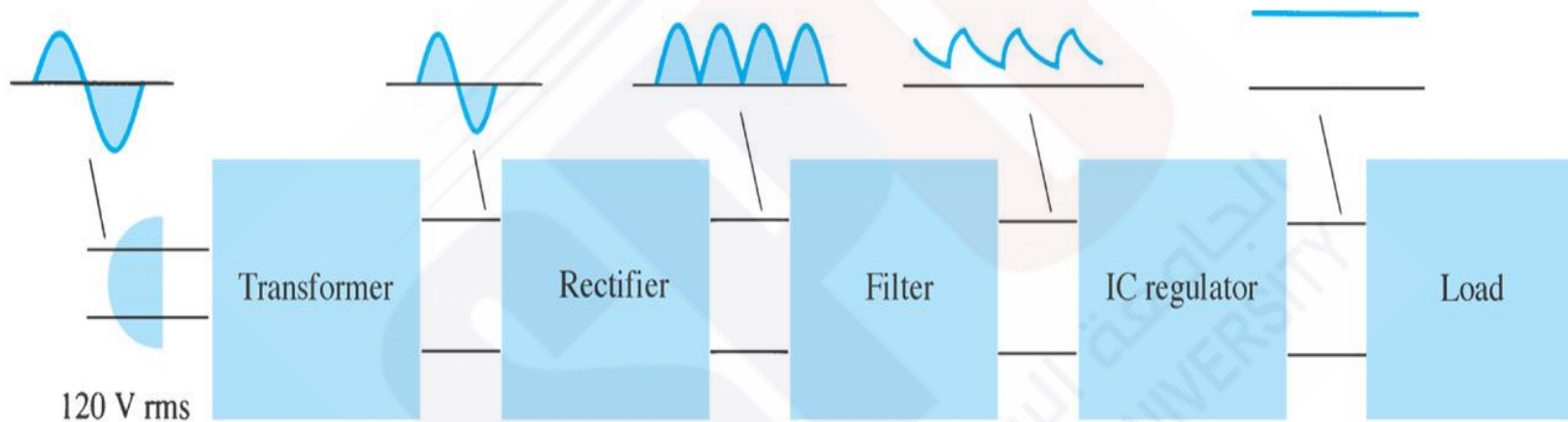

Block Diagram of a typical power supply

8.2 General Filter Considerations

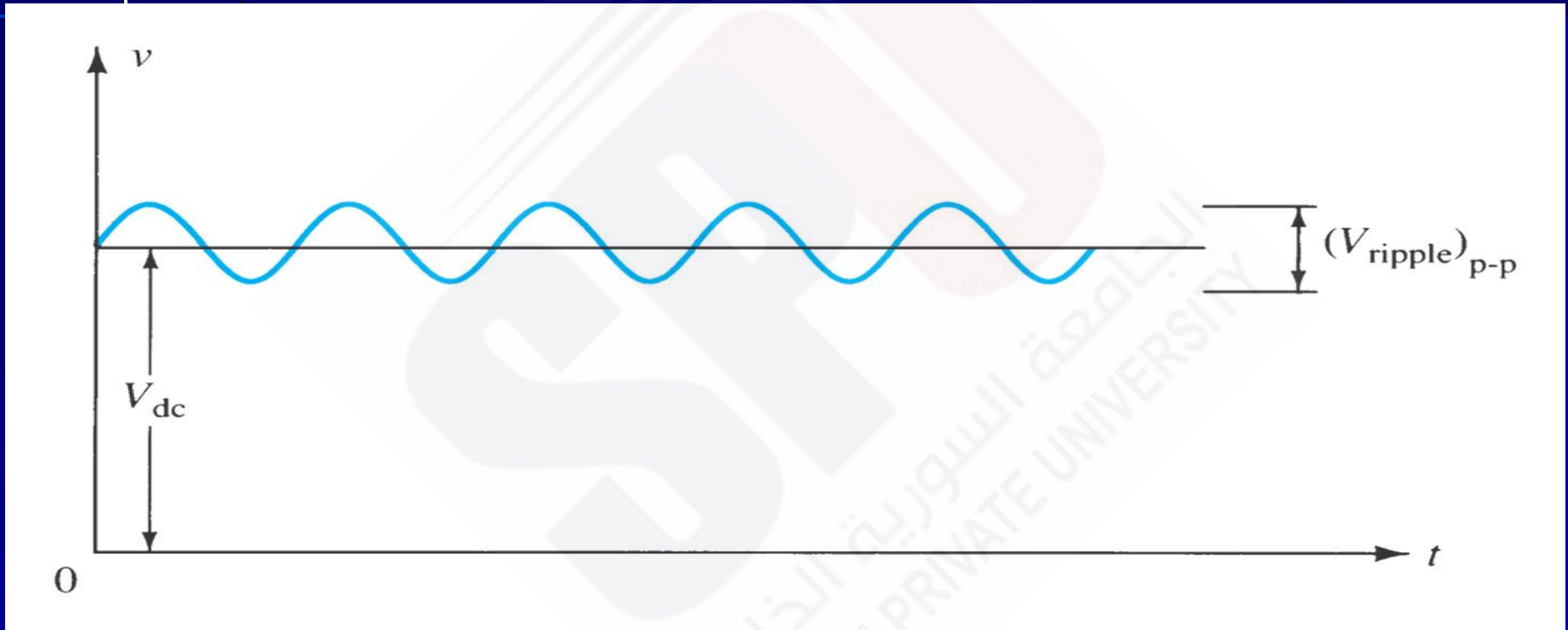

Ripple Factor

$$r = \frac{\text{ripple voltage(rms)}}{\text{dc voltage}} = \frac{V_r (rms)}{V_{dc}} \times 100\%$$


Voltage Regulation

Voltage Regulation = $\frac{\text{no load voltage} - \text{full load voltage}}{\text{full load voltage}}$

$$V.R. = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$



Ideal Regulation \Rightarrow V.R. = 0 (Ideal voltage source)

8.3 Capacitor Filter


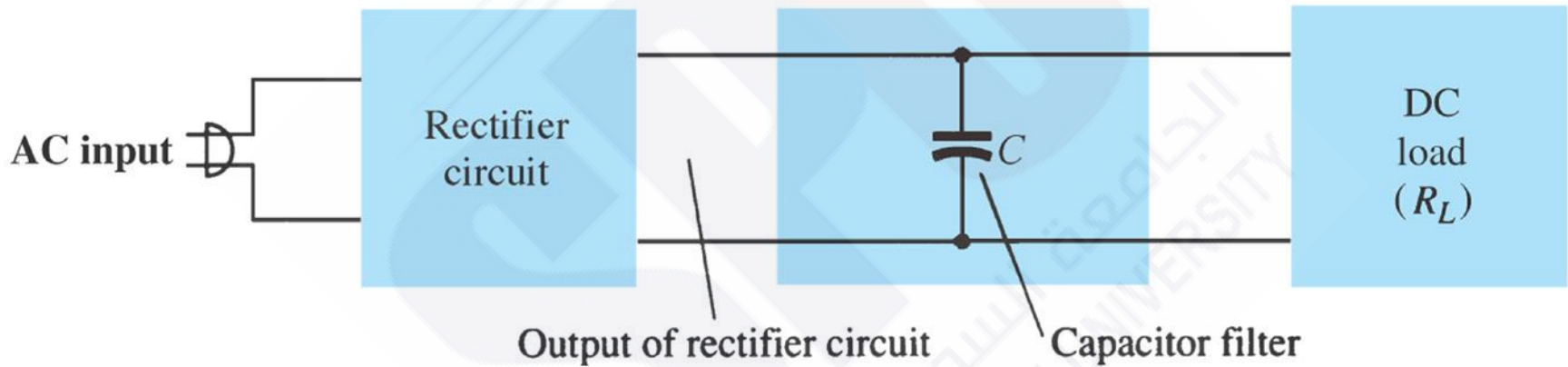


Simple Capacitor Filter

Simple Capacitor Filter

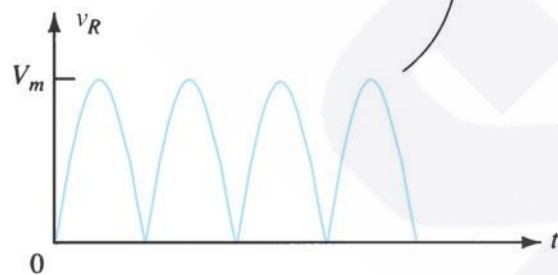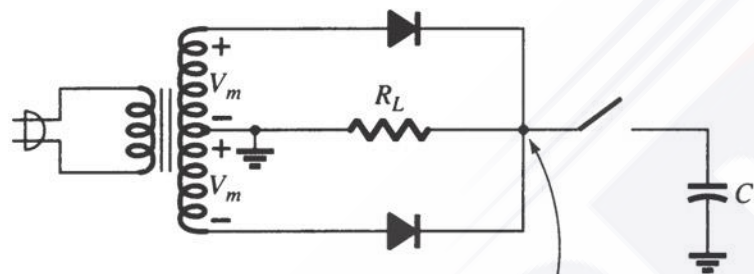


(a)

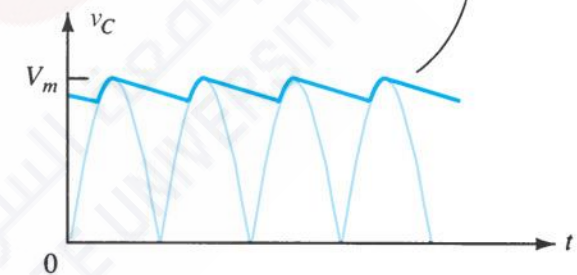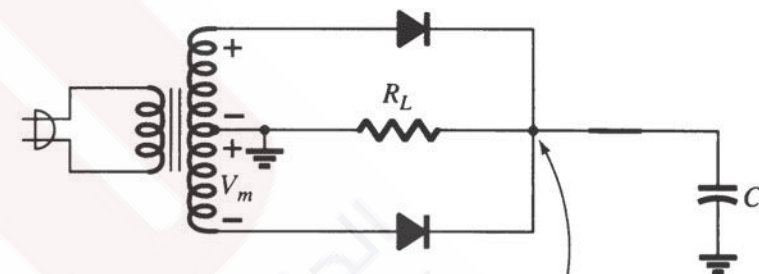


(b)

Simple Capacitor Filter

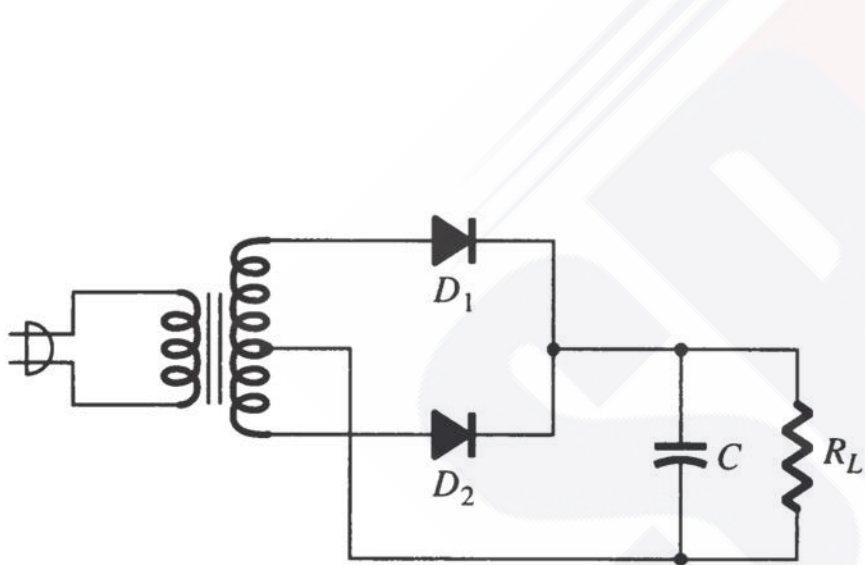


(a)

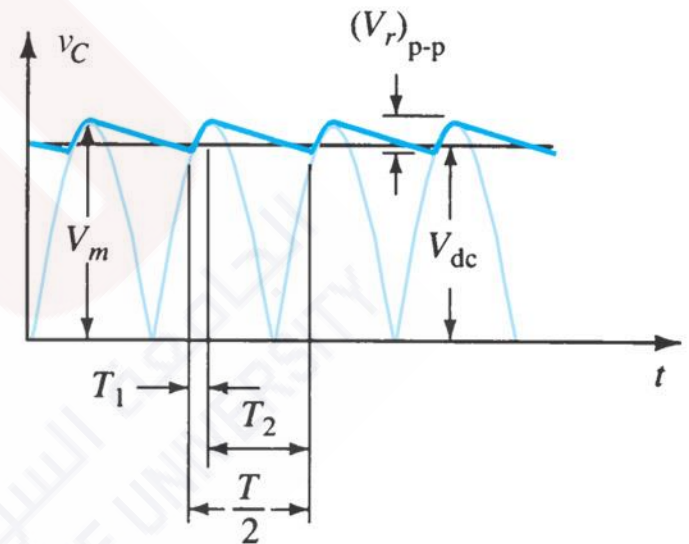


(b)

Effect of Load R_L

Simple Capacitor Filter

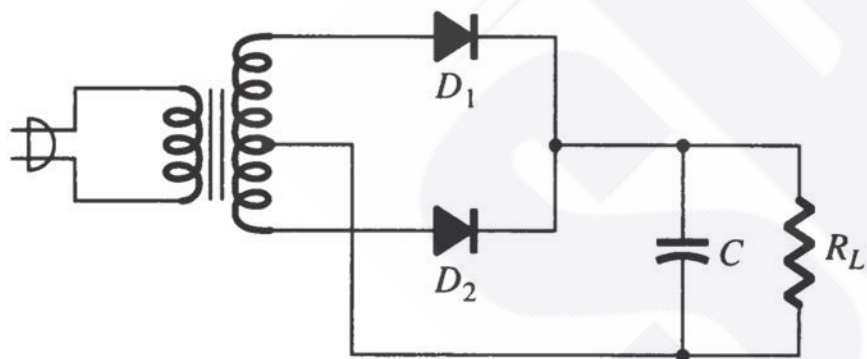


(a)

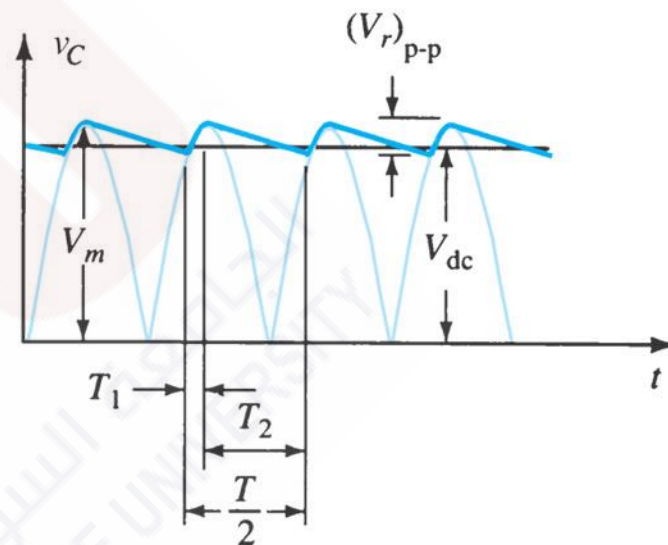

(b)

Effect of Load R_L : $V_m = V_{dc}$ if $R_L = \infty$


Output Waveform Times

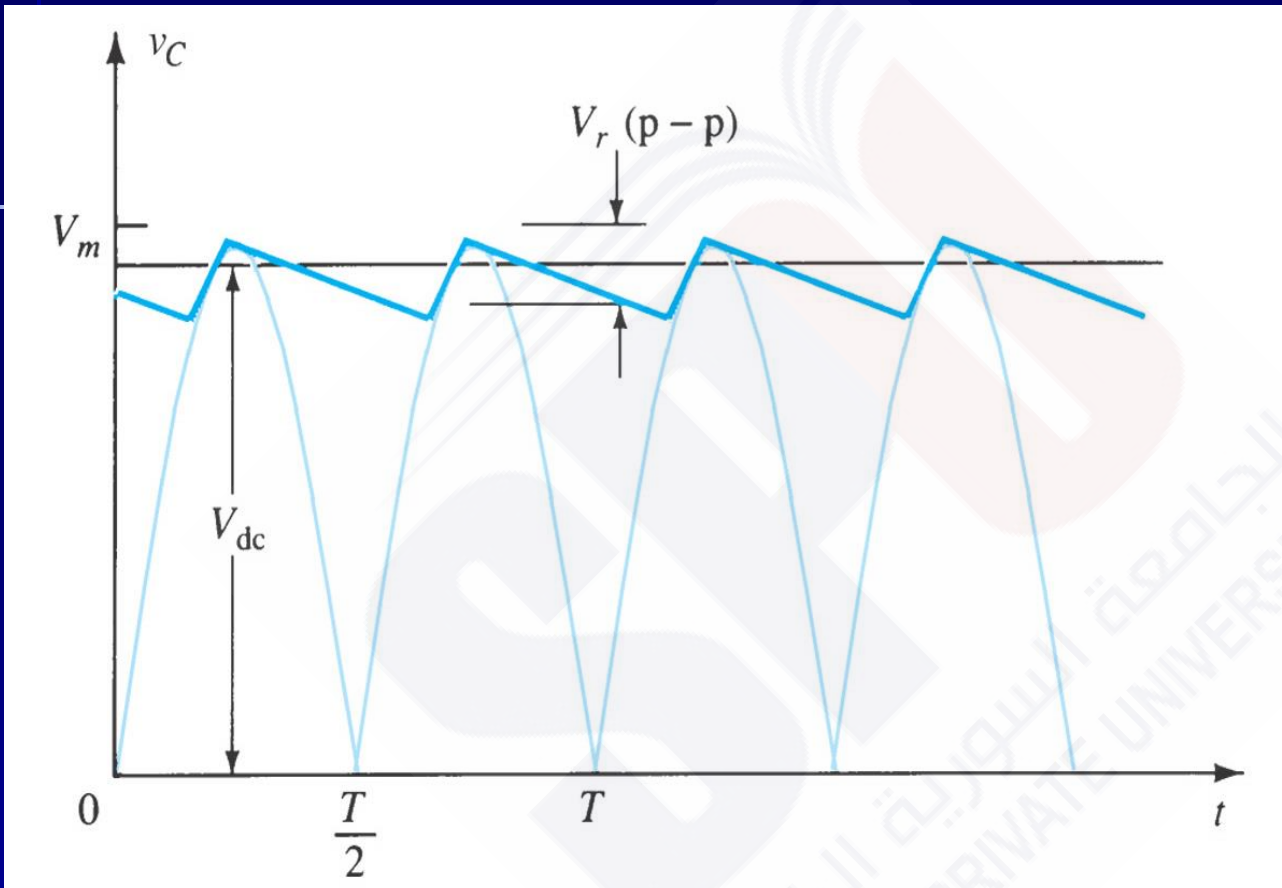

$$\text{Ripple Voltage : } V_r (rms) = \frac{I_{dc}}{4\sqrt{3}fc} = \frac{2.4I_{dc}}{C} = \frac{2.4V_{dc}}{CR_L}$$


$f = 60Hz$, I_{dc} in mA (ref. appendix C)

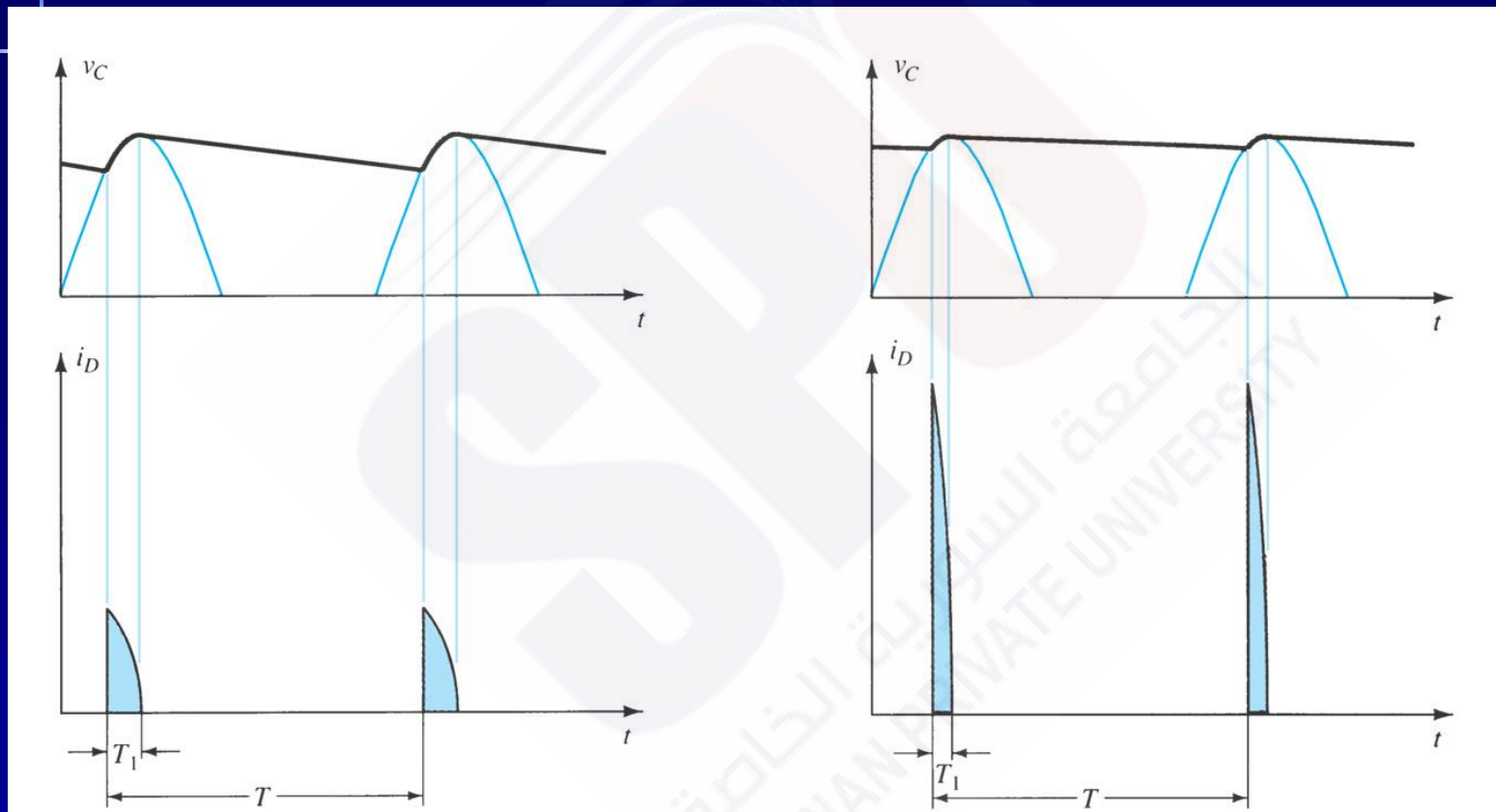Diode Conduction Period and Peak Diode Current




$$I_{dc} = \frac{T_1}{T} I_{peak} ; I_{peak} = \frac{T}{T_1} ; I_{dc} : \text{average current drawn from the filter}$$

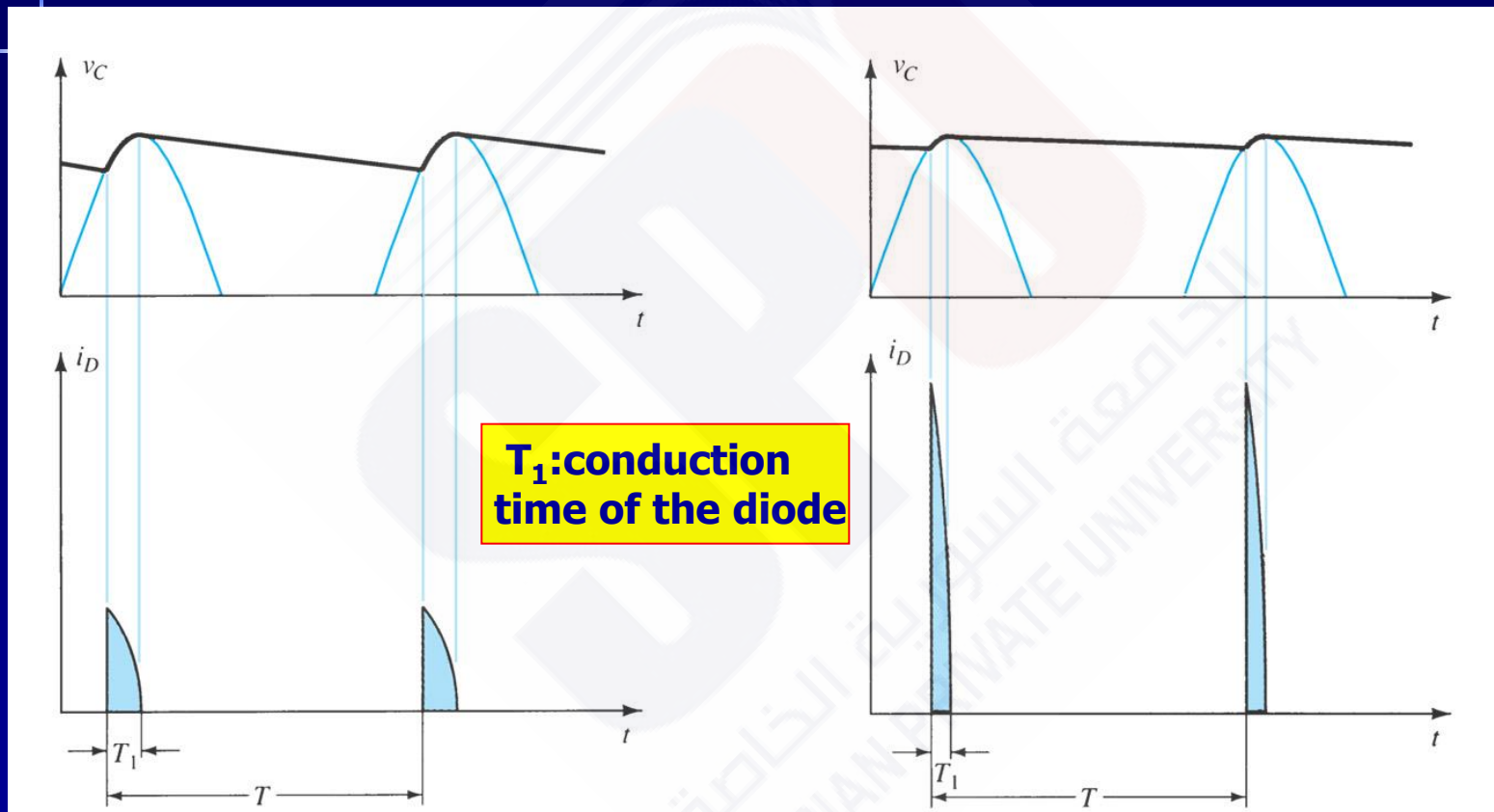Diode Conduction Period and Peak Diode Current




$$I_{dc} = \frac{T_1}{T} I_{peak} ; I_{peak} = \frac{T}{T_1} I_{dc} ; I_{dc} : \text{average current drawn from the filter}$$

8.4 RC Filter

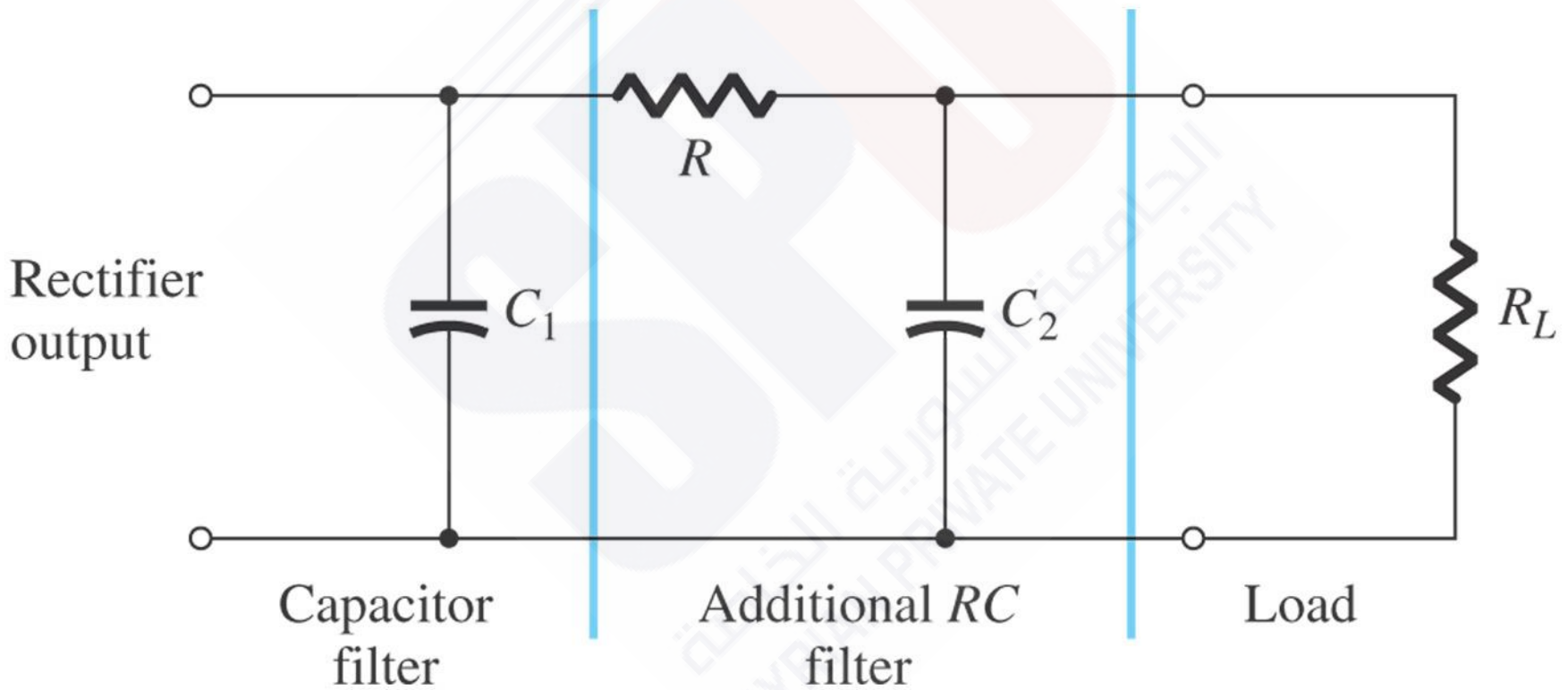

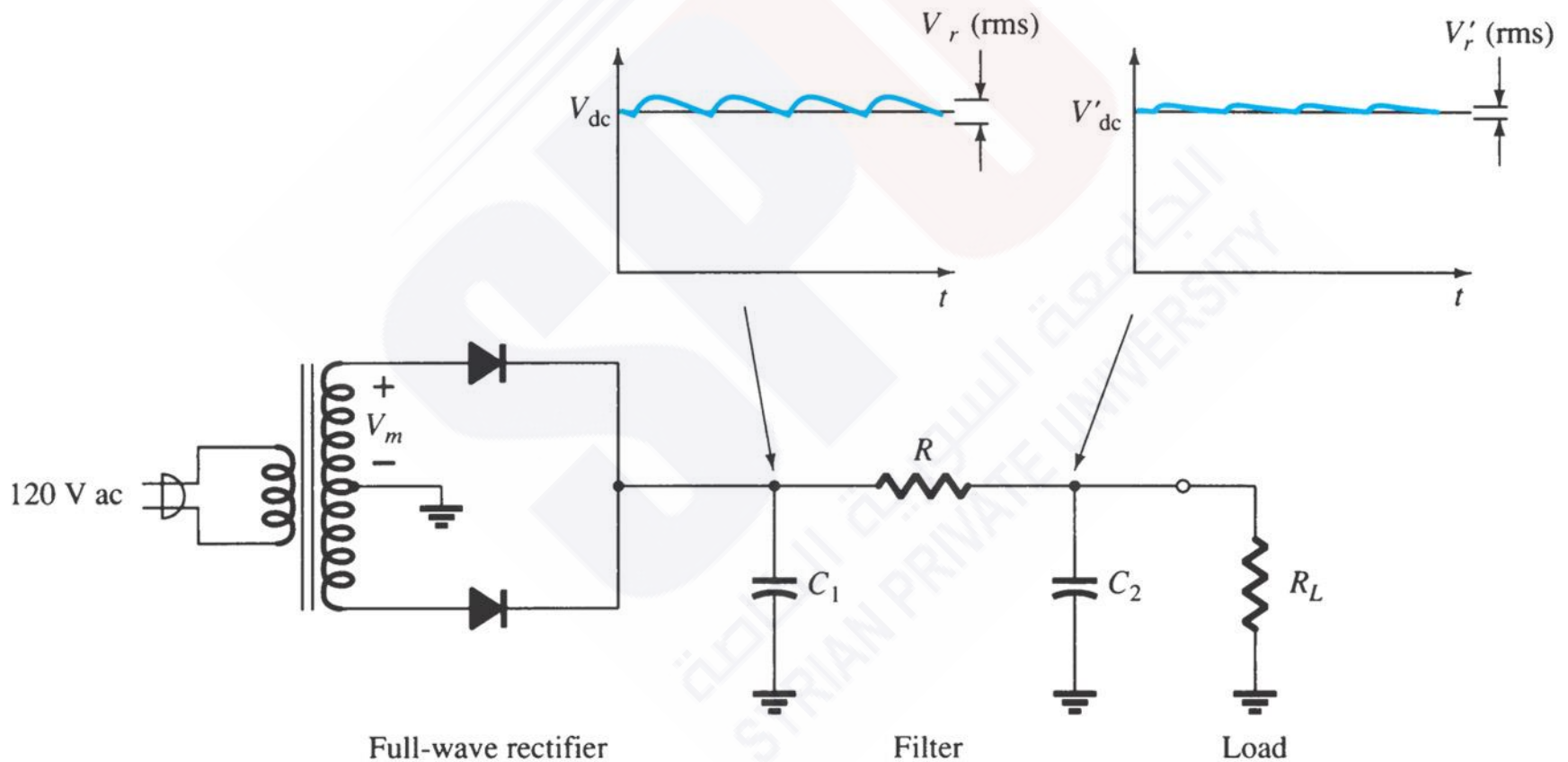
Full-wave rectifier and RC filter circuit




AC and DC Operation of RC Filter

dc voltage level
developed across
capacitor C_1

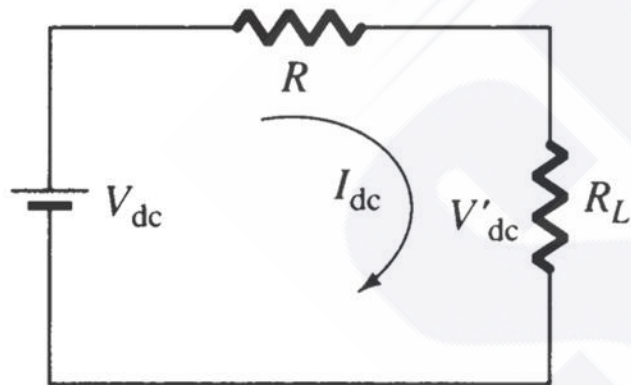ac ripple voltage developed
across capacitor C_1



(a)

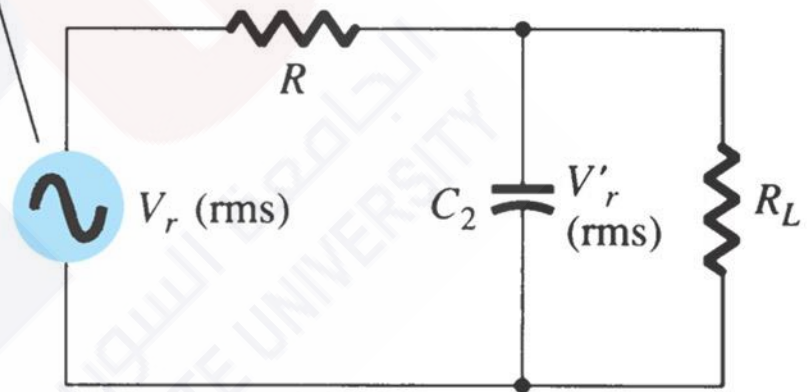


(b)

$$V'_r(rms) \approx \frac{1.3}{RC} V_r(rms)$$


AC and DC Operation of RC Filter

dc voltage level developed across capacitor C_1

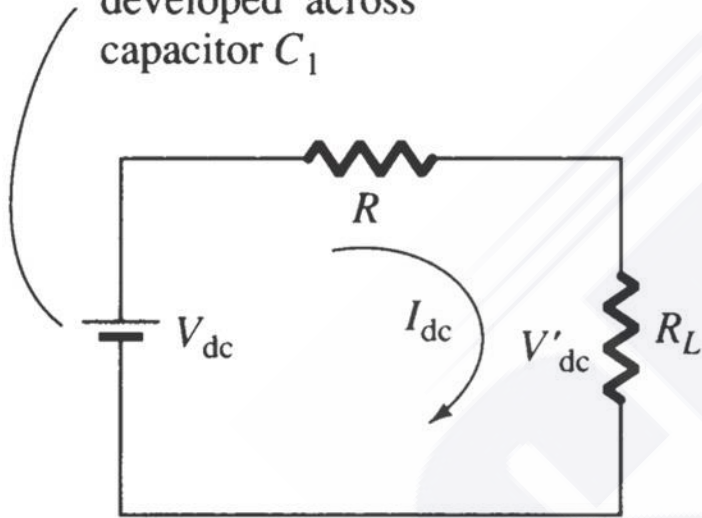ac ripple voltage developed across capacitor C_1




(a)

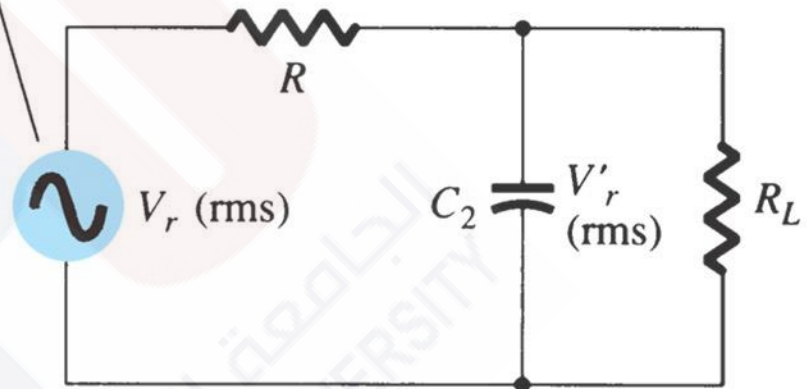

(b)
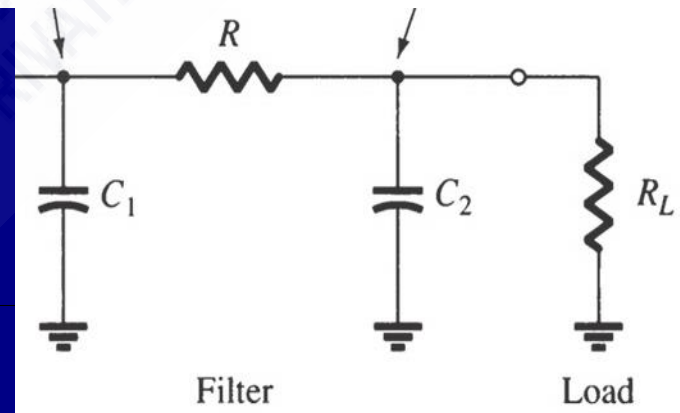
$$V'_r (rms) \approx \frac{1.3}{RC} V_r (rms)$$



Filter

Load

EXAMPLE 15.7 Calculate the dc and ac components of the output signal across load R_L in the circuit of Fig. 15.11. Calculate the ripple of the output waveform.

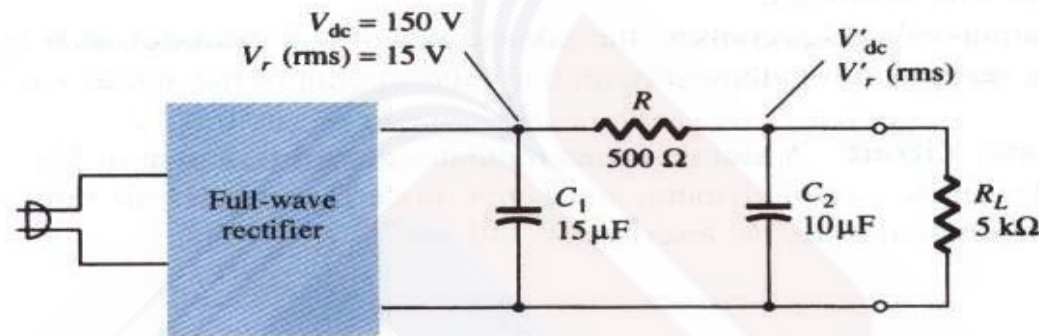


FIG. 15.11

RC filter circuit for Example 15.7.

Solution:

DC Calculation We obtain

$$\text{Eq. (15.13): } V'_{dc} = \frac{R_L}{R + R_L} V_{dc} = \frac{5 \text{ k}\Omega}{500 + 5 \text{ k}\Omega} (150 \text{ V}) = 136.4 \text{ V}$$

AC Calculation The RC -section capacitive impedance is

$$\text{Eq. (15.15): } X_C = \frac{1.3}{C} = \frac{1.3}{10} = 0.13 \text{ k}\Omega = 130 \Omega$$

The ac component of the output voltage, calculated using Eq. (15.14), is

$$V'_r(\text{rms}) = \frac{X_C}{R} V_r(\text{rms}) = \frac{130}{500} (15 \text{ V}) = 3.9 \text{ V}$$


The ripple of the output waveform is then

$$r = \frac{V'_r(\text{rms})}{V'_{dc}} \times 100\% = \frac{3.9 \text{ V}}{136.4 \text{ V}} \times 100\% = 2.86\%$$

8.5 Discrete Transistor Voltage Regulation


Series Voltage Regulation

Shunt Voltage Regulation

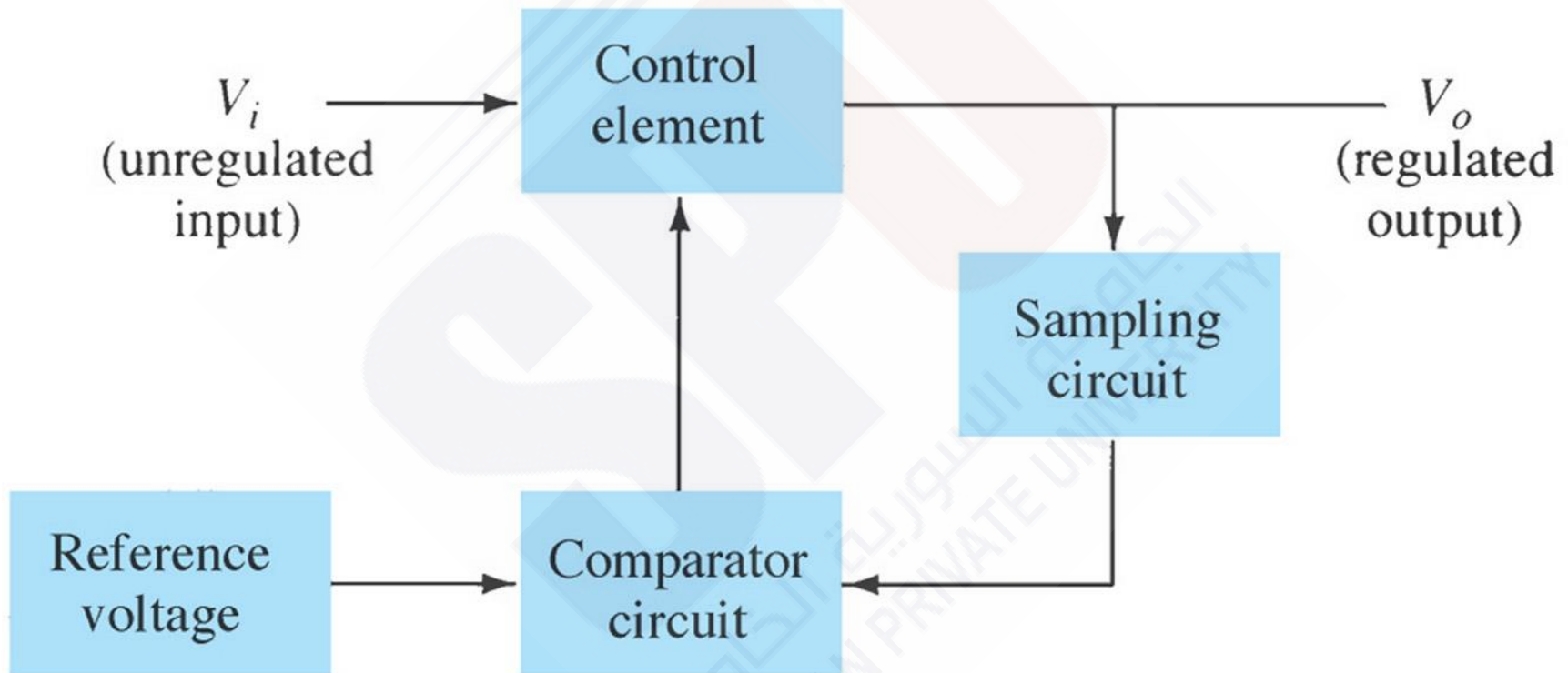


Series regulator block diagram

Series regulator circuit

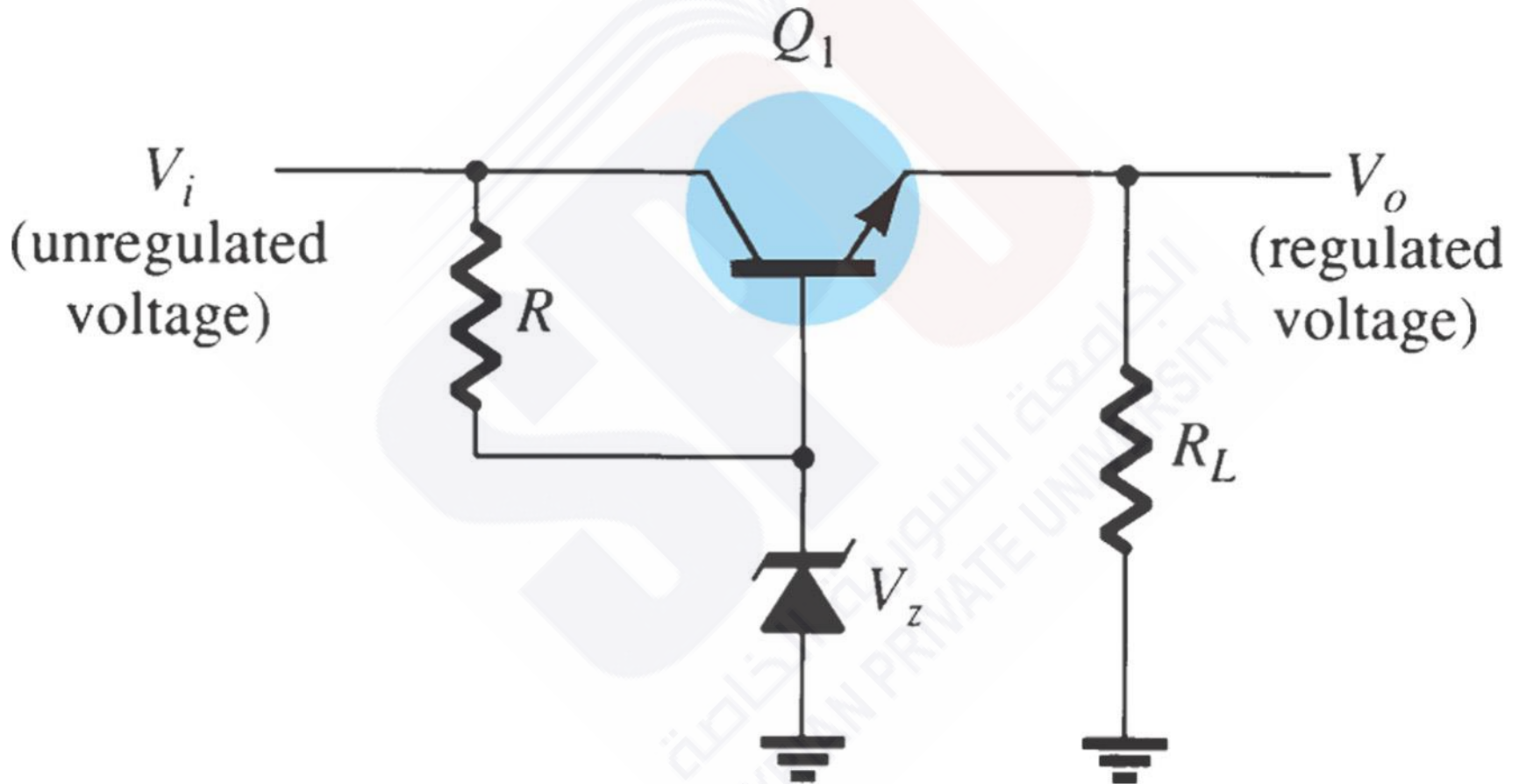


V_o increase $\rightarrow V_{BE}$ decrease \rightarrow less $I_L \rightarrow V_o$ decrease

Improved Series regulator circuit

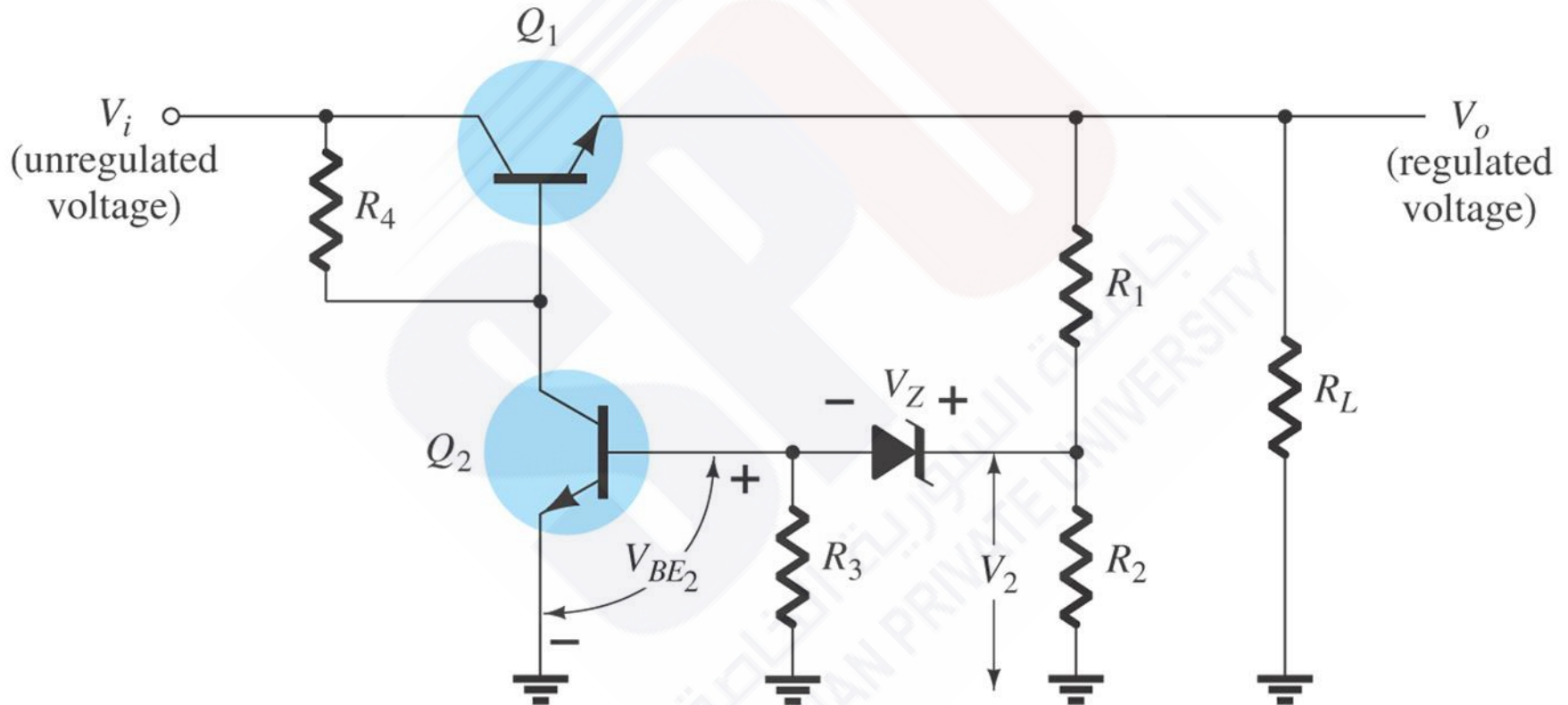


$$V_o = (V_Z + V_{BE2})(R_1 + R_2) / R_2$$

Op-amp series regulator circuit

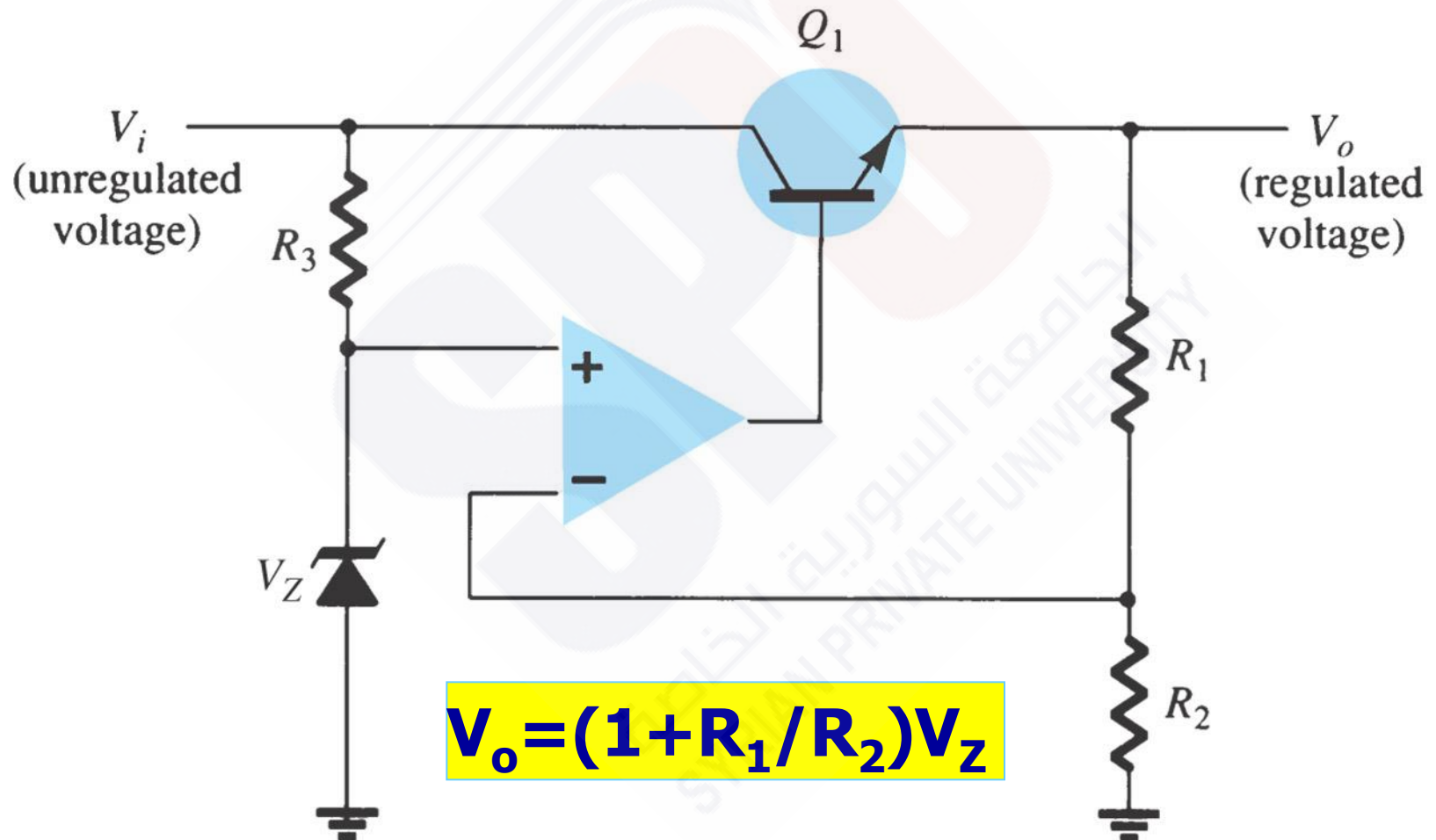


Current-limiting voltage regulator

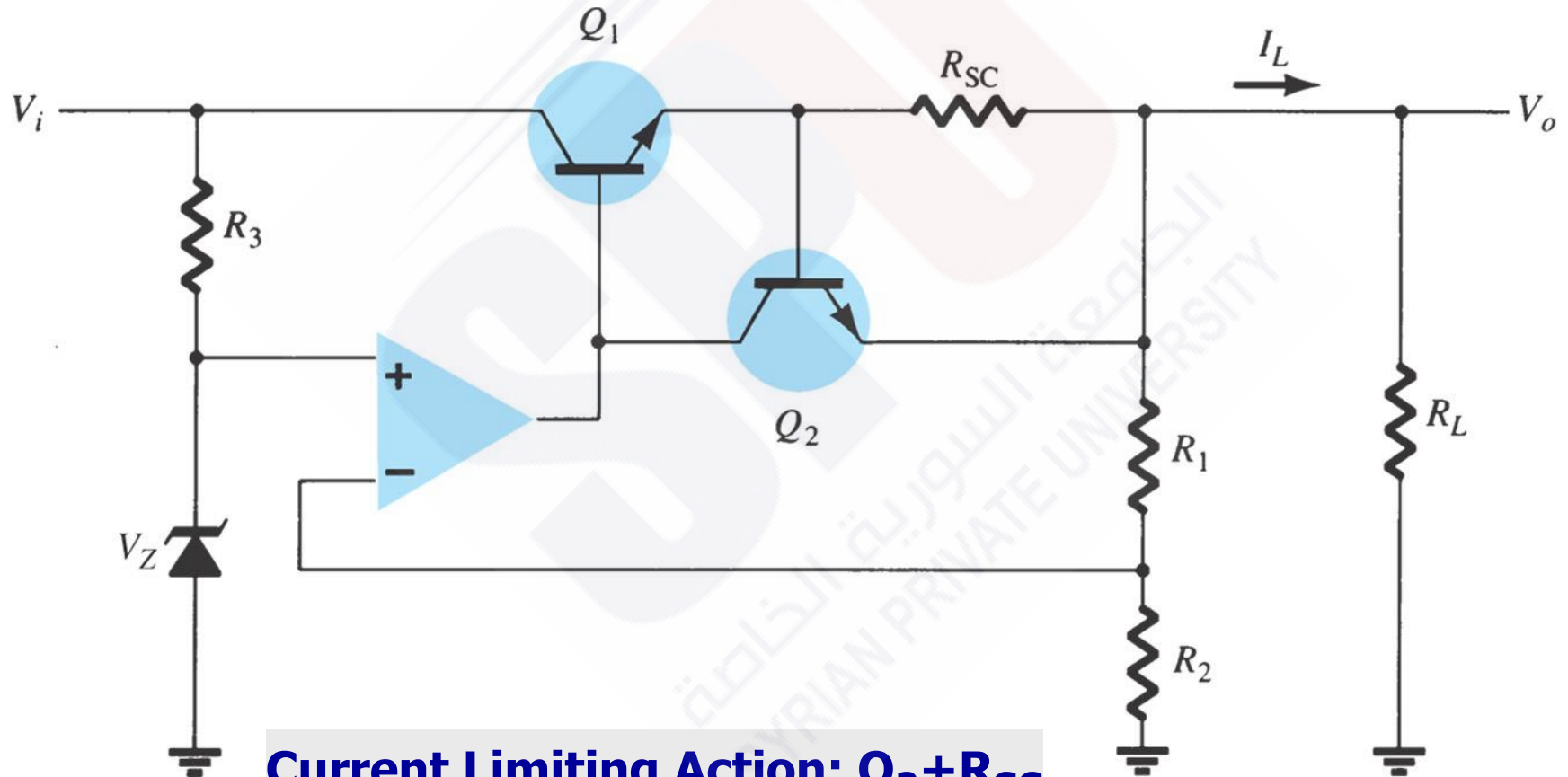


Current Limiting Action: $Q_2 + R_{SC}$

Block diagram of shunt voltage regulator

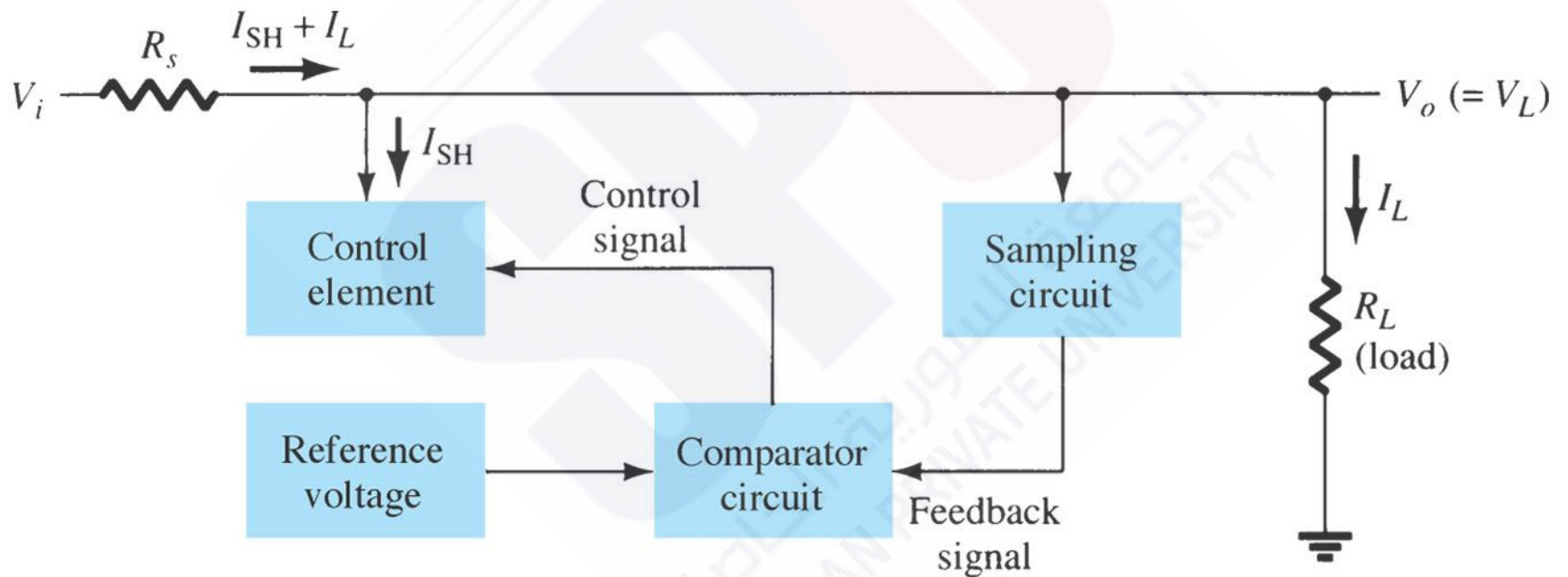

Transistor shunt voltage regulator

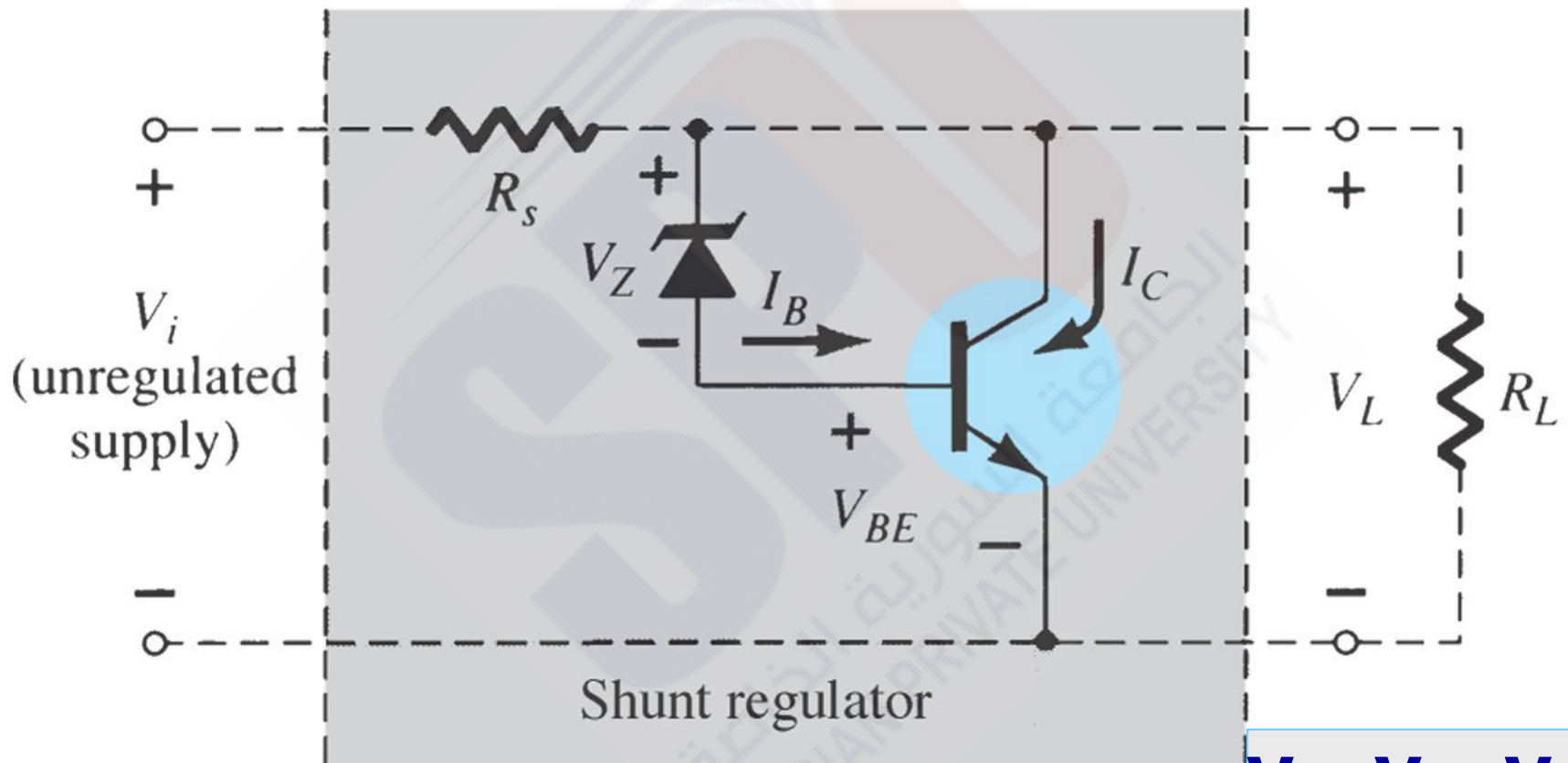

$$V_L = V_Z + V_{BE}$$

EXAMPLE 15.11 Determine the regulated voltage and circuit currents for the shunt regulator of Fig. 15.22.

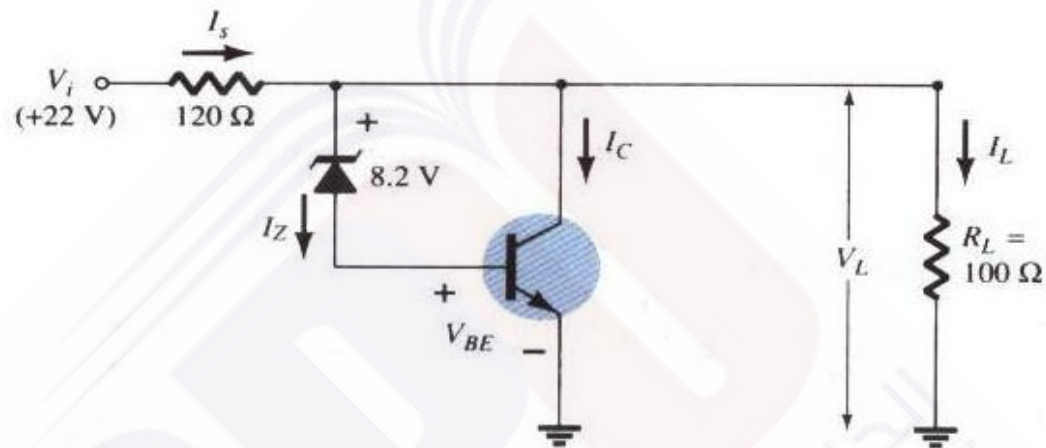


FIG. 15.22
Circuit for Example 15.11.

Solution: The load voltage is

$$\text{Eq. (15.19): } V_L = 8.2 \text{ V} + 0.7 \text{ V} = \mathbf{8.9 \text{ V}}$$

For the given load,

$$I_L = \frac{V_L}{R_L} = \frac{8.9 \text{ V}}{100 \Omega} = \mathbf{89 \text{ mA}}$$


With the unregulated input voltage at 22 V, the current through R_s is

$$I_S = \frac{V_i - V_L}{R_S} = \frac{22 \text{ V} - 8.9 \text{ V}}{120} = \mathbf{109 \text{ mA}}$$

so that the collector current is


$$I_C = I_S - I_L = 109 \text{ mA} - 89 \text{ mA} = \mathbf{20 \text{ mA}}$$

Improved shunt voltage regulator

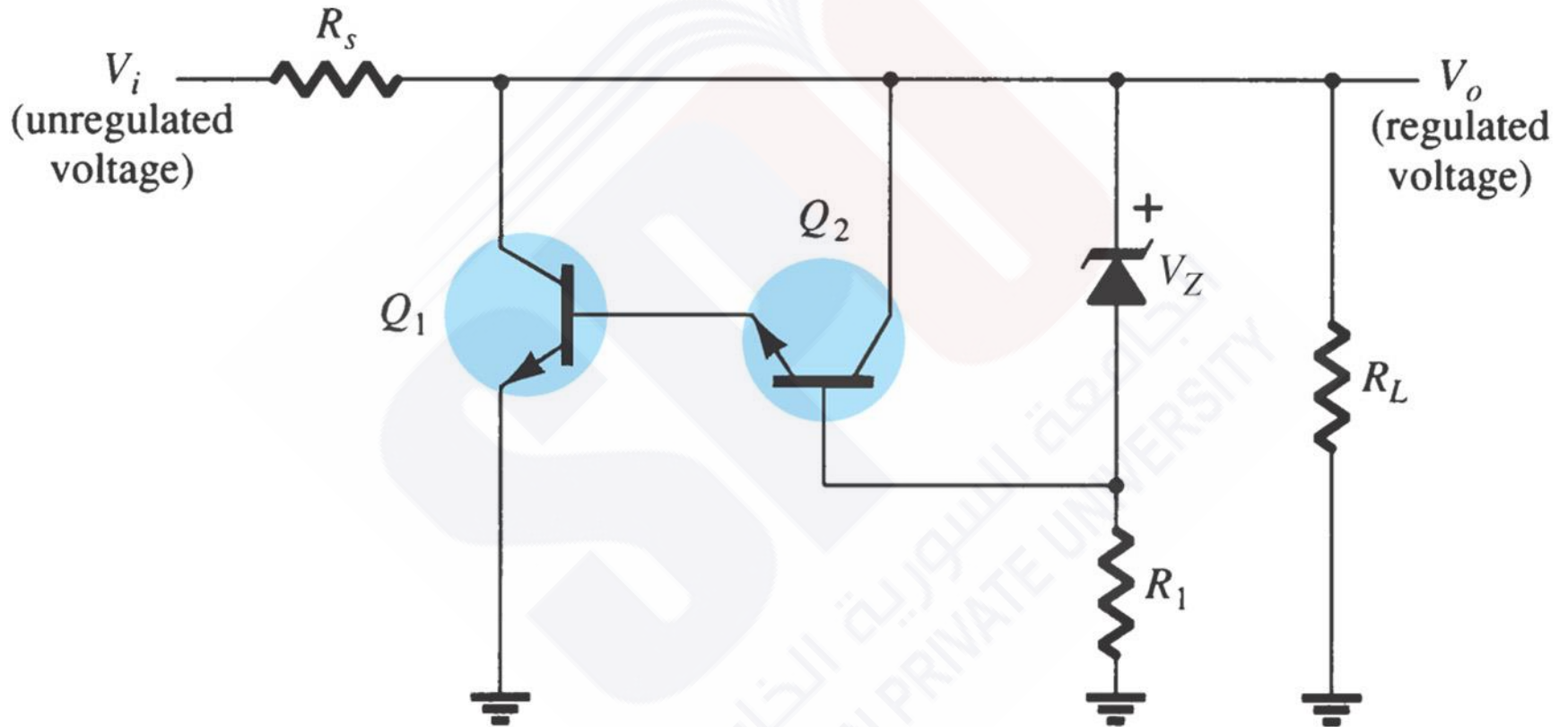


$$V_L = V_Z + V_{BE1} + V_{BE2}$$


Shunt voltage regulator using op-amp

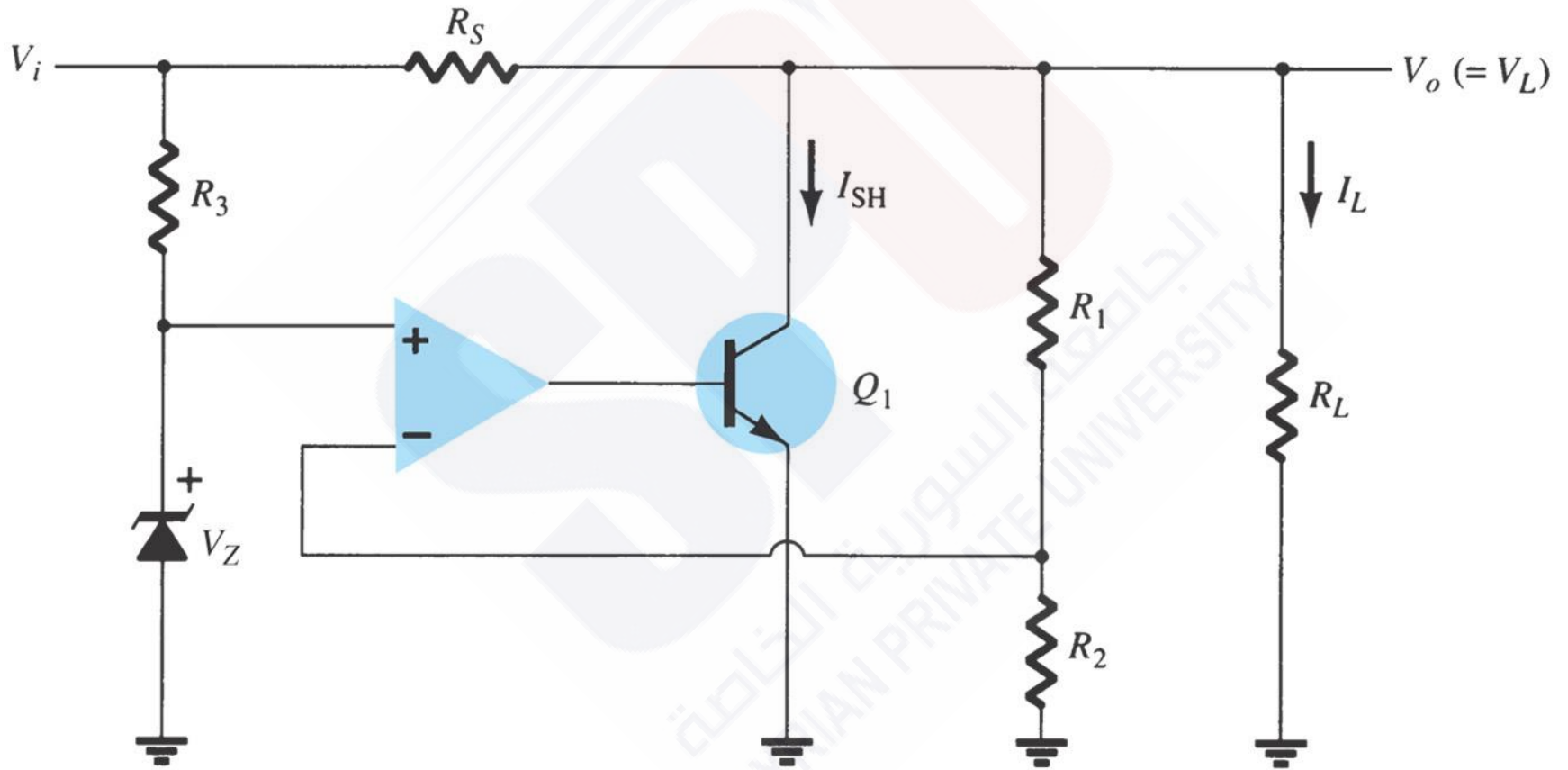

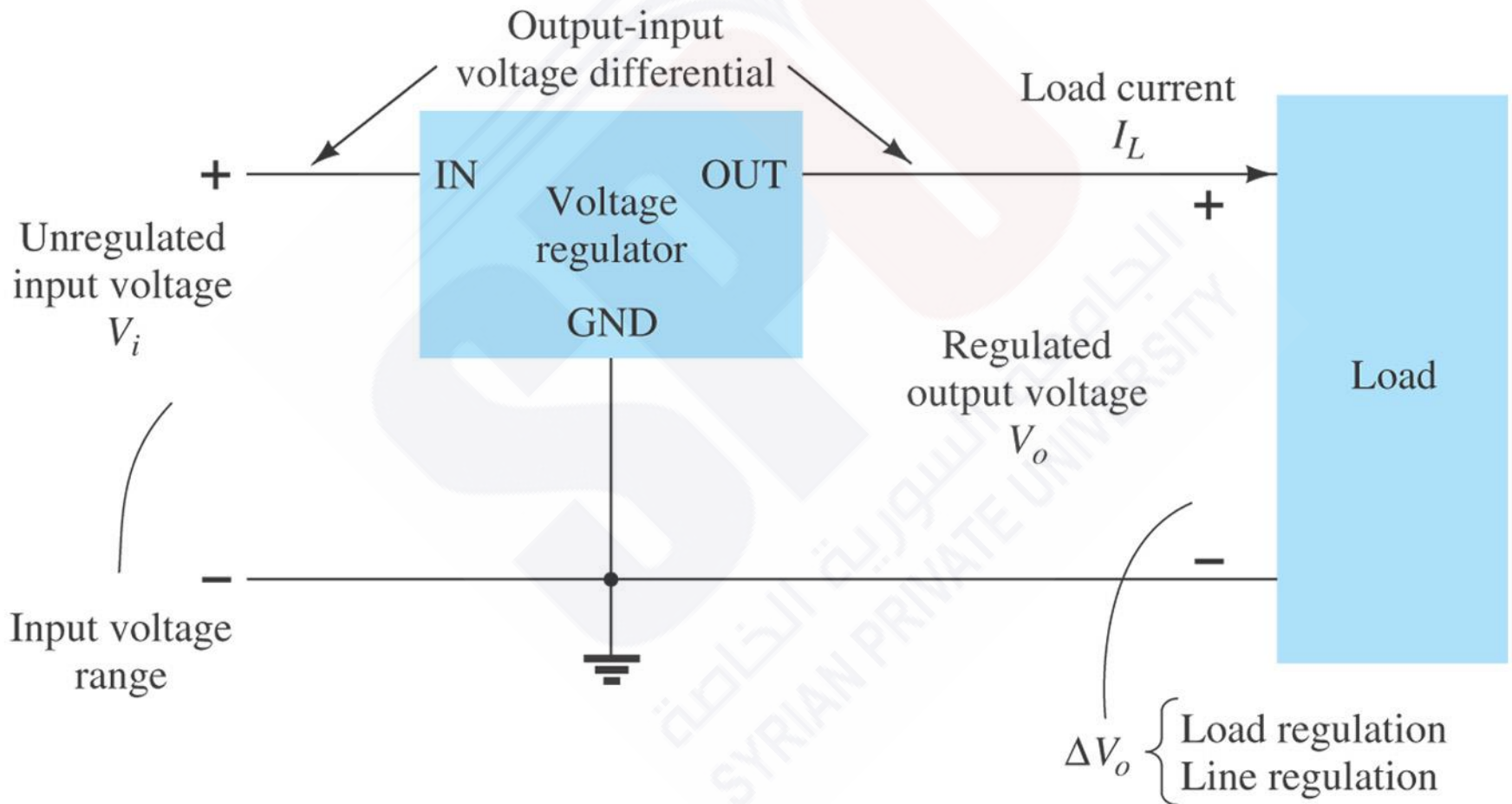Block representation of three-terminal voltage regulator





8.6 IC Voltage Regulators

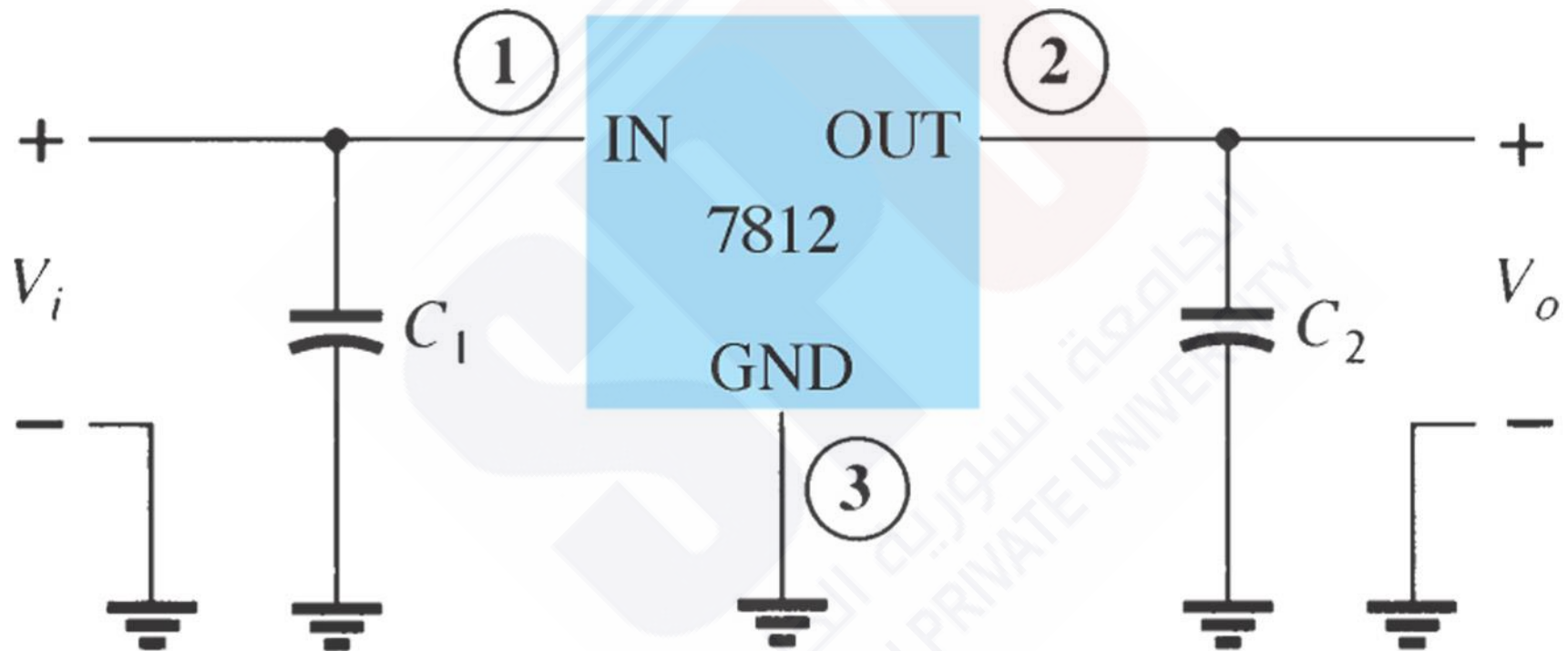

Reference Source + Comparator Amp + Control Device + Overload Protection

A +12 V power supply

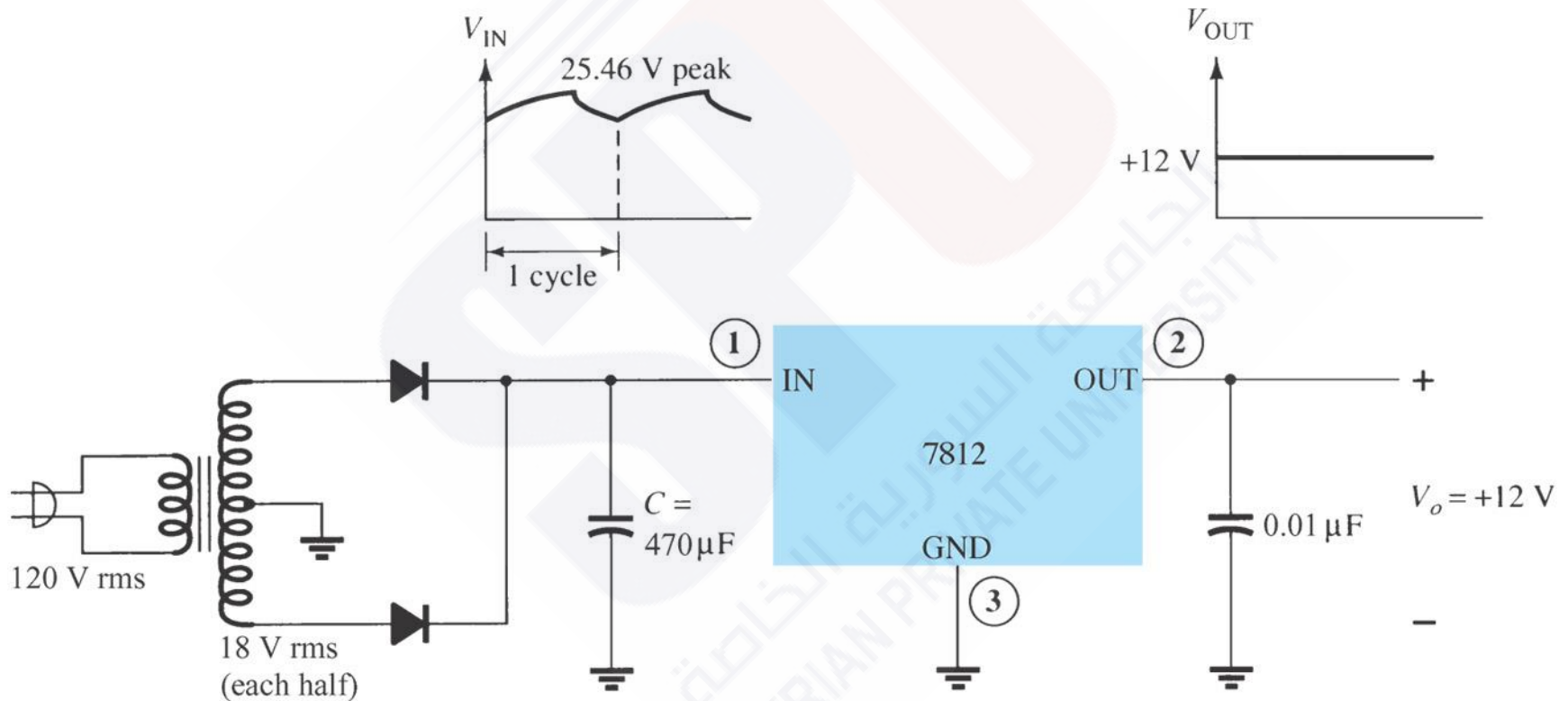

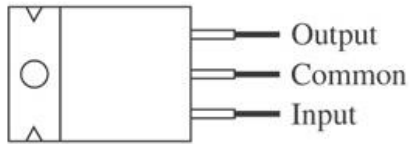

Nominal output voltage	Regulator
5 V	7805
6 V	7806
8 V	7808
10 V	7810
12 V	7812
15 V	7815
18 V	7818
24 V	7824

Absolute maximum ratings:

Input voltage 40 V
 Continuous total dissipation 2 W
 Operating free-air temperature range -65 to 150°C


µA 7812C electrical characteristics:

Parameter	Min.	Typ.	Max.	Units
Output voltage	11.5	12	12.5	V
Input regulation		3	120	mV
Ripple rejection	55	71		dB
Output regulation		4	100	mV
Output resistance		0.018		Ω
Dropout voltage		2.0		V
Short-circuit output current		350		mA
Peak output current		2.2		A

Specification data-sheet of voltage regulator ICs

IC	VO (V)	Min.Vi (V)
7805	+5	7.3
7806	+6	8.3
7808	+8	10.5
7810	+10	12.5

A +5-V power supply

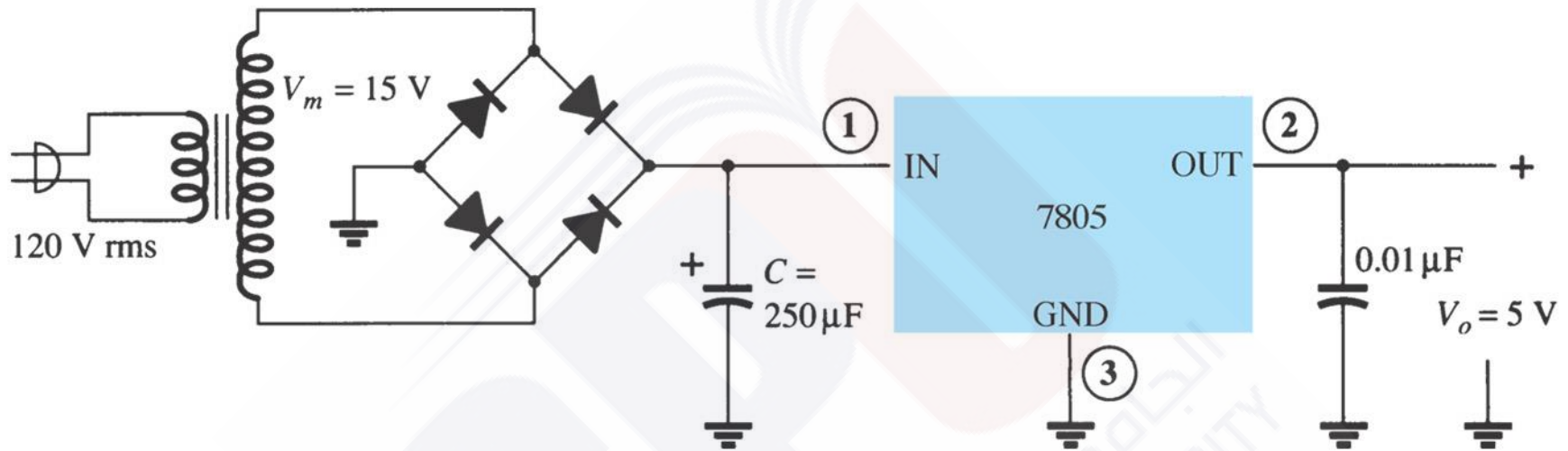


Calculate $V_{i\min} = V_{dc} - V_r(p)$, when $I_L = 400 \text{ mA}$?

$$V_r(\text{peak}) = \sqrt{3}V_r(\text{rms}) = \sqrt{3} \frac{2.4I_{dc}}{C} = \sqrt{3} \frac{2.4(400)}{250} = 6.65V$$


$$V_{dc} = V_m - V_r(\text{peak}) = 15V - 6.65V = 8.35V$$

$$V_i(\text{low}) = V_{dc} - V_r(\text{peak}) = 15 - 6.65 = 8.35V$$

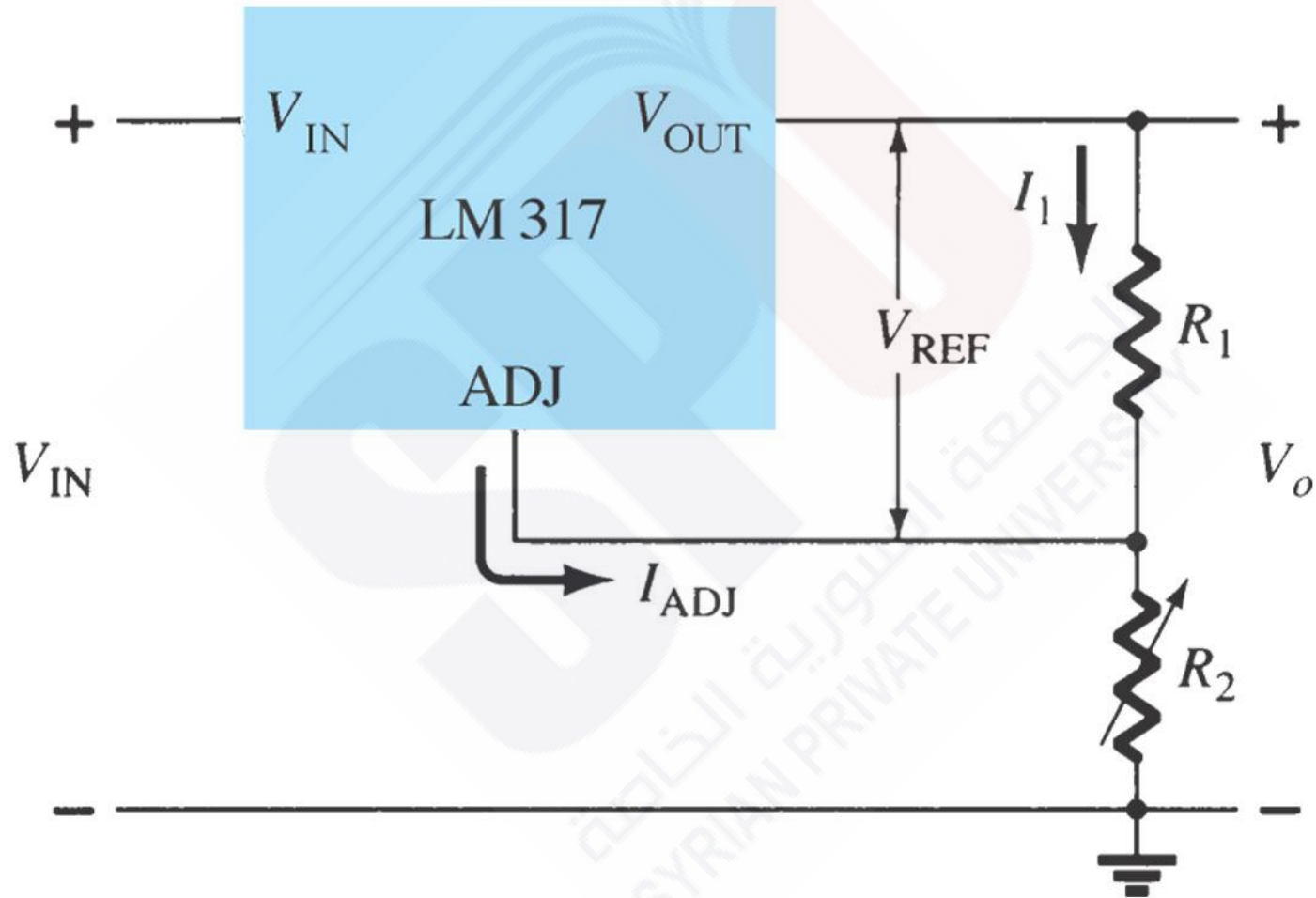Connection of LM317 adjustable-voltage regulator




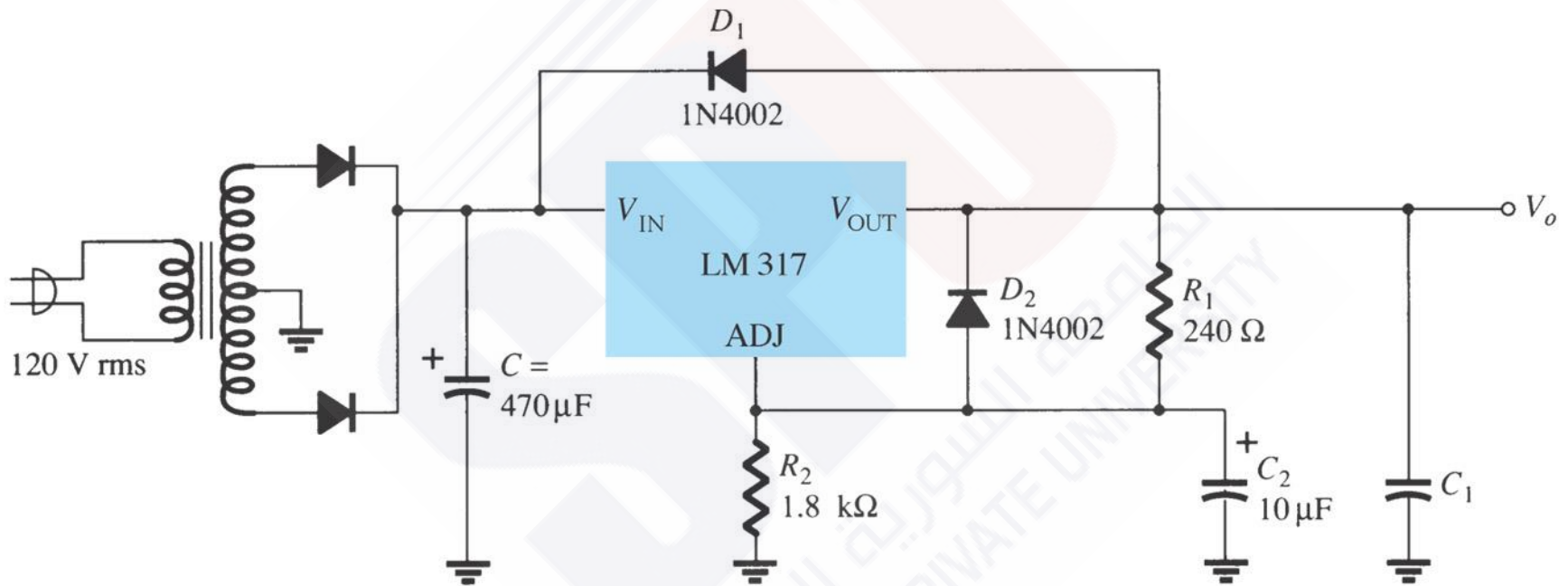Positive adjustable-voltage regulator Example





Determine the regulated V_o ?

8.7 Applications

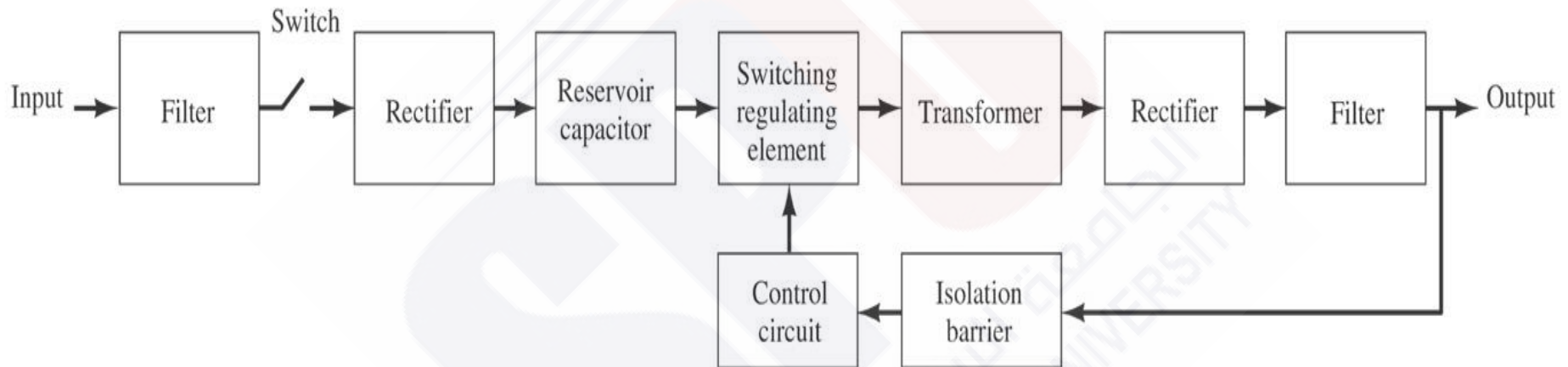


Block diagram of chopper power supply

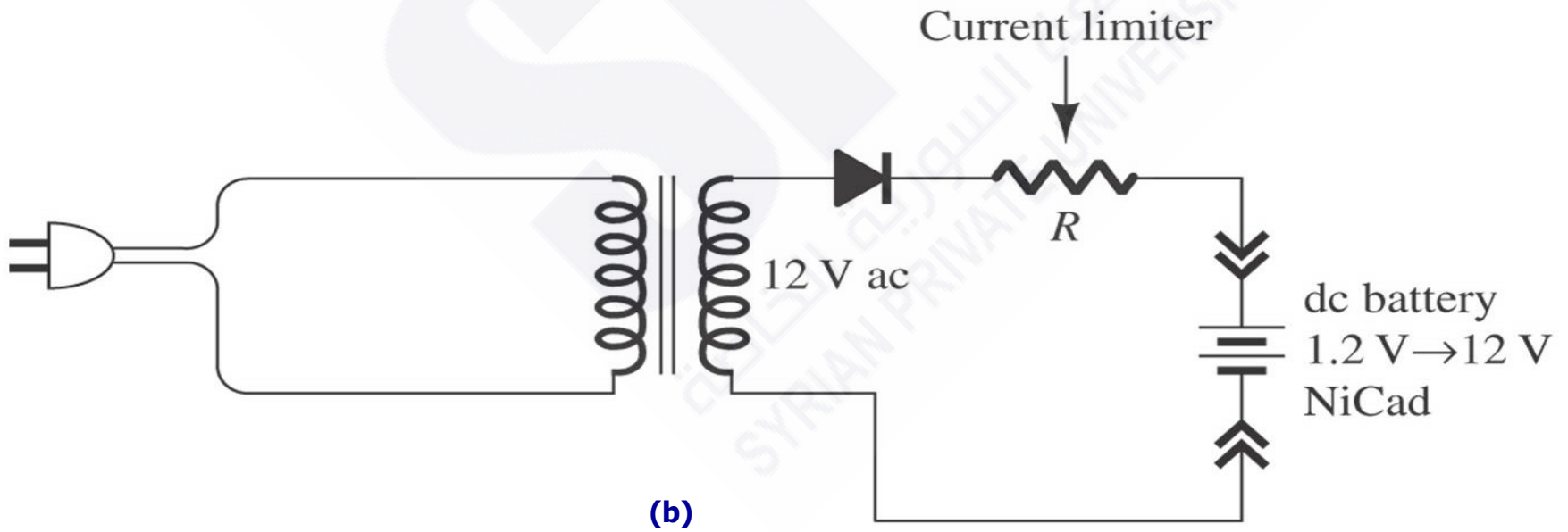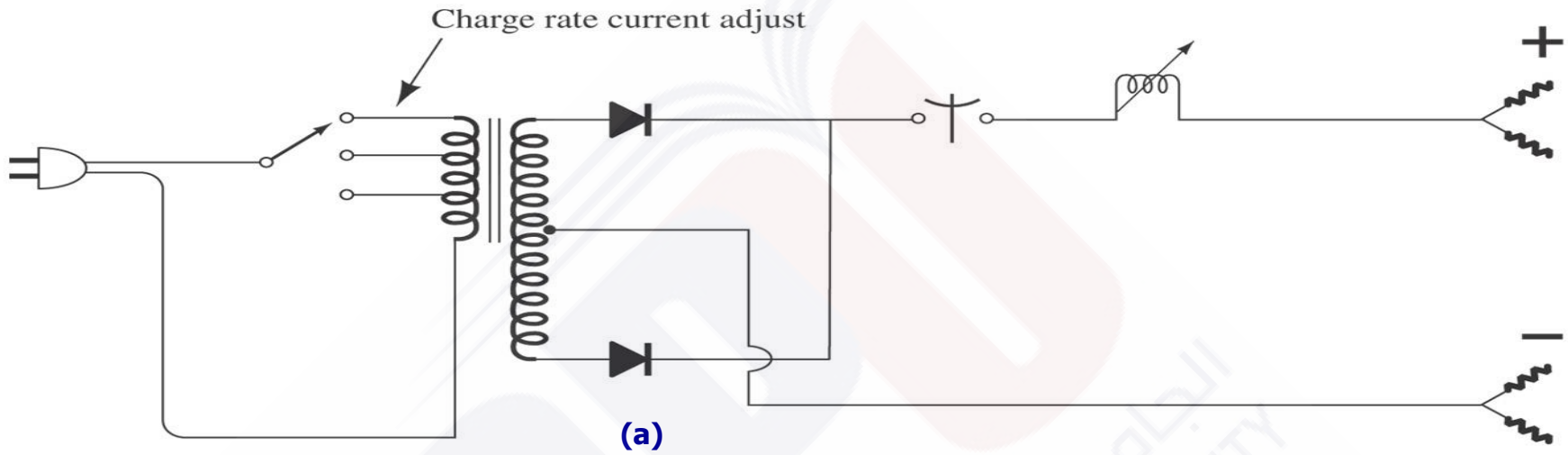Battery charger circuits: (a) Single charging circuit; (b) typical NiCad charging circuit



Calculate V_o ?

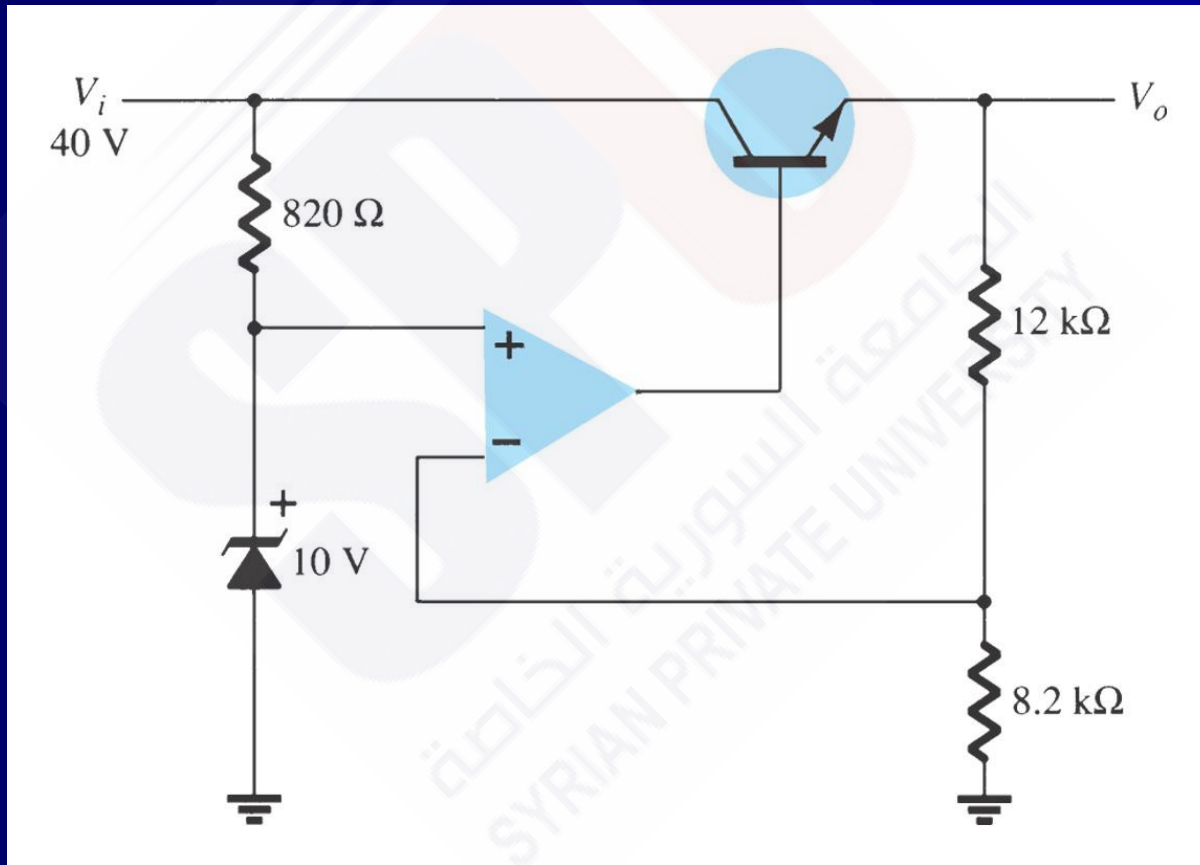

Calculate the I_{Lmax} to maintain regulated V_o

