
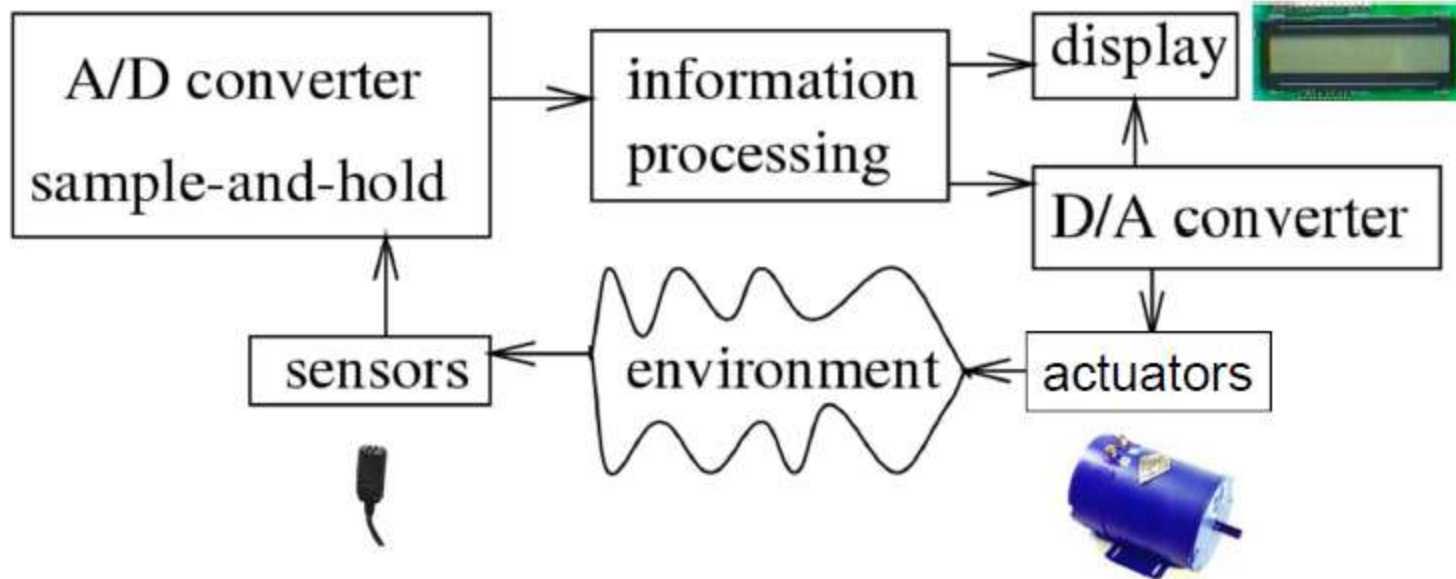


Embedded System Hardware

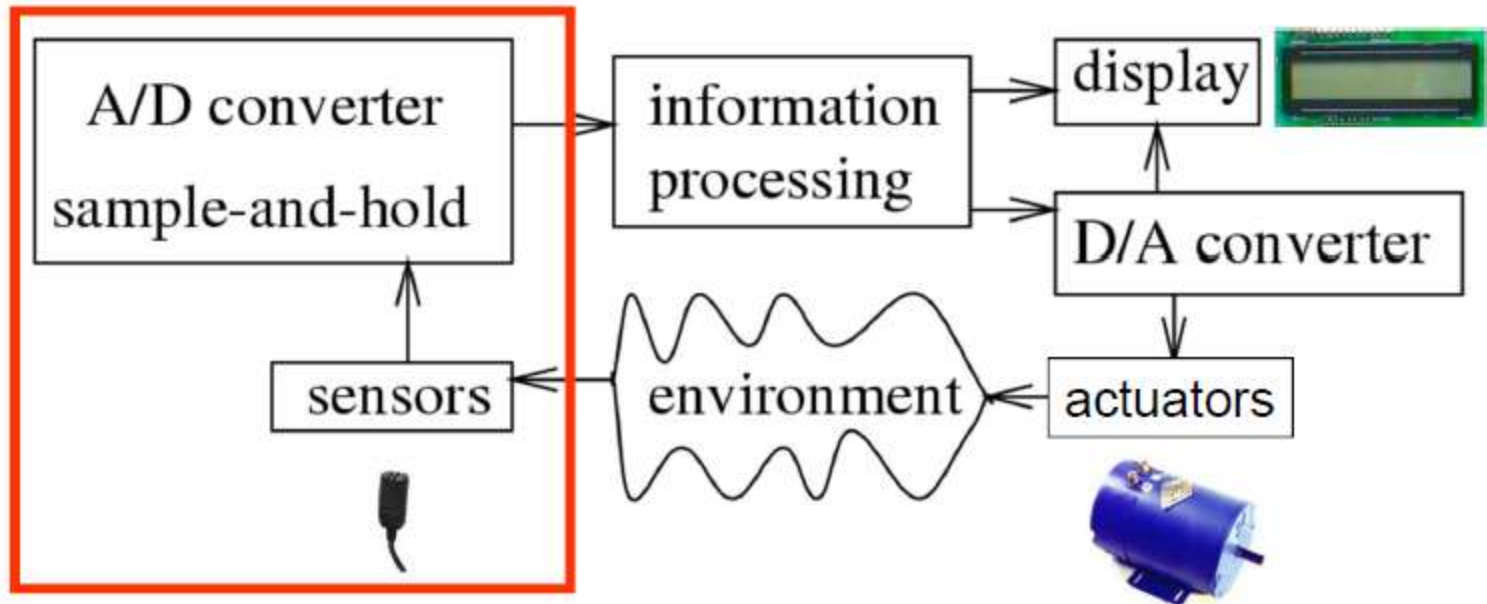
- Embedded system hardware is frequently used in a loop



Sensors







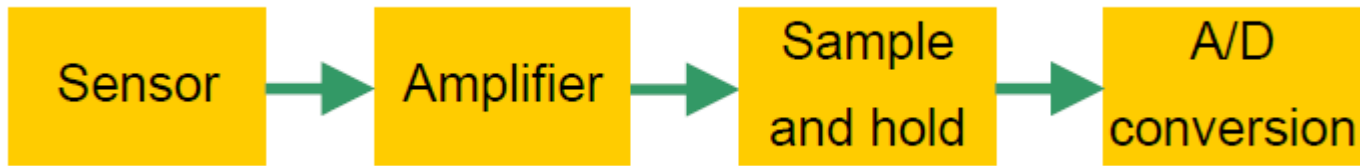- Processing of physical data starts with capturing this data.
- Sensors can be designed for virtually every physical and chemical quantity:
 - ❑ including weight, velocity, acceleration, electrical current, voltage, temperatures etc.
 - ❑ chemical compounds.



- Sensor: detects/measures entity and converts it to electrical domain
- Amplifier: adjusts signal to the dynamic range of the A/D Conversion
- Sample + hold: samples signal at discrete time instants
- A/D conversion: converts samples to digital domain

Discretization of time

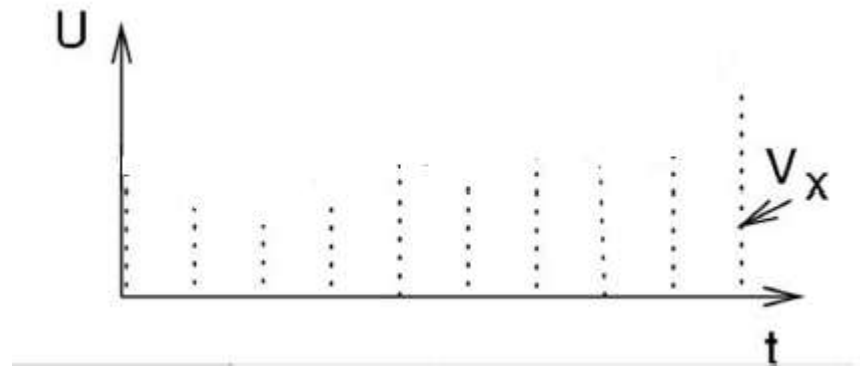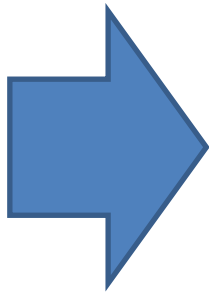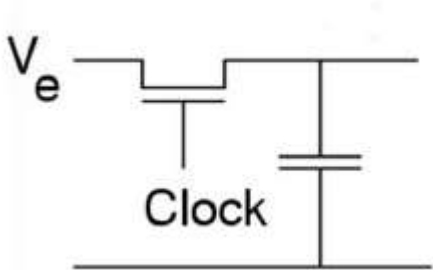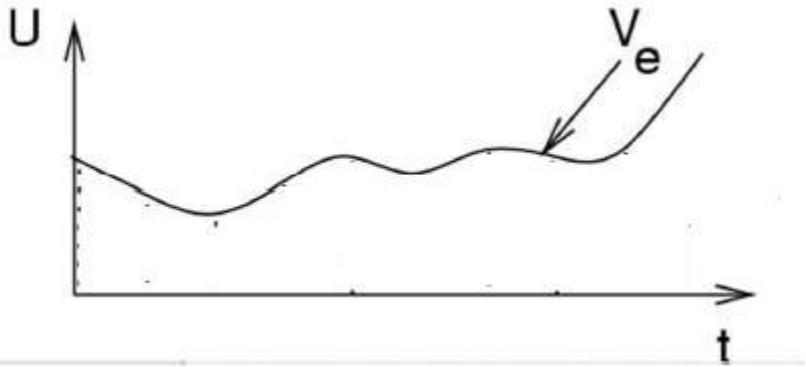


A/D-converters

- **Flash A/D converter:**

- Basic element: analog comparator:

- ❖ Output = '1' if voltage at input + exceeds that at input "-".

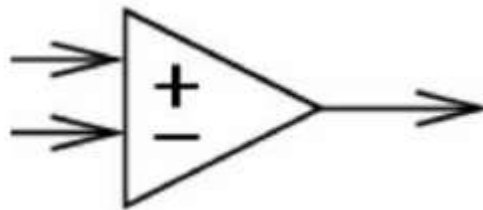- ❖ Output = '0' if voltage at input - exceeds that at input "+".





- Generate n different voltages by voltage divider (resistors),

e.g. V_{ref} , $\frac{3}{4} V_{ref}$, $\frac{1}{2} V_{ref}$, $\frac{1}{4} V_{ref}$.

- Use n comparators for parallel comparison of input voltage V_x to these voltages.
- Encoder to compute digital output.

Flash A/D converter


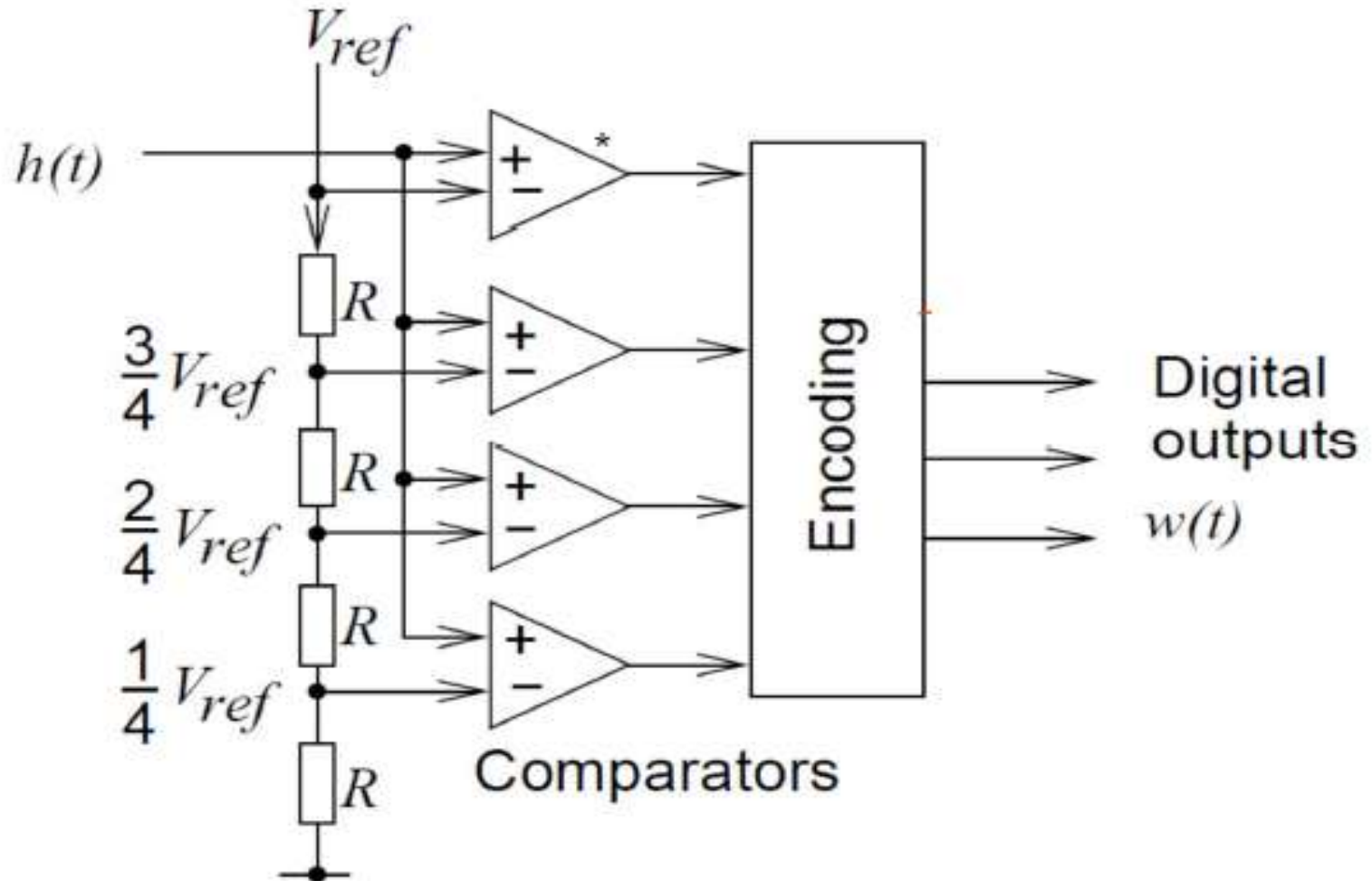


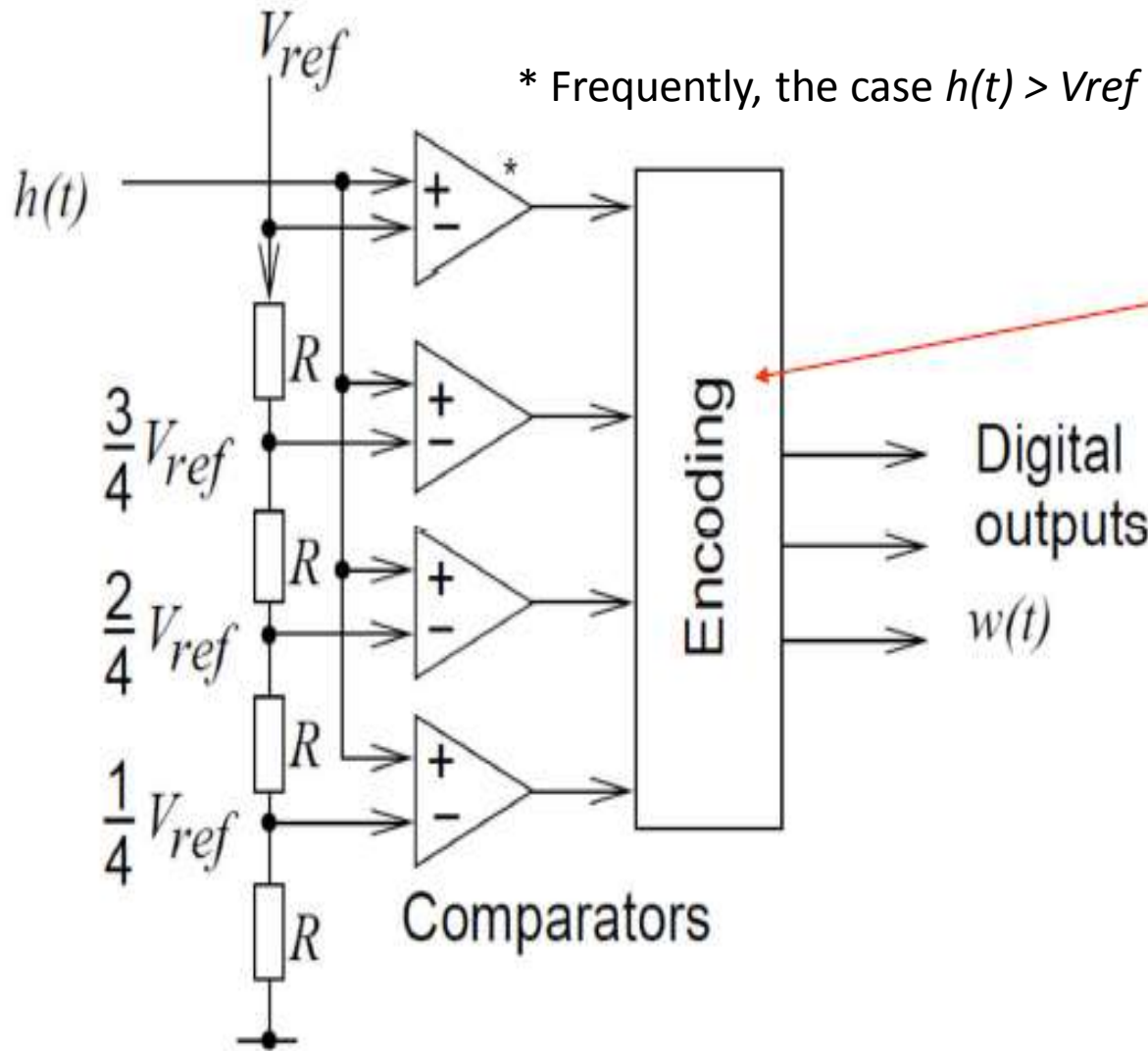

* Frequently, the case $h(t) > V_{ref}$ would not be decoded

- Encodes input number of most significant '1' as an unsigned number, e.g.
 - "1111" -> "100",
 - "0111" -> "011",
 - "0011" -> "010",
 - "0001" -> "001",
 - "0000" -> "000"
 (Priority encoder).

Assuming $0 \leq h(t) \leq V_{ref}$

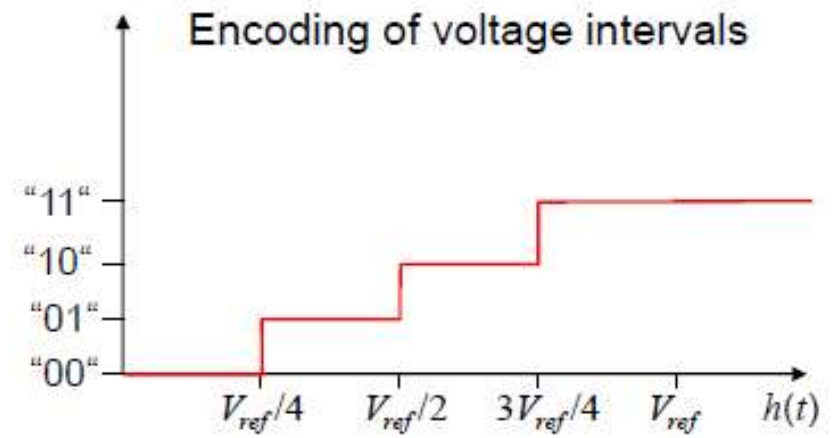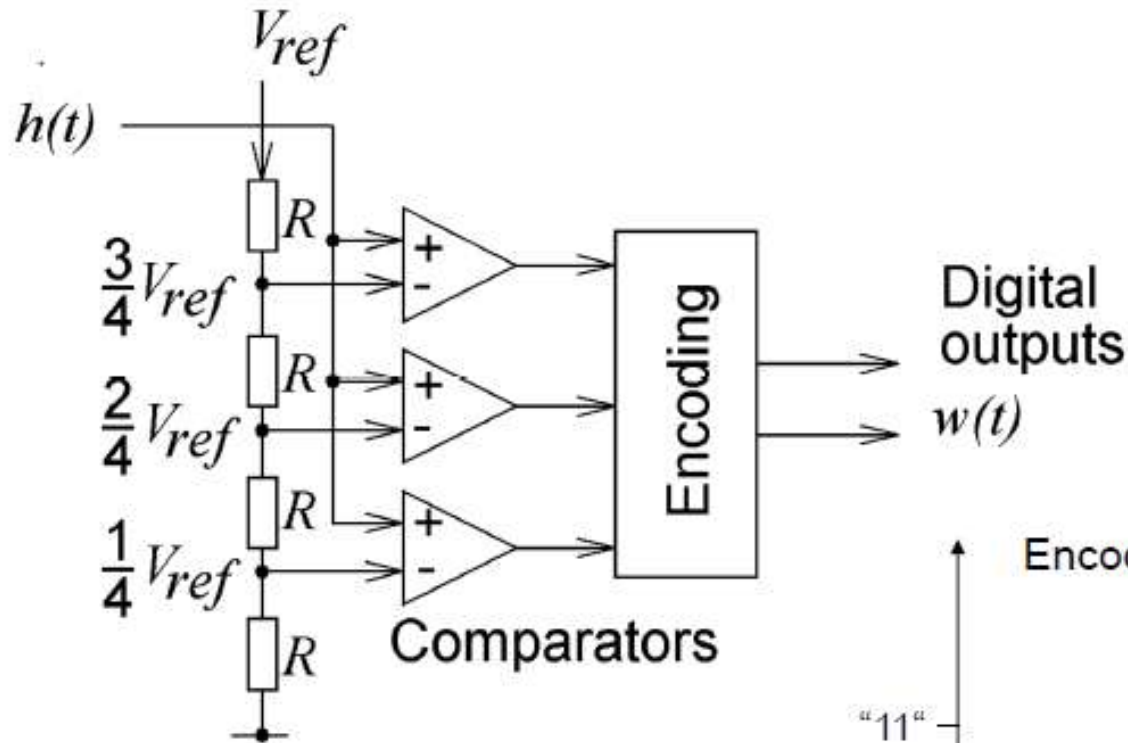

Resolution and speed of Flash A/D-converter


- Resolution (in bits): number of bits produced
- \square Resolution Q (*in volts*): *difference between two input voltages* causing the output to be incremented by 1

$$Q = \frac{V_{FSR}}{n}$$


- *Q: resolution in volts per step*
- *VFSR: difference between largest and smallest voltage*
- *n: number of voltage intervals*

- Example:
- *$Q = V_{ref} / 4$ for the*
- previous slide


Higher resolution:

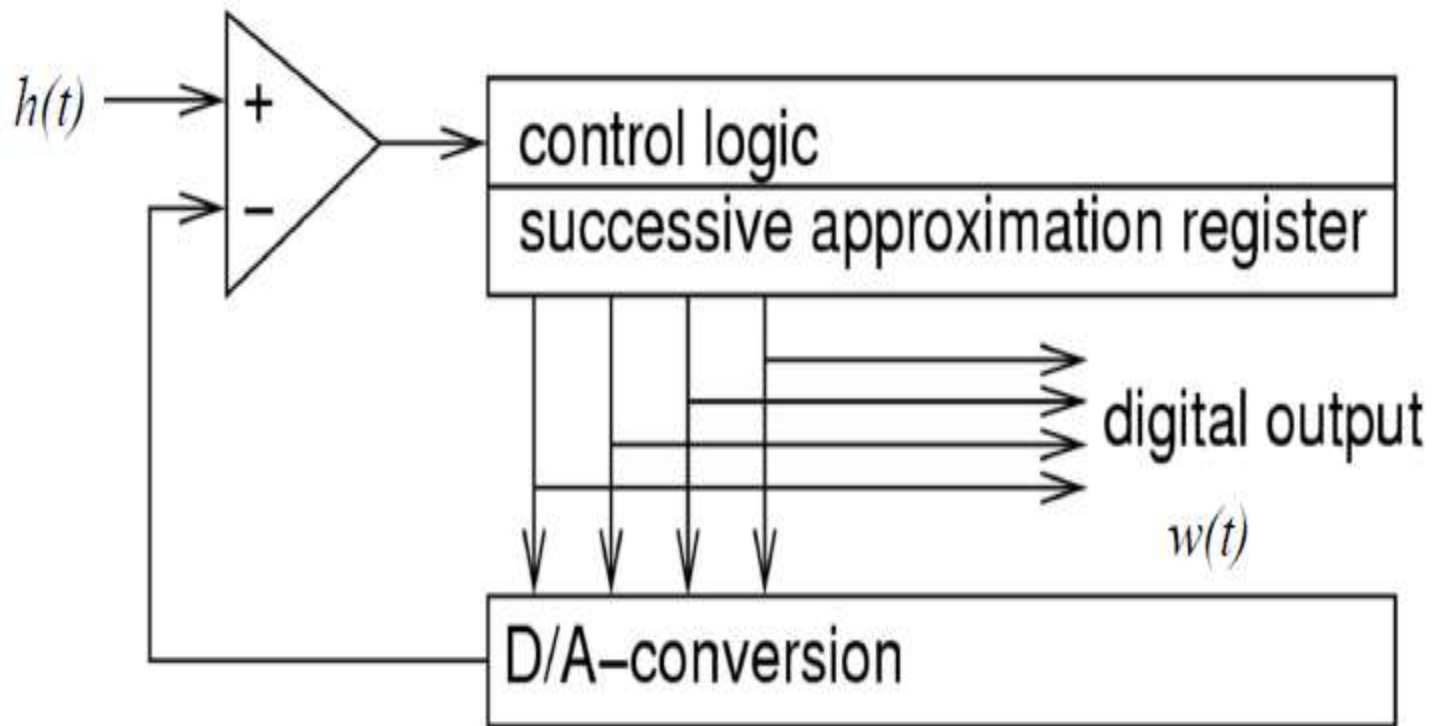

Higher resolution:

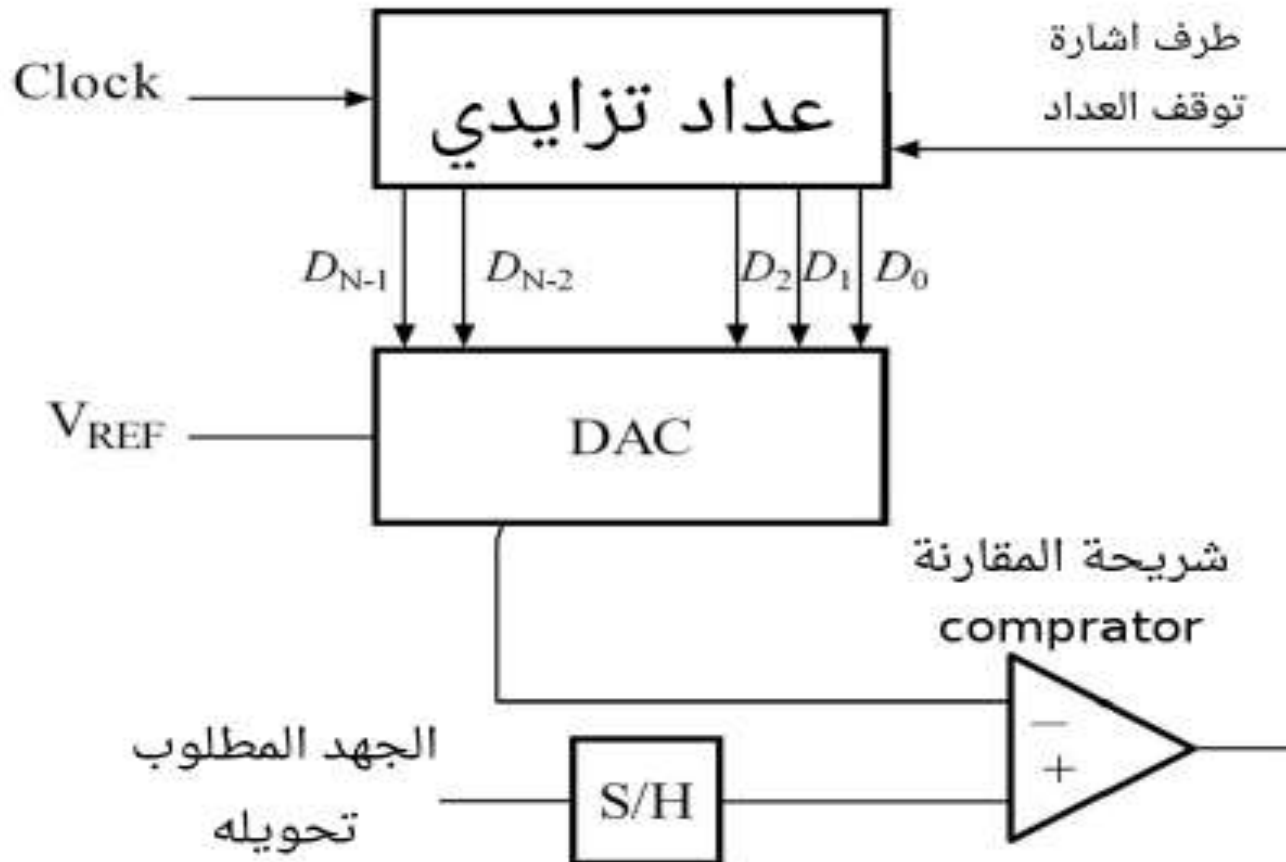

Digital-to-Analog (D/A) Converters

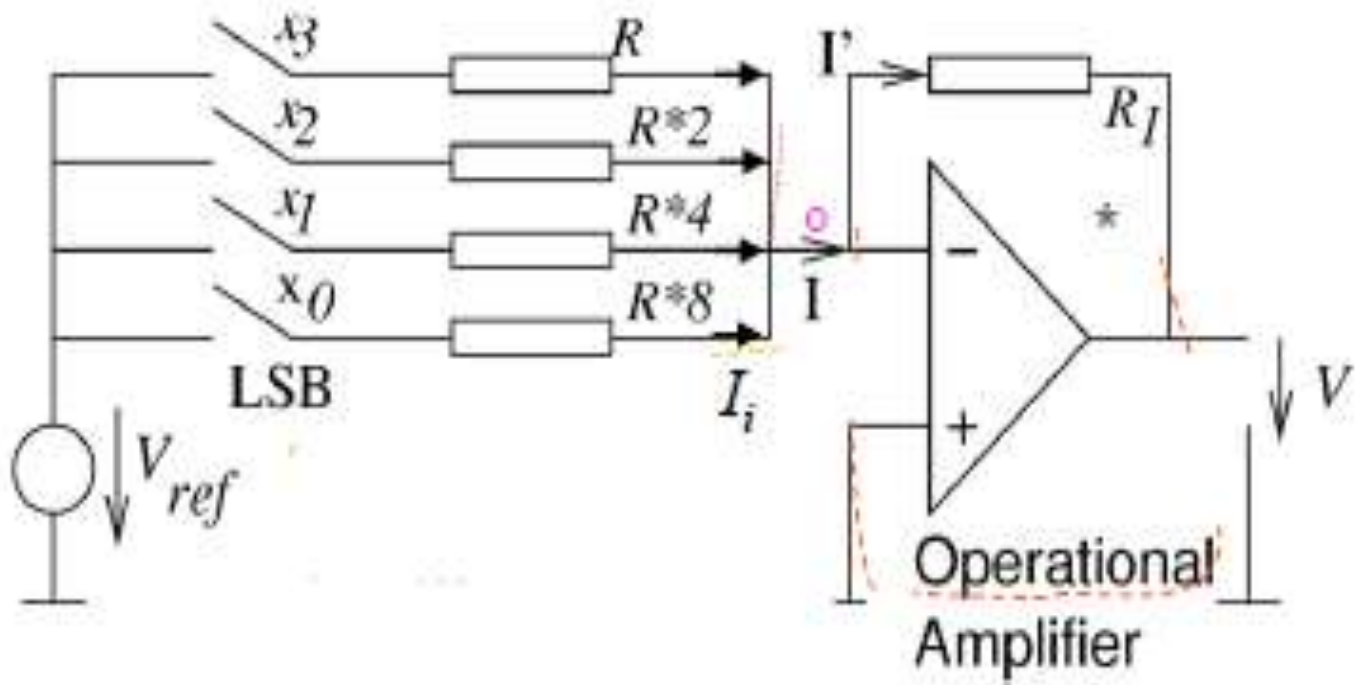


Junction rule:

$$I = \sum_i I_i$$

Loop rule:
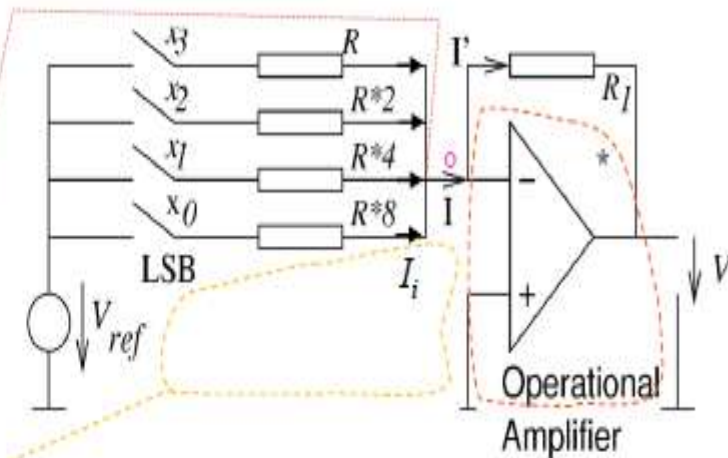
$$I_i = x_i \times \frac{V_{ref}}{2^{3-i} \times R}$$



$$\Rightarrow I = x_3 \times \frac{V_{ref}}{R} + x_2 \times \frac{V_{ref}}{2 \times R} + x_1 \times \frac{V_{ref}}{4 \times R} + x_0 \times \frac{V_{ref}}{8 \times R} = \frac{V_{ref}}{8 \times R} \times \sum_{i=0}^3 x_i \times 2^i$$

