



الجامعة السورية الخاصة
SYRIAN PRIVATE UNIVERSITY

كلية هندسة الحاسوب والمعلوماتية
Computer and Informatics Engineering
Faculty

Electric Circuits I

Dr. Eng.

Hassan M. Ahmad

Hassan.Ahmad@spu.edu.sy,

istamo48@mail.ru

Chapter 2

Basic Laws

2.1 Ohm's Law.

2.2 Nodes, Branches, and Loops.

2.3 Kirchhoff's Laws.

2.4 Series Resistors and Voltage Division.

2.5 Parallel Resistors and Current Division.

2.6 Wye-Delta Transformations.


2.1 Ohms Law

- **Ohm's law** states that the **voltage** across a resistor is **directly proportional** to the **current i** flowing through the **resistor R** .
- Mathematical expression for Ohm's Law is as follows:


$$v = iR$$

- The **resistance R** of an element denotes its **ability to resist** the flow of electric current; it is measured in **ohms (Ω)**.
- Two extreme possible values of R : **0 (zero)** and **∞ (infinite)** are related with two basic circuit concepts:


- short circuit;**
- open circuit.**

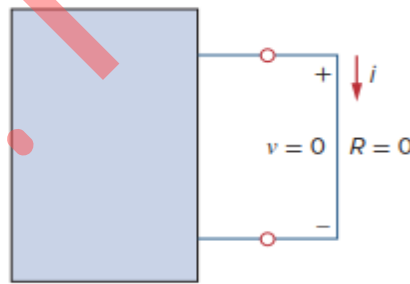

(a)


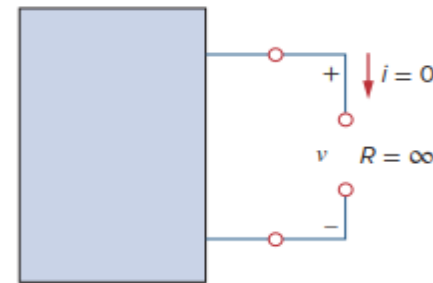


(b)

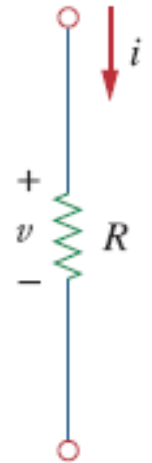

Types of resistors

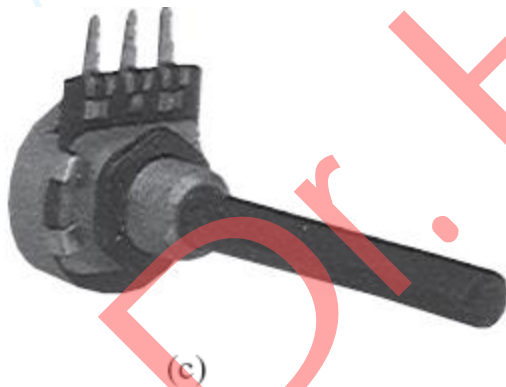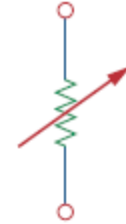- **Fixed resistor:** its resistance remains constant.
 - ❖ There are two common types of fixed resistors:
 - Wirewound, Fig. (a);
 - Composition, Fig. (b), used when large resistance is needed.
- **Variable resistor:** its resistance is variable.
 - Wirewound, Fig. (c);
 - Composition, Fig. (d).



(c)



(d)



(a)



(b)

- **Conductance** is the ability of an element to conduct electric current; it is the reciprocal of resistance R and is measured in **siemens (S)**.

$$G = \frac{1}{R} = \frac{i}{v}$$

- **Power dissipated** by a resistor: $p = vi = i^2R = \frac{v^2}{R} = v^2G = \frac{i^2}{G}$

Example 2.1.

An electric iron draws 2 A at 120 V. Find its resistance.

Solution:

$$R = \frac{v}{i} = \frac{120}{2} = 60\Omega$$

Example 2.2

In the circuit shown in Fig., calculate i , G , and p .

Solution:

$$i = \frac{v}{R} = \frac{30}{5 \times 10^3} = 6 \text{ mA}; \quad G = \frac{1}{R} = \frac{1}{5 \times 10^3} = 0.2 \text{ mS}$$



We can calculate the power in various ways:

$$p = vi = 30(6 \times 10^{-3}) = 180 \text{ mW}; \text{ or } p = i^2 R = (6 \times 10^{-3})^2 5 \times 10^3 = 180 \text{ mW}$$

$$p = v^2 G = (30)^2 0.2 \times 10^{-3} = 180 \text{ mW}$$

Example 2.3

A voltage source of $20 \sin \pi t$ V is connected across a 5-k Ω resistor. Find the current through the resistor and the power dissipated.

Solution:

$$i = \frac{v}{R} = \frac{20 \sin \pi t}{5 \times 10^{-3}} = 4 \sin \pi t \text{ mA}$$



$$p = vi = 80 \sin^2 \pi t \text{ mW}$$

2.2 Nodes, Branches and Loops

- A **branch** represents a single element such as a voltage source or a resistor.
- A **node** is the point of connection between two or more branches.
- A **loop** is any closed path in a circuit.
- A network with b branches, n nodes, and l independent loops will satisfy the fundamental theorem of **network topology**:

$$b = l + n - 1$$

- Two or more elements are in **series** if they exclusively **share a single node** and consequently carry the **same current**.
- Two or more elements are in **parallel** if they are connected to the **same two nodes** and consequently have the **same voltage across them**.

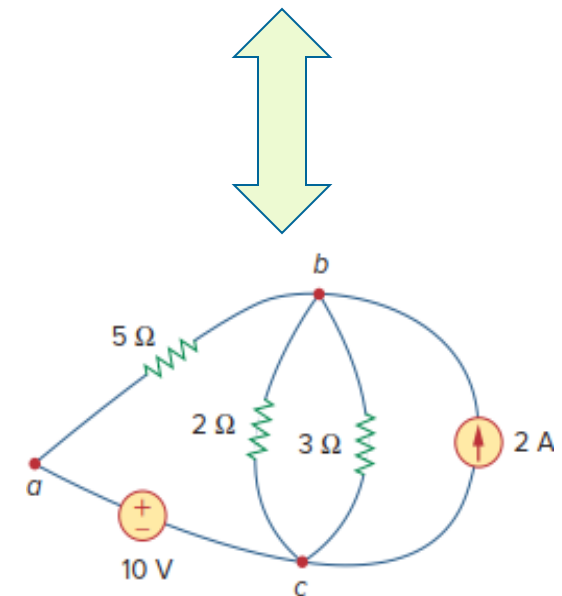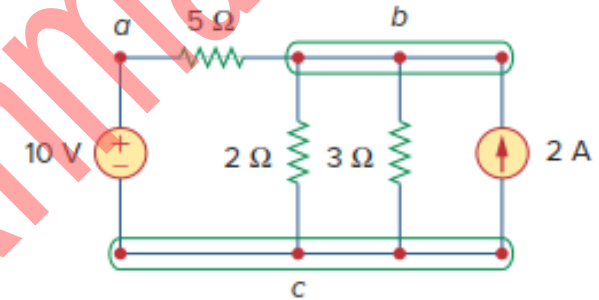


Example 2.3.

Determine the number of branches and nodes in the circuit shown in Fig. Identify which elements are in series and which are in parallel.


Solution:

- Since there are four elements in the circuit, the circuit has four branches: 10 V, 5 Ω , 6 Ω and 2 A.
- The circuit has three nodes as identified in Fig.
- The 5- Ω resistor is in series with the 10-V voltage source because the same current would flow in both.
- The 6- Ω resistor is in parallel with the 2-A current source because both are connected to the same nodes 2 and 3.

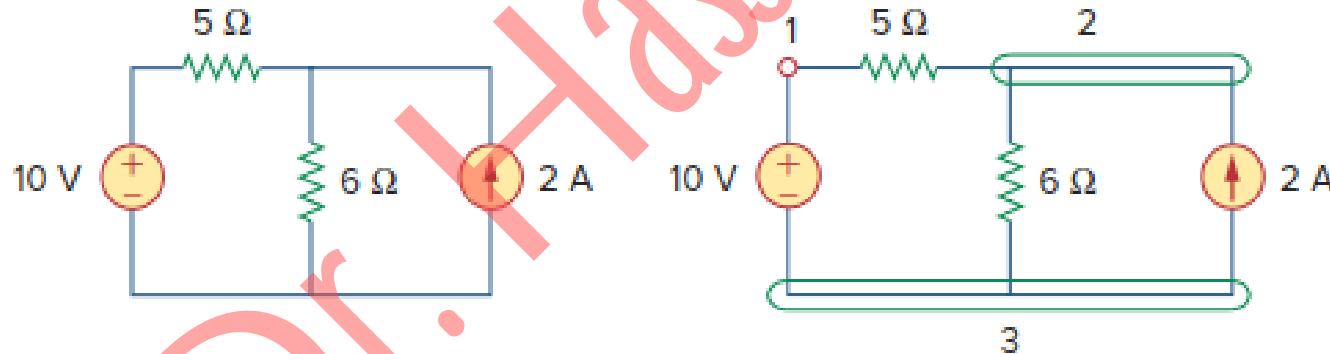

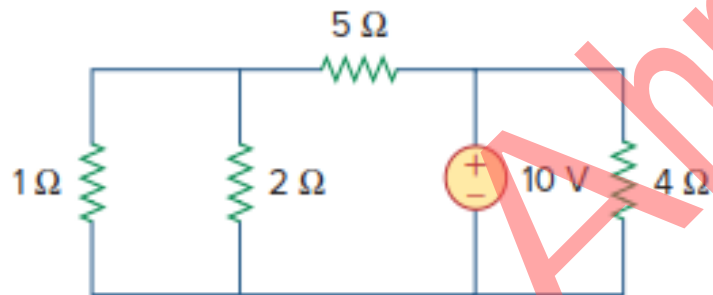Example 2.4

How many branches and nodes does the circuit in Fig. have? Identify the elements that are in series and in parallel.




Solution:

Five branches and three nodes are identified in Fig.

The 1- Ω and 2- Ω resistors are in parallel.

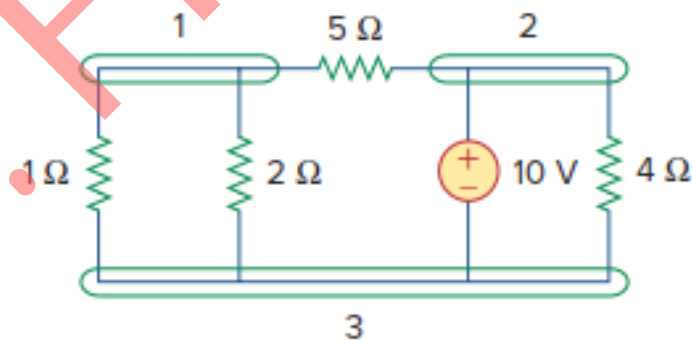The 4- Ω resistor and 10-V source are also in parallel.




2.3 Kirchhoff's Laws

- **Kirchhoff's current law (KCL)** states that the algebraic sum of currents entering a node (or a closed boundary) is zero.

- Mathematically,
$$\sum_{n=1}^N i_n = 0 \Rightarrow i_1 + (-i_2) + i_3 + i_4 + (-i_5) = 0$$

- In other words, KCL states that the sum of the currents **entering** a node is equal to the sum of the currents **leaving** the node.

$$i_1 + i_3 + i_4 = i_2 + i_5$$

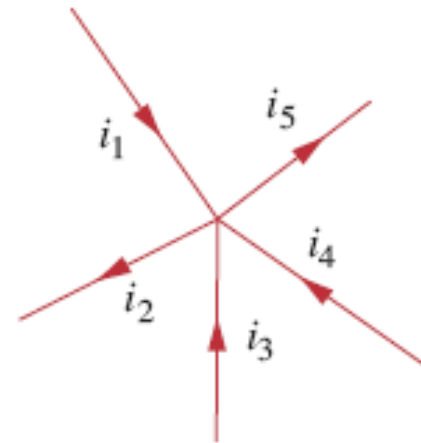


Application of KCL


- A simple *application* of KCL is **combining current sources in parallel**.
- The combined current is the algebraic sum of the current supplied by the individual sources.
- For example, the current sources shown in Fig. (a) can be combined as in Fig. (b).
- Applying KCL to node *a*:

$$I_T + I_2 = I_1 + I_3 \Rightarrow I_T = I_1 - I_2 + I_3$$

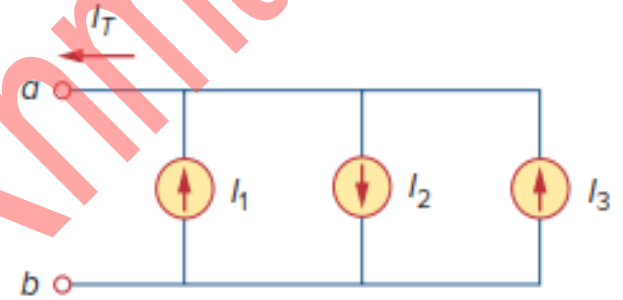- A circuit cannot contain two different currents, and , in series, unless $I_1 = I_2$; otherwise KCL will be violated.



(a)

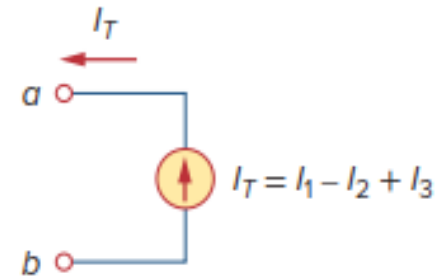


(b)

- **Kirchhoff's voltage law (KVL)** states that the algebraic sum of all voltages around a closed path (or loop) is zero.

- Mathematically,

$$\sum_{m=1}^M v_n = 0$$

- Consider the circuit in Fig.

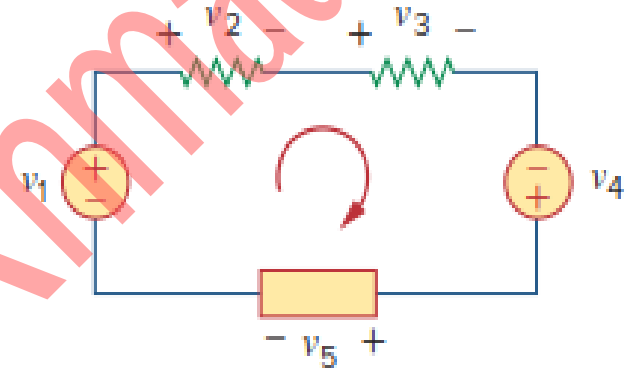

- Suppose we start with the voltage source and go **clockwise** around the loop as shown; then voltages would be $-v_1$, $+v_2$, $+v_3$, $-v_4$, and $+v_5$ in that order.


- Thus, KVL yields $-v_1 + v_2 + v_3 - v_4 + v_5 = 0 \Leftrightarrow v_2 + v_3 + v_5 = v_1 + v_4$

Application of KVL


- When **voltage sources** are connected in **series**, KVL can be applied to obtain the **total voltage**.
- Consider the voltage sources shown in Fig.(a).
- Applying KVL gives the combined or equivalent voltage source in Fig.(b).

$$-V_{ab} + V_1 + V_2 - V_3 = 0 \Rightarrow V_{ab} = V_1 + V_2 - V_3$$

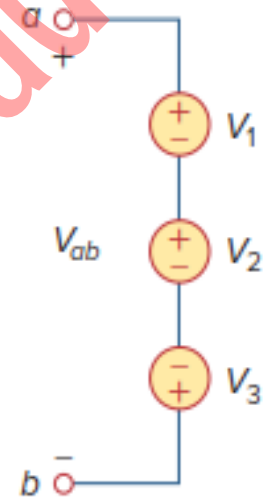- To avoid violating KVL, a circuit cannot contain two different voltages V_1 and V_2 in parallel unless $V_1 = V_2$.



(a)

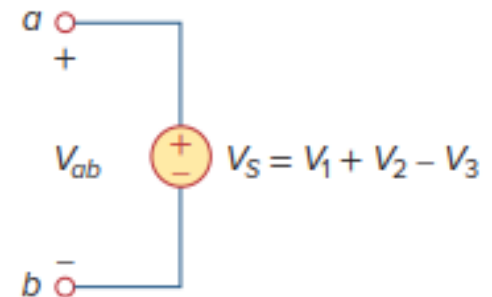

(b)


Example 2.5

For the circuit in Fig.(a), find voltages v_1 and v_2 .


Solution:

- To find v_1 and v_2 we apply Ohm's law and Kirchhoff's voltage law.
- Assume that current i flows through the loop as shown in Fig.(b).
- From Ohm's law, $v_1 = 2i$, $v_2 = -3i$ (1)
- Applying KVL around the loop gives
$$-20 + v_1 - v_2 = 0 \quad (2)$$
- By Substituting Eq.(1) into Eq.(2):
$$-20 + 2i + 3i = 0 \Rightarrow i = 4 \text{ A} \quad (3)$$
- By Substituting Eq.(3) into Eq.(1):
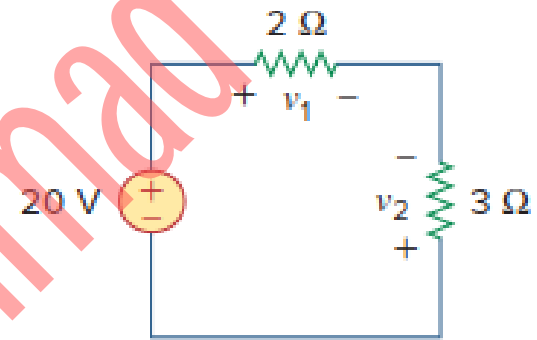
$$v_1 = 8 \text{ V}, \quad v_2 = -12 \text{ V}$$




(a)

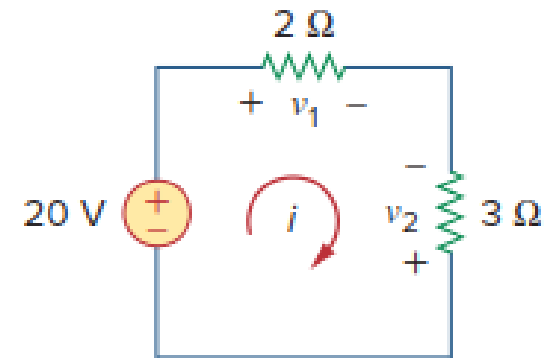

(b)

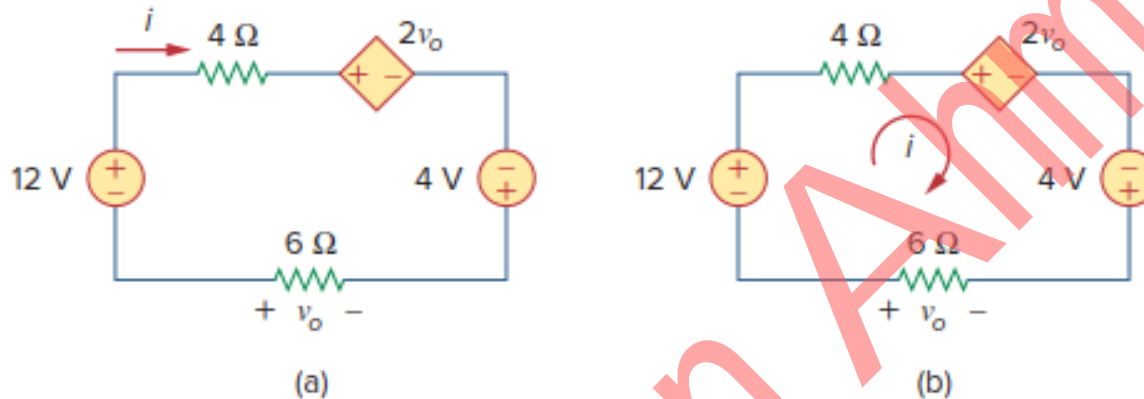Example 2.6

Determine v_o and i in the circuit shown in Fig.(a).



Solution:

- We apply KVL around the loop as shown in Fig. (b).

$$-12 + 4i + 2v_o - 4 + 6i = 0 \quad (1)$$


- Applying Ohm's law to the 6-Ω resistor gives: $v_o = -6i$ (2)

- Substituting Eq. (2) into Eq. (1): $-16 + 10i - 12i = 0 \Rightarrow i = -8\text{A}$

- Then, $v_o = -6 \times (-8) = 48\text{V}$

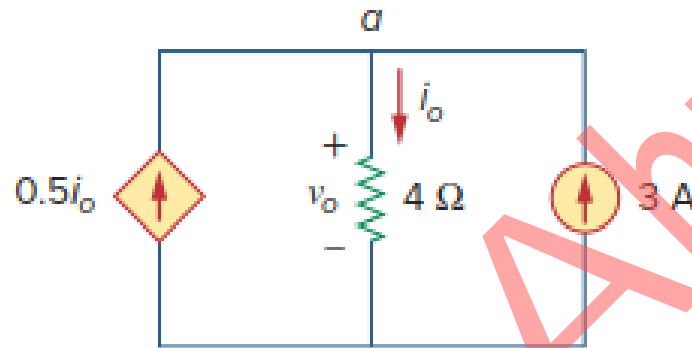Example 2.7

Find current i_o and voltage v_o in the circuit shown in Fig.



Solution:

- Applying KCL to node a , we obtain $3 + 0.5i_o = i_o \Rightarrow i_o = 6\text{ A}$
- For the $4\text{-}\Omega$ resistor, Ohm's law gives $v_o = 4i_o = 24\text{ V}$

Example 2.8

Find currents and voltages in the circuit shown in Fig.(a).

Solution:

- By Ohm's law,

$$v_1 = 8i_1, \quad v_2 = 3i_2, \quad v_3 = 6i_3 \quad (1)$$

- At node a , KCL gives $i_1 - i_2 - i_3 = 0$ (2)

- Applying KVL to loop 1 as in Fig. (b),

$$-30 + v_1 + v_2 = 0 \quad (3)$$

- Substituting from Eq. (1) into Eq. (3):



$$-30 + 8i_1 + 3i_2 = 0 \Rightarrow i_1 = \frac{30 - 3i_2}{8} \quad (4)$$

- Applying KVL to loop 2, $-v_2 + v_3 = 0 \Rightarrow v_3 = v_2$ or $6i_3 = 3i_2 \Rightarrow i_3 = \frac{i_2}{2}$ (5)

- Substituting Eqs. (4) and (5) into (2) gives $\frac{30 - 3i_2}{8} - i_2 - \frac{i_2}{2} = 0 \Rightarrow i_2 = 2 \text{ A}$

- Then,
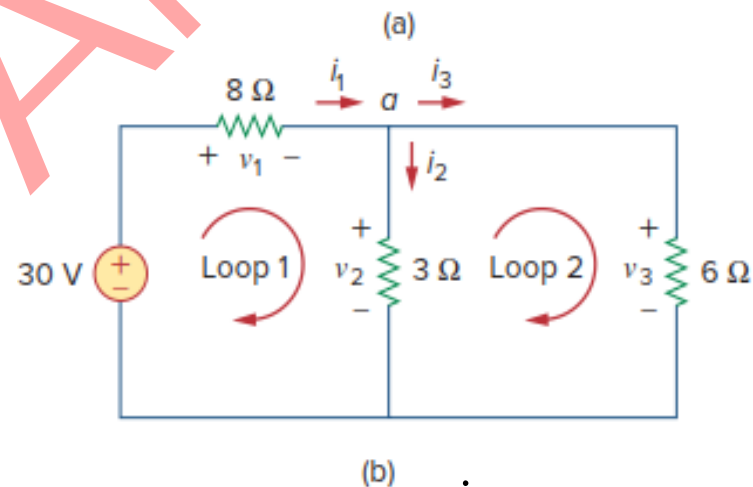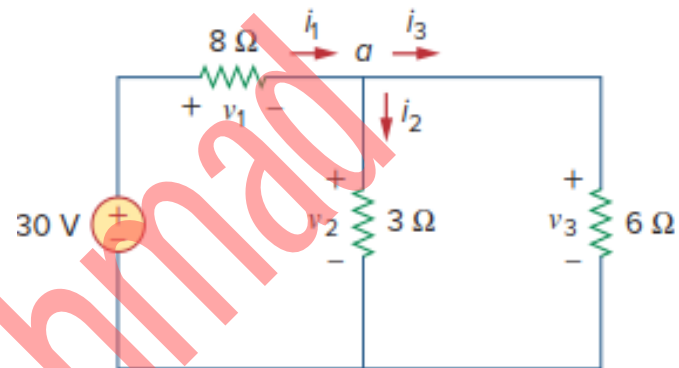
$$i_1 = 3 \text{ A}, \quad i_3 = 1 \text{ A}, \quad v_1 = 24 \text{ V}, \quad v_2 = 6 \text{ V}, \quad v_3 = 6 \text{ V}$$



2.4 Series Resistors and Voltage Division

- **Series:** two or more elements are in **series** if they are cascaded or connected sequentially and consequently carry the **same current**.
- The **equivalent resistance** of any number of resistors connected in a series is the sum of the individual resistances.



$$R_{eq} = R_1 + R_2 + \dots + R_N = \sum_{n=1}^N R_n$$

- The **voltage divider rule (VDR)** can be expressed as

$$v_n = \frac{R_n}{R_1 + R_2 + \dots + R_N} v$$

- Applying VDR to given circuit gives
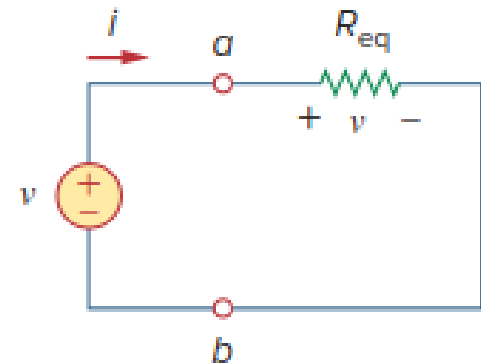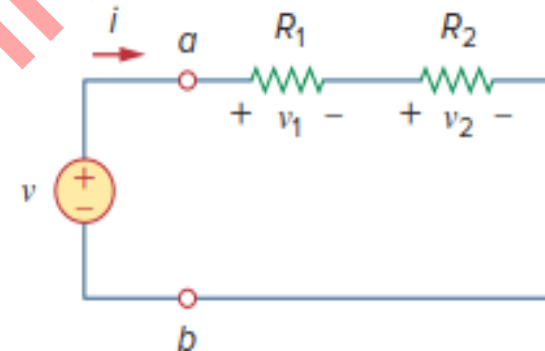
$$v_1 = \frac{R_1}{R_1 + R_2} v; \quad v_2 = \frac{R_2}{R_1 + R_2} v$$



2.5 Parallel Resistors and Current Division


- **Parallel:** Two or more elements are in **parallel** if they are connected to the **same two nodes** and consequently have the **same voltage** across them.
- The **equivalent resistance** of a circuit with N resistors in *parallel* is:

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

- For given circuit: $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$

- The **total current** i is shared by the resistors in **inverse proportion** to their resistances.
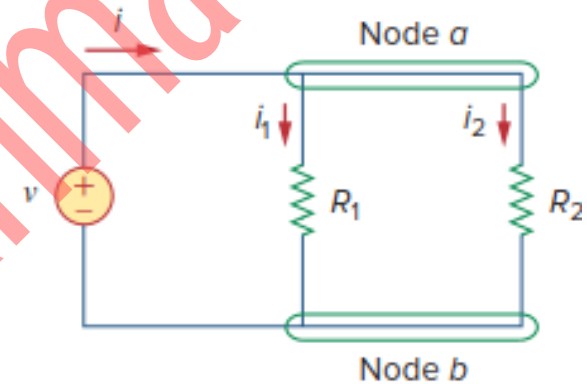
$$i = i_1 + i_2 = \frac{v}{R_1} + \frac{v}{R_2} = v \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = v \frac{1}{R_{eq}}$$



- The **equivalent conductance** of resistors connected in parallel is the sum of their individual conductance.


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} \Leftrightarrow G_{eq} = G_1 + G_2 + G_3 + \dots + G_N$$

- Given the total current i entering node a in Fig., how do we obtain current i_1 and i_2 ?
- The **current divider rule (CDR)**.

$$v = iR_{eq} = i \frac{R_1 R_2}{R_1 + R_2}; \quad i_1 = \frac{v}{R_1}; \quad i_2 = \frac{v}{R_2}$$

$$\Rightarrow i_1 = \frac{R_2}{R_1 + R_2} i \quad \text{and} \quad i_2 = \frac{R_1}{R_1 + R_2} i$$

$$i_1 = \frac{G_1}{G_1 + G_2} i, \quad i_2 = \frac{G_2}{G_1 + G_2} i \Rightarrow i_n = \frac{G_n}{G_1 + G_2 + \dots + G_N} i$$

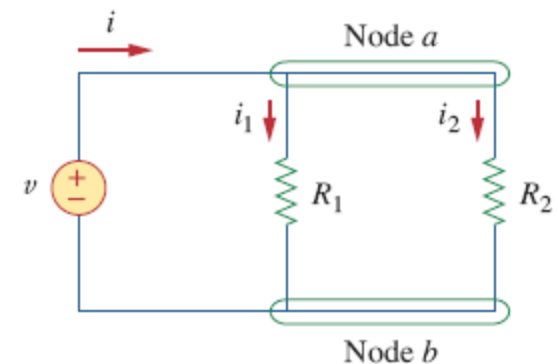

Example 2.9

Find R_{eq} for the circuit shown in Fig.

Solution:




$$6\Omega \parallel 3\Omega = \frac{6 \times 3}{6 + 3} = 2\Omega$$

$$1\Omega + 5\Omega = 6\Omega$$

$$2\Omega + 2\Omega = 4\Omega$$

$$4\Omega \parallel 6\Omega = \frac{4 \times 6}{4 + 6} = 2.4\Omega$$

$$R_{eq} = 4\Omega + 2.4\Omega + 8\Omega = 14.4\Omega$$

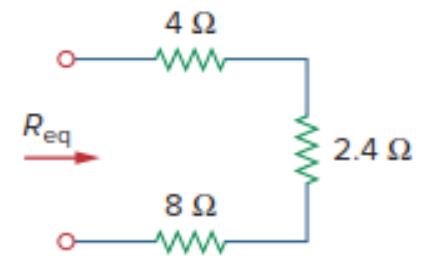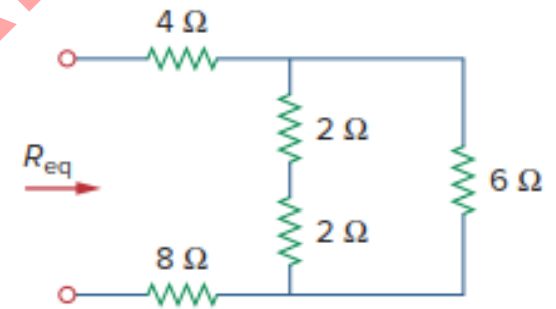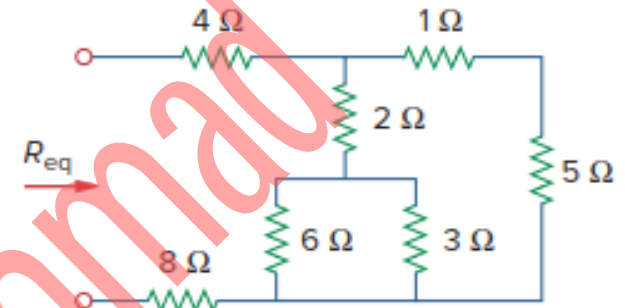

Example 2.10

Find the equivalent conductance G_{eq} for the circuit in Fig.(a).

Solution:

- The 8-S and 12-S resistors are in parallel, so

$$8S + 12S = 20S$$


- This 20-S resistor is now in series with 5 S as shown in Fig. (b), so

$$\frac{20 \times 5}{20 + 5} = 4S$$


- This 4-S is in parallel with the 6-S resistor.

Hence,

$$G_{eq} = 6 + 4 = 10S$$

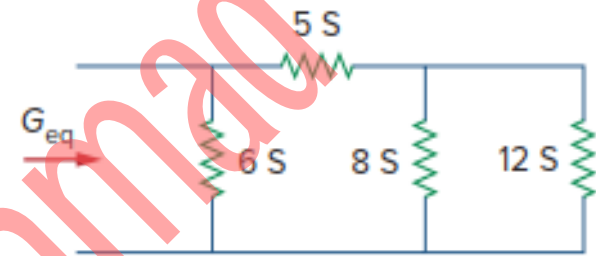

(a)

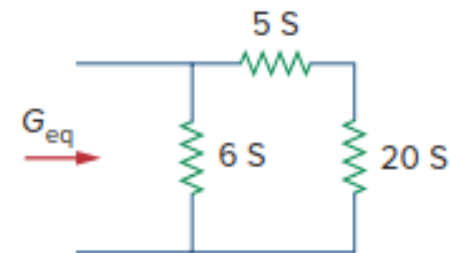

(b)

Example 2.11

Find i_o and v_o in the circuit shown in Fig.(a).

Calculate the power dissipated in the 3- Ω resistor.

Solution:

$$6\Omega \parallel 3\Omega = \frac{6 \times 3}{6 + 3} = 2\Omega$$

Because the resistors 6- Ω and 3- Ω are in parallel, therefore they have the same voltage v_o .

So, we can obtain v_o in **two ways**.

One way is to apply Ohm's law to get:


$$i = \frac{12}{4 + 2} = 2 \text{ A} \Rightarrow v_o = 2i = 2 \times 2 = 4 \text{ V}$$

$$\text{and, } v_o = 3i_o = 4 \Rightarrow i_o = \frac{4}{3} \text{ A}$$


Another way is to apply voltage division (VDR) and current division (CDR) to the circuit, then

$$v_o = \frac{2}{2 + 4} (12 \text{ V}) = 4 \text{ V}, \quad i_o = \frac{6}{6 + 3} i = \frac{2}{3} (2 \text{ A}) = \frac{4}{3} \text{ A}$$

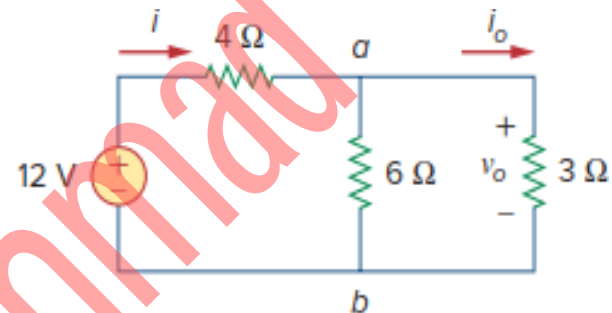The power dissipated in the 3- Ω resistor is $p_o = v_o i_o = 4 \left(\frac{4}{3} \right) = 5.333 \text{ W}$



(a)

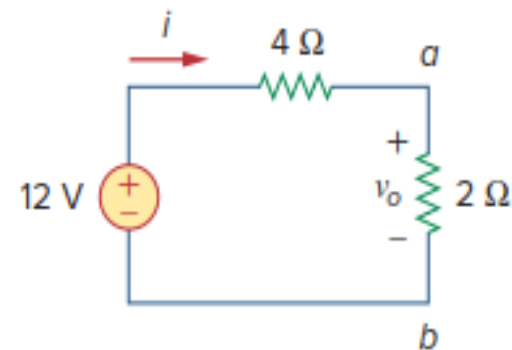

(b)

Example 2.12

For the circuit shown in Fig.(a), determine:

- the voltage v_o ,
- the power supplied by the current source,
- the power absorbed by each resistor.

Solution:

The 6-k Ω and 12-k Ω in series $\rightarrow 6 + 12 = 18$ k Ω .

Thus \rightarrow Fig.(b). Now, apply the current division technique to find i_1 and i_2 .

$$i_1 = \frac{18 \times 10^3}{(9 + 18) \times 10^3} (30 \text{ mA}) = 20 \text{ mA}, \quad i_2 = \frac{9 \times 10^3}{(9 + 18) \times 10^3} (30 \text{ mA}) = 10 \text{ mA}$$

Notice that the voltage across the 9-k Ω and 18-k Ω resistors is the same, and $v_o = 9,000i_1 = 18,000i_2 = 180$ V, as expected.

Power supplied by the source is $p_o = v_o i_o = 180 \text{ V} \times 30 \text{ mA} = 5.4 \text{ W}$

Power absorbed by the 12-k Ω resistor is

$$p = iv = i_2 (i_2 R) = i_2^2 R = (10 \times 10^{-3})^2 (12 \times 10^3) = 1.2 \text{ W}$$


Power absorbed by the 6-k Ω resistor is

$$p = i_2^2 R = (10 \times 10^{-3})^2 (6 \times 10^3) = 0.6 \text{ W}$$


Power absorbed by the 9-k Ω resistor is

$$p = i_1 v_o = \frac{v_o}{R} v_o = \frac{v_o^2}{R} = (180)^2 (6 \times 10^3) = 3.6 \text{ W}$$

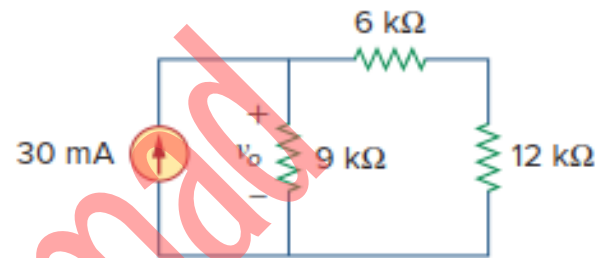Power supplied = the power absorbed = 3.6 W



(a)

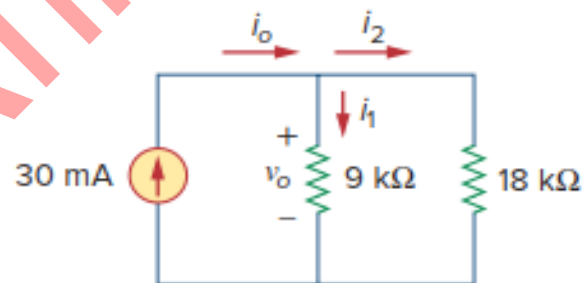

(b)

2.6 Wye-Delta Transformations


Delta to Wye (Star) Conversion

$$\Delta \rightarrow Y$$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$
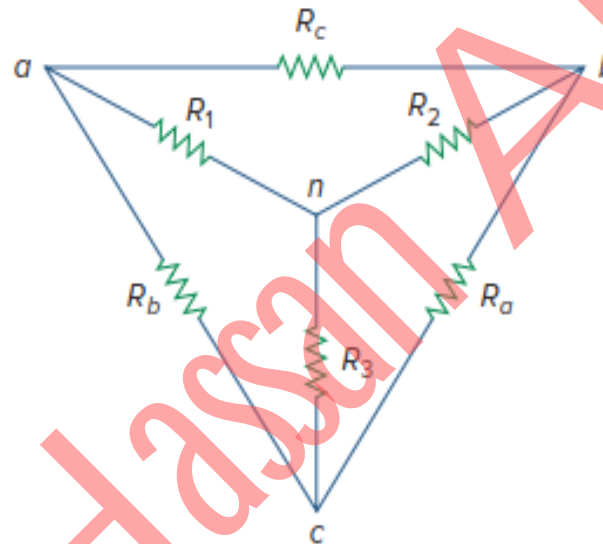
$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$



Wye (Star) to Delta Conversion

$$Y \rightarrow \Delta$$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$



The Y and Δ networks are said to be **balanced** when

$$R_1 = R_2 = R_3 = R_Y, \quad R_a = R_b = R_c = R_\Delta$$

$$R_Y = \frac{R_\Delta}{3} \quad \text{or} \quad R_\Delta = 3R_Y$$

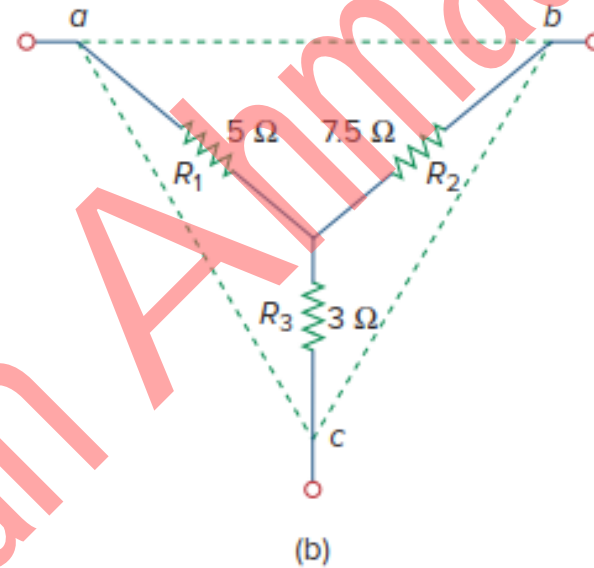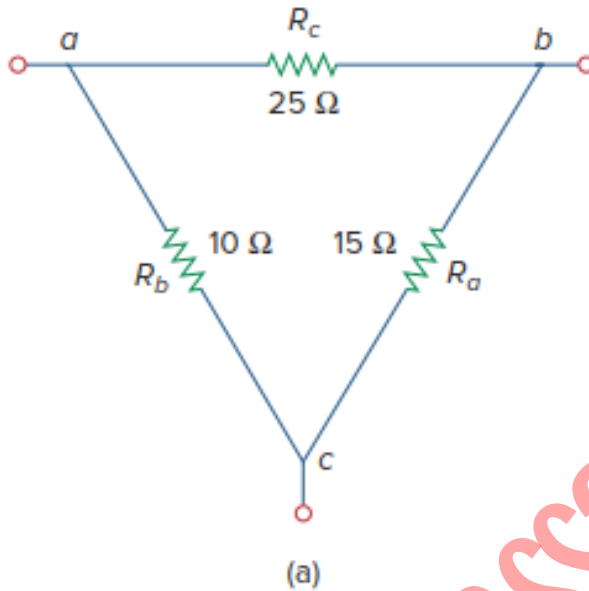Example 2.13

Convert the Δ network in Fig. (a) to an equivalent Y network.



Solution:

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} = \frac{10 \times 25}{15 + 10 + 25} = 5\ \Omega$$


$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c} = \frac{25 \times 15}{15 + 10 + 25} = 7.5\ \Omega$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c} = \frac{15 \times 10}{15 + 10 + 25} = 3\ \Omega$$

The equivalent Y network is shown in Fig.(b).

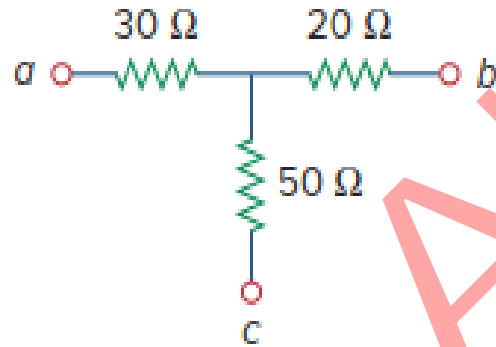Example 2.14

Convert the Y network in Fig. to an equivalent Δ network.



Solution:

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} = \frac{30 \times 20 + 30 \times 50 + 20 \times 50}{30} = 103.3\ \Omega$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} = \frac{30 \times 20 + 30 \times 50 + 20 \times 50}{20} = 155\ \Omega$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = \frac{30 \times 20 + 30 \times 50 + 20 \times 50}{50} = 62\ \Omega$$



The end of chapter 2