



الجامعة السورية الخاصة
SYRIAN PRIVATE UNIVERSITY

كلية هندسة الحاسوب والمعلوماتية
Computer and Informatics Engineering
Faculty

Electric Circuits I

Dr. Eng.

Hassan M. Ahmad

Hassan.Ahmad@spu.edu.sy,

istamo48@mail.ru

Chapter 7

First-Order Circuits

7.1 The Source-Free RC Circuit

7.2 The Source-Free RL Circuit

7.3 Unit-step Function

7.4 Step Response of an RC Circuit

7.5 Step Response of an RL Circuit

Introduction


- A simple circuit comprising a resistor and capacitor is called **RC circuit**;
- A simple circuit comprising a resistor and an inductor is called **RL circuit**.
- These types of circuits find continual applications in electronics, communications, and control systems.
- We carry out the analysis of **RC** and **RL** circuits by applying Kirchhoff's laws:
 - Apply Kirchhoff's laws to purely resistive circuits results in algebraic equations;
 - Apply the laws to **RC** and **RL** circuits produces differential equations.
 - The differential equations resulting from analyzing **RC** and **RL** circuits are of the first order.
 - Hence, the circuits are collectively known as **first-order circuits**.
- ✓ **A first-order circuit is characterized by a first-order differential equation.**

7.1 The Source-Free RC Circuit

- A **source-free RC circuit** occurs when its dc source is suddenly disconnected.
 - The **energy** already stored in the **capacitor** is released to the **resistors**.
 - Applying KCL at the top node gives:

$$i_C + i_R = 0 \Leftrightarrow C \frac{dv}{dt} + \frac{v}{R} = 0 \quad \text{or} \quad \frac{dv}{dt} + \frac{v}{RC} = 0$$

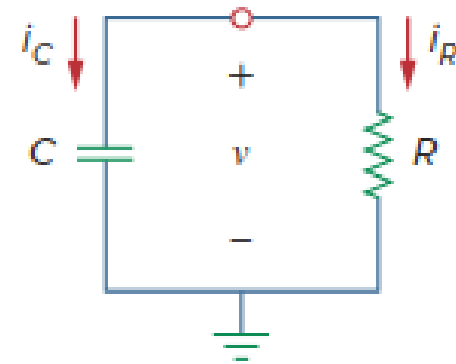- This is a **first-order differential** equation.



The natural response of RC Circuit

- Since the capacitor is *initially charged*, we can assume that at time $t = 0$, the *initial voltage* is $v(0) = V_0$, with the corresponding value of the *energy stored* as

$$w(0) = \frac{1}{2} CV_0^2$$

- The **first-order differential** equation can be rewrite as

$$\frac{dv}{dt} + \frac{v}{RC} = 0 \Leftrightarrow \frac{dv}{v} = -\frac{1}{RC} dt$$

- Integrating both sides, we get $\ln v = -\frac{t}{RC} + \ln A \Leftrightarrow \ln \frac{v}{A} = -\frac{t}{RC}$

where $\ln A$ is the integration constant.

- Taking powers of e produces: $v(t) = Ae^{-t/RC}$

- From the *initial conditions* $v(0) = A = V_0$. Hence,

$$v(t) = V_0 e^{-t/RC}$$

- This Eq. is called the **natural response of the circuit**.

- The *natural response* of a circuit refers to the *behavior* (in terms of voltages and currents) of the circuit itself, with *no external sources* of excitation.


- The natural response is illustrated graphically in Fig. with time constant $\tau = RC$.

- The *time constant* τ of a circuit is the *time* required for the response to *decay* to a factor of $1/e$ or 36.8 percent of its initial value.

- At $t = \tau \rightarrow V_0 e^{-t/RC} = V_0 e^{-1} = 0.368V_0$


- In terms of the *time constant*, Eq. for The *natural response* can be written as
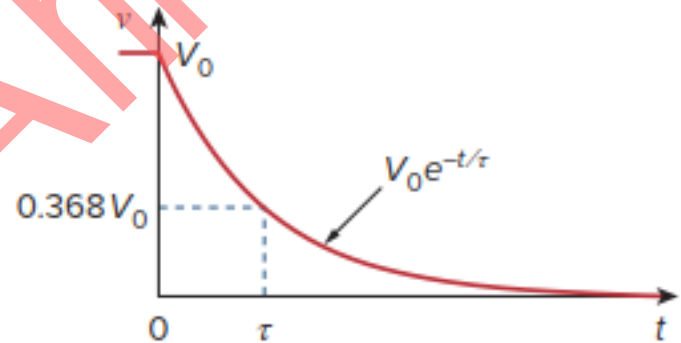
$$v(t) = V_0 e^{-t/\tau} \quad \text{or} \quad \frac{v(t)}{V_0} = e^{-t/\tau}$$



- *Natural response* as

$$\frac{v(t)}{V_0} = e^{-t/\tau}$$

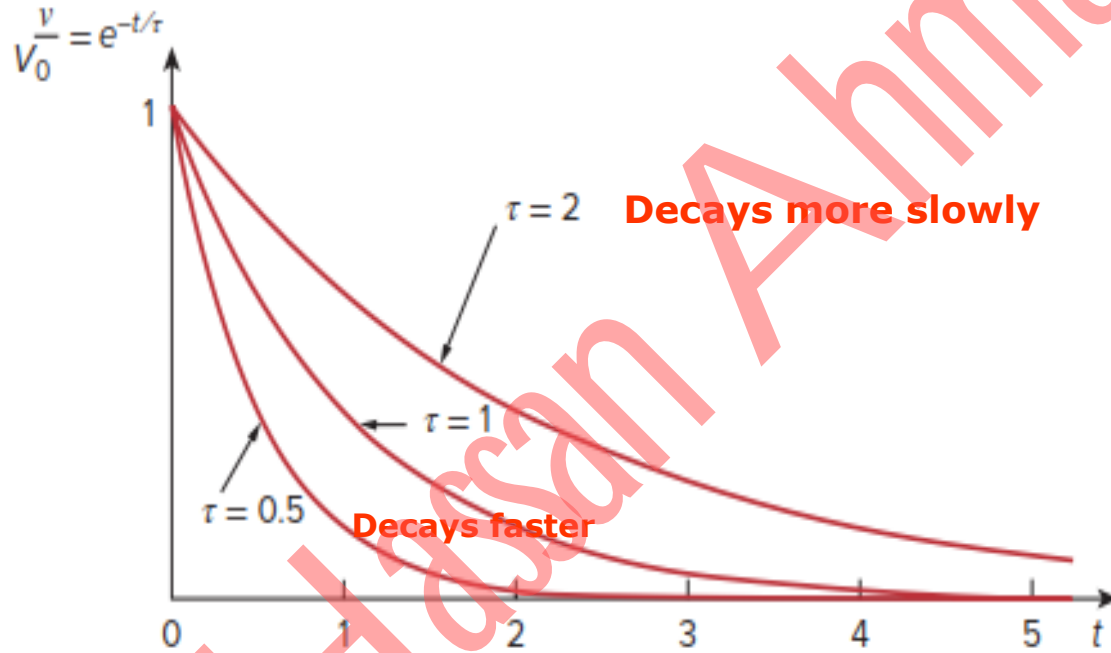

- v decays faster for small τ and slower for large τ .


Current, Power and Energy of RC Circuit

- The **current** $i_R(t)$ is defined as

$$i_R(t) = \frac{v(t)}{R} = \frac{V_0}{R} e^{-t/\tau}$$

- The **power** dissipated in the resistor is
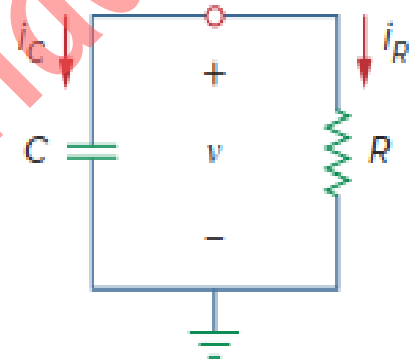
$$p(t) = vi_R = \frac{V_0^2}{R} e^{-2t/\tau}$$



- The **energy absorbed** by the resistor *up to time* t is

$$w_R(t) = \int_0^t p(\lambda) d\lambda = \int_0^t \frac{V_0^2}{R} e^{-2\lambda/\tau} d\lambda = -\frac{\tau V_0^2}{2R} e^{-2\lambda/\tau} \Big|_0^t = \frac{1}{2} CV_0^2 (1 - e^{-2t/\tau}), \quad \tau = RC$$

- The **initial energy stored** in the capacitor is

$$w_C(0) = \frac{1}{2} CV_0^2$$

The Key to Working with a Source-Free RC Circuit Is Finding:

- The initial voltage $v(0) = V_0$ across the capacitor.
- The time constant τ .

Example 7.1

In Fig., let $v_C(0) = 15 \text{ V}$. Find v_C , v_x , and i_x for $t > 0$.

Solution

First, conform the given circuit to the standard RC circuit.

The 8- Ω and 12- Ω resistors in series = 20 Ω .

This 20- Ω resistor in parallel with the 5- Ω resistor \rightarrow

$$R_{\text{eq}} = \frac{20 \times 5}{20 + 5} = 4 \Omega$$



Hence, the equivalent circuit is as shown in Fig.

The time constant is $\tau = R_{\text{eq}} C = 4(0.1) = 0.4 \text{ s}$

Thus, $v = v(0)e^{-t/\tau} = 15e^{-t/0.4} \text{ V} \Rightarrow v_C = v = 15e^{-2.5t} \text{ V}$

Use VDR to get: $v_x = \frac{12}{12 + 8} v = 0.6(15e^{-2.5t}) = 9e^{-2.5t} \text{ V}$

Finally, $i_x = \frac{v_x}{12} = 0.75e^{-2.5t} \text{ A}$

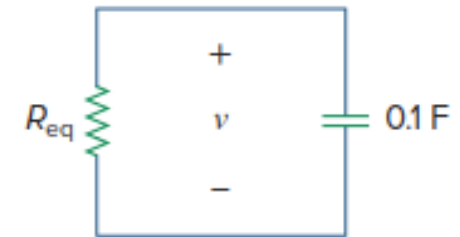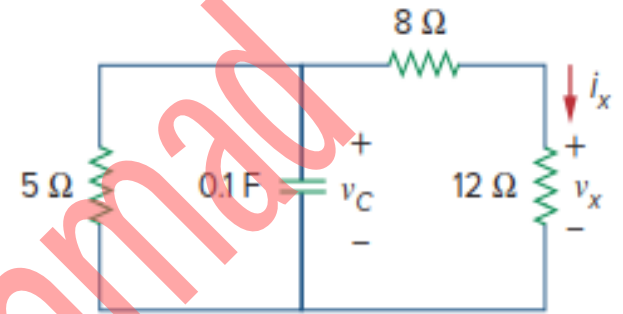

Example 7.2. The switch in the circuit in Fig. has been closed for a long time, and it is opened at $t = 0$. Find $v(t)$ for $t \geq 0$. Calculate the initial energy stored in the capacitor.

Solution

For $t < 0$, the switch is closed; the capacitor is an open circuit to dc, Fig.(a). Using VDR

$$v_C(t) = \frac{9}{9+3}(20) = 15V, \quad t < 0$$

Since the voltage across a capacitor cannot change instantaneously, the voltage across the capacitor at $t = 0^-$ is the same at $t = 0$, or $v_C(0) = V_0 = 15V$

For $t > 0$, the switch is opened, and we have the RC circuit shown in Fig. (b).




$$R_{eq} = 1 + 9 = 10\Omega \Rightarrow \tau = R_{eq}C = 10 \times 20 \times 10^{-3} = 0.2s$$

Thus, the voltage across the capacitor for $t \geq 0$ is

$$v(t) = v(0)e^{-t/\tau} = 15e^{-t/0.2} \text{ V} \quad \text{or} \quad v(t) = 15e^{-5t} \text{ V}$$

The initial energy stored in the capacitor is
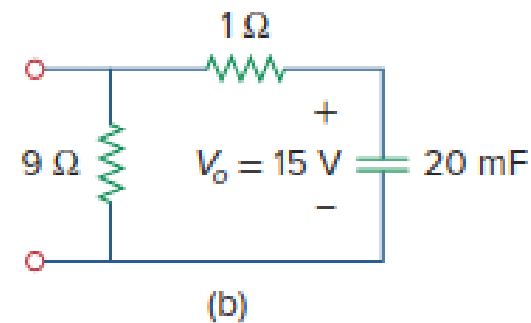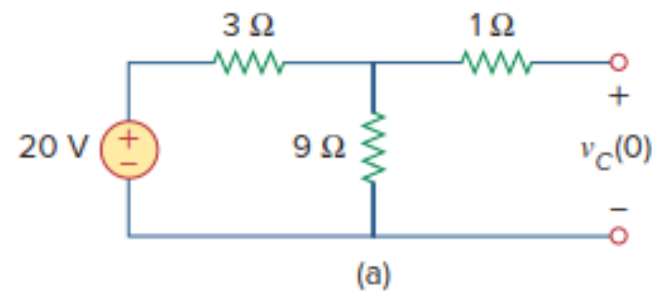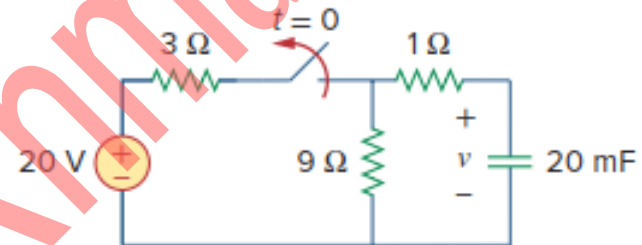
$$w_C(0) = \frac{1}{2}CV_0^2(0) = \frac{1}{2} \times 20 \times 10^{-3} \times (15)^2 = 2.25 \text{ J}$$



7.2 The Source-Free RL Circuit

- A **first-order RL circuit** consists of a **inductor L** (or its equivalent) and a **resistor** (or its equivalent).
 - The **circuit response** is assumed to be the **current $i(t)$** through the **inductor**.
 - At $t = 0$, we assume that the inductor has an **initial current I_0** , or $i(0) = I_0$

with the corresponding **energy stored** in the *inductor* as


$$w(0) = \frac{1}{2} LI_0^2$$

- Applying KVL around the loop in Fig.

$$v_L + v_R = 0; \quad v_L = L di/dt, \quad v_R = iR$$

$$\Rightarrow L \frac{di}{dt} + Ri = 0 \Rightarrow \frac{di}{i} = -\frac{R}{L} dt \Rightarrow \int_{I_0}^{i(t)} \frac{di}{i} = -\int_0^t \frac{R}{L} dt$$

$$\Rightarrow i(t) = I_0 e^{-Rt/L}$$

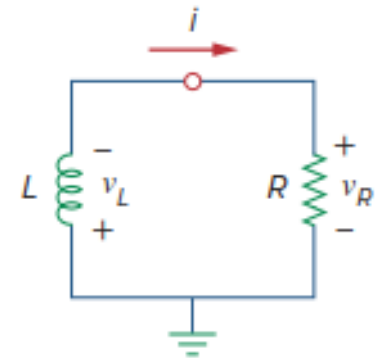

- The **time constant** for the RL circuit is

$$\tau = \frac{L}{R} \text{ (second)}$$

- The **current** through the inductor is,

$$i(t) = I_0 e^{-t/\tau}$$

- The **current response** of the RL circuit is as in Fig.

- The **voltage across the resistor** is

$$v_R(t) = iR = I_0 R e^{-t/\tau}$$


- The **power dissipated** in the resistor is

$$p = v_R i = I_0^2 R e^{-2t/\tau}$$

- The energy absorbed by the resistor is

$$w_R(t) = \frac{1}{2} L I_0^2 (1 - e^{-2t/\tau}), \quad \tau = L/R$$

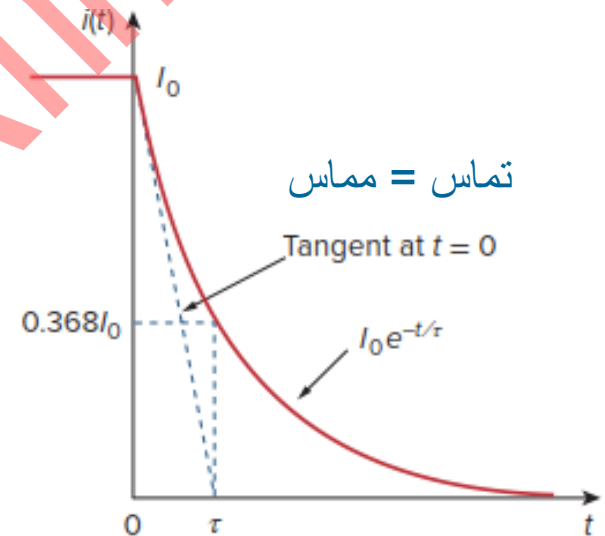- Note that as $t \rightarrow \infty$, $w_R(\infty) \rightarrow \frac{1}{2} L I_0^2$, which is the same as $w_L(0)$, the **initial energy stored** in the inductor.



The Key to Working with a Source-Free RL Circuit is to Find:

The initial current $i(0) = I_0$ through the inductor.

The time constant τ of the circuit.

Example 7.3. The switch in the circuit in Fig. has been closed for a long time, and it is opened at $t = 0$. Find $i(t)$ for $t > 0$.

Solution

For $t < 0$, the switch is closed; and the inductor acts as a short circuit to dc. The 16- Ω resistor is short-circuited; the resulting circuit is shown in Fig.(a).

The 4- Ω and 12- Ω resistors in parallel: $4 \parallel 12 = 3\Omega$

The 2- Ω and 3- Ω resistors in series: $2 + 3 = 5\Omega$.

Hence, $i_1 = \frac{40}{5} = 8\text{ A}$

Using CDR, we get $i(t) = \frac{12}{12+4} i_1 = 6\text{ A}, t < 0$



Since the current through an inductor cannot change instantaneously, $i(0) = i(0^-) = 6\text{ A}$

When $t > 0$, the switch is open and the voltage source is disconnected. We now have the source-free RL circuit in Fig. (b).


$R_{eq} = (12 + 4) \parallel 16 = 8\Omega$

The time constant is $\tau = \frac{L}{R_{eq}} = \frac{2}{8} = \frac{1}{4}\text{ s}$

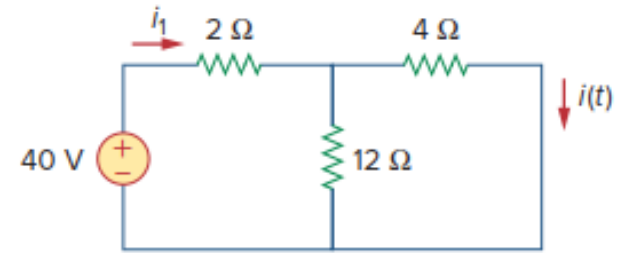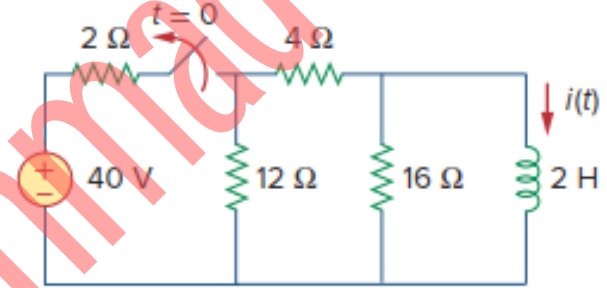Thus, $i(t) = i(0)e^{-t/\tau} = 6e^{-4t}\text{ A}$



(a)

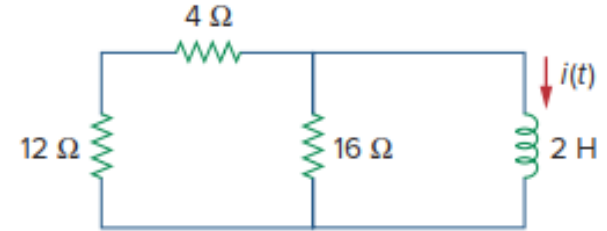

(b)

Example 7.4. In the circuit shown in Fig. , find i_o , v_o , and i for **all time**, assuming that the switch was open for a long time. Plot of i and i_o .

Solution

For $t < 0$, the switch is open. Since the inductor acts like a short circuit to dc, the 6-Ω resistor is short-circuited, Fig. (a). Hence, $i_o = 0$, and




$$i(t) = \frac{10}{2+3} = 2 \text{ A}, \quad t < 0 \Rightarrow v_o(t) = 3i(t) = 6 \text{ V}, \quad t < 0 \Rightarrow i(0) = 2 \text{ A}$$

For $t > 0$, the switch is closed, so that the voltage source is short-circuited. We now have a source-free RL circuit as shown in Fig. (b).

At the inductor terminals: $R_{eq} = R_{Th} = 3 \parallel 6 = 2 \Omega$

The time constant is

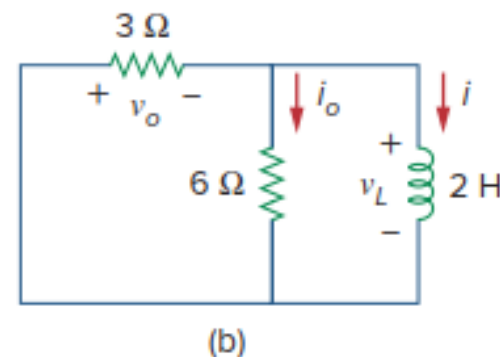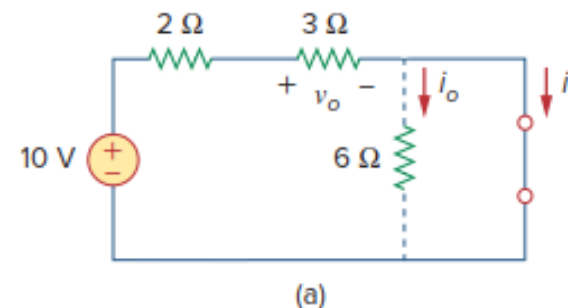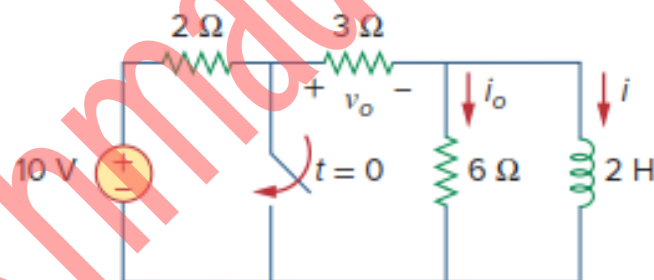
$$\tau = \frac{L}{R_{Th}} = \frac{2}{2} = 1 \text{ s} \Rightarrow i(t) = i(0)e^{-t/\tau} = 2e^{-t} \text{ A}, \quad t > 0$$



Because the inductor is in parallel with the 6- and 3- Ω resistors,

$$v_o(t) = -v_L = -L \frac{di}{dt} = -2(-2e^{-t}) = 4e^{-t} \text{ V}, \quad t > 0$$

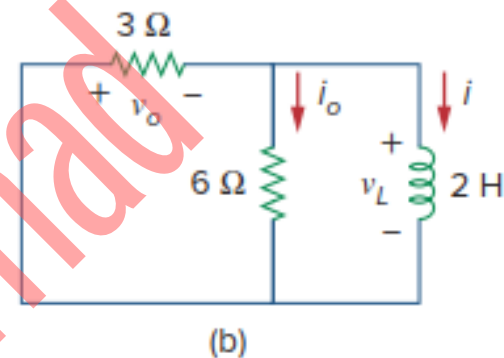
$$i_o(t) = \frac{v_L}{6} = \frac{-v_o}{6} = -\frac{4e^{-t}}{6} = -\frac{2}{3}e^{-t} \text{ A}, \quad t > 0$$



Thus, for all time,

$$i_o(t) = \begin{cases} 0 \text{ A}, & t < 0 \\ -\frac{2}{3}e^{-t} \text{ A}, & t > 0 \end{cases}, \quad v_o(t) = \begin{cases} 6 \text{ V}, & t < 0 \\ 4e^{-t} \text{ V}, & t > 0 \end{cases}$$
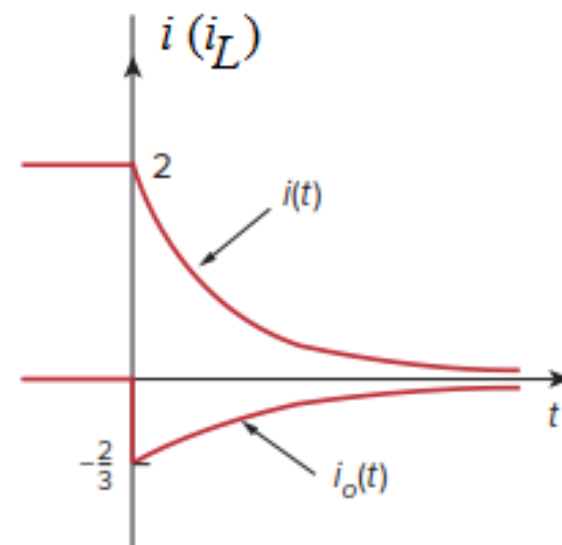
$$i(t) = \begin{cases} 2 \text{ A}, & t < 0 \\ 2e^{-t} \text{ A}, & t \geq 0 \end{cases}$$




7.3 Unit-Step Function

- The **unit step function** $u(t)$ is 0 for negative values of t and 1 for positive values of t .


$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$

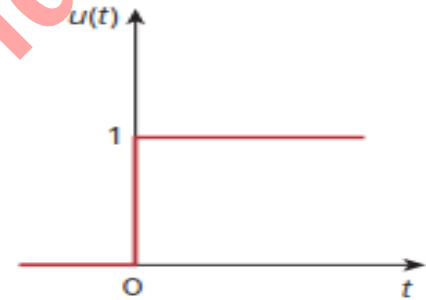- At $t = 0$, where it changes abruptly from 0 to 1.




- At $t = t_0$ (where $t_0 > 0$):
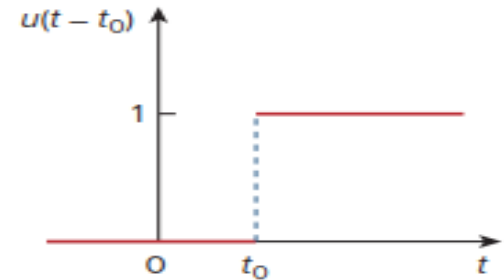
$$u(t - t_0) = \begin{cases} 0, & t < t_0 \\ 1, & t > t_0 \end{cases} \quad (u(t) \text{ is delayed by } t_0 \text{ seconds})$$



- At $t = -t_0$
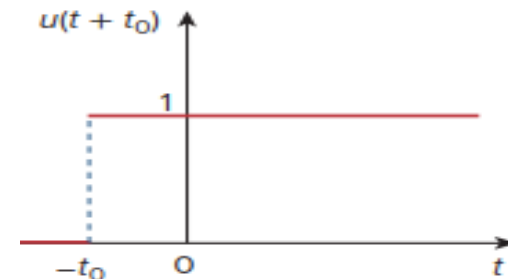
$$u(t + t_0) = \begin{cases} 0, & t < -t_0 \\ 1, & t > -t_0 \end{cases} \quad (u(t) \text{ is advanced by } t_0 \text{ seconds})$$



- The **step function** is used to represent an **abrupt change** in **voltage** or **current**, like the changes that occur in the circuits of control systems and digital computers.

- **For example**, the voltage


$$v(t) = \begin{cases} 0, & t < t_0 \\ V_0, & t > t_0 \end{cases}$$

may be expressed in terms of the **unit step function** as

$$v(t) = V_0 u(t - t_0)$$


- at $t_0 = 0$, then $v(t)$ is simply the step voltage $V_0 u(t)$.

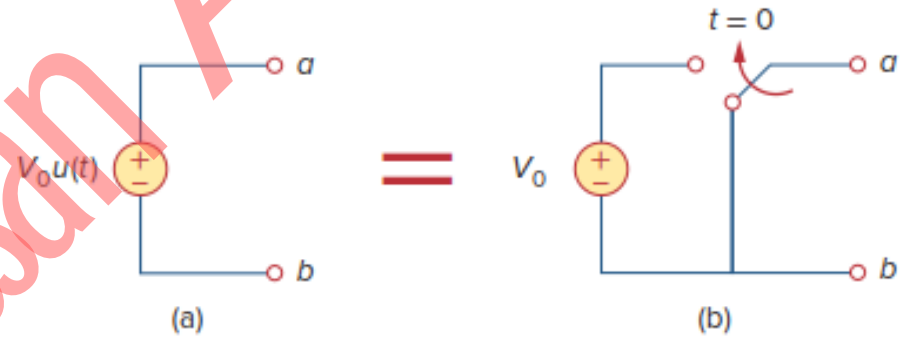- (a) Voltage source of $V_0 u(t)$,
- (b) its equivalent circuit.



- For $t < 0 \rightarrow$ the terminals $a-b$ are **short-circuited** ($v = 0$),
- For $t > 0 \rightarrow$ at the terminals $a-b$ appear $v = V_0$,

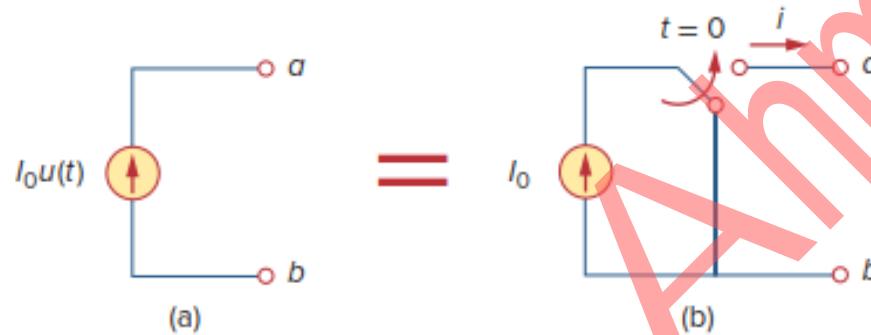- Similarly, a **current source** of $I_0u(t)$ is shown in Fig. (a), while its *equivalent circuit* is in Fig. (b).



- For $t < 0$ → there is an open circuit ($i = 0$),
- For $t > 0$ → flow current $i = I_0$,

7.4 The Step-Response of a RC Circuit

- The **step response** of a circuit is its **behavior** when the **excitation** (إثارة = تحريض) is the **step function**, which may be a voltage or a current source.

- Initial condition:** $v(0^-) = v(0^+) = V_0$
 where $v(0^-)$ is the voltage across the capacitor *just before switching*, $v(0^+)$ is its voltage *immediately after switching*.

- Applying KCL:



$$C \frac{dv}{dt} + \frac{v - V_s u(t)}{R} = 0 \Leftrightarrow \frac{dv}{dt} + \frac{v}{RC} = \frac{V_s}{RC} u(t)$$

For $t > 0 \rightarrow$

$$\frac{dv}{dt} + \frac{v}{RC} = \frac{V_s}{RC} \Rightarrow \frac{dv}{dt} = -\frac{v - V_s}{RC} \text{ or } \frac{dv}{v - V_s} = -\frac{dt}{RC}$$

By integrating and taking the exponential, we have
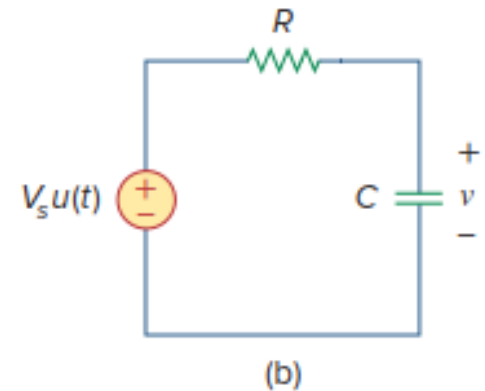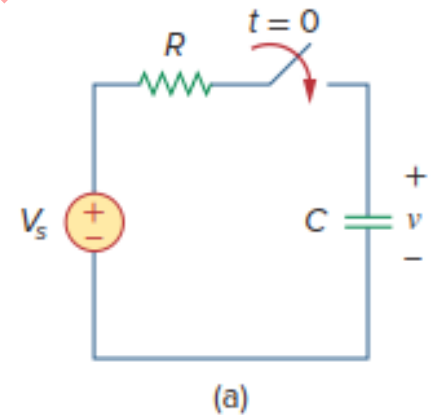
$$v(t) = V_s + (V_0 - V_s)e^{-t/\tau}, \quad \tau = RC, \quad t > 0$$



- The **complete response** (or **total response**) of a **RC circuit** to a *sudden application* of a *dc voltage source* with *initially charged capacitor* (with V_0).




$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau}, & t > 0 \end{cases}$$

- If the capacitor is *uncharged* initially ($V_0 = 0$).

$$v(t) = \begin{cases} 0, & t < 0 \\ V_s(1 - e^{-t/\tau}), & t > 0 \end{cases} \Leftrightarrow v(t) = V_s(1 - e^{-t/\tau})u(t)$$

$$\Rightarrow i(t) = C \frac{dv}{dt} = \frac{C}{\tau} V_s e^{-t/\tau}, \quad \tau = RC, \quad t > 0$$
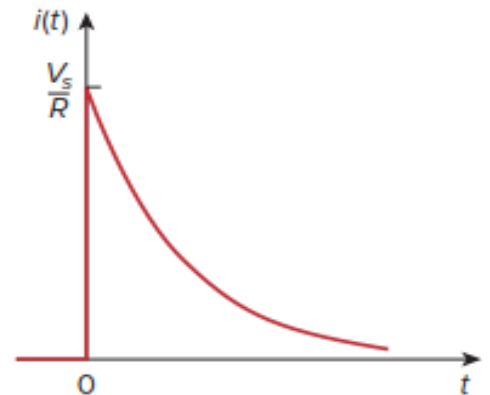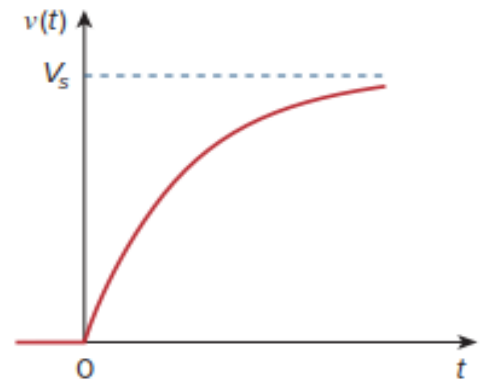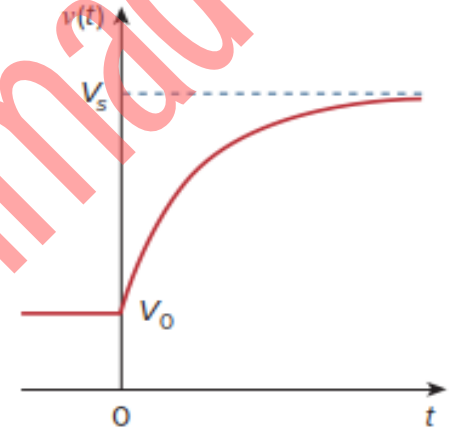
$$\Rightarrow i(t) = \frac{V_s}{R} e^{-t/\tau} u(t)$$



- The **complete response can be looked by tow ways:**

- **One way:** Complete response = $\underbrace{\text{natural response}(v_n)}_{\text{stored energy}} + \underbrace{\text{forced response}(v_f)}_{\text{independent source}}$

$$v = v_n + v_f; \quad v_n = V_0 e^{-t/\tau}, \quad v_f = V_s (1 - e^{-t/\tau})$$

- **Another way:**

- Complete response = $\underbrace{\text{transient response}(v_t)}_{\text{temperary part}} + \underbrace{\text{steady-state response}(v_{ss})}_{\text{permanent part}}$

$$v = v_t + v_{ss}; \quad v_t = (V_0 - V_s) e^{-t/\tau}, \quad v_{ss} = V_s$$

- The **transient response** is the circuit's temporary response (الاستجابة المؤقتة) that will die out (تتقرض = تموت) with time.
- The **steady-state response** is the behavior of the circuit a *long time after* an external excitation is applied.
- Finally, the **complete response can be written as:**

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$

- where $v(0)$ is the *initial voltage* at $t = 0^+$ and $v(\infty)$ is the *final or steady-state value*.

Three steps to find out the *step response* of an *RC* circuit:

1. The initial capacitor voltage $v(0)$.
2. The final capacitor voltage $v(\infty)$.
3. The time constant τ .

We obtain item 1 from the given circuit for $t < 0$ and items 2 and 3 from the circuit for $t > 0$

Note that if the switch changes position at time $t = t_0$ instead of at $t = 0$, there is a **time delay** in the response so that the **complete response** becomes:


$$v(t) = v(\infty) + [v(t_0) - v(\infty)]e^{-(t-t_0)/\tau}$$

where $v(t_0)$ is the *initial value* at $t = t_0^+$

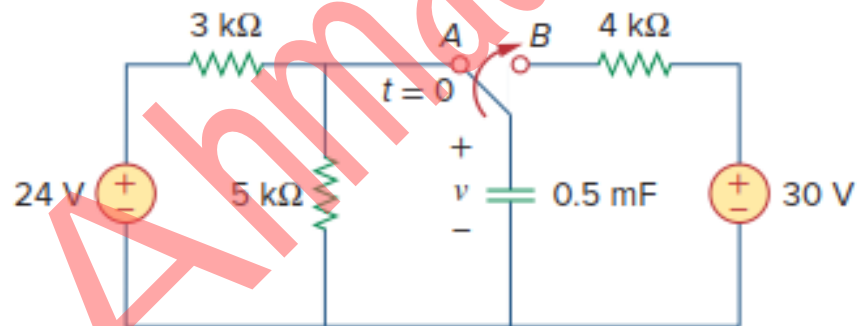Example 7.5. The switch in Fig. has been in position *A* for a long time. At $t = 0$, the switch moves to *B*. Determine $v(t)$ for $t > 0$ and calculate its value at $t = 1$ and 4 s.

Solution

For $t < 0$, the switch is at position *A*. The capacitor acts like an open circuit to dc, but v is the same as the voltage across the 5-k Ω resistor.



Hence, the voltage across the capacitor just before $t = 0$ is obtained by voltage division as

$$v(0^-) = \frac{5}{5+3}(24) = 15 \text{ V}$$

The capacitor voltage cannot change instantaneously: $v(0) = v(0^-) = v(0^+) = 15 \text{ V}$

For $t > 0$, the switch is in position *B*. The Thevenin resistance connected to the capacitor is $R_{Th} = 4 \text{ k}\Omega$, and the time constant is $\tau = R_{Th}C = 4 \times 10^3 \times 0.5 \times 10^{-3} = 2 \text{ s}$. Since the capacitor acts like an open circuit to dc at steady state, $v(\infty) = 30 \text{ V}$.

Thus,

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau} = 30 + (15 - 30)e^{-t/2} = (30 - 15e^{-0.5t}) \text{ V}$$

$$t = 1 \Rightarrow v(1) = 30 - 15e^{-0.5} = 20.9 \text{ V}$$

$$t = 4 \Rightarrow v(4) = 30 - 15e^{-2} = 27.97 \text{ V}$$

Example 7.6. In Fig., the switch has been closed for a long time and is opened at $t = 0$. Find i and v for all time.

Solution

At $t = 0$, The current i can be discontinuous (منقطع), while the capacitor voltage v cannot.

Hence, it is always better to find v and then obtain i from v .



The unit step function is $30u(t) = \begin{cases} 0, & t < 0 \\ 30, & t > 0 \end{cases}$

For $t < 0$,

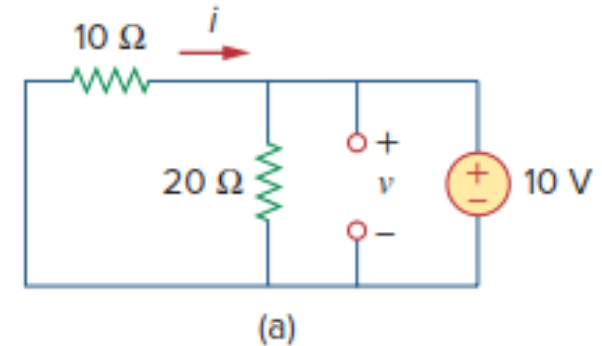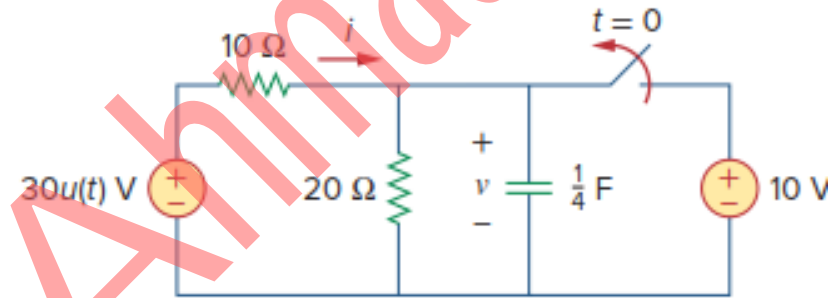- 1) the switch is closed and $30u(t) = 0$, so that the $30u(t)$ voltage source is replaced by a **short circuit**.
- 2) Since the switch has been closed for a long time, the capacitor voltage has reached steady state and the capacitor acts like an **open circuit**, Fig. (a).

From this circuit we obtain $v = 10 \text{ V} \Rightarrow i = -\frac{v}{10} = -1 \text{ A}$

Since the capacitor voltage cannot change instantaneously, $v(0) = v(0^-) = 10 \text{ V}$



For $t > 0$,

- 1) the switch is opened and the 10-V voltage source is disconnected from the circuit.
- 2) The $30u(t)$ voltage source is now operative, Fig.(b).
- 3) After a long time, the circuit reaches *steady state* and the capacitor acts like an **open circuit** again.

We obtain $v(\infty)$ by using VDR, writing

$$v(\infty) = \frac{20}{20+10} (30) = 20 \text{ V}$$

The Thevenin resistance at the capacitor terminals



is

$$R_{Th} = 10 \parallel 20 = \frac{20}{3} \Omega$$

The time constant is

$$\tau = R_{Th} C = \frac{20}{3} \times \frac{1}{4} = \frac{5}{3} \text{ s}$$

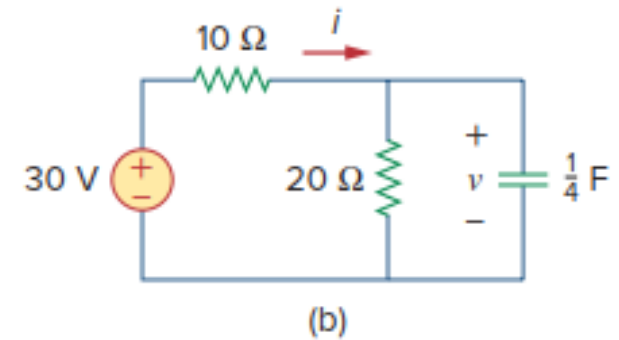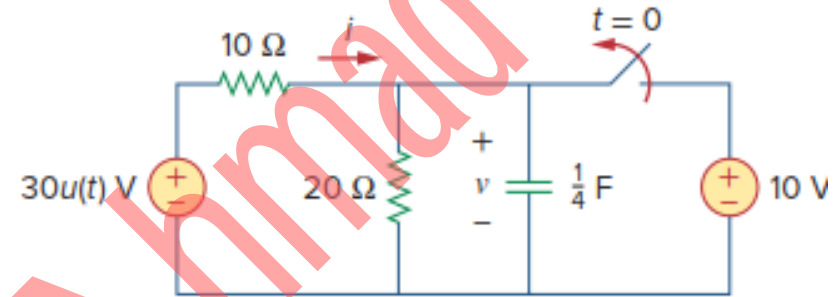Thus, $v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau} = 20 + (10 - 20)e^{-(3/5)t} = (20 - 10e^{-0.6t}) \text{ V}$



To obtain i , from Fig. (b):


$$i = \frac{v}{20} + C \frac{dv}{dt} = \frac{20 - 10e^{-0.6t}}{20} + \frac{1}{4} \cdot \frac{d(20 - 10e^{-0.6t})}{dt}$$

$$= 1 - 0.5e^{-0.6t} + 0.25(-0.6)(-10)e^{-0.6t} = (1 + e^{-0.6t}) \text{ A}$$

(Alternately, $v + 10i = 30\text{V}$)

Finally,
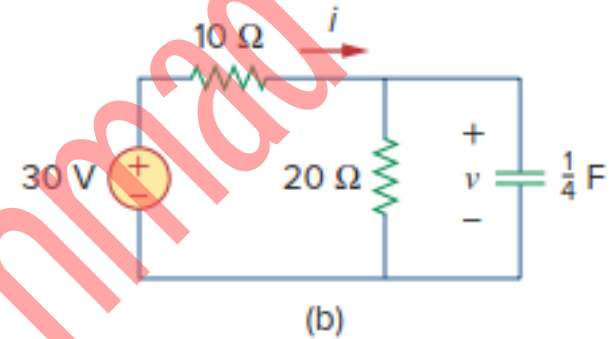
$$v = \begin{cases} 10\text{V}, & t < 0 \\ (20 - 10e^{-0.6t})\text{V}, & t \geq 0 \end{cases}; \quad i = \begin{cases} -1\text{A}, & t < 0 \\ (1 + e^{-0.6t})\text{A}, & t \geq 0 \end{cases}$$



7.5 The Step-response of a RL Circuit

- The **step response** of a circuit is its behavior when the excitation is the step function, which may be a voltage or a current source.
- The **circuit response** is the inductor current $i = ???$.
 - The *response* is the sum of the *transient response* and the *steady-state response*:


$$i = i_t + i_{ss}$$

- The *transient response* is always a **decaying exponential**: $i_t = Ae^{-t/\tau}$, $\tau = \frac{L}{R}$, A – constant
- The *steady-state response* is the **value** of the **current** a long time after the switch is closed.


$$i_{ss} = \frac{V_s}{R}$$

- Thus,

$$i = Ae^{-t/\tau} + \frac{V_s}{R}$$

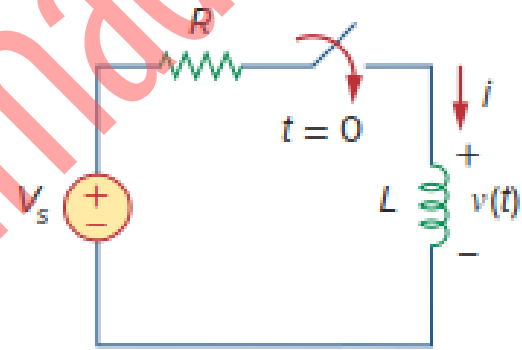

(a)

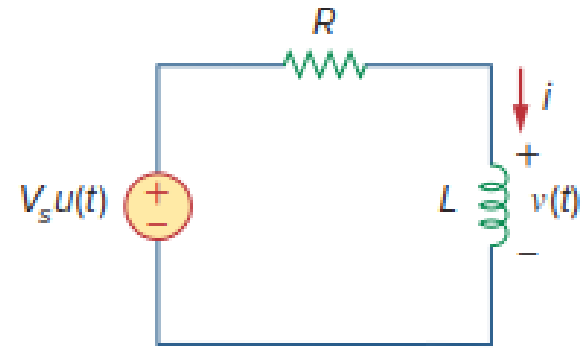

(b)

- Since the current through the inductor cannot change instantaneously,

- at $t = 0$, the **initial current** is $i(0^+) = i(0^-) = I_0$


$$i = Ae^{-t/\tau} + \frac{V_s}{R} \Rightarrow I_0|_{t=0} = A + \frac{V_s}{R} \Rightarrow A = I_0 - \frac{V_s}{R}$$

at $t = \infty$, the **Final inductor current** is

$$i(\infty) = \frac{V_s}{R}$$

- This is the **complete response** of the *RL* circuit
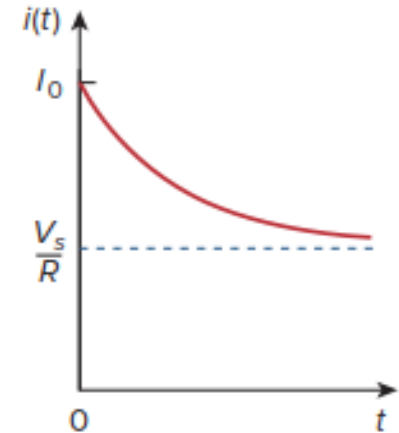
$$i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-t/\tau} \Leftrightarrow i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$



Three steps to find out the step response of an *RL* circuit:

1. The initial inductor current $i(0)$ at $t = 0$.
2. The final inductor current $i(\infty)$.
3. The time constant τ .

- at time $t = t_0$: $i(t) = i(\infty) + [i(t_0) - i(\infty)]e^{-(t-t_0)/\tau}$

- If $I_0 = 0$, then, the *step response* of the *RL* circuit with no initial inductor current.

$$i(t) = \begin{cases} 0, & t < 0 \\ \frac{V_s}{R}(1 - e^{-t/\tau}), & t > 0 \end{cases} \Leftrightarrow i(t) = \frac{V_s}{R}(1 - e^{-t/\tau})u(t)$$


- The **voltage** across the inductor is

$$v(t) = L \frac{di}{dt} = L \frac{d}{dt} \left(\frac{V_s}{R} (1 - e^{-t/\tau}) \right) = V_s \frac{1}{\tau} \frac{L}{R} e^{-t/\tau}$$


- With $\tau = \frac{L}{R} \rightarrow v(t) = V_s e^{-t/\tau} u(t)$

(a) current response.

(b) voltage response.

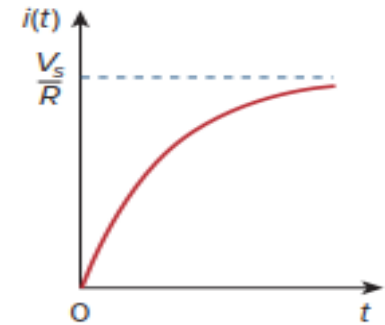

(a)

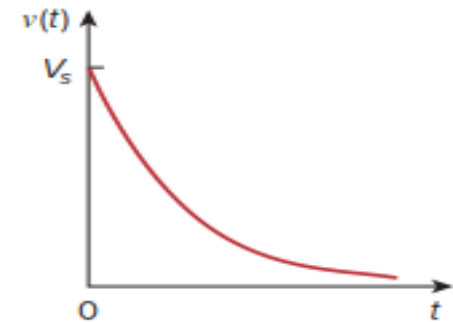

(b)

Example 7.7. Find $i(t)$ in the circuit of Fig. $t > 0$. Assume that the switch has been closed for a long time.

Solution

- 1) When $t < 0$, the $3\text{-}\Omega$ resistor is short-circuited, and the inductor acts like a short circuit, so that

$$i(0^-) \Big|_{t=0^-} = \frac{10}{2} = 5 \text{ A}$$

Because the inductor current *cannot change instantaneously*, $i(0) = i(0^-) = i(0^+) = 5 \text{ A}$

- 2) When $t > 0$, the switch is open. The $2\text{-}\Omega$ and $3\text{-}\Omega$ resistors are in series, so that


$$i(\infty) = \frac{10}{2+3} = 2 \text{ A}$$

The Thevenin resistance across the inductor terminals is $R_{Th} = 2 + 3 = 5 \Omega$

- 3) The time constant,

$$\tau = \frac{L}{R_{Th}} = \frac{1}{5} = \frac{1}{15} \text{ s}$$

Finally, $i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau} = 2 + (5 - 2)e^{-15t} = 2 + 3e^{-15t} \text{ A}, t > 0$

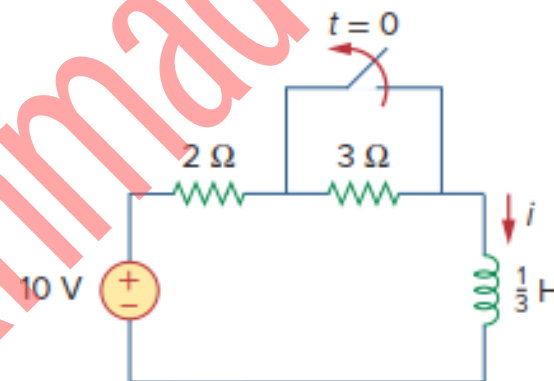

Example 7.8. At $t = 0$, switch 1 in Fig. is closed, and switch 2 is closed 4 s later (time delay).

Find $i(t)$ for $t > 0$. Calculate i for $t = 2$ s and $t = 5$ s.

Solution

We need to consider the three time intervals $t \leq 0$, $0 \leq t \leq 4$, and $t \geq 4$ separately.


For $t < 0$, switches S1 and S2 are open so that

$$i = 0: \quad i(0^-) = i(0) = i(0^+) = 0$$


For $0 \leq t \leq 4$, S1 is closed and S2 is still open, so that the 4- and 6- Ω resistors are in series.

$$\text{Hence, } i(\infty) = \frac{40}{4+6} = 10 \text{ A, } R_{Th} = 4+6 = 10\Omega, \quad \tau = \frac{L}{R_{Th}} = \frac{5}{10} = \frac{1}{2} \text{ s}$$
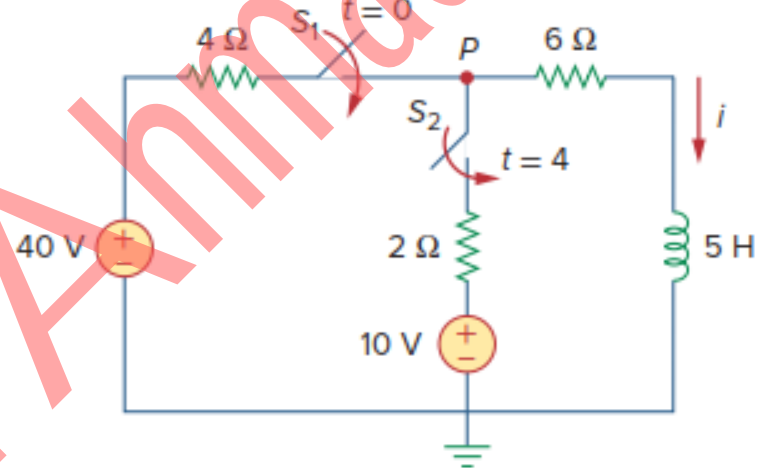
$$\text{Thus, } i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau} = 4 + (0 - 4)e^{-2t} = 4(1 - e^{-2t}) \text{ A, } 0 \leq t \leq 4$$



For $t \geq 4$, S2 is closed (S1 is still closed); the 10-V voltage source is connected, and the circuit changes. This *sudden change* does not affect the inductor current because the current *cannot change abruptly* (مفاجئ). Thus, the initial current is $i(t)|_{t=4} = i(4) = i(4^-) = 4(1 - e^{-8}) \approx 4$ A

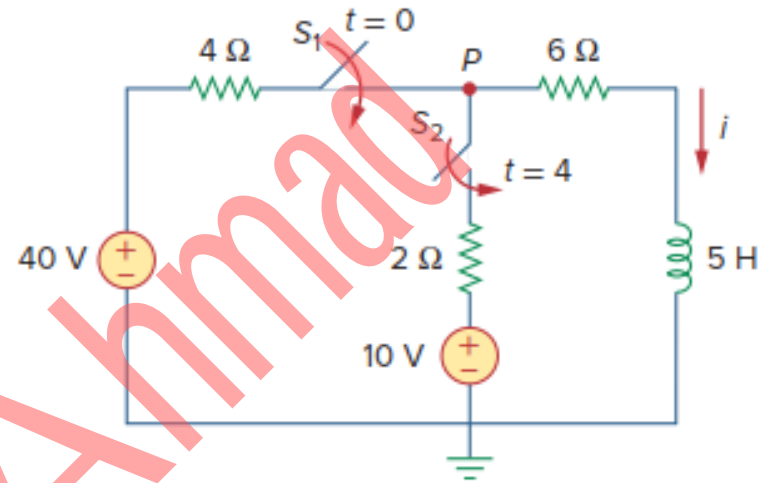

To find $i(\infty)$, let v be the **voltage** at node P in Fig. Using KCL,

$$\frac{40-v}{4} + \frac{10-v}{2} = \frac{v}{6} \Rightarrow v = \frac{180}{11} \text{ V}, \quad i(\infty) = \frac{V_s}{R} = \frac{v}{6} = 2.727 \text{ A}$$

The Thevenin resistance at the inductor terminals is

$$R_{Th} = (4 \parallel 2) + 6 = \frac{22}{3} \Omega \Rightarrow \tau = \frac{L}{R_{Th}} = \frac{5}{\frac{22}{3}} = \frac{15}{22} \text{ s}$$


Hence,

$$i(t) = i(\infty) + [i(t_0) - i(\infty)]e^{-(t-t_0)/\tau} \Big|_{t_0=4} = 2.727 + [4 - 2.727]e^{-(t-4)/\tau}, \quad \tau = \frac{15}{22}$$

$$= 2.727 + 1.273e^{-1.4667(t-4)}, \quad t \geq 4$$

Finally,
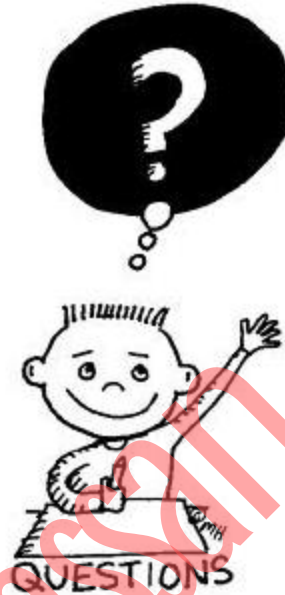
$$i(t) = \begin{cases} 0, & t \leq 0 \\ 4(1 - e^{-2t}), & 0 \leq t \leq 4 \\ 2.727 + 1.273e^{-1.4667(t-4)}, & t \geq 4 \end{cases}$$



The end of chapter 7