



الجامعة السورية الخاصة  
SYRIAN PRIVATE UNIVERSITY

كلية هندسة الحاسوب والمعلوماتية  
Computer and Informatics Engineering  
Faculty

# Electric Circuits I

*Dr. Eng.*

*Hassan M. Ahmad*

[Hassan.Ahmad@spu.edu.sy](mailto:Hassan.Ahmad@spu.edu.sy),

[istamo48@mail.ru](mailto:istamo48@mail.ru)


# Chapter 5

## Operational Amplifier

- 5.1 What is an Op Amp?
- 5.2 Ideal Op Amp
- 5.3 Configuration of Op Amp
- 5.4 Cascaded Op Amp
- 5.5 Application
  - Digital-to Analog Converter


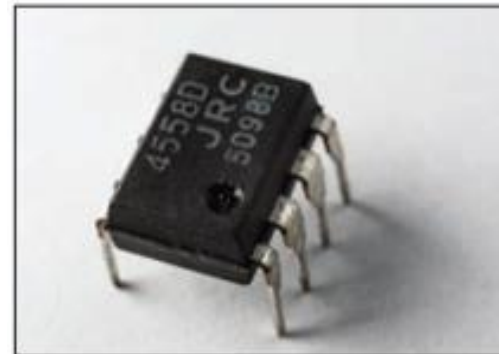
# 5.1 What is an Op Amp

- ❑ The **operational amplifier** , or (**op amp** for short) is an electronic unit that behaves like a **voltage-controlled voltage source (VCVS)**.
- ❑ It is an **active circuit element** designed to perform mathematical operations of ***addition, subtraction, multiplication, division, differentiation*** and ***integration***.
- ❑ Op amps are *commercially* available in *integrated circuit (IC) packages* in several forms as shown in Fig. for a typical operational amplifier.


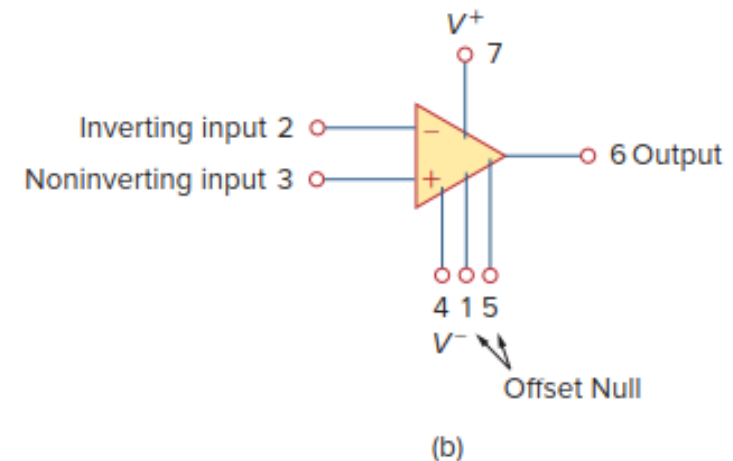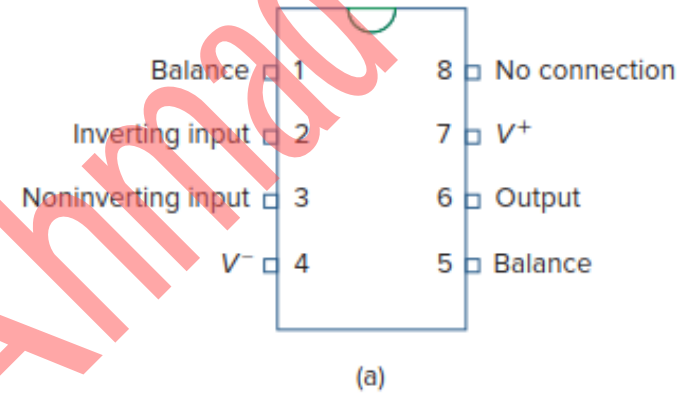
# Op Amp

- A typical Op amp is the eight-pin dual in-line package (or DIP), Fig. (a).
- Pin or terminal 8 is unused, and terminals 1 and 5 are of little concern to us.
- The five important terminals are:
  - The inverting input, pin 2.
  - The noninverting input, pin 3.
  - The output, pin 6.
  - The positive power supply  $V^+$ , pin 7.
  - The negative power supply  $V^-$ , pin 4.
- The circuit symbol for the op amp is the triangle in Fig.(b);
  - The inputs are marked with minus (-) and plus (+) to specify *inverting* and *noninverting* inputs.



# Op Amp

- As an active element, the **op amp** must be powered by a voltage supply ( $V_{CC}$ ), Fig. (a)

- By applying KCL:

$$i_o = i_1 + i_2 + i_+ + i_-$$

- The **equivalent circuit model** of an op amp, Fig.(b).

- $R_i$  is the **Thevenin equivalent resistance** seen at the input terminals, while  $R_o$  is the **Thevenin equivalent resistance** seen at the output.
- The **differential input voltage**  $v_d$  is given by


$$v_d = v_2 - v_1$$

where  $v_1$  - inverting terminal voltage;  $v_2$  - noninverting terminal voltage.


- The **output**  $v_o$  is given by  $v_o = Av_d = A(v_2 - v_1)$

where  $A$  is called the **open-loop voltage gain** because it is the gain of the op amp *without any external feedback* from output to input.

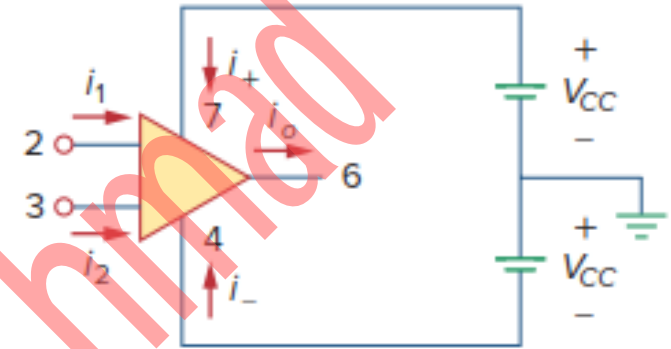- When there is a **feedback path** from output to input, the **ratio of the output voltage to the input voltage** is called the **closed-loop gain**.



(a)

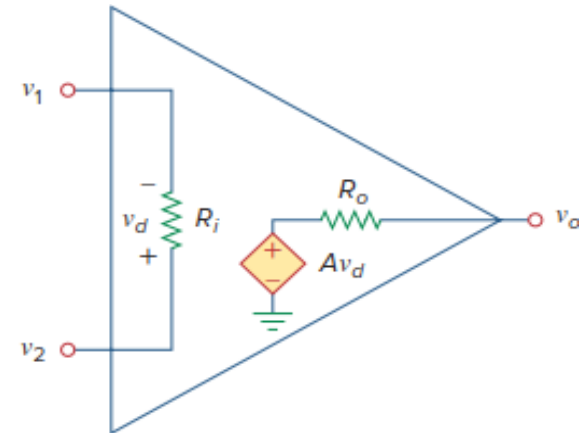

(b)

# Op Amp

- Typical ranges for op amp parameters (see table).

- The op amp can operate in **three modes**, depending on the differential input voltage  $v_d$ , as shown in Fig.

1. Positive saturation,  $v_o = V_{CC}$ .

2. Linear region ,


$$-V_{CC} \leq v_o = Av_d \leq V_{CC}.$$

3. Negative saturation,  $v_o = -V_{CC}$ .

- We will assume that our op amps operate in the linear mode, the output voltage is restricted by

$$-V_{CC} \leq v_o \leq V_{CC}$$

Parameter	Typical range	Ideal values
Open-loop gain, $A$	$10^5$ to $10^8 \Omega$	$\infty \Omega$
Input resistance, $R_i$	$10^5$ to $10^{13} \Omega$	$\infty \Omega$
Output resistance, $R_o$	10 to 100 $\Omega$	0 $\Omega$
Supply voltage, $V_{CC}$	5 to 24 V	

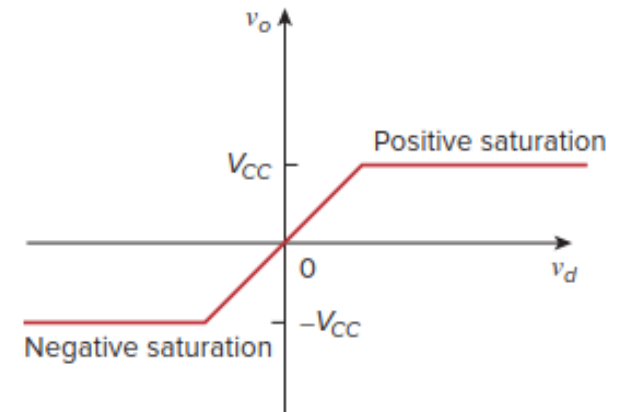

## Example 5.1

A 741 op amp has an open-loop voltage gain of  $2 \times 10^5$ , input resistance of  $2 \text{ M}\Omega$ , and output resistance of  $50 \Omega$ . The op amp is used in the circuit of Fig.(a).

- Find the closed-loop gain  $v_o/v_s$ .
- Determine current  $i$  when  $v_s = 2 \text{ V}$ .

### Solution

Using the equivalent circuit model for op amp, we obtain the equivalent circuit of Fig.(a) as shown in Fig.(b).

At **node 1**, KCL gives

$$\frac{v_s - v_1}{10 \times 10^3} = \frac{v_1}{2000 \times 10^3} + \frac{v_1 - v_o}{20 \times 10^3} \Rightarrow 200v_s = 301v_1 - 100v_o \Rightarrow 2v_s = 3v_1 - v_o$$

$$\Rightarrow v_1 = \frac{2v_s + v_o}{3} \quad (1)$$


At **node O**,  $\frac{v_1 - v_o}{20 \times 10^3} = \frac{v_o - Av_d}{50}$ , but  $v_d = v_1$

$$\Rightarrow v_1 - v_o = 400[v_o + (2 \times 10^5)v_1] \quad (2)$$


Substituting  $v_1$  from Eq. (1) into Eq. (2) gives

$$0 = 26667067v_o + 53333333v_s \Rightarrow \frac{v_o}{v_s} = -1.9999699$$
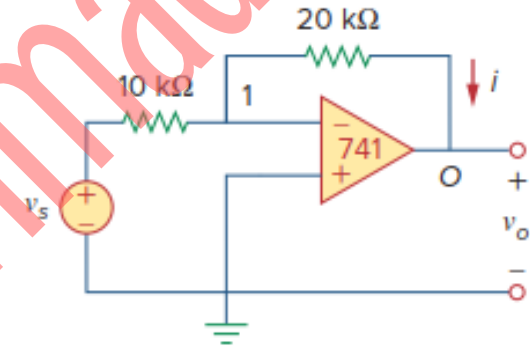
$$v_s = 2\text{V} \Rightarrow v_o = -3.9999398\text{V} \text{ and } v_1 = 20.066667\text{V} \Rightarrow i = \frac{v_1 - v_o}{20 \times 10^3} = 0.19999\text{mA}$$



(a)

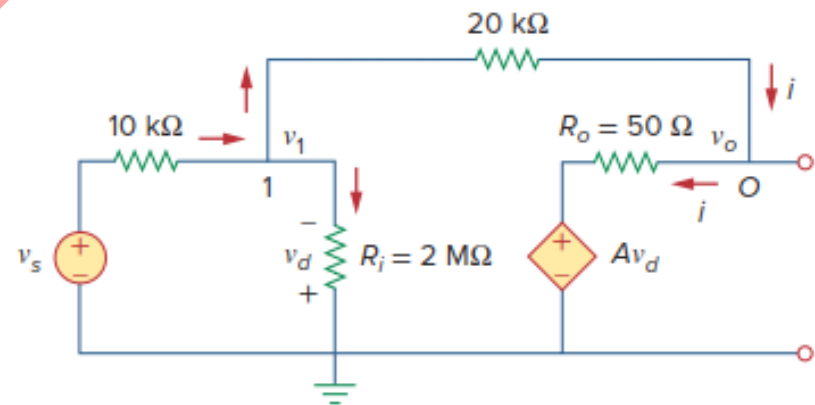


(b)
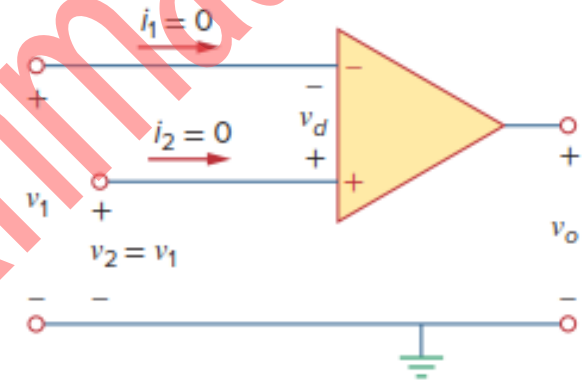
## 5.2 Ideal Op Amp

- An **ideal op amp** has the following **characteristics**:

- Infinite open-loop gain,  $A \approx \infty$
- Infinite input resistance,  $R_i \approx \infty$
- Zero output resistance,  $R_o \approx 0$ .



- **Two important characteristics** of the ideal op amp are:

1. The currents into both input terminals are zero:

$$i_1 = 0, \quad i_2 = 0$$

2. The voltage across the input terminals is equal to zero; i.e.,

$$v_d = v_2 - v_1 = 0 \Rightarrow v_1 = v_2$$



## Example 5.2.

Using the ideal op amp model in Fig.

- Find the closed-loop gain  $v_o/v_s$ .
- Determine current  $i_o$  when  $v_s = 1$  V.

### Solution:

- Notice that  $v_2 = v_s$
- Since  $i_1 = 0$ , the 40-k $\Omega$  and 5-k $\Omega$  resistors are in series; The same current flows through them.
- $v_1$  is the voltage across the 5-k $\Omega$  resistor.
- Hence, using the voltage division principle (VDR),


$$v_1 = \frac{5}{5+40} v_o = \frac{v_o}{9}$$

- For ideal op amp, we know that  $v_2 = v_1$

So,  $v_2 = v_1 = v_s = \frac{v_o}{9} \Rightarrow \frac{v_o}{v_s} = 9$

- At node  $O$ , (KCL):
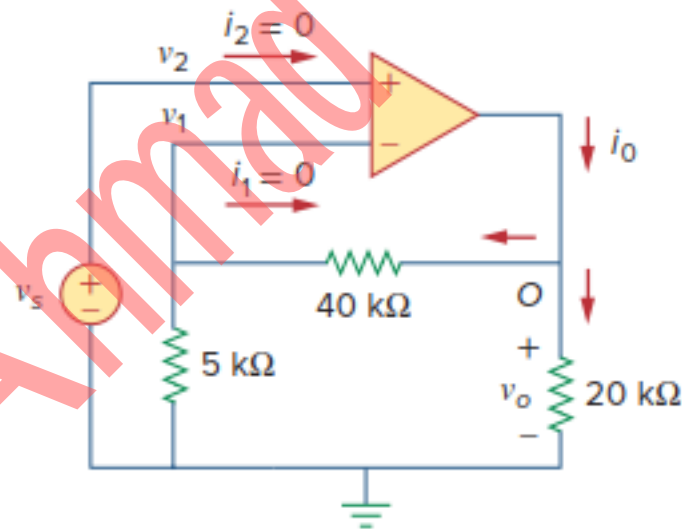
$$i_o = \frac{v_o}{40+5} + \frac{v_o}{20} \text{ mA}$$



- When  $v_s = 1$  V  $\rightarrow v_o = 9$  V.  
Then,

$$i_o = 0.2 + 0.45 = 0.65 \text{ mA}$$

# 5.3 Configuration of Op amp

1. **Inverting amplifier** reverses the polarity of the input signal while amplifying it.

□ The circuit of inverting amplifier is shown in Fig.(a).

- The noninverting input is grounded,
- $v_i$  is connected to the inverting input through  $R_1$ ,
- The **feedback resistor**  $R_f$  is connected between the inverting input and output.



□ Our goal is to obtain the **relationship** between the **input voltage**  $v_i$  and the **output voltage**  $v_o$ .

- Applying KCL at node 1,  $i_1 = i_2 \Rightarrow \frac{v_i - v_1}{R_1} = \frac{v_1 - v_o}{R_f}$
- But  $v_1 = v_2 = 0$  for an ideal op amp, since the noninverting terminal is grounded. Hence,

$$\frac{v_i}{R_1} = -\frac{v_o}{R_f} \Rightarrow v_o = -\frac{R_f}{R_1} v_i$$

$$A_v = \frac{v_o}{v_i} = -\frac{R_f}{R_1}$$

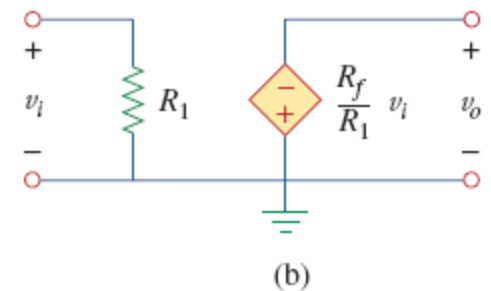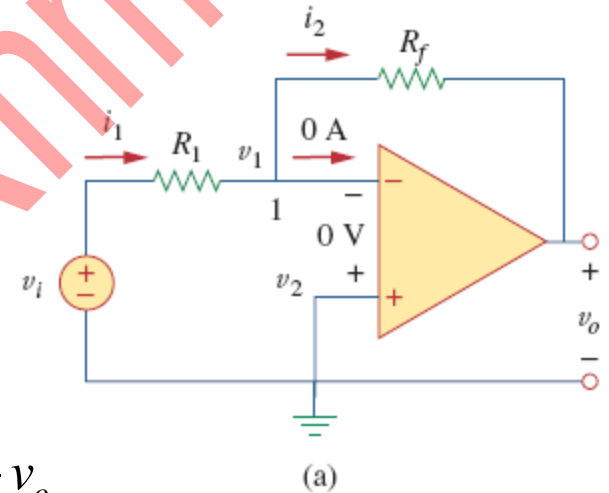- The **voltage gain** is
- The **equivalent circuit for the inverting amplifier** is shown in Fig. (b)



### Example 5.3.

Refer to the op amp in Fig. If  $v_i = 0.5\text{V}$ , calculate:

- (a) the output voltage,  $v_o$  ;
- (b) the current in the  $10\text{k}\Omega$  resistor.


**Solution:**

- a) Output voltage:

$$v_o = -\frac{R_f}{R_1} v_i = -\frac{25}{10} (0.5) = -1.25 \text{ V}$$

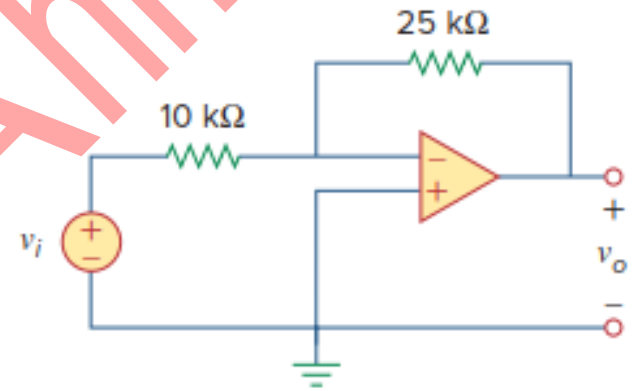- b) the current through the  $10\text{k}\Omega$  resistor is:

$$i = \frac{v_i - 0}{R_1} = \frac{0.5 - 0}{10 \times 10^3} = 50 \mu\text{A}$$



### Example 5.4.

Determine  $v_o$  in the op amp circuit shown in Fig.

**Solution:**

Applying KCL at node  $a$ ,


$$\frac{v_a - v_o}{40\text{k}\Omega} = \frac{6 - v_a}{20\text{k}\Omega} \Rightarrow v_a - v_o = 12 - 2v_a$$

$$\Rightarrow v_o = 3v_a - 12$$

But  $v_a = v_b = 2\text{ V}$  for an ideal op amp. Hence,

$$v_o = 3 \times 2 - 12 = -6\text{ V}$$

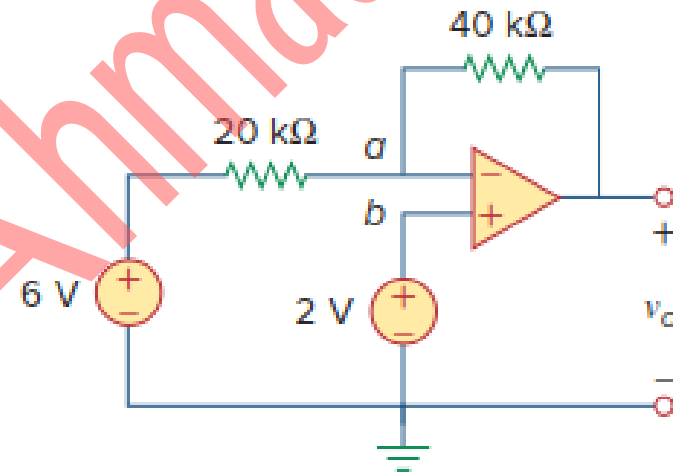**Notice** that if  $v_b = 0 = v_a$ , then  $v_o = -12$ .



**2. Non-inverting amplifier** is designed to produce positive voltage gain.

- The circuit of the op amp is the noninverting amplifier is shown in Fig.
  - Application of KCL at the inverting terminal gives

$$i_1 = i_2 \Rightarrow \frac{0 - v_1}{R_1} = \frac{v_1 - v_o}{R_f}$$

- But  $v_1 = v_2 = v_i$ ,


so 
$$\frac{-v_i}{R_1} = \frac{v_i - v_o}{R_f} \Rightarrow v_o = \left( 1 + \frac{R_f}{R_1} \right) v_i$$

- The **voltage gain** is

$$A_v = \frac{v_o}{v_i} = 1 + \frac{R_f}{R_1}$$

which **does not** have a **negative sign**.


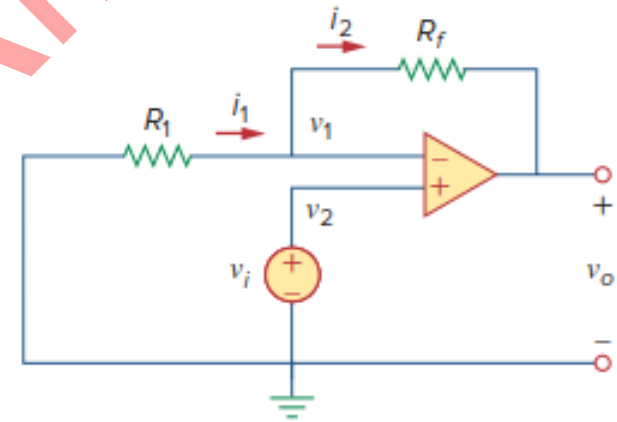
Thus, the output has the same polarity as the input.



- In noninverting amplifier circuit, if feedback resistor  $R_f = 0$  (short circuit) or  $R_1 = \infty$  (open circuit) or **both**, the **gain becomes 1**.

- Under these conditions, the circuit is called a **voltage follower** (تابع/متتبع الجهد) (or *unity gain amplifier*). Hence, 
$$v_o = v_i$$

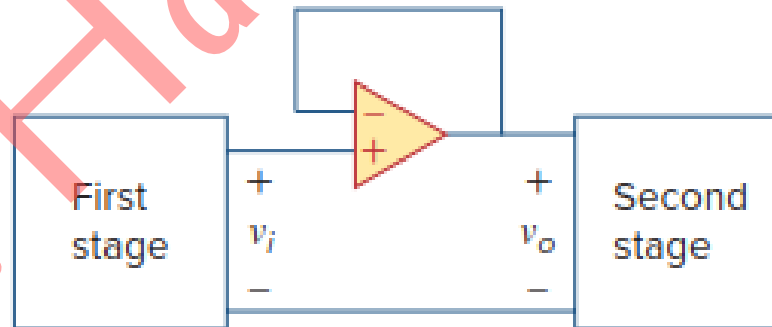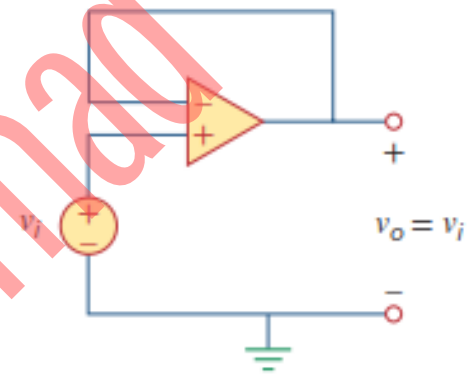- Such a circuit has a **very high input impedance** and is therefore useful as an **intermediate-stage** (or **buffer**) amplifier (مكبر صنادّ للتغذية المرتدة) to isolate one circuit from another, as in Fig.



## Example 5.5.

For the op amp shown in Fig., calculate the output voltage  $v_o$ .

**Solution:**

**METHOD 1.** Using **superposition**, we let

$$v_o = v_{o1} + v_{o2}$$

where  $v_{o1}$  is due to the 6-V voltage source, and  $v_{o2}$  is due to the 4-V input.

- To get  $v_{o1}$ , we set the 4-V source equal to zero.

The circuit becomes an **invert. amp.**

$$v_{o1} = -\frac{10}{4}(6) = -15 \text{ V}$$

- To get  $v_{o2}$ , we set the 6-V source equal to zero. The circuit becomes a **noninvert. amp.**, so that

$$v_{o2} = \left(1 + \frac{10}{4}\right)4 = 14 \text{ V}$$


- Thus,  $v_o = v_{o1} + v_{o2} = -15 + 14 = -1 \text{ V}$

**METHOD 2.** Using **nodal analysis**.

- Applying KCL at node  $a$ ,

$$\frac{6 - v_a}{4} = \frac{v_a - v_o}{10}$$

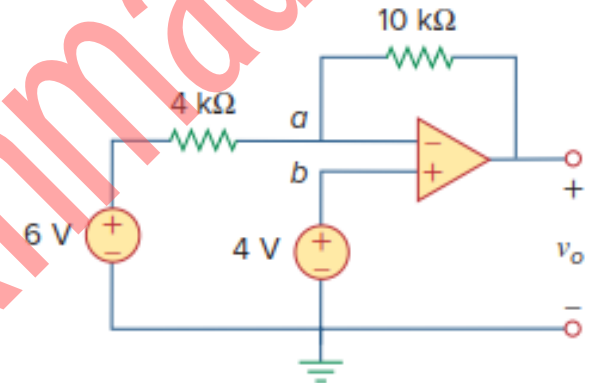- But  $v_a = v_b = 4$ , so  $5 = 4 - v_o \Rightarrow v_o = -1 \text{ V}$



**3. Summing Amplifier** is an op amp circuit that combines several inputs and produces an output that is the weighted sum of the inputs.

- Applying KCL at node *a* gives:

$$i = i_1 + i_2 + i_3$$


- But

$$i_1 = \frac{v_1 - v_a}{R_1}; i_2 = \frac{v_2 - v_a}{R_2}$$

$$i_3 = \frac{v_3 - v_a}{R_3}; i = \frac{v_a - v_o}{R_f}$$

- We note that  $v_a = 0$ , thus
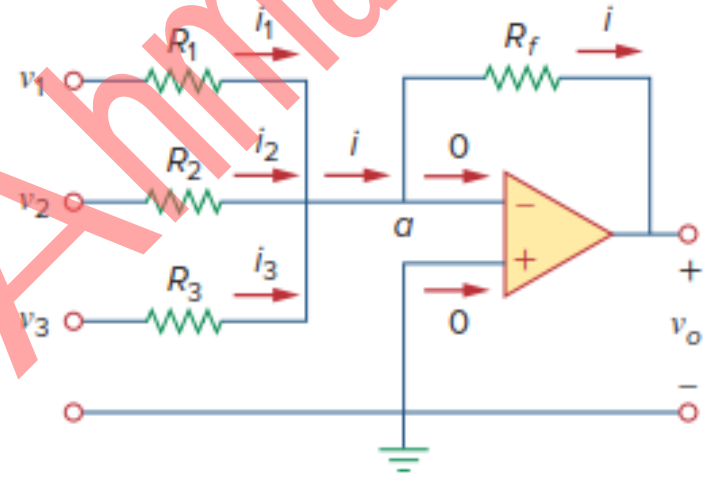
$$v_o = - \left( \frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right)$$





## Example 5.6.

Calculate  $v_o$  and  $i_o$  in the op amp circuit shown below.


### Solution:

This is a summer with two inputs.

$$v_o = -\left[\frac{10}{5}(2) + \frac{10}{2.5}(1)\right] = -(4 + 4) = -8 \text{ V}$$

- The current  $i_o$  is the sum of the currents through the 10-k $\Omega$  and 2-k $\Omega$  resistors.
- Both of these resistors have voltage  $v_o = -8 \text{ V}$  across them, since  $v_a = v_b = 0$ .
- Hence,
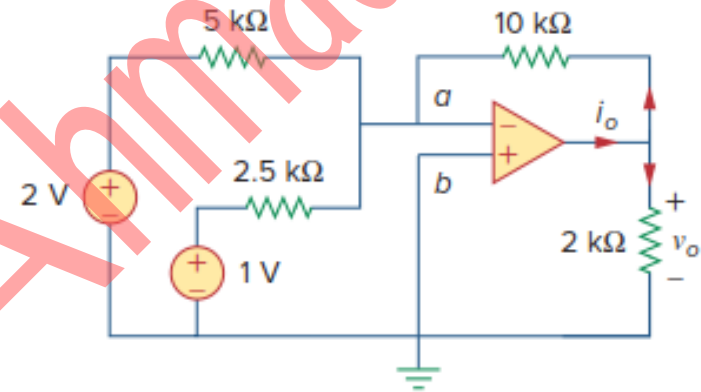
$$i_o = \frac{v_o - 0}{10} + \frac{v_o - 0}{2} = -0.8 - 4 = -4.8 \text{ mA}$$



**4. Difference amplifier** is a device that amplifies the difference between two inputs but rejects any signals common to the two inputs.

- Applying KCL to node  $a$ ,

$$\frac{v_1 - v_a}{R_1} = \frac{v_a - v_o}{R_2} \Rightarrow v_o = \left( \frac{R_2}{R_1} + 1 \right) v_a - \frac{R_2}{R_1} v_1$$

- Applying KCL to node  $b$ ,


$$\frac{v_2 - v_b}{R_3} = \frac{v_b - 0}{R_4} \Rightarrow v_b = \frac{R_4}{R_3 + R_4} v_2$$

- But  $v_a = v_b$ , thus

or

$$v_o = \left( \frac{R_2}{R_1} + 1 \right) \frac{R_4}{R_3 + R_4} v_2 - \frac{R_2}{R_1} v_1$$
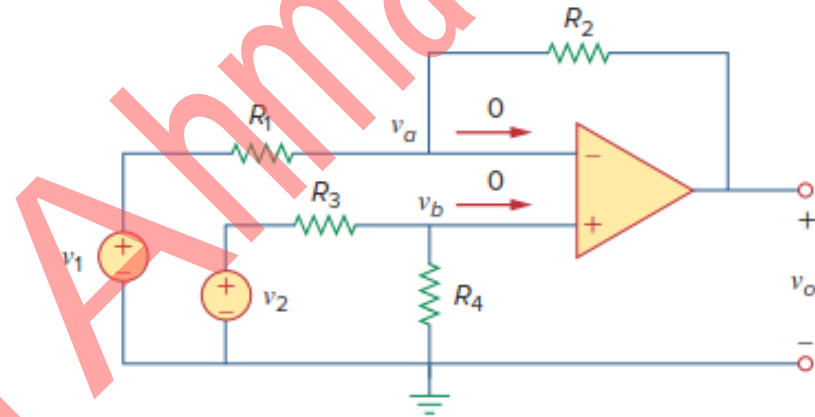
$$v_o = \frac{R_2(1 + R_1/R_2)}{R_1(1 + R_3/R_4)} v_2 - \frac{R_2}{R_1} v_1$$



The difference amplifier becomes a **subtractor**, with the output

if  $\frac{R_2}{R_1} = \frac{R_3}{R_4} = 1 \Rightarrow v_o = v_2 - v_1$

### Example 5.7.

Determine  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$  so that  $v_o = -5v_1 + 3v_2$  for the circuit shown below.

**Solution:**

- The output for this amplifier is

$$v_o = \frac{R_2(1 + R_1/R_2)}{R_1(1 + R_3/R_4)} v_2 - \frac{R_2}{R_1} v_1$$

- Comparing with

$$v_o = 3v_2 - 5v_1$$

we see that

$$\frac{R_2}{R_1} = 5 \Rightarrow R_2 = 5R_1$$


Also,

$$5 \frac{(1 + R_1/R_2)}{(1 + R_3/R_4)} = 3 \Rightarrow \frac{6}{5} \frac{1}{(1 + R_3/R_4)} = \frac{3}{5}$$

Or

$$2 = 1 + \frac{R_3}{R_4} \Rightarrow R_3 = R_4$$

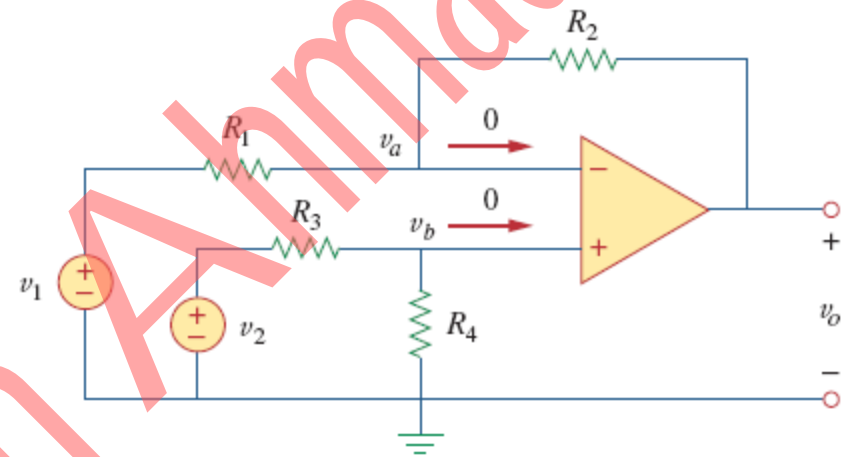If we choose  $R_1 = 10\text{k}\Omega$  and  $R_3 = 20\text{k}\Omega$ , then  $R_2 = 50\text{k}\Omega$  and  $R_4 = 20\text{k}\Omega$ .




## 5.4 Cascaded Op Amp

□ A **cascade connection** is a head-to-tail arrangement of two or more op amp circuits such that the output to one is the input of the next.

- When op amp circuits are cascaded, each circuit in the string is called a *stage*.
- The original input signal is *increased* by the *gain* of the individual stage.
- Figure displays a block diagram representation of three op amp circuits in cascade.
- Since the **output of one stage is the input to the next stage**, the **overall gain of the cascade connection is the product of the gains of the individual op amp circuits**, or

$$A = A_1 A_2 A_3$$

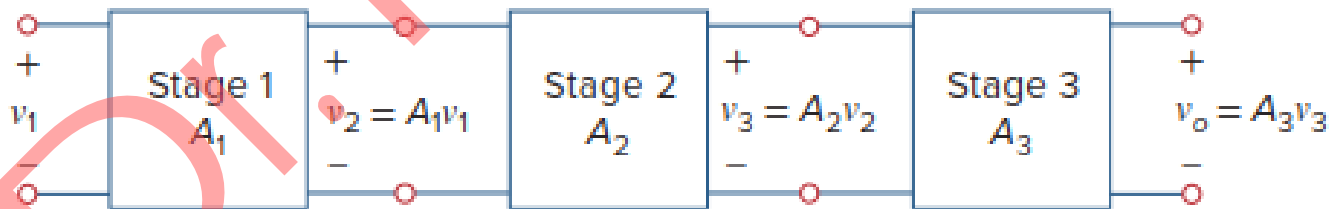

### Example 5.8.

Find  $v_o$  and  $i_o$  in the circuit shown in Fig.

#### Solution:

This circuit consists of two noninverting amplifiers cascaded.

- At the output of the first op amp,


$$v_a = \left(1 + \frac{12}{3}\right)(20) = 100 \text{ mV}$$

- At the output of the second op amp,  $v_o = \left(1 + \frac{10}{4}\right)v_a = 350 \text{ mV}$

- The required current  $i_o$  is the current through the 10-k $\Omega$  resistor:  $i_o = \frac{v_o - v_b}{10} \text{ mA}$

- But  $v_b = v_a = 100 \text{ mV}$

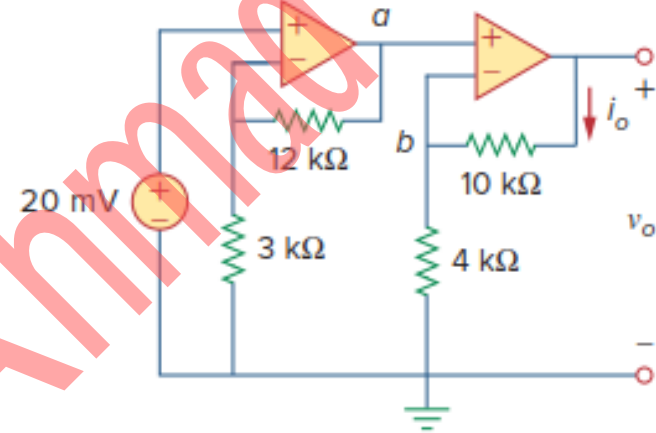- Hence,  $i_o = \frac{(350 - 100) \times 10^{-3}}{10 \times 10^3} = 25 \mu\text{A}$



## Example 5.9.

Find  $v_o$  in the op amp circuit of Fig.

### Solution:

- Let  $v_1$  output of the first op amp and  $v_2$  output of the second op amp.


- The *first stage* is an **inverting** amplifier:  $v_1 = -\frac{50}{25} v_{s1}$

- The *second state* is a **summer**:

$$v_2 = -\left(\frac{100}{50} v_{s2} + \frac{100}{100} v_1\right) = -2v_{s2} - v_1 = -2v_{s2} + 2v_{s1}$$

- The *third state* is a **noninverting** amplifier:
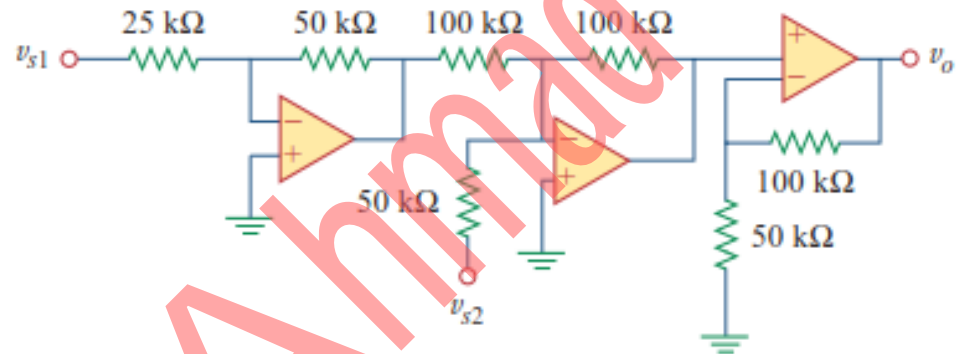
$$v_o = \left(1 + \frac{100}{50}\right) v_2 = 3v_2 = 3(-2v_{s2} + 2v_{s1}) = 6v_{s1} - 6v_{s2}$$





## 5.5 Application: Digital-to Analog Converter

- The **digital-to-analog converter (DAC)** transforms digital signals into analog form.
  - A typical example of a **four-bit DAC** is illustrated in Fig.(a).
  - The **four-bit DAC** can be realized in many ways.
  - A simple realization is the **binary weighted ladder** (سلم = درج موزون (ثنائي), Fig. (b).

$$-V_o = \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 + \frac{R_f}{R_4} V_4$$

where:  $V_1$  – MSB (most significant bit),  $V_4$  – LSB (least significant bit );

$V_1$  to  $V_4$  are either 0 or 1 V.

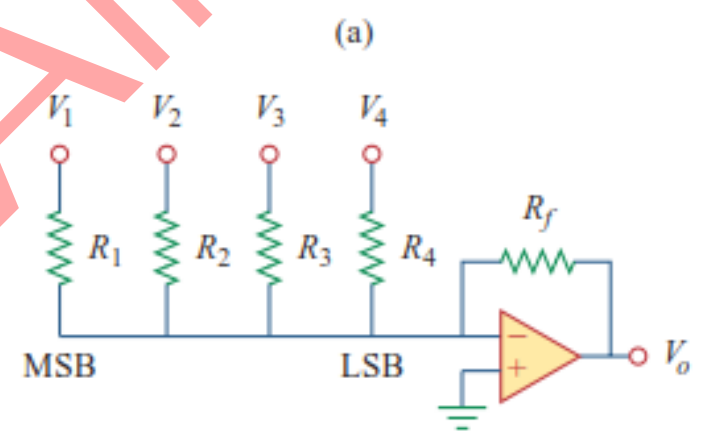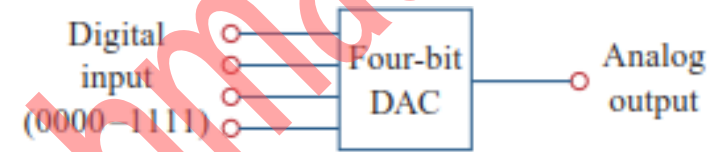

## Example 5.10.

In the op amp circuit of Fig. , let  $R_f = 10 \text{ k}\Omega$ ,  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 20 \text{ k}\Omega$ ,  $R_3 = 40 \text{ k}\Omega$ , and  $R_4 = 80 \text{ k}\Omega$ . obtain the analog output for binary inputs [0000], [0001], [0010], . . . , [1111].

### Solution:

Substituting the given values of the input and feedback resistors in following Eq.

gives

$$-V_o = \frac{R_f}{R_1}V_1 + \frac{R_f}{R_2}V_2 + \frac{R_f}{R_3}V_3 + \frac{R_f}{R_4}V_4 = V_1 + 0.5V_2 + 0.25V_3 + 0.125V_4$$

Using this equation, a digital inputs produce an analog output as following:

$$[V_1V_2V_3V_4] = [0000] \Rightarrow -V_o = 0 \text{ V}$$

$$[V_1V_2V_3V_4] = [0001] \Rightarrow -V_o = 0.125 \text{ V}$$


$$[V_1V_2V_3V_4] = [0010] \Rightarrow -V_o = 0.25 \text{ V}$$

$$[V_1V_2V_3V_4] = [0011] \Rightarrow -V_o = 0.25 + 1.125 = 0.375 \text{ V}$$

$$[V_1V_2V_3V_4] = [0100] \Rightarrow -V_o = 0.5 \text{ V}$$


⋮
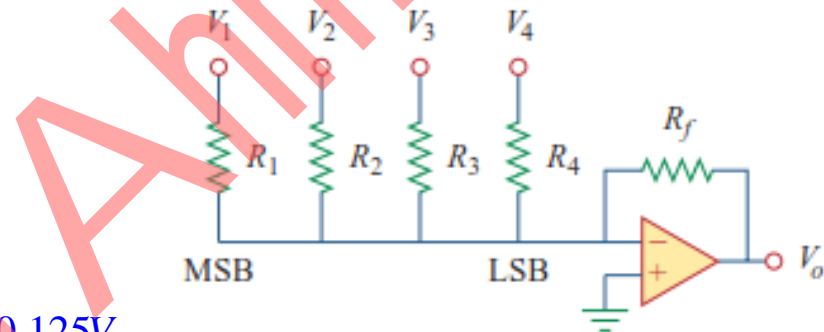
$$[V_1V_2V_3V_4] = [1111] \Rightarrow -V_o = 1 + 0.5 + 0.25 + 0.125 = 1.875 \text{ V}$$






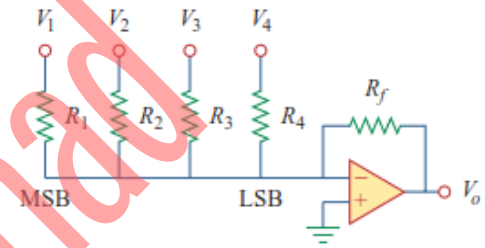Input and output values of the four-bit DAC.



Binary input [ $V_1V_2V_3V_4$ ]	Decimal value	Output $-V_o$
0000	0	0
0001	1	0.125
0010	2	0.25
0011	3	0.375
0100	4	0.5
0101	5	0.625
0110	6	0.75
0111	7	0.875
1000	8	1.0
1001	9	1.125
1010	10	1.25
1011	11	1.375
1100	12	1.5
1101	13	1.625
1110	14	1.75
1111	15	1.875

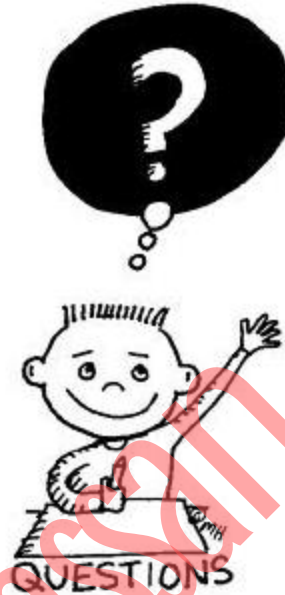

The end of chapter 5