



الجامعة السورية الخاصة  
SYRIAN PRIVATE UNIVERSITY

كلية هندسة الحاسوب والمعلوماتية  
Computer and Informatics Engineering  
Faculty

# Electric Circuits I

*Dr. Eng.*

*Hassan M. Ahmad*

[Hassan.Ahmad@spu.edu.sy](mailto:Hassan.Ahmad@spu.edu.sy),

[istamo48@mail.ru](mailto:istamo48@mail.ru)



# Chapter 6

## Capacitors and Inductors

6.1 Capacitors

6.2 Series and Parallel Capacitors

6.3 Inductors

6.4 Series and Parallel Inductors

# 6.1 Capacitors



- A capacitor is a passive element designed to **store energy** in its **electric field**.
- A **capacitor** consists of two **conducting plates** separated by an insulator (or dielectric).
- The amount of **charge** stored, represented by  $q$ :

$$q = Cv$$

- **Capacitance**  $C$  is the **ratio** of the charge  $q$  on one plate of a capacitor to the voltage difference  $v$  between the two plates, measured in **farads (F)**.
- **For example**, for the parallel plate capacitor shown in Fig., the capacitance is given by




$$C = \frac{\epsilon A}{d}$$

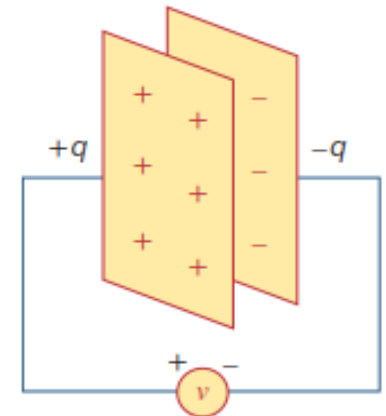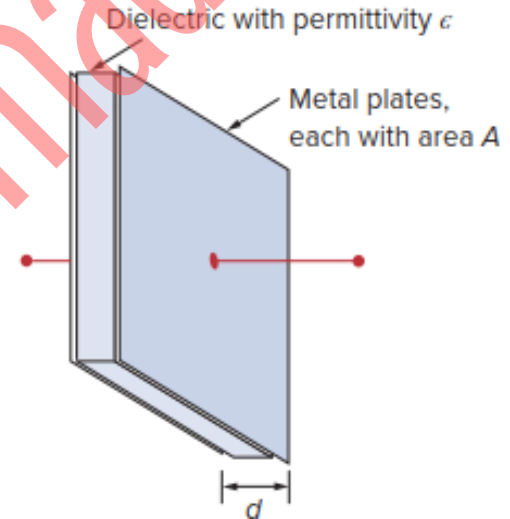where  $\epsilon$  is the permittivity (سماحية) of the dielectric material between the plates,  $A$  is the surface area (مساحة السطح) of each plate,  $d$  is the distance between the plates.


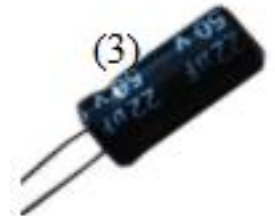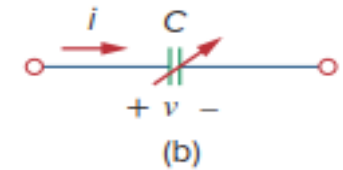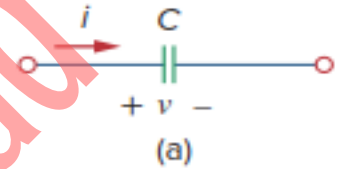
# Types of Capacitors

- Typically, capacitors have values in the picofarad (pF,  $10^{-12}$ ), nanofarad (nF,  $10^{-9}$ ), microfarad ( $\mu\text{F}$ ,  $10^{-6}$ ).
- There are two types: (a) **fixed** and (b) **variable**, with circuit symbols as shown in Fig.
- If  $v > 0$  and  $i > 0$  or if  $v < 0$  and  $i < 0$ , the capacitor is being **charged**, and if  $v \cdot i < 0$ , the capacitor is **discharging**.
- **Fixed capacitors:** (1) polyester, (2) ceramic, (3) electrolytic.
- **Variable capacitors:** (4) trimmer, (5) filmtrim.
- In addition, capacitors are used to block dc, pass ac, shift phase, store energy, start motors, and suppress noise.



# Current & Voltage of the capacitor



- If  $v > 0$  and  $i > 0$  or if  $v < 0$  and  $i < 0$ , the capacitor is being **charged**, and if  $v \cdot i < 0$ , the capacitor is **discharging**.
- The **current-voltage relationship** of the capacitor is defined as following:

$$q = Cv \text{ and } i = \frac{dq}{dt} \Rightarrow i = C \frac{dv}{dt}$$

- The **voltage-current relation** of the capacitor can be

obtained by  $v(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$  or  $v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$

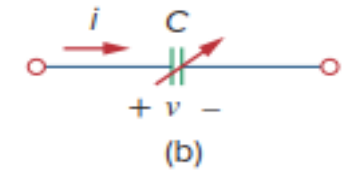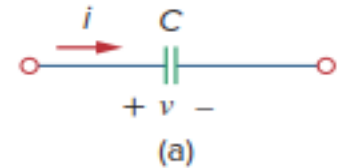- where  $v(t_0) = q(t_0)/C$  is the voltage across the capacitor at time  $t_0$ .



# Power & Energy of the capacitor

- The **instantaneous power delivered** to the capacitor is  $p = vi = Cv \frac{dv}{dt}$
- The **energy stored** in the capacitor is

$$w = \int_{-\infty}^t p(\tau) d\tau = C \int_{-\infty}^t v \frac{dv}{d\tau} d\tau = C \int_{v(-\infty)}^{v(t)} v dv = \frac{1}{2} Cv^2 \Big|_{v(-\infty)}^{v(t)}$$

- We note that  $v(-\infty) = 0$ , because the capacitor was uncharged at  $t = -\infty$ .

- Thus,  $w = \frac{1}{2} Cv^2$ . We may rewrite energy stored as  $w = \frac{q^2}{2C}$

- **Important properties of a capacitor:**

- 1) A capacitor is an **open circuit** to dc voltage (the current through the capacitor is zero). (**dc conditions**)
- 2) The voltage on a capacitor cannot change abruptly (فجأة).

## Example 6.1

- 1) Calculate the charge stored on a 3-pF capacitor with 20 V across it.
- 2) Find the energy stored in the capacitor.

### Solution

1) Since  $q = Cv$ ,  $\rightarrow q = 3 \times 10^{-12} \times 20 = 60 \text{ pC}$

$$w = \frac{1}{2} Cv^2 = \frac{1}{2} \times 3 \times 10^{-12} \times (20)^2 = 600 \text{ pJ}$$

2) The energy stored is

\*\*\*\*\*

## Example 6.2

The voltage across a 5- $\mu\text{F}$  capacitor is  $v(t) = 10 \cos 6000t$  V  
Calculate the current through it.

### Solution

$$\begin{aligned} i(t) &= C \frac{dv}{dt} = 5 \times 10^{-6} \frac{d}{dt} (10 \cos 6000t) \\ &= -5 \times 10^{-6} \times 6000 \times 10 \sin 6000t \\ &= -0.3 \sin 6000t \text{ A} \end{aligned}$$

### Example 6.3

Determine the voltage across a 2- $\mu$ F capacitor if the current through it is

$$i(t) = 6e^{-3000t} \text{ mA}$$

Assume that the initial capacitor voltage is zero.

#### Solution

$$v = \frac{1}{C} \int_0^t i d\tau + v(0) \quad \text{and} \quad v(0) = 0$$

$$v = \frac{1}{2 \times 10^{-6}} \int_0^t 6e^{-3000\tau} \times 10^{-3} d\tau = \frac{3 \times 10^3}{-3000} e^{-3000\tau} \Big|_0^t = (1 - e^{-3000t}) \text{ V}$$



## Example 6.4

Obtain the energy stored in each capacitor in Fig. (a) under dc conditions.

### Solution

Under dc conditions, we replace each capacitor with an open circuit, as shown in Fig. (b).

The current through the series combination of the 2-k $\Omega$  and 4-k $\Omega$  resistors is obtained by current division (CDR) as

$$i = \frac{3}{3+2+4} 6 \text{ mA} = 2 \text{ mA}$$



Hence, the voltages  $v_1$  and  $v_2$  across the capacitors are

$$v_1 = 2000i = 4 \text{ V}; \quad v_2 = 4000i = 8 \text{ V}$$

and the energies stored in them are

$$w_1 = \frac{1}{2} C_1 v_1^2 = \frac{1}{2} \times (2 \times 10^{-3}) (4)^2 = 16 \text{ mJ}$$
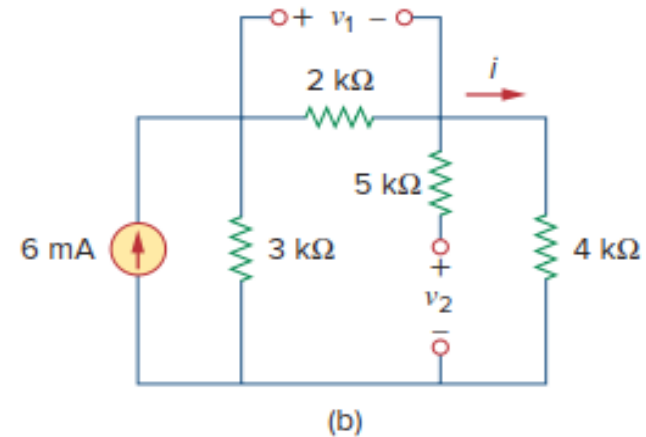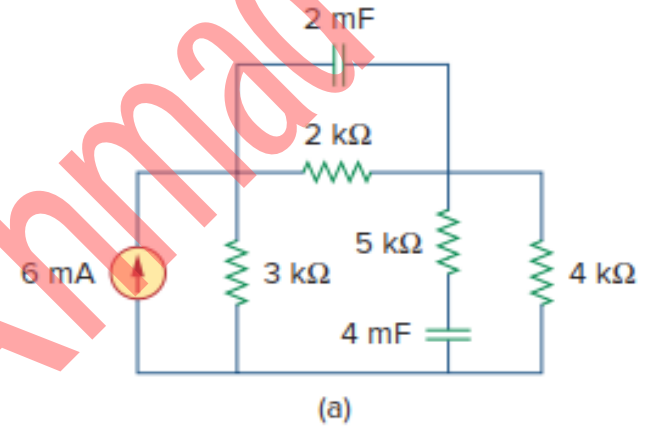
$$w_2 = \frac{1}{2} C_2 v_2^2 = \frac{1}{2} \times (4 \times 10^{-3}) (8)^2 = 128 \text{ mJ}$$



# 6.2 Series and Parallel Capacitors

## Parallel capacitors

The **equivalent capacitance** of  $N$  parallel-connected capacitors is the **sum** of the **individual capacitances**.

$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$$





## Series capacitors

The **equivalent capacitance** of series-connected capacitors is the **reciprocal of the sum of the reciprocals of the individual capacitances**.

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N}$$

For  $N = 2$  (i.e., two capacitors in series):

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

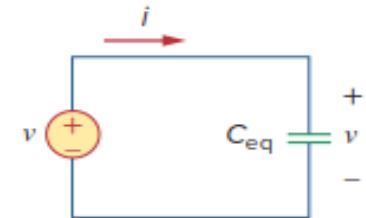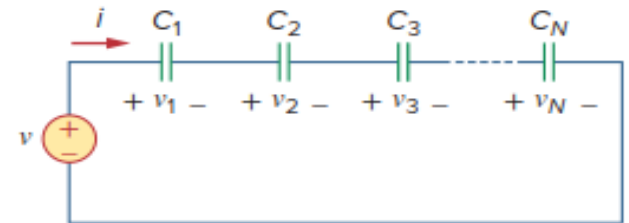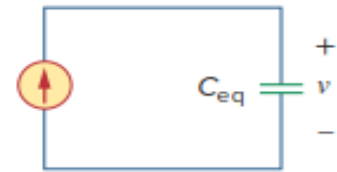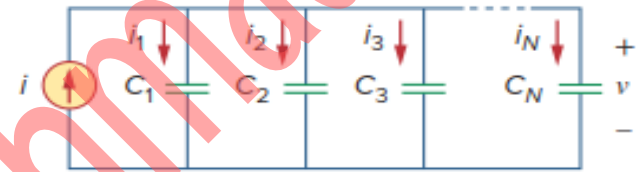

## Example 6.5

Find the equivalent capacitance seen between terminals  $a$  and  $b$  of the circuit in Fig.

### Solution


20-  $\mu\text{F}$  and 5-  $\mu\text{F}$  in series:

$$\frac{20 \times 5}{20 + 5} = 4 \mu\text{F}$$

4- $\mu\text{F}$  in parallel with the 6-  $\mu\text{F}$  and 20-  $\mu\text{F}$ :

$$4 + 6 + 20 = 30 \mu\text{F}$$

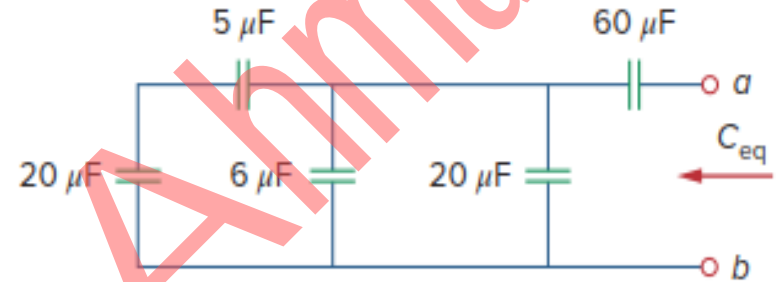30- $\mu\text{F}$  in series with 60-  $\mu\text{F}$ :  $C_{\text{eq}} = \frac{30 \times 60}{30 + 60} = 20 \mu\text{F}$



## Example 6.6

For the circuit in Fig., find the voltage across each capacitor.

### Solution

We first find the equivalent capacitance  $C_{eq}$ :

$$40\text{ mF} \parallel 20\text{ mF} \Rightarrow 40 + 20 = 60\text{ mF}$$

60-mF in series with 20-mF and 30-mF:

$$\frac{1}{C_{eq}} = \frac{1}{60} + \frac{1}{30} + \frac{1}{20} \text{ mF} \Rightarrow C_{eq} = 10\text{ mF}$$



The total charge is  $q = C_{eq} v = 10 \times 10^{-3} \times 30 = 0.3 \text{ C}$

This is the charge on the 20-mF and 30-mF capacitors, because with the 30-V source. (the charge acts like current, since  $i = dq/dt$ .)

Therefore,  $v_1 = \frac{q}{C_1} = \frac{0.3}{20 \times 10^{-3}} = 15 \text{ V}; \quad v_2 = \frac{q}{C_2} = \frac{0.3}{30 \times 10^{-3}} = 10 \text{ V}$

Using KVL:  $v_3 = 30 - v_1 - v_2 = 5 \text{ V}$

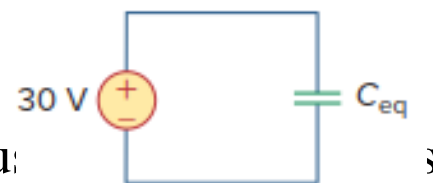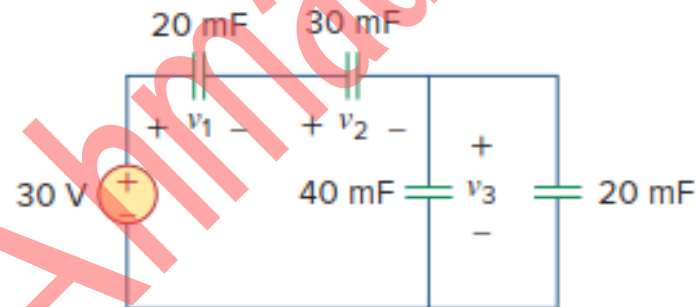
Alternatively, the 20-mF, 30-mF and 60-mF in series, so they have the same charge on it. Hence,  $v_3 = \frac{q}{60\text{ mF}} = \frac{0.3}{60 \times 10^{-3}} = 5 \text{ V}$



## 6.3 Inductors

- An **inductor** is a **passive element** designed to **store energy** in its **magnetic field**.
- An **inductor** consists of a **coil** of **conducting wire**.
- The **voltage** across the inductor is

$$v = L \frac{di}{dt}$$

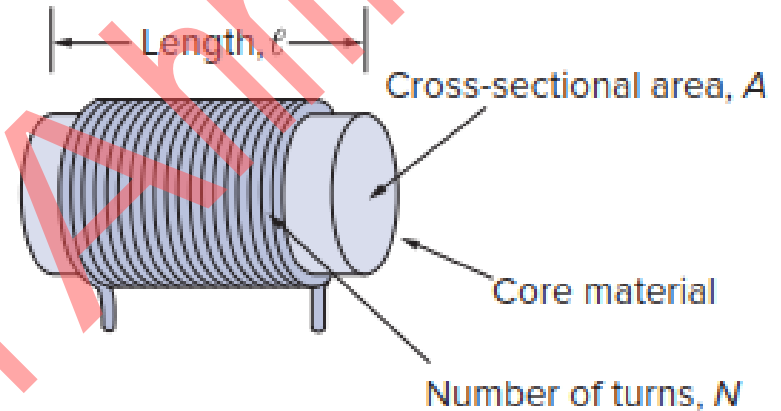

where  $L$  is the constant, called the **inductance** of the inductor.

- **Inductance** is the property whereby an inductor exhibits opposition to the change of current flowing through it, measured in **henrys** (H):

$$L = \frac{N^2 \mu A}{l}$$

where:

$N$  is the number of turns,  $l$  is the length,  $A$  is the cross-sectional area, and  $\mu$  is the permeability (النفاذية) of the core.



# Common Types of Inductors

Various **types** of inductors:

- solenoidal wound (ملفوف بشكل لولبي) inductor,
- toroidal (حلقي) inductor,
- axial lead (سلك موصل محوري) inductor.

The **circuit symbols** for inductors:

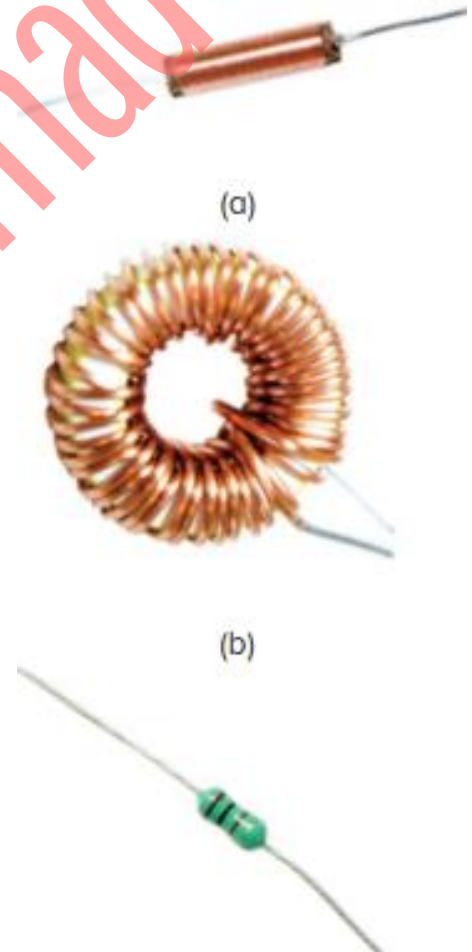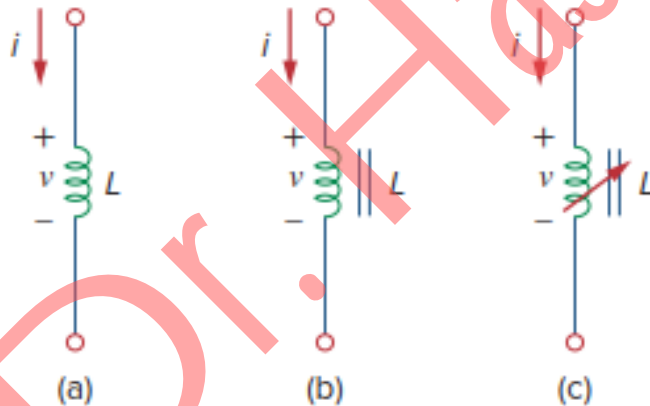(a) air-core, (b) iron-core, (c) variable iron-core.



# Current-Voltage relationship , Power & Energy of Inductor

- The **current-voltage** relationship is obtained as:  $di = \frac{1}{L} v dt \Rightarrow i = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau$

$$i = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$$

or

where  $i(t_0)$  is the total current for  $-\infty < t < t_0$  and  $i(-\infty) = 0$ .

- The **power delivered** to the inductor is

$$p = vi = \left(L \frac{di}{dt}\right) i$$

- The **energy stored**:  $w = \int_{-\infty}^t p(\tau) d\tau = L \int_{-\infty}^t \frac{di}{d\tau} i d\tau = L \int_{-\infty}^t i di = \frac{1}{2} Li^2(t) - \frac{1}{2} Li^2(-\infty)$

Since  $i(-\infty) = 0$ ,

$$w = \frac{1}{2} Li^2$$

## Important properties of an inductor:

- 1) An inductor acts like a **short circuit to dc**.
- 2) The current through an inductor **cannot change instantaneously**.

## Example 6.7

The current through a 0.1-H inductor is  $i(t) = 10te^{-5t}$  A .

Find the voltage across the inductor and the energy stored in it.

### Solution

Since  $v = L di/dt$  and  $L = 0.1$  H,

$$v = 0.1 \frac{d}{dt} (10te^{-5t}) = e^{-5t} + t(-5)e^{-5t} = e^{-5t} (1 - 5t) \text{ V}$$

The energy stored is

$$w = \frac{1}{2} Li^2 = \frac{1}{2} (0.1) \times 100t^2 e^{-10t} = 5t^2 e^{-10t} \text{ J}$$



## Example 6.8

Find the current through a 5-H inductor if the voltage across it is

$$v(t) = \begin{cases} 30t^2, & t > 0 \\ 0, & t < 0 \end{cases}$$

Also, find the energy stored at  $t = 5$  s. Assume  $i(v) > 0$ .

### Solution

Since  $L = 5$  H  $\rightarrow$  
$$i = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0) = i = \frac{1}{5} \int_0^t 30\tau^2 d\tau + 0 = 6 \times \frac{t^3}{3} = 2t^3 \text{ A}$$

The power : 
$$p = vi = 30t^2 \times 2t^3 = 60t^5 \text{ W}$$

The energy stored: 
$$w = \int p dt = \int_0^5 60t^5 dt = 60 \left. \frac{t^6}{6} \right|_0^5 = 156.25 \text{ kJ}$$

Alternatively,

$$w \Big|_0^5 = \frac{1}{2} Li^2(5) - \frac{1}{2} Li^2(0) = \frac{1}{2} (5)(2 \times 5^3)^2 - 0 = 156.25 \text{ kJ}$$

## Example 6.9

Consider the circuit in Fig.(a). Under dc conditions, find:

- $i$ ,  $v_C$ , and  $i_L$ ,
- the energy stored in the capacitor and inductor.

### Solution

- Under dc conditions, we replace the capacitor with an open circuit and the inductor with a short circuit, as in Fig. (b).



$$i = i_L = \frac{12}{1+5} = 2 \text{ A}$$

The voltage  $v_C$  is the same as the voltage across the 5- $\Omega$  resistor. Hence,

$$v_C = 5i = 10 \text{ V}$$

- The energy in the capacitor is
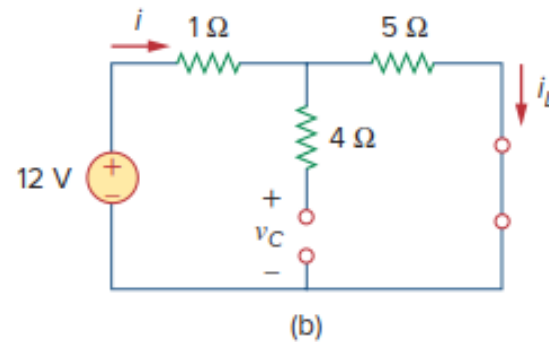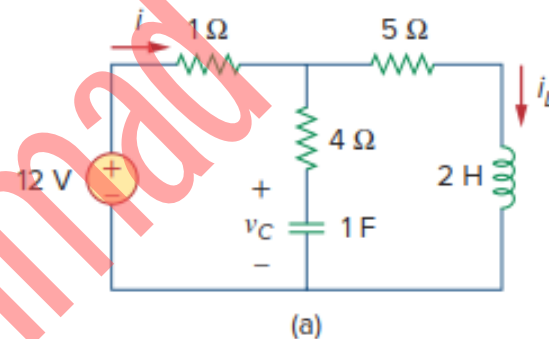
$$w_C = \frac{1}{2} C v_C^2 = \frac{1}{2} (1)(10)^2 = 50 \text{ J}; \quad w_L = \frac{1}{2} L i_L^2 = \frac{1}{2} (2)(2)^2 = 4 \text{ J}$$




# 6.4 Series and Parallel Inductors
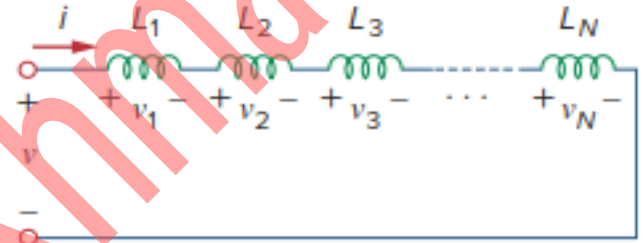
## Series inductors

The equivalent inductance of series-connected inductors is the sum of the individual inductances.




$$L_{eq} = L_1 + L_2 + L_3 + \dots + L_N$$


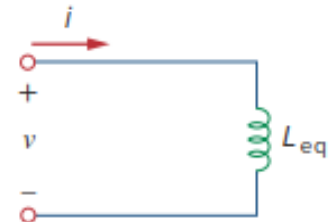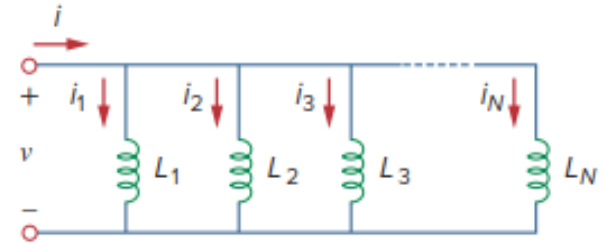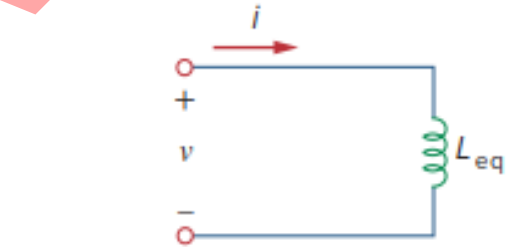
## Parallel inductors

The equivalent inductance of parallel inductors is the reciprocal of the sum of the reciprocals of the individual inductances.

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_N}$$



For two inductors in parallel ( $N = 2$ ),

$$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$

# Important characteristics of the basic elements.

Relation	Resistor ( $R$ )	Capacitor ( $C$ )	Inductor ( $L$ )
$v-i$ :	$v = iR$	$v = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$	$v = L \frac{di}{dt}$
$i-v$ :	$i = v/R$	$i = C \frac{dv}{dt}$	$i = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$
$p$ or $w$ :	$p = i^2 R = \frac{v^2}{R}$	$w = \frac{1}{2} C v^2$	$w = \frac{1}{2} L i^2$
Series:	$R_{eq} = R_1 + R_2$	$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$	$L_{eq} = L_1 + L_2$
Parallel:	$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$	$C_{eq} = C_1 + C_2$	$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$
At dc:	Same	Open circuit	Short circuit

## Example 6.10

Find the equivalent inductance of the circuit shown in Fig.

### Solution

The 10-H, 12-H, and 20-H inductors are in series;


thus,  $10 + 12 + 20 = 42\text{ H}$

This 42-H is in parallel with the 7-H :

$$\frac{7 \times 42}{7 + 42} = 6\text{ H}$$

This 6-H in series with 4-H and 8-H. Hence,
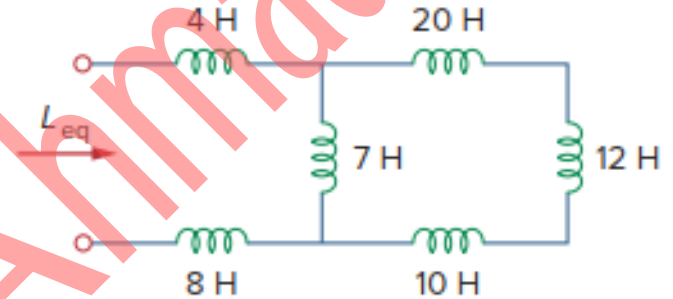
$$L_{\text{eq}} = 4 + 6 + 8 = 18\text{ H}$$



## Example 6.11

For the circuit in Fig. ,  $i(t) = 4(2 - e^{-10t})$  mA . If  $i_2(0) = -1$  mA, find:

$i_1(0)$ ;  $v(t)$ ,  $v_1(t)$ , and  $v_2(t)$ ;  $i_1(t)$  and  $i_2(t)$ .

### Solution

a) From  $i(t) = 4(2 - e^{-10t})$  mA  $\Rightarrow i(0) = 4(2 - 1) = 4$  mA

Since  $i = i_1 + i_2 \Rightarrow i_1(0) = i(0) - i_2(0) = 4 - (-1) = 5$  mA


b) The equivalent inductance is  $L_{eq} = 2 + 4 \parallel 12 = 5$  H

Thus,

$$v(t) = L_{eq} \frac{di}{dt} = 5(4)(-1)(-10)e^{-10t} = 200e^{-10t} \text{ mV}$$

$$v_1(t) = 2 \frac{di}{dt} = 2(-4)(-10)e^{-10t} = 80e^{-10t} \text{ mV}$$
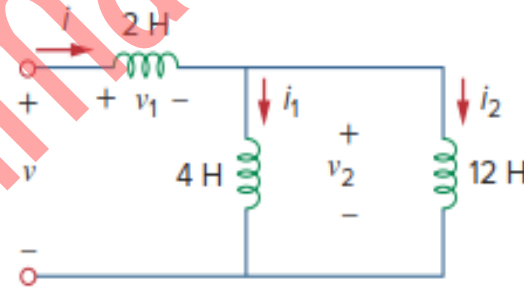
$$v = v_1 + v_2 \Rightarrow v_2(t) = v(t) - v_1(t) = 120e^{-10t} \text{ mV}$$



c) The current  $i_1$  is obtained as

$$i_1(t) = \frac{1}{4} \int_0^t v_2 dt + i_1(0) = \frac{120}{4} \int_0^t e^{-10t} dt + 5 \text{ mA}$$

$$= 30 \times \left( -\frac{1}{10} \right) e^{-10t} \Big|_0^t + 5 \text{ mA} = -3e^{-10t} + 3 + 5 = 8 - 3e^{-10t} \text{ mA}$$

Similarly,

$$i_2(t) = \frac{1}{12} \int_0^t v_2 dt + i_2(0) = \frac{120}{12} \int_0^t e^{-10t} dt - 1 \text{ mA}$$


$$= 10 \times \left( -\frac{1}{10} \right) e^{-10t} \Big|_0^t - 1 \text{ mA} = -e^{-10t} + 1 - 1 = -e^{-10t} \text{ mA}$$

Note that

$$i_1(t) + i_2(t) = i(t)$$

$$(8 - 3e^{-10t} \text{ mA}) + (-e^{-10t} \text{ mA}) = 4(2 - e^{-10t}) \text{ mA}$$

$$i(t) = 4(2 - e^{-10t}) \text{ mA}$$

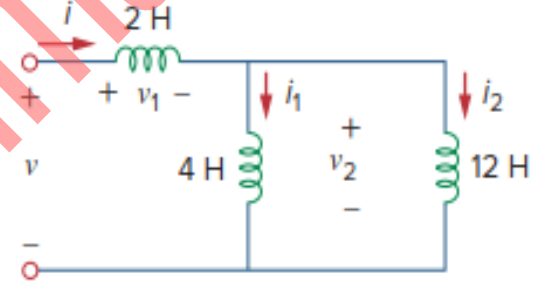



The end of chapter 6