

Logic Circuits

Dr. Eng.

Hassan M. Ahmad

Hassan.Ahmad@spu.edu.sy, istamo48@mail.ru

Chapter_ 4

Boolean Algebra

(الجبر البولياني)

Lecture _06

Boolean Operations & Laws

(القوانين والعمليات البوليانية)


6-1. Boolean Operations and Expressions (التعابير والعمليات البوليانية)

Variable, **complement** and **literal** are terms used in Boolean algebra.

- A **variable** (عنصر متغير) is a symbol used to represent an **action**, a condition, or data. A **single variable** can only have a value of **1** or **0**.
- The **complement** (متمم) represents the **inverse** of a variable and is indicated with an **overbar** (خط فوق الرمز).
Thus, the complement of **A** is \overline{A} .
- A **literal** (بيانات حرفية) is a variable or its complement.

Boolean Addition operation

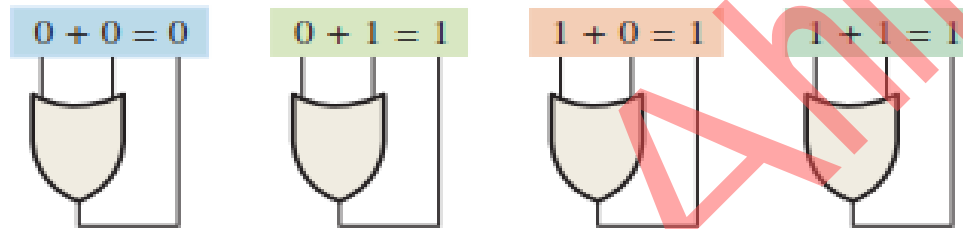□ Addition is equivalent to the **OR** operation. The basic rules are shown in Fig.




- In Boolean algebra, a **sum term** is a sum of literals.
- In logic circuits, a **sum term** is produced by an **OR** operation with **no AND** operations involved. Some examples of sum terms are

$$A + B; A + \bar{B}; A + B + \bar{C}; \bar{A} + B + C + \bar{D}$$

Boolean Multiplication operation

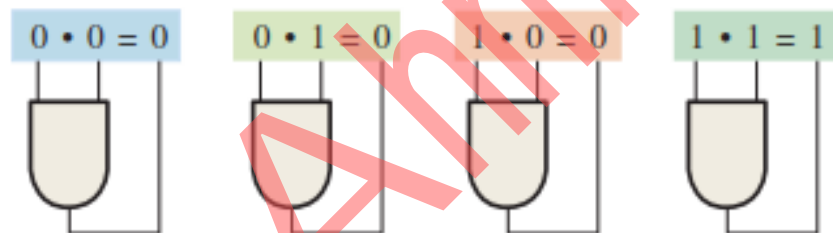- In Boolean algebra, **multiplication** is equivalent to the **AND** operation. The **basic rules** are shown in Fig.



- In Boolean algebra, a **product term** is the product of **literals**.
- In logic circuits, a **product term** is produced by an **AND** operation with no **OR operations** involved.
- Some examples of product terms are: AB ; $A\bar{B}$; ABC ; $A\bar{B}C\bar{D}$

Example 6-1

Determine the values of A , B , C and D that make the sum term of the expression $A + \bar{B} + C + \bar{D} = 0$?

Solution

For the sum term to be 0, **each literal** must = 0;
therefore $A = 0$, $B = 1$ (so that $\bar{B} = 0$), $C = 0$, and $D = 1$ (so that $\bar{D} = 0$).

$$A + \bar{B} + C + \bar{D} = 0 + \bar{1} + 0 + \bar{1} = 0 + 0 + 0 + 0 = 0$$

Example 6-2

Determine the values of A , B , C and D that make the product term of the expression $A\bar{B}C\bar{D} = 1$?

Solution

For the sum term to be 1, each literal must = 1;
therefore $A = 1$, $B = 0$ (so that $\bar{B} = 1$), $C = 1$, and $D = 0$ (so that $\bar{D} = 1$).


$$A\bar{B}C\bar{D} = 1 \cdot \bar{0} \cdot 1 \cdot \bar{0} = 1 \cdot 1 \cdot 1 \cdot 1 = 1$$

6-2. Laws of Boolean Algebra (قوانين الجبر البولياني)


Commutative Laws (قوانين التبادل)

❑ The commutative laws are applied to addition and multiplication.

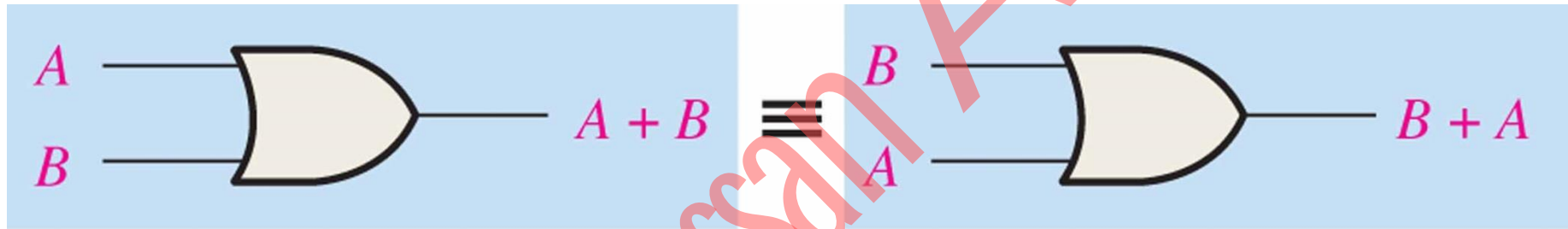➤ For **addition**, the commutative law states $A + B = B + A$



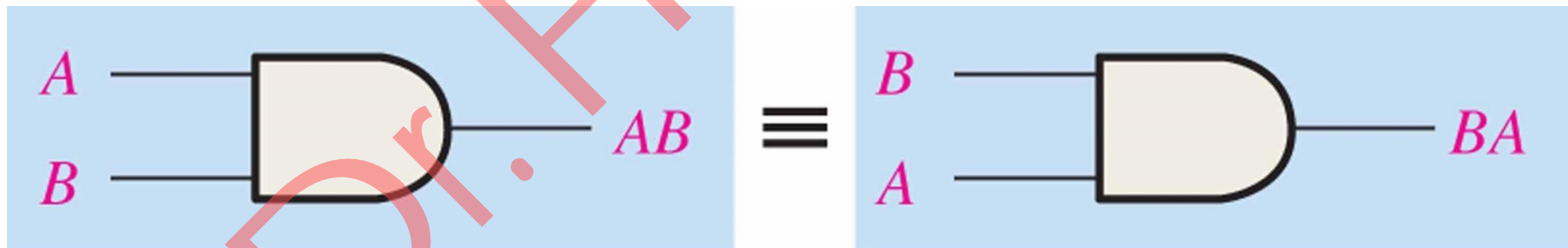➤ For **multiplication**, the commutative law states $A \cdot B = B \cdot A$




Associative Laws (قوانين التجميع)

❑ The **associative laws** are also applied to **addition** and **multiplication**.


➤ For **addition**, the commutative law states

$$A + (B + C) = (A + B) + C$$

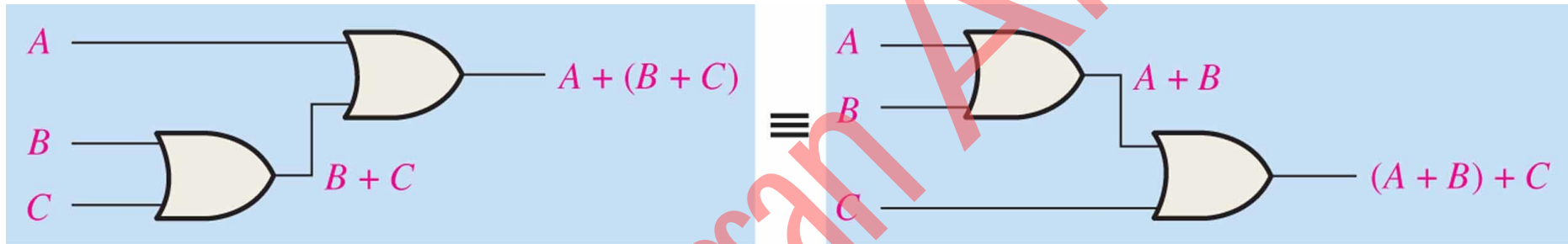

➤ For **multiplication**, the commutative law states
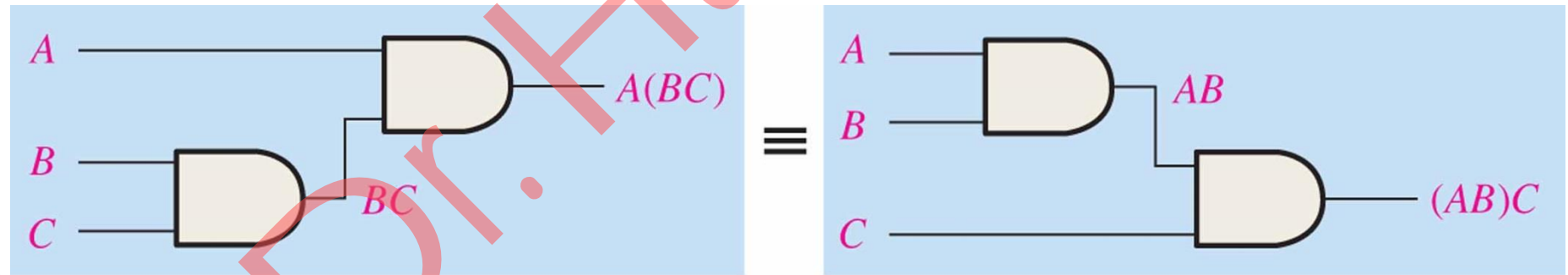
$$A \cdot (B \cdot C) = (A \cdot B) \cdot C$$




Distributive Law (قانون التوزيع)


❑ The **distributive law** is the **factoring law** (قانون العوامل).

➤ A common variable can be **factored** (محللة إلى عوامل) from an expression just as in ordinary algebra. That is
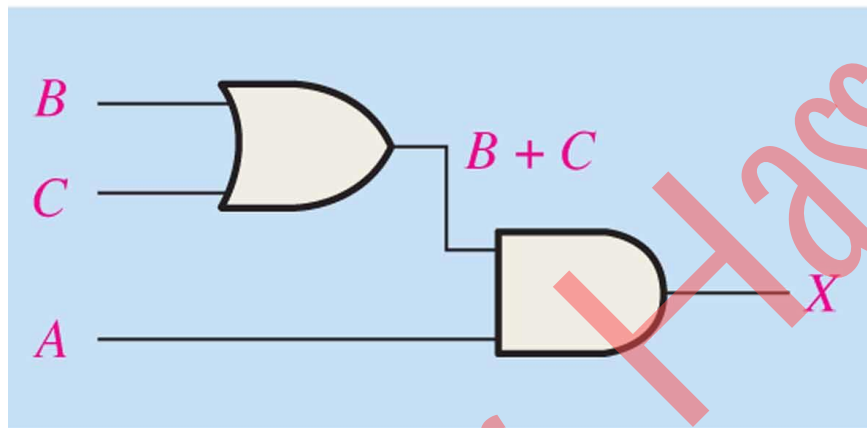
$$A \cdot (B + C) = A \cdot B + A \cdot C$$



$$X = A(B + C)$$

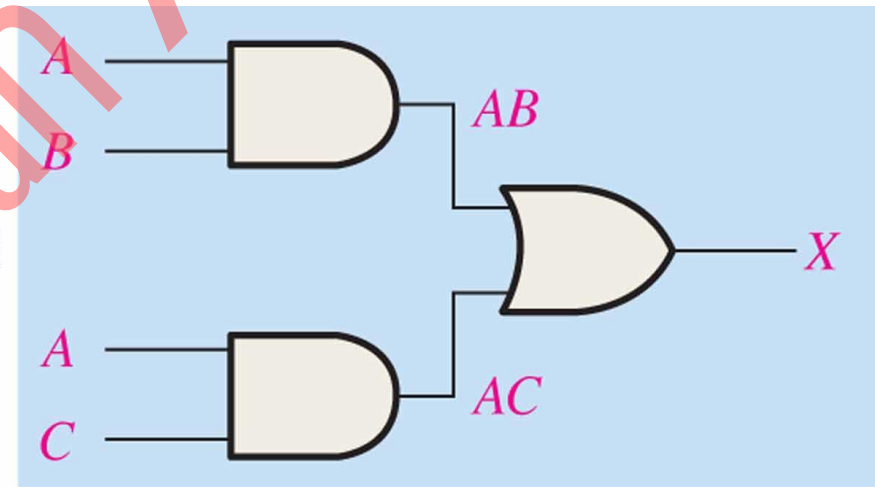

$$X = AB + AC$$


6-3. Rules of Boolean Algebra (قواعد الجبر البولياني)

Rule_1: $A + 0 = A$



$$X = A + 0 = A$$

Rule_2: $A + 1 = 1$

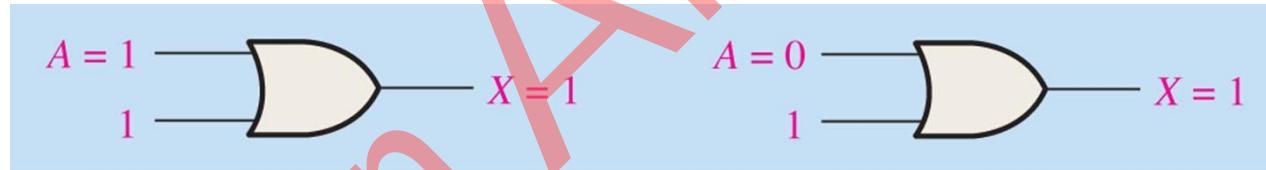

$$X = A + 1 = 1$$

Rule_3: $A \cdot 0 = 0$



$$X = A \cdot 0 = 0$$

Rule_4: $A \cdot 1 = A$



$$X = A \cdot 1 = A$$

Rules of Boolean Algebra

Rule_5: $A + A = A$



$$X = A + A = A$$

Rule_6: $A + \bar{A} = 1$



$$X = A + \bar{A} = 1$$

Rule_7: $A \cdot A = A$



$$X = A \cdot A = A$$

Rule_8: $A \cdot \bar{A} = 0$



$$X = A \cdot \bar{A} = 0$$

Rule_9: $\bar{\bar{A}} = A$



$$\bar{\bar{A}} = A$$

Rules of Boolean Algebra

Rule_10: $A + AB = A$

This rule can be proved by applying the distributed law, rule_2, and rule_4 as follows:

$$A + AB = A(1 + B) \quad \text{Distributive law}$$

$$= A \cdot 1 \quad \text{Rul_2: } (1 + B) = 1$$


$$= A \quad \text{Rul_4: } A \cdot 1 = A$$

The truth table and resulting logic circuit simplification is

Rule 10: $A + AB = A$

A	B	AB	A + AB
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

↑ equal ↑

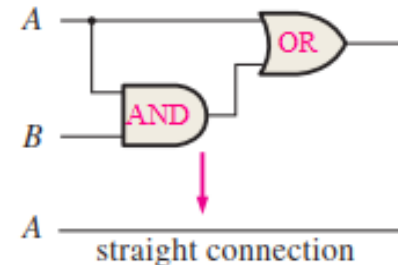

Rules of Boolean Algebra

Rule_11: $A + \bar{A}B = A + B$

This rule can be proved as follows:

$$A + \bar{A}B = (A + AB) + \bar{A}B$$

$$= (AA + AB) + \bar{A}B$$

$$= AA + AB + A\bar{A} + \bar{A}B$$

$$= (A + \bar{A})(A + B)$$

$$= 1 \cdot (A + B)$$

$$= A + B$$

Rul_10: $A = A + AB$

Rul_7: $A = AA$

Rul_8: adding $A\bar{A} = 0$

Distributed law

Rul_6: $A + \bar{A} = 1$

The truth table and resulting logic circuit simplification is

Rule 11: $A + \bar{A}B = A + B$

A	B	$\bar{A}B$	$A + \bar{A}B$	$A + B$
0	0	0	0	0
0	1	1	1	1
1	0	0	1	1
1	1	0	1	1

↑ equal ↑

Rules of Boolean Algebra

Rule_12: $(A + B)(A + C) = A + BC$

This rule can be proved as follows:

$$\begin{aligned}
 (A + B)(A + C) &= AA + AC + AB + BC && \text{Distributed law} \\
 &= A + AC + AB + BC && \text{Rul_7: } A = AA \\
 &= A(1 + C) + AB + BC && \text{Distributed law} \\
 &= A \cdot 1 + AB + BC && \text{Rul_2: } 1 + C = 1 \\
 &= A(1 + B) + BC && \text{Distributed law} \\
 &= A \cdot 1 + BC && \text{Rul_2: } 1 + B = 1 \\
 &= A + BC && \text{Rul_4: } A \cdot 1 = A
 \end{aligned}$$

The truth table and resulting logic circuit simplification is

Rule 12: $(A + B)(A + C) = A + BC$.

A	B	C	A + B	A + C	(A + B)(A + C)	BC	A + BC
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

↑ equal ↑

Basic rules of Boolean algebra.

1. $A + 0 = A$

2. $A + 1 = 1$

3. $A \cdot 0 = 0$

4. $A \cdot 1 = A$

5. $A + A = A$

6. $A + \bar{A} = 1$

7. $A \cdot A = A$

8. $A \cdot \bar{A} = 0$

9. $\bar{\bar{A}} = A$

10. $A + \bar{A}B = A$

11. $A + \bar{A}B = A + B$

12. $(A + B)(A + C) = A + BC$


A , B , or C can represent a single variable or a combination of variables.

6-4. DeMorgan's Theorems

DeMorgan's first Theorem

DeMorgan's first theorem is stated as follows:

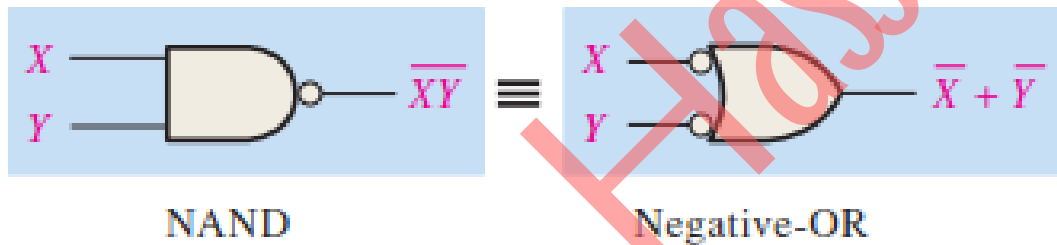- The complement of a product of variables is equal to the sum of the complements of the variables.
- The formula for expressing this theorem for two variables is $\overline{XY} = \overline{X} + \overline{Y}$




Inputs		Output	
X	Y	\overline{XY}	$\overline{X} + \overline{Y}$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

DeMorgan's second Theorem

DeMorgan's second theorem is stated as follows:

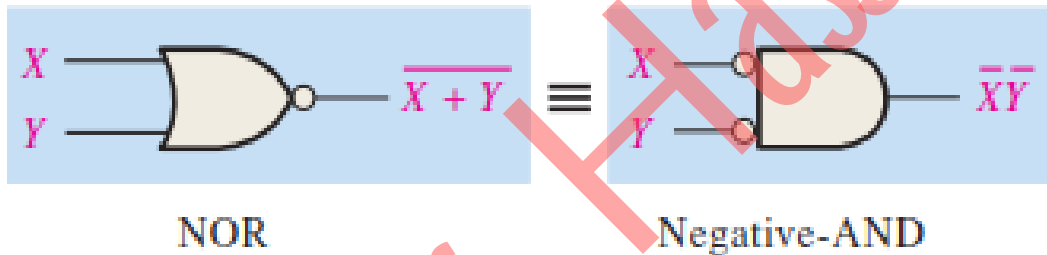- The complement of a sum of variables is equal to the product of the complements of the variables.
- The formula for expressing this theorem for two variables is $\overline{X + Y} = \overline{X} \cdot \overline{Y}$



Inputs		Output	
X	Y	$\overline{X + Y}$	$\overline{X} \overline{Y}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

Example 6-3 Applying DeMorgan's theorems to the expressions

$$\overline{XYZ}; \quad \overline{X + Y + Z}$$

$$\overline{WXYZ}; \quad \overline{W + X + Y + Z}$$

Solution

$$\overline{XYZ} = \overline{X} + \overline{Y} + \overline{Z}$$

$$\overline{WXYZ} = \overline{W} + \overline{X} + \overline{Y} + \overline{Z}$$

$$\overline{X + Y + Z} = \overline{X} \overline{Y} \overline{Z}$$

$$\overline{W + X + Y + Z} = \overline{W} \overline{X} \overline{Y} \overline{Z}$$

Applying DeMorgan's Theorems

The following **procedure** illustrates the application of DeMorgan's theorems and Boolean algebra to the specific expression

$$\overline{\overline{A + \overline{BC} + D(\overline{E + \overline{F}})}}$$

Step 1: Identify the terms to which you can apply DeMorgan's theorems, and think of each term as a single variable. Let $\overline{A + \overline{BC}} = X$ and $\overline{D(\overline{E + \overline{F}})} = Y$.

Step 2: Since $\overline{X + Y} = \overline{X}\overline{Y}$,

$$\overline{\overline{A + \overline{BC}} + \overline{D(\overline{E + \overline{F}})}} = \overline{\overline{A + \overline{BC}}} \overline{\overline{D(\overline{E + \overline{F}})}}$$

Step 3: Use rule 9 ($\overline{\overline{A}} = A$) to cancel the double bars over the left term (this is not part of DeMorgan's theorem).

$$\overline{\overline{A + \overline{BC}}} \overline{\overline{D(\overline{E + \overline{F}})}} = (A + \overline{BC}) \overline{\overline{D(\overline{E + \overline{F}})}}$$

Step 4: Apply DeMorgan's theorem to the second term.

$$(A + \overline{BC}) \overline{\overline{D(\overline{E + \overline{F}})}} = (A + \overline{BC}) (\overline{\overline{D}} + \overline{\overline{E + \overline{F}}})$$

Step 5: Use rule 9 ($\overline{\overline{A}} = A$) to cancel the double bars over the $E + \overline{F}$ part of the term.

$$(A + \overline{BC}) (\overline{\overline{D}} + \overline{\overline{E + \overline{F}}}) = (A + \overline{BC}) (\overline{\overline{D}} + E + \overline{F})$$

Example 6-4

Apply DeMorgan's theorems to each of the following expressions:

(a) $\overline{(A + B + C)D}$

(b) $\overline{ABC + DEF}$

(c) $\overline{A\bar{B} + \bar{C}D + EF}$

Solution

- (a) Let $A + B + C = X$ and $D = Y$. The expression $\overline{(A + B + C)D}$ is of the form $\overline{XY} = \bar{X} + \bar{Y}$ and can be rewritten as

$$\overline{(A + B + C)D} = \overline{A + B + C} + \bar{D}$$

Next, apply DeMorgan's theorem to the term $\overline{A + B + C}$.

$$\overline{A + B + C} + \bar{D} = \bar{A}\bar{B}\bar{C} + \bar{D}$$

- (b) Let $ABC = X$ and $DEF = Y$. The expression $\overline{ABC + DEF}$ is of the form $\overline{X + Y} = \bar{X}\bar{Y}$ and can be rewritten as

$$\overline{ABC + DEF} = (\overline{ABC})(\overline{DEF})$$

Next, apply DeMorgan's theorem to each of the terms \overline{ABC} and \overline{DEF} .

$$(\overline{ABC})(\overline{DEF}) = (\bar{A} + \bar{B} + \bar{C})(\bar{D} + \bar{E} + \bar{F})$$

- (c) Let $A\bar{B} = X$, $\bar{C}D = Y$, and $EF = Z$. The expression $\overline{A\bar{B} + \bar{C}D + EF}$ is of the form $\overline{X + Y + Z} = \bar{X}\bar{Y}\bar{Z}$ and can be rewritten as


$$\overline{A\bar{B} + \bar{C}D + EF} = (\overline{A\bar{B}})(\overline{\bar{C}D})(\overline{EF})$$

Next, apply DeMorgan's theorem to each of the terms $\overline{A\bar{B}}$, $\overline{\bar{C}D}$, and \overline{EF} .

$$(\overline{A\bar{B}})(\overline{\bar{C}D})(\overline{EF}) = (\bar{A} + B)(C + \bar{D})(\bar{E} + \bar{F})$$

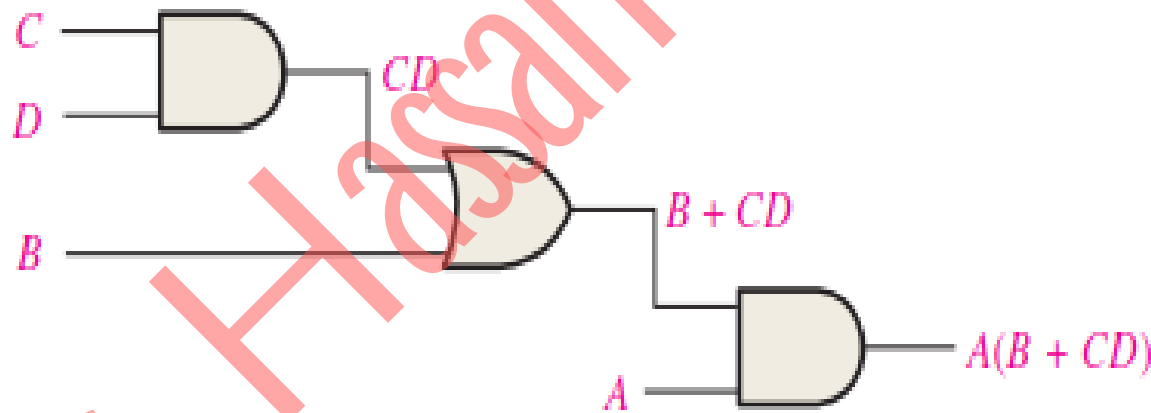6-5. Boolean Analysis of Logic Circuits


- Combinational (التوافقية) logic circuits can be analyzed by writing the expression for each gate and combining the expressions according to the rules for Boolean algebra.
- For the example, circuit in Fig.



Therefore, the expression for this AND gate is $A(B + CD)$, which is the final output expression for the entire circuit.

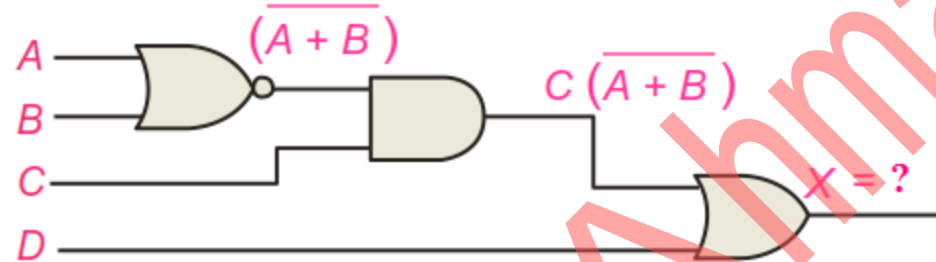Example 6-5

Given the logic circuit. Apply Boolean algebra to derive the expression for X .



Solution

Write the expression for each gate:


- 1) For NOR (NOT-OR) gate with A and B inputs we have: $\overline{A+B}$
- 2) For AND gate with $\overline{A+B}$ and C inputs we have: $C\overline{A+B}$
- 3) For OR gate with $C\overline{A+B}$ and D inputs we have: $C\overline{A+B} + D$

Therefore, $X = C\overline{A+B} + D$

Applying DeMorgan's theorems and the distribution law:

$$\overline{A+B} = \overline{A} \cdot \overline{B} \Rightarrow X = C(\overline{A} \cdot \overline{B}) + D = \overline{A} \cdot \overline{B} \cdot C + D$$

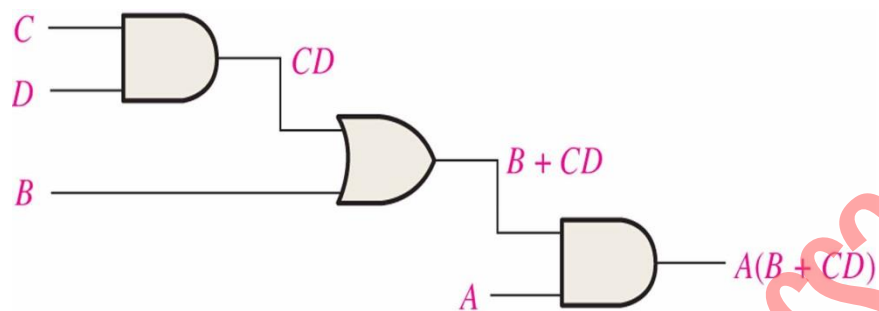Constructing a Truth Table for a Logic Circuit



Inputs				Output
A	B	C	D	$A(B + CD)$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

6-6. Logic Simplification Using Boolean Algebra (التبسيط المنطقي)

A **simplified Boolean expression** uses the **fewest gates possible** to implement a given expression.

Example 6-6 Using Boolean algebra techniques, simplify this expression:

$$AB + A(B + C) + B(B + C)$$

Solution

Step 1: Apply the distributive law to the second and third terms in the expression, as follows:

$$AB + AB + AC + BB + BC$$

Step 2: Apply rule 7 ($BB = B$) to the fourth term.

$$AB + AB + AC + B + BC$$

Step 3: Apply rule 5 ($AB + AB = AB$) to the first two terms.

$$AB + AC + B + BC$$

Step 4: Apply rule 10 ($B + BC = B$) to the last two terms.

$$AB + AC + B$$

Step 5: Apply rule 10 ($AB + B = B$) to the first and third terms.

$$B + AC$$

Basic rules of Boolean algebra.

1. $A + 0 = A$

7. $A \cdot A = A$

2. $A + 1 = 1$

8. $A \cdot \bar{A} = 0$

3. $A \cdot 0 = 0$

9. $\bar{\bar{A}} = A$

4. $A \cdot 1 = A$

10. $A + AB = A$

5. $A + A = A$

11. $A + \bar{A}B = A + B$


6. $A + \bar{A} = 1$

12. $(A + B)(A + C) = A + BC$

A , B , or C can represent a single variable or a combination of variables.

$$AB + A(B + C) + B(B + C) \equiv B + AC$$

The simplified circuit

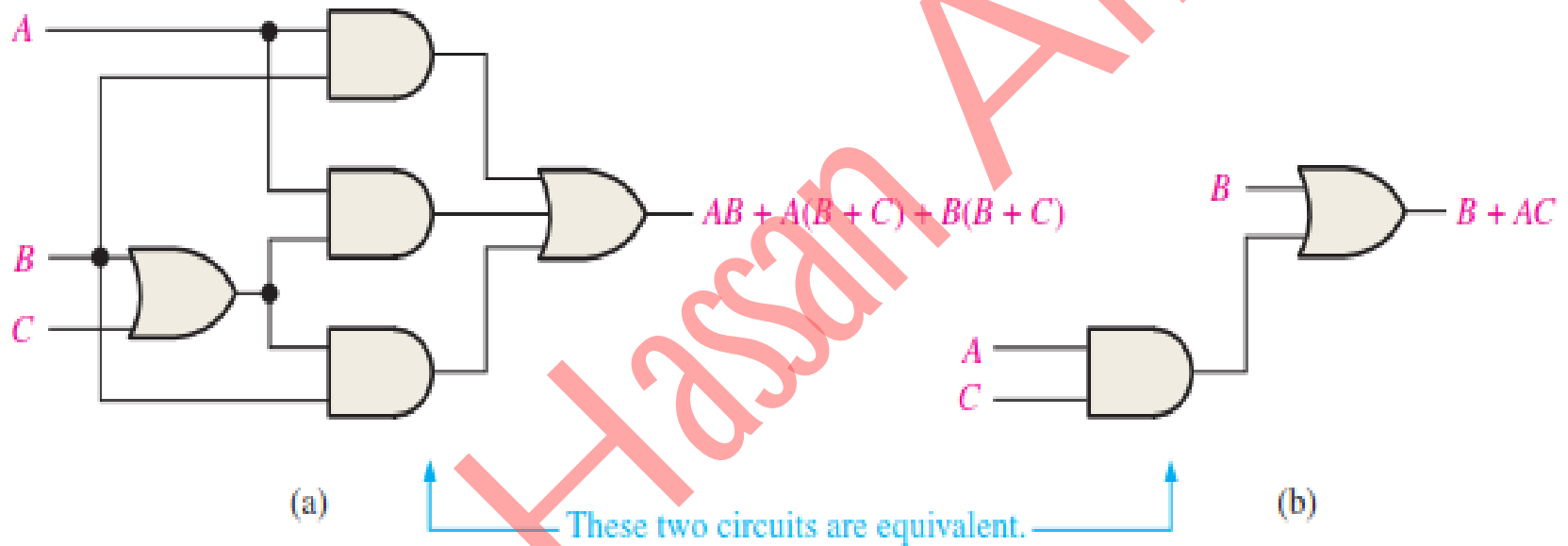

Example 6-7

Solution

Simplify the following Boolean expression:

$$\overline{A}BC + A\overline{B}\overline{C} + \overline{A}\overline{B}\overline{C} + A\overline{B}C + ABC$$

Step 1: Factor BC out of the first and last terms.

$$BC(\overline{A} + A) + A\overline{B}\overline{C} + \overline{A}\overline{B}\overline{C} + A\overline{B}C$$

Step 2: Apply rule 6 ($\overline{A} + A = 1$) to the term in parentheses, and factor $A\overline{B}$ from the second and last terms.

$$BC \cdot 1 + A\overline{B}(\overline{C} + C) + \overline{A}\overline{B}\overline{C}$$

Step 3: Apply rule 4 (drop the 1) to the first term and rule 6 ($\overline{C} + C = 1$) to the term in parentheses.

$$BC + A\overline{B} \cdot 1 + \overline{A}\overline{B}\overline{C}$$

Step 4: Apply rule 4 (drop the 1) to the second term.

$$BC + A\overline{B} + \overline{A}\overline{B}\overline{C}$$

Step 5: Factor \overline{B} from the second and third terms.

$$BC + \overline{B}(A + \overline{A}\overline{C})$$

Step 6: Apply rule 11 ($A + \overline{A}\overline{C} = A + \overline{C}$) to the term in parentheses.

$$BC + \overline{B}(A + \overline{C})$$

Step 7: Use the distributive and commutative laws to get the following expression:

$$BC + A\overline{B} + \overline{B}\overline{C}$$

6-6. Standard Forms of Boolean Expressions

(الصيغ النموذجية/المعيارية للتعبير البوليانية)


The Sum-of-Products (SOP) Form (جمع الجداءات)

- When two or more product terms are summed by Boolean addition, the resulting expression is a **sum-of-products (SOP)**.

Examples: $AB + ABC$; $ABC + CDE + \overline{BCD}$; $\overline{AB} + \overline{ABC} + AC$


AND/OR Implementation of an SOP Expression:

$$AB + BCD + AC$$

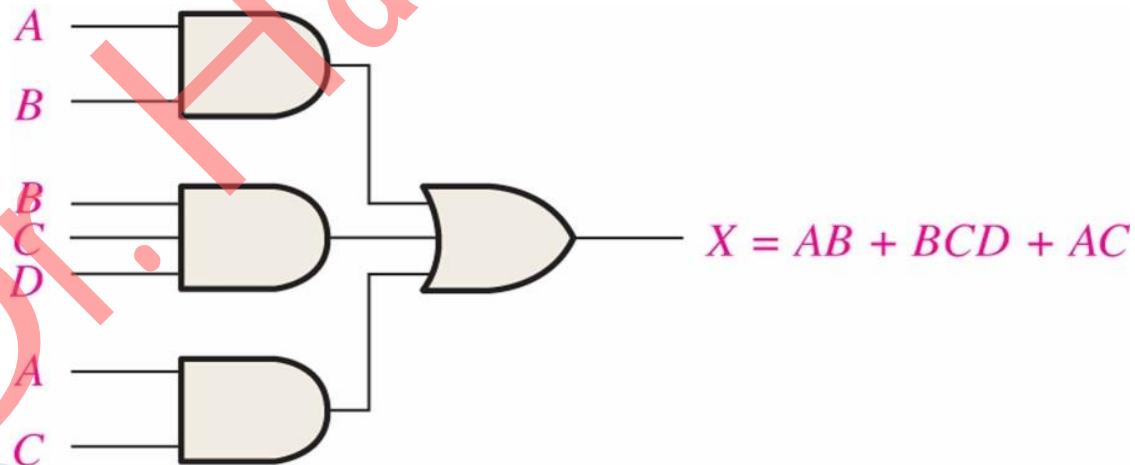


NAND/NAND Implementation of an SOP Expression:

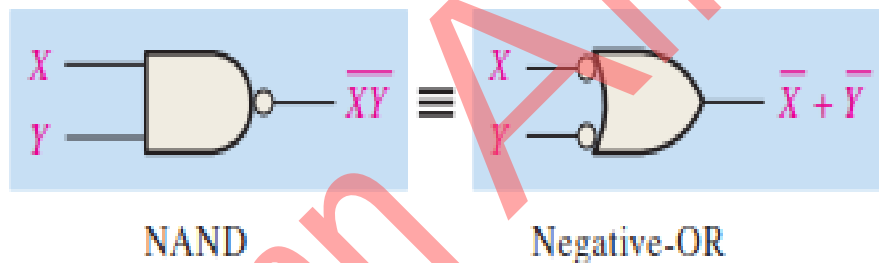- By using only **NAND** gates, an **AND/OR** function can be accomplished (= يُنجز (يتحقق), as illustrated in Figure.
- The **first level** of **NAND** gates feed into (يغذي) a NAND gate that acts as a **negative-OR** gate.



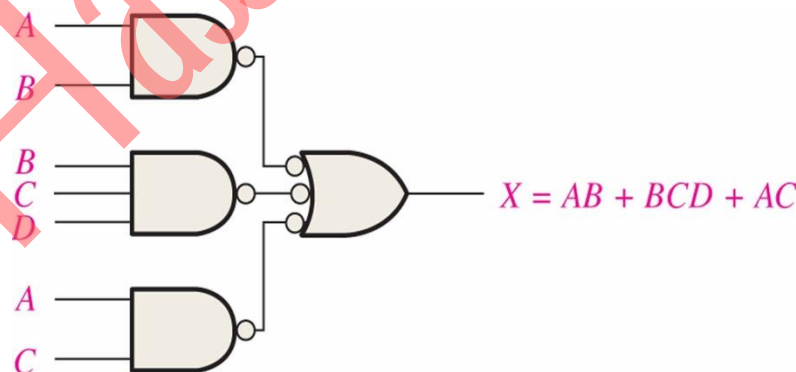- The NAND and negative-OR inversions cancel and the result is effectively an **AND/OR** circuit.



Conversion of General Expression to SOP Form

□ Any logic expression can be changed into SOP form by applying Boolean algebra techniques.

For example, the expression $A(B+CD)$ can be converted to SOP form by applying the distributive law: $A(B+CD) = AB + ACD$

Example 6-8

Solution

Convert each of the following Boolean expressions to SOP form:

$$AB + B(CD + EF); \quad (A + B)(B + C + D); \quad \overline{\overline{A + B} + C}$$

$$AB + B(CD + EF) = AB + BCD + BEF;$$

$$(A + B)(B + C + D) = AB + AC + AD + BB + BC + BD;$$

$$\overline{\overline{A + B} + C} = \overline{\overline{A + B}} \overline{C} = (A + B) \overline{C} = A \overline{C} + B \overline{C}$$

SOP Standard form

- ❑ In **SOP standard form**, every variable in the domain must appear in each term.

Another state is called **nonstandard form**.

For example:

Standard form: $\overline{A}\overline{B}CD + \overline{A}\overline{B}C\overline{D} + A\overline{B}C\overline{D}$

Nonstandard form: $\overline{A}\overline{B}C + \overline{A}\overline{B}\overline{D} + A\overline{B}C\overline{D}$

Converting Product Terms to Standard SOP

- A **nonstandard SOP** expression can be converted into standard form using Boolean algebra rule 6 ($A + \overline{A} = 1$).

Step 1: Multiply each nonstandard product term by a term made up of the **sum** of a **missing variable** (المتغيرة الضائعة) and its **complement**.

Step 2: Repeat Step 1 until all resulting product terms contain all variables in the domain in either complemented or uncomplemented form.

Example 6-9 Convert the following Boolean expression into standard SOP form:

$$\overline{A}\overline{B}C + \overline{A}\overline{B} + AB\overline{C}D$$

Solution

The **first** term, $\overline{A}\overline{B}C$, is missing variable D or \overline{D} , so multiply the first term by $D + \overline{D}$ as follows:

$$\overline{A}\overline{B}C = \overline{A}\overline{B}C(D + \overline{D}) = \overline{A}\overline{B}CD + \overline{A}\overline{B}C\overline{D}$$

The **second** term, $\overline{A}\overline{B}$, is missing variables C or \overline{C} and D or \overline{D} , so first multiply the second term by $C + \overline{C}$ as follows:

$$\overline{A}\overline{B} = \overline{A}\overline{B}(C + \overline{C}) = \overline{A}\overline{B}C + \overline{A}\overline{B}\overline{C}$$

The two resulting terms are missing variable D or \overline{D} , so multiply both terms by $D + \overline{D}$ as follows:

$$\begin{aligned}\overline{A}\overline{B} &= \overline{A}\overline{B}C + \overline{A}\overline{B}\overline{C} = \overline{A}\overline{B}C(D + \overline{D}) + \overline{A}\overline{B}\overline{C}(D + \overline{D}) \\ &= \overline{A}\overline{B}CD + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}\overline{C}\overline{D}\end{aligned}$$

The **third** term, $AB\overline{C}D$, is already in standard form.

The **complete standard SOP form** of the original expression is as follows:

$$\overline{A}\overline{B}CD + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}\overline{C}\overline{D} + AB\overline{C}D$$


The Product-of-Sums (POS) Form (جداء المجاميع)

- When two or more sum terms are multiplied, the resulting expression is a **product-of-sums (POS)**.

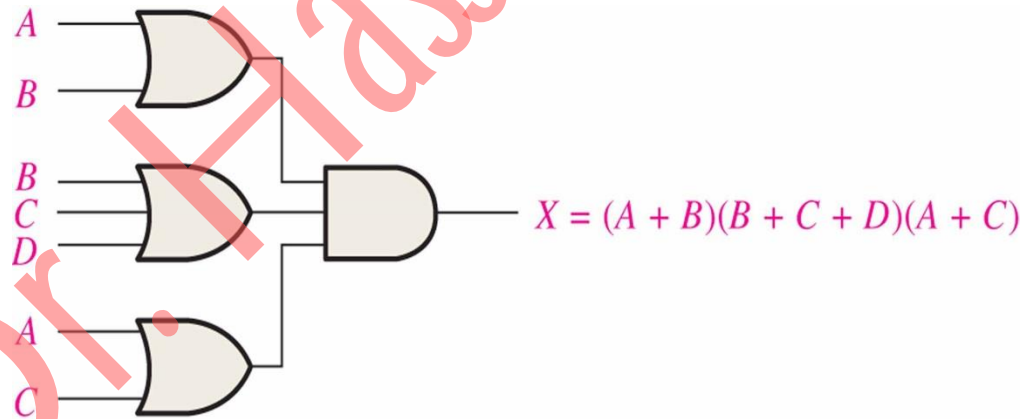Examples

$$(\bar{A} + B)(A + \bar{B} + C); \quad (\bar{A} + \bar{B} + \bar{C})(C + \bar{D} + E)(\bar{B} + C + D);$$
$$(A + B)(A + \bar{B} + C)(\bar{A} + C);$$

Implementation of a POS Expression: $(A + B)(B + C + D)(A + C)$



Standard Form of POS

❑ In **POS standard form**, every variable in the domain must appear in each sum term of the expression. Another state is called **nonstandard** form.

❑ For example,

Standard form: $(\bar{A} + \bar{B} + \bar{C} + \bar{D})(A + \bar{B} + C + D)(A + B + \bar{C} + D)$

Nonstandard form: $(\bar{A} + \bar{B} + C)(A + B + \bar{D})(A + \bar{B} + \bar{C} + D)$

Converting a Sum Term to Standard POS

- A **nonstandard POS** expression is converted into standard form using Boolean algebra rule 8 ($A \cdot \bar{A} = 0$).

Step 1: **Add** to each nonstandard product term a term made up of the **product** of the **missing variable** and its **complement**.

Step 2: Apply rule 12 : $A + BC = (A + B)(A + C)$.

Step 3: Repeat Step 1 until all resulting sum terms contain all variables in the domain in either complemented or uncomplemented form.

Example 6-10

Convert the following Boolean expression into standard POS form:

$$(A + \bar{B} + C)(\bar{B} + C + \bar{D})(A + \bar{B} + \bar{C} + D)$$

Solution

The first term, $(A + \bar{B} + C)$, is missing variable D or \bar{D} , so add $D\bar{D}$ and apply **rule 12** as follows:

$$A + \bar{B} + C + D\bar{D} = (A + \bar{B} + C + D)(A + \bar{B} + C + \bar{D})$$

The second term, $(\bar{B} + C + \bar{D})$, is missing variable A or \bar{A} , so add $A\bar{A}$ and apply **rule 12** as follows:

$$\bar{B} + C + \bar{D} + A\bar{A} = (A + \bar{B} + C + \bar{D})(\bar{A} + \bar{B} + C + \bar{D})$$

The third term, $A + \bar{B} + \bar{C} + D$, is already in standard form.

The standard POS form of the original expression is as follows:

$$\begin{aligned} &(A + \bar{B} + C)(\bar{B} + C + \bar{D})(A + \bar{B} + \bar{C} + D) = \\ &(A + \bar{B} + C + D)(A + \bar{B} + C + \bar{D})(A + \bar{B} + C + \bar{D})(\bar{A} + \bar{B} + C + \bar{D})(A + \bar{B} + \bar{C} + D) \end{aligned}$$

Converting SOP Expressions to Truth Table Format

- The **first step** in constructing a truth table is to list all possible combinations of binary values of the variables in the expression.
- **Next**, convert the SOP expression to standard form if it is not already.
- **Finally**, place a **1** in the **output** column (**X**) for each binary value that makes the standard **SOP expression equal to 1** and place a **0** for all the remaining (المتبقية) binary values.

This procedure is illustrated in Example 6-11.

Example 6-11

Develop a truth table for the standard SOP expression

$$\overline{A}\overline{B}C + A\overline{B}\overline{C} + ABC$$

Solution

The binary values that make the product terms in the expressions equal to 1 are

$$\overline{A}\overline{B}C : 001; \quad A\overline{B}\overline{C} : 100; \quad ABC : 111$$

For each of these binary values, place a 1 in the output column as shown in the table. For each of the remaining binary combinations, place a 0 in the output column.

Inputs			Output	Product Term
A	B	C	X	
0	0	0	0	
0	0	1	1	$\overline{A}\overline{B}C$
0	1	0	0	
0	1	1	0	
1	0	0	1	$A\overline{B}\overline{C}$
1	0	1	0	
1	1	0	0	
1	1	1	1	ABC

Converting POS Expressions to Truth Table Format

To construct a truth table from a POS expression,

- **First**, list all the possible combinations of binary values of the variables just as was done for the SOP expression.
- **Next**, convert the POS expression to standard form if it is not already.
- **Finally**, place a **0** in the output column (**X**) for each binary value that makes the expression **equal to 0** and place a **1** for all the remaining binary values.

This procedure is illustrated in Example 6–12.

Example 6-12

expression:

Solution

Determine the truth table for the following standard POS

$$(A + B + C)(A + \bar{B} + C)(A + \bar{B} + \bar{C})(\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + C)$$

The binary values that make the sum terms in the expression equal to 0 are

$$A + B + C : 000; \quad A + \bar{B} + C : 010; \quad A + \bar{B} + \bar{C} : 011; \quad \bar{A} + B + \bar{C} : 101; \quad \bar{A} + \bar{B} + C : 110;$$

For each of these binary values, place a 0 in the output column as shown in the table. For each of the remaining binary combinations, place a 1 in the output column.

Inputs			Output	Sum Term
A	B	C	X	
0	0	0	0	$(A + B + C)$
0	0	1	1	
0	1	0	0	$(A + \bar{B} + C)$
0	1	1	0	$(A + \bar{B} + \bar{C})$
1	0	0	1	
1	0	1	0	$(\bar{A} + B + \bar{C})$
1	1	0	0	$(\bar{A} + \bar{B} + C)$
1	1	1	1	



The end of Lecture_06, chapter 4